

COMMUNICATIONS

INCLUDING "RADIO ENGINEERING" AND "TELEVISION ENGINEERING"



★ TESTING TV TRANSMITTERS

★ V-H-F RAILROAD RADIO LINK SYSTEMS


JULY



3-Phase Regulation

MODEL	LOAD RANGE VOLT-AMPERES	*REGULATION ACCURACY
3P15,000	1500-15,000	0.5%
3P30,000	3000-30,000	0.5%
3P45,000	4500-45,000	0.5%

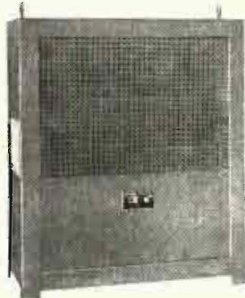* Harmonic Distortion on above models 3%.
Lower capacities also available.



Extra Heavy Loads

MODEL	LOAD RANGE VOLT-AMPERES	*REGULATION ACCURACY
5,000*	500 - 5,000	0.5%
10,000*	1000-10,000	0.5%
15,000*	1500-15,000	0.5%



General Application

MODEL	LOAD RANGE VOLT-AMPERES	*REGULATION ACCURACY
150	25 - 150	0.5%
250	25 - 250	0.2%
500	50 - 500	0.5%
1000	100-1000	0.2%
2000	200-2000	0.2%




400-800 Cycle Line INVERTER AND GENERATOR REGULATORS FOR AIRCRAFT.

Single Phase and Three Phase

MODEL	LOAD RANGE VOLT-AMPERES	*REGULATION ACCURACY
D500	50 - 500	0.5%
D1200	120-1200	0.5%
3PD250	25 - 250	0.5%
3PD750	75 - 750	0.5%

Other capacities also available

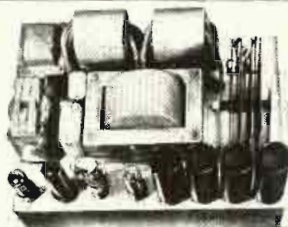

The NOBATRON Line

Output Voltage DC	Load Range Amps.
6 volts	15-40-100
12 "	15
28 "	10-30
48 "	15
125 "	5-10

* Regulation Accuracy 0.25% from 1/4
to full load.

SORENSEN

The First Line of standard electronic AC Voltage Regulators and Nobatrons

GENERAL SPECIFICATIONS:

- Harmonic distortion max. 5% basic, 2% "S" models
- Input voltage range 95-125: 220-240 volts (-2 models)
- Output adjustable bet. 110-120: 220-240 (-2 models)
- Recovery time: 6 cycles; \pm (9 cycles)
- Input frequency range: 50 to 65 cycles
- Power factor range: down to 0.7 P.F.
- Ambient temperature range: -50°C to $+50^{\circ}\text{C}$

All AC Regulators & Nobatrons may be used with no load.

*Models available with increased regulation accuracy.

Special Models designed to meet your unusual applications.

Write for the new Sorensen catalog. It contains complete specifications on standard Voltage Regulators, Nobatrons, Incevolts, Transformers, DC Power Supplies, Saturable Core Reactors and Meter Calibrators.

SORENSEN & CO., INC.
STAMFORD CONNECTICUT

Represented in all principal cities.

**For keeping video operations under control—
from modest start to mighty operations...**

DU MONT **MASTER CONTROL** *Equipment*



FUNCTIONS...

1. Generation of synchronizing signals conforming to RMA recommendations.
2. Distribution of sync signals.
3. Push-button selection of program sources for use by the transmitter ("on-the-air" signal).
4. Monitoring and distribution of the "on-the-air" picture signal.
5. Push-button selection of program sources next to be used as "on-the-air" signal (preview signal).
6. Monitoring and distribution of preview picture signal.
7. Monitoring of "on-the-air" and preview signal waveforms.
8. Stabilization of picture and sync signals from remote program sources.
9. Test monitoring of master control signals for maintenance purposes.
10. Exclusive Du Mont "fully automatic" lap dissolve and fade control—the standard of all Du Mont control equipment.

► Split-second timing
—smooth-flowing program continuity—
that's the assurance

the Du Mont Master Control Line offers television broadcasters.

Multiple-studio live programs, network participation, local remote pickups, films and rehearsals, are selected and integrated at will. The Du Mont Master Control Line consists of groups of integrated equipment capable of performing any desired function of

television broadcasting in the professional manner long associated with sound broadcasting.

The number of functions incorporated in any one master control "package" depends on the complexity of the telecasting station. Five basic Du Mont master control "packages" meet the requirements of the smallest to the largest telecasting station. In typical Du Mont manner, you can start as small as you like and grow as large as you like, with Du Mont equipment.

► **DESCRIPTIVE LITERATURE ON REQUEST**

© ALLEN B. DU MONT LABORATORIES

DU MONT

First with the Finest in Television

ALLEN B. DU MONT LABORATORIES, INC. • TELEVISION EQUIPMENT DIVISION, 42 HARDING AVE., CLIFTON, N. J. • DU MONT NETWORK AND STATION WABD, 515 MADISON AVE., NEW YORK 22, N. Y. • DU MONT'S JOHN WANAMAKER TELEVISION STUDIOS, WANAMAKER PLACE, NEW YORK 3, N. Y. • STATION WTTG, WASHINGTON, D. C. • HOME OFFICES AND PLANTS, PASSAIC, N. J.

COMMUNICATIONS

Including Television Engineering, Radio Engineering, Communication & Broadcast Engineering, The Broadcast Engineer, Registered U. S. Patent Office.

LEWIS WINNER

Editor

F. WALEN

Assistant Editor

Bryan S. Davis, President

Paul S. Weil, Vice Pres.-Gen. Mgr.

F. Walen, Secretary

A. Goebel, Circulation Manager

Cleveland Representative:

James C. Munn

2253 Delaware Dr., Cleveland 6, Ohio
Telephone: Erievlew 1726

Pacific Coast Representative:

Brand & Brand

7052 W. Sixth St., Los Angeles 14, Calif.
Telephone Michigan 1732

345 Montgomery St., San Francisco 4, Calif.
Telephone Douglas 4475

Wellington, New Zealand: Te Ara Book Depot.
Melbourne, Australia: McGill's Agency.

Entered as second-class matter Oct. 1, 1937 at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$5.00 per year in foreign countries; 35 cents per copy.

COMMUNICATIONS is indexed in the Industrial Arts Index.

COVER ILLUSTRATION

Control room setup at WMCP-FM, Baltimore, operating at 94.7 mc. with an effective radiated power of 20 kw.
(Courtesy Westinghouse)

MICROWAVE TRANSMISSION

Frequency Stabilization in the Region of 10,000 Mc. A. V. Donnelly 7
Microwave Oscillator and Reflex Klystron Used in Feedback Setup.

BROADCAST STATION MAINTENANCE

Maintenance of Preamplifier Equipment in Broadcast Transmission-Reproducing System Ralph G. Peters 9
Procedure Developed by NBC, Using Tests to Determine Frequency Response, Distortion and Operating Levels.

TELEVISION ENGINEERING

TV Transmitter Design G. Edward Hamilton 10
Linear Amplifier Design Features, Output Load Considerations, Transmitter Tests.

TRANSMITTING TUBES

Tube Engineering News 14
Army-Navy Recommended Subminiatures and Preferred Transmitting Tubes, Vest Pocket Subminiature Tube Transmitter-Design Features.

RAILROAD RADIO

V-H-F Railroad-Radio Link with Six-Channel Telephone Carrier System Philip B. Patton 16
Southern Pacific 44-Mc Link Operates on 158.19 and 164.57 mc Using a 6-Channel System for Telephone Pulse Signalling and Teletype Work.

SOUND ENGINEERING

Noise Measurements Robert L. Morgan 21
Indian Measurement Procedures, Direct and Reverberant Sound Problems, Acoustic Test Room Methods.
Coaxial and Separate 2-Way Speaker System Design Howard Souther 22
Design, Production, Performance and Cost Considerations, Cabinet Planning, H-F and L-F Unit Applications.

COMMUNICATIONS CIRCUITRY

Impedance Matching Techniques William J. Kessler 26
Relationships Which Exist Between Source and Load Impedance Analyzed, Networks Containing Elements Which Are Linear Considered.

MONTHLY FEATURES

News and Views Lewis Winner 5
Veteran Wireless Operators' Association News 25
News Briefs of the Month 27
The Industry Offers 28
Advertising Index 40

Entire contents Copyright 1948, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



Choose your Radiotelephone on the basis of



FACTS "NOT" BRAGS

Radiotelephone is too important an investment to be made on the basis of high-flown phrases and advertising slogans. It's easy to make claims that can't be proved and to so word statements that they seem to mean more than they do.

So, choose carefully. Make sure that claims are provable, that features mean something, and that specifications are understandable. The best test is to talk to people who have bought the equipment in question. Is it performing according to claims? *How much does it cost to maintain?* What kind of service does the manufacturer give? The manufacturer who has nothing to hide will welcome your skepticism.

Here are the FACTS about *Motorola* -compare them with all the others:

INDUSTRY LEADERSHIP

Motorola manufactures and installs more radiotelephone equipment than any other — **BAR NONE**. Motorola has more fully qualified mobile-radio developmental engineers in their laboratories devoting time *exclusively* to mobile radio problems than any other manufacturer — **BAR NONE**. Motorola has the largest mobile radiotelephone research laboratory and offers more product development than any other — **BAR NONE**. Motorola has pioneered more FM mobile radiotelephone "firsts" than any other manufacturer — **BAR NONE**: **FIRST** with 20 D.B. quieting at 0.4 microvolt input. **FIRST** commercially successful FM 2-way radiotelephone with **FIRST** noise compensated squelch that makes present day radio communications practicable. **FIRST** to successfully build equipment for the 152-162 mc. band. **FIRST** to develop the vibrator power supply in receivers, now accepted as the best power supply system. **FIRST** with "Precision Selectivity" for channel conservation. **FIRST** with Precision Cavity for intermodulation control.

ADVANCED DESIGN

Only Motorola guarantees full channel utilization through "PRECISION SELECTIVITY." P.S. provides extraordinary channel protection from nearby central stations and other man-made interference. Motorola's advanced design is your guarantee against early obsolescence.

**VERIFY THE
FACTS WITH THE
PEOPLE WHO USE**

Motorola
EQUIPMENT

OVER-ALL COST

It's been proved — Motorola continues to operate when others fail. *Motorola takes less time out... costs you far less over the years than any other equipment regardless of initial price!*

PROVED PERFORMANCE

Hundreds of official records show Motorola equipment giving "like-new" service for over six years — with only limited routine maintenance required. Part for part, Motorola is the sturdiest equipment in the field today — and Motorola's rugged construction pays off for you.

A Motorola Communications Engineer will be glad to call and discuss radiotelephone as it concerns your specific problems. He'll put you in touch with people in your business who are using Motorola equipment. He'll give you **FACTS**, not fiction, **FIGURES**, not fables —

Write Today!

Motorola
**FM
2-WAY
RADIOTELEPHONE**

Motorola Inc.

COMMUNICATIONS DIVISION • Chicago 51, Illinois

In Canada: Rogers Majestic, Ltd., Toronto-Montreal



SECURITY QUIZ

for MANAGEMENT MEN

can you answer these important questions?

How many of your employees are buying U. S. Security Bonds regularly via the Payroll Savings Plan? (35% to 50% of employees buy Security Bonds on the Payroll Savings Plan in those companies in which top management backs the Plan.)

- How does their average holding compare with the national average? (The national average among P.S.P. participants is \$1200 per family.)

- Why is it vital—to you, your company, and your country—that you personally get behind the Payroll Savings Plan this month? You and your business have an important stake in wise management of the public debt. Bankers, economists, and industrialists agree that business and the public will derive maximum security from distribution of the debt as widely as possible.

Every Security Bond dollar that is built up in the Treasury is used to retire a dollar of the national debt that is potentially inflationary. Moreover, every Security Bond held by anyone means fewer dollars go to market to bid up prices on scarce goods.

- Can't your employees buy Bonds at banks? Banks don't provide Security Bonds on the "installment plan"—which is the way most workers pre-

fer to obtain them. Such workers want and need Payroll Savings.

- What direct benefits are there for your company? In 19,000 industrial concerns operating Payroll Savings, employees are more contented. Worker production has increased, absenteeism has decreased—even accidents have been fewer!

All these benefits accrue in addition to extra security for the individual who gets and holds Bonds. (Every \$3 invested pay \$4 at maturity.)

But even a plan with all these benefits requires the sponsorship of top management for real success.

- What do you have to do? The Treasury has prepared a kit of material especially for you to distribute among certain key men in your company. This will be your part in the all-out campaign—starting April 15—for America's economic security.

Make sure you get your kit. Be sure to give it your personal attention. Keep the Payroll Savings Plan operating at its full potential in your company. It's a major factor in America's security—your best business security!

For any help you want, call on your Treasury Department's State Director, Savings Bonds Division.

The Treasury Department acknowledges with appreciation the publication of this message by

COMMUNICATIONS

This is an official U.S. Treasury Advertisement prepared under auspices of the Treasury Department and the Advertising Council



COMMUNICATIONS

LEWIS WINNER, Editor

JULY, 1948

The TV Allocation Hearings

TELECAST ENGINEERING research and development activity was quite a featured topic during the recent tv allocation sessions in Washington. At this, the first comprehensive hearings on the channel problem, since the channels were set up two years ago, over 100 presented volumes of engineering data as testimony for and against the FCC plan which would nearly double the present channel setup. The acute problem of co-channel or adjacent interference served as a major point of most arguments. Exhibits disclosed that up to 180-mile separation may be required in some instances to avoid interference. Directionalized co-channel operation was offered as one solution.

One exhibit, wherein the proposed use of channel 6 by WNHC-TV, New Haven, Conn., was described, showed that based on separation versus a 100:1 and 2:1 signal ratios for co-channel and adjacent channel clearances, the overlap of WNHC-TV, operating with a power of 20 kw at 500 feet elevation above surrounding terrain, as against 50 kw at 500 feet for WABD on channel 5 and likewise Worcester with 50 kw at 500 feet, was not greater than anticipated for the whole scheme of allocations for the New York and New England areas on channels 5 and 6.

A plan offered by DuMont suggested an addition of 8 channels which are now in use by the Interdepartment Radio Advisory Committee (112-118, 132-138, 138-144, 162-168, 168-174, 216-222, 222-228, 228-234 mc or 162-168, 168-174, 221-227, 227-233, 233-239, 239-245, 251-257 mc). To justify this transfer, the government might be given an equal number of frequencies in the u-h-f band reserved for television.

Since on September 20, the u-h-f band allocations will be probed, this approach to the problem will, undoubtedly, be reviewed again with, perhaps, the entire 2 to 13 channel allocation testimony serving as an additional report for the basis of allocation judgment. Several witnesses at the 2 to 13 channel sessions indicated that no

final decision could be made until both hearings were completed and studied carefully.

It appears as if this fall may see a revised allocation pattern which will bring new horizons to tv.

Intercarrier TV-Sound Reception

THE USE OF INTERCARRIER SOUND in tv receivers has been the subject of many investigations. For instance, the matter has been receiving careful study by the Television Transmitter Committee of the RMA Engineering Department.

At present and in the future, to make intercarrier reception feasible, at least three conditions must be met: (1)—The picture carrier must never disappear so that it is always available to provide the 4.5 mc beat upon which the system functions. Local generation of the 4.5 mc carrier is, of course, possible but brings with it unwanted complexity. (2)—The separation between the picture and sound carriers, nominally 4.5 mc, should be held with the minimum variation possible so that the bandwidth of the audio discriminator may be kept reasonably small, and to insure that a-m noise may be rejected with a minimum of limiting involved. (3)—Incidental f-m or phase modulation of the picture carrier, with respect to the audio carrier, must be minimized so as to avoid the introduction of hum or unwanted signal into the f-m sound channel.

Initial opinions indicated that some of these limitations would restrict the practicality of the system. However, recent surveys by S. W. Seeley indicated that these objections may not be too well founded. From stations in metropolitan New York currently surveyed, indications were that with no design or operational changes, the limiting performance of the intercarrier receivers was not found excessively wanting. To further safeguard performance, however, there is likely to be a concerted campaign by proponents of the intercarrier system for further safeguards with respect to transmitting equipment.

Commenting on the problem, Leonard Mautner, head of the television

transmitter division of the Allen B. DuMont Labs, stated that although it may be argued that a substantial modification of the design or operation of the transmitting gear is warranted to further the production of low-cost tv receivers, an engineering compromise which will give the greatest freedom to both transmitter and set designers is indicated. He said: "Inevitably, further study of present transmitter capabilities and deficiencies must be made before a standards review is indicated for the transmitter gear. Likewise, a review of the intercarrier set requirements must be made before the minimum requirements of intercarrier set designers could be adequately defined.

"For the interim period during which the intercarrier system holds forth with no modification of the transmitter equipment, it would appear that broadcasters may expect most favorable comments of their programs on intercarrier sets if they will . . .

(a) Carefully monitor their video transmission to insure that maximum white transmitted corresponds to no less than 10% of maximum carrier.

(b) Monitor the frequencies of the audio and video carriers so as to maintain the 4.5-mc nominal separation to as much within the present FCC standard of .002% for the individual carriers as operations will permit.

"These conditions may be readily met by telecasters with careful attention to operating practice. The remaining condition of phase modulation appears at the moment to be less of a limiting factor to satisfactory performance of intercarrier receivers and one that can only be resolved when additional information is forthcoming from both transmitting and receiving groups


"The extent to which intercarrier receivers will approach the optimum performance that such a system will permit, assuming that the requisite transmitter deficiencies could be overcome, will rest primarily with the intercarrier set makers and the self-imposed economic conditions."—L. W.

Frequency Stabilization In



Figure 1
Frequency multiplier unit.

Figure 2
Block diagram of the frequency multiplier unit.

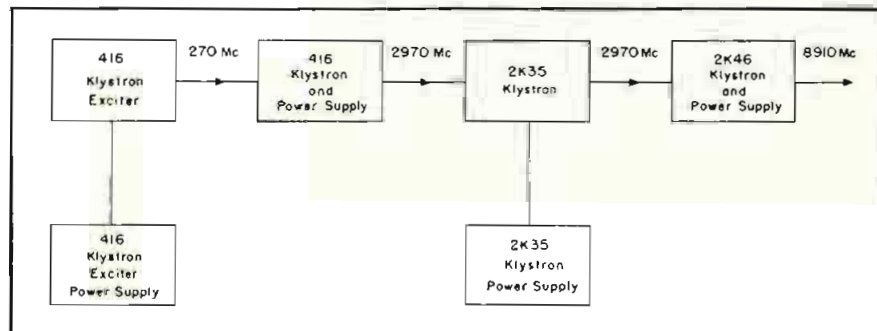

Frequency Stabilization Procedure, Using Feedback Technique, Permits Construction of Compact Easy-To-Tune Equipment. Uses Microwave Oscillator, Reflex Klystron, H-F Discriminator and Direct Coupled (D-C) Amplifier Setup.

by A. V. DONNELLY**

Assistant Professor
Department of Electrical Engineering
The State University of Iowa

THERE ARE two basic methods of obtaining a stabilized oscillator at microwave frequencies. The first is frequency multiplication. This is the practice of employing a quartz crystal vibrating at a relatively low radio frequency, whose output is multiplied the number of times necessary to give the desired frequency. The second method involves feedback techniques. In this scheme some type of frequency-sensitive control circuit is used which is capable of changing the oscillator frequency in a manner which will maintain the frequency within specified limits.

Frequency Multiplication

A frequency multiplier unit used by the author is shown in Figure 1. The general plan of its construction appears in the block diagram of Figure 2. A crystal whose frequency is approximately 7.5 mc is used as the basic element in a 416-klystron exciter. Employing conventional doubler and tripler circuits, this frequency

is multiplied 36 times providing an output frequency of approximately 270 mc with a power of about 10 watts. This feeds the input of a 416-klystron multiplier tube where an eleven-fold multiplication takes place. (This multiplication may be ten, eleven, or twelve times depending on the tuning adjustment.) This multiplier tube is not very efficient, and at 2,970 mc the output is about 10 milliwatts. The output is then fed to a 2K35, a klystron cascade amplifier, with a power gain of 1,000. This provides a 1-watt (approximately) input to a 2K46 klystron, a multiplier tube, the output frequency of which is three times the input frequency, or 8,910 mc at a power of approximately 10 milliwatts.

The output of such a unit will have the same degree of stability as the 1-f quartz crystal used in the exciter unit. By employing temperature-regulated crystal units, the frequency deviation can be kept to a minimum.

Two commercial applications*** of this system have been made: a microwave blind landing system¹ and a two-way microwave f-m system for use in a railroad installation.² Both of these systems, however, operate on a frequency in the region of 3,000 mc, and do not use the 2K46 multiplier stage.

One of the greatest disadvantages of the aforementioned system has been the difficulty in tuning up. There are

¹Based in part on a dissertation submitted for Ph.D. requirements at the State University of Iowa.

**Formerly with Collins Radio Company.

***Systems installed by Sperry Gyroscope Co.

The Region of 10,000 Mc*

nine cavities in the system, three on each of three klystron tubes, which require delicate adjustment. The problem was recently solved by the National Bureau of Standards who now employ the modified setup as its *microwave frequency standard* at the Central Radio Propagation Laboratory.³ No klystron generators are used in this system. Instead, harmonics of the output frequencies from the conventional multipliers are generated by silicon-crystal multipliers. Thus there is no need for the tedious cavity adjustments required with the klystrons.

Feedback Stabilization

In this type of stabilization, the frequency of oscillation is generated at the value at which it is to be used and not derived from multiplication of a lower frequency. The frequency of the oscillator tube is controlled by a correction voltage obtained from a frequency discriminator circuit. This discriminator circuit converts any change of frequency to a corresponding change in voltage. This correction voltage, in turn, is applied to the oscillator tube so that the frequency is maintained at a desired value.

The discriminating action can take place at one of two different levels in the system; either at (1) a low frequency, usually the intermediate frequency in a superheterodyne receiver or at (2), a high frequency, such as the microwave frequency of the oscillator to be stabilized.

Low-Frequency (I-F) Discrimination

In the low-frequency discriminating system, the discriminator circuit is of conventional design and operates from the intermediate frequency. The output from this circuit is allowed to control the frequency of the oscillator by changing one of the electrode voltages. This system was used considerably in radar systems in which the magnetron source was fairly unstable. To keep the receiver tuned so that the i-f was confined within the bandwidth of the i-f amplifier the frequency of the local oscillator was changed so that it could follow the variations of the signal source. (Actually this is opposite to frequency stabilization but it is included so that the theory presented will be complete.) Three of the many

radar systems that used this method were the MPG-1 Fire Control Radar,⁴ the APS-15 and the APQ-13⁵ Radars for Blind Bombing. In these cases the i-f was 30 mc.

High-Frequency (R-F) Discrimination

As a contrast to the l-f discriminating system, h-f discrimination involves the use of a discriminator circuit which is capable of converting deviations at the microwave frequency into voltage variations. Suitable combinations of wave-guide components can provide an appropriate discriminator circuit, the output of which can be made to control the voltage of an electrode of the oscillator. The electrode used in the case of the reflex klystron is the reflector.

A Feedback Stabilization System

This type of stabilization system consists chiefly of a microwave oscillator (a reflex klystron such as the 723 A/B of the 2K39), a h-f discriminator circuit, a direct-coupled (d-c) amplifier and a power supply. Figure 3 shows the relationship of these units. One of the simplest h-f discriminator circuits may be formed by a combination of a hybrid tee, a shorting plunger, a resonant cavity and a crystal termination, as shown in Figure 4. With proper adjustment, an amplitude variation in the output can be obtained


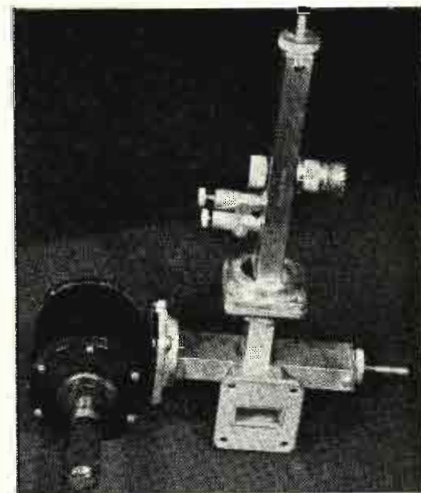


Figure 4
High frequency discriminator.

with a variation in frequency of the input. To minimize variations due to temperature changes, the resonant cavity used as a reference standard was enclosed in a temperature-regulated oven (not shown in the photograph). The output of the discriminator is fed to a direct-coupled amplifier where the minute fluctuations are amplified to larger fluctuations. The output of the d-c amplifier is connected in series with the reflector power supply of the oscillator tube. The variations from the d-c amplifier then can vary the voltage of the reflector which

Figure 3
Setup of a feedback stabilization system.

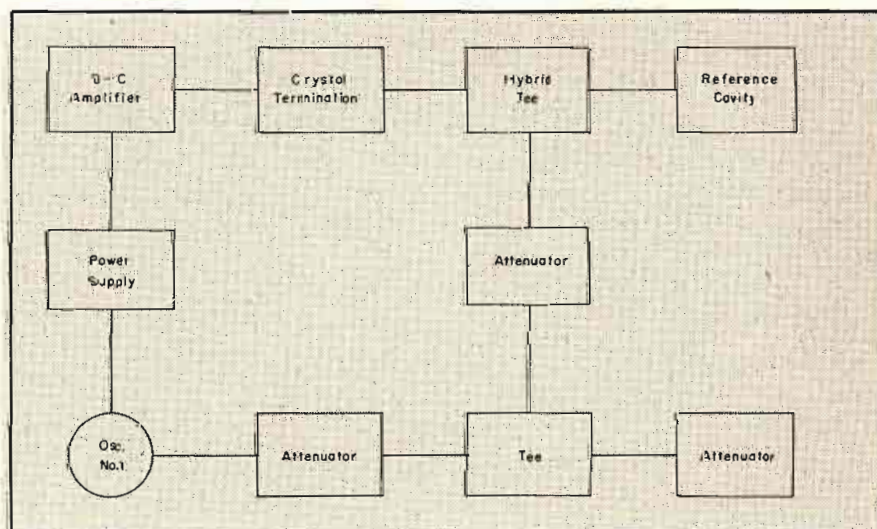

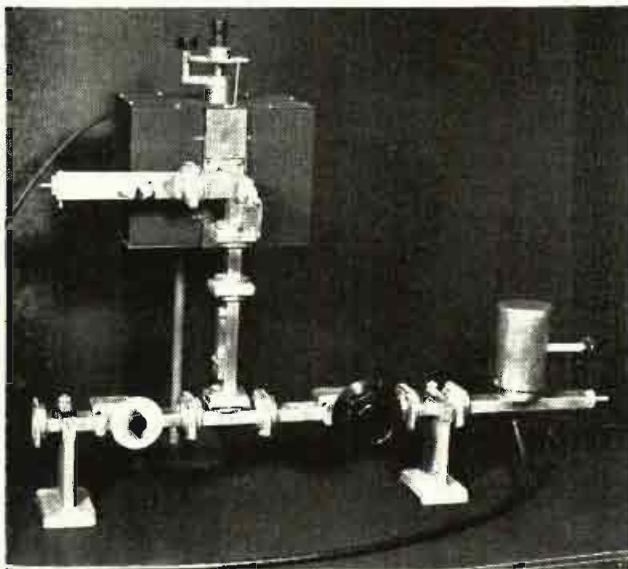


Figure 5

Feedback stabilization system power supply.

Figure 6

Feedback stabilization system waveguide plumbing.

will cause the frequency of the system to return to its original value. Figure 5 shows a complete laboratory unit incorporating the power supply and the d-c amplifier, and Figure 6 shows a representative arrangement of waveguide plumbing.

Numerous modifications and refinements are possible but the simplest type is presented so that complications of apparatus and involved theory of waveguide components would not overshadow the basic operation of the system.

Determination of Stability

An engineer or a laboratory technician working with a stabilized oscillator always demands that the value of the stability be given. In the case of the frequency multiplier units, this value can be easily determined. The output of the frequency multiplier unit will have the same percentage deviation as the original crystal oscillator. Hence, all that is necessary is to determine the percentage deviation of the l-f crystal. This procedure presents no problem. The output of the crystal oscillator can be compared with that of a secondary frequency standard previously calibrated from the signals received from WWV of the National Bureau of Standards.

The determination of the stability of a feedback stabilization system is, however, an entirely different problem. To determine the stability of a feedback stabilization system, one could compare the output with the output of a frequency multiplier unit whose deviation was known. This method could not be universally adopted because of the few microwave frequency multi-

plier units available. In addition, it is assumed that the percentage deviation of the frequency multiplier unit is of a comparable value with that of the feedback stabilization unit to be measured. This restriction further reduces the number of frequency multiplier units that would be suitable for this purpose. Because of this difficulty, other methods of determining frequency deviation must be conceived.

One method which could be utilized would be that involving a frequency comparison similar to that encountered at the lower frequencies. In this method, however, the two frequencies being compared would both have to be unknown. To be more explicit, two identical oscillating systems of unknown frequency deviations could be beat together giving some intermediate frequency. The frequency deviation of this intermediate frequency could then be determined by conventional methods. This procedure will not give an absolute value because one unknown is being compared with another. Instead, a relative figure of merit is obtained indicating the maximum deviation of either of the two units.

During an investigation, an attempt was made to utilize the above method. Difficulty was encountered with noise modulation on the two oscillators which did not permit a satisfactory beat frequency to be obtained. As a consequence, a modification of the above method was used.

The two unknown oscillator systems were allowed to beat together at a frequency of approximately two megacycles per second. This intermediate frequency was passed through an r-f



amplifier whose bandwidth could be varied over a known range. A cathode-ray tube indicated the output from the r-f amplifier. The operation of this method was based on the fact that as long as the cathode-ray tube indicated that an output was being obtained, the frequency deviation was less than the bandwidth of the r-f amplifier. By varying the width of the tuned circuits of the amplifier, the limiting value of the frequency deviation could be determined. Satisfactory results have been obtained with a limiting value of stability of the order of one part in 25,000,000 being measured when employing an oscillator frequency in the region of 10,000 mc.

Summary

The frequency multiplier unit employing klystron multiplier tubes is not satisfactory since tedious adjustment of the various cavities are involved. In addition, the use of the multiplier tubes requires a number of high-voltage power supplies which should be well regulated; items which are costly and space consuming. These disadvantages have been more or less overcome by the substitution of silicon-crystal multipliers for the klystrons. With super refinement in the driving oscillator, it is possible to obtain a frequency standard with a variation of less than one part in 100 million.

As a contrast with the frequency multiplier units, a feedback stabilization system can provide the same degree of stabilization with much less equipment resulting in a much lower cost and a lower space factor. This

(Continued on page 31)

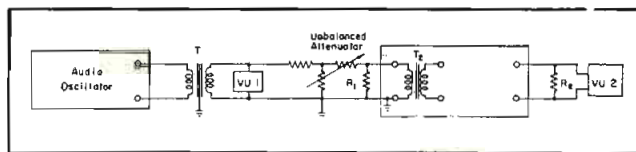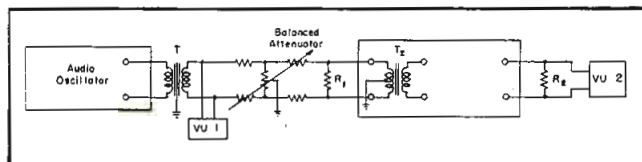

Figures 1 (left) and 2 (right)

Figure 1: Recommended method of determining frequency and linearity characteristics of a preamp containing a balanced input transformer. If the preamp has a bridging impedance or is to be fed from a source impedance of R_1 ohms, then R_1 should be made equal to the required impedance. This can be a pure resistance, either carbon or non-inductive wire wound, with a value of about 250 ohms. If the preamp has an input impedance, then R_1 is not necessary since the amplifier will terminate the attenuator. The ground in the balanced attenuator circuit need not necessarily be used for low and medium gain amplifiers. It is, however, required for high gain amplifiers.

The T transformer is desirable to isolate from the unbalanced ground effects which may be present within the audio oscillator. It should be a 1:1 ratio and have an electrostatic shield. Typical impedance ratios are from 200/200 to 600/600 ohms.

Figure 2. Circuit recommended for measuring a preamp containing an unbalanced-to-ground input transformer.

Maintenance of Preamp Equipment

In Broadcast Transcription-Reproducing Systems

THE PREAMP is a particularly vital link in the broadcast transcription-reproducing system and accordingly must be carefully checked, at least once a month, for its frequency response, distortion and operating level.

To determine the frequency response of the preamp, the Figure 1 circuit can be used. The audio oscillator used in this setup should cover the 30- to 15,000-cps range. The output of the oscillator should not contain more than 1% total harmonic distortion at the normal operating level used for the proposed tests (approximately +4 vu).

The use of an isolation transformer between the oscillator and the preamp input is indicated in this circuit. Experience has indicated that the use of proper isolation will greatly minimize errors, particularly when measurements are made at the higher frequencies with circuits which are balanced to ground. The isolation transformer should provide the correct impedance matching between the oscillator output and the preamp input; it should also

Maintenance Program, Developed by NBC Radio-Recording Division, Features Tests Which Determine Frequency Response, Distortion and Operating Levels of Preamp Units.

by RALPH G. PETERS

include an electrostatic shield, which should be connected to a good ground.

Measurement Technique

The frequency response characteristic of the preamp can be determined by a direct comparison between the volume indicator connected to the audio oscillator, and the volume indicator connected to the output of the preamp. To eliminate any possibility of error due to inaccuracies in the vol-

ume indicators, the tracking of the volume indicators should be compared by connecting them in parallel across the output of the audio oscillator and sweeping over the frequency range to be used. The two volume indicators should agree with ± 3 db to be considered satisfactory for use. If the departure should be greater than this limit one volume indicator should be considered as a standard (usually the volume indicator associated with the oscillator output), and a correction curve used to correct the final reading.

Many preamps have relatively high input impedance. If such a type is to

(Continued on page 30)

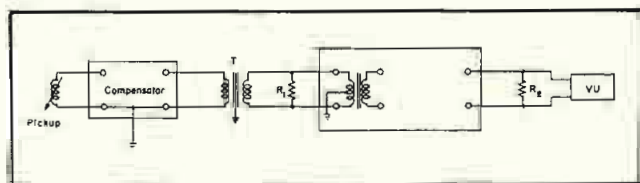


Figure 3

Another preamp setup where the isolation transformer must be used since the preamp input is balanced to ground, while the compensator has a ground on one leg. Should the preamp have a ground on one side of its input, then the isolation transformer can be deleted.


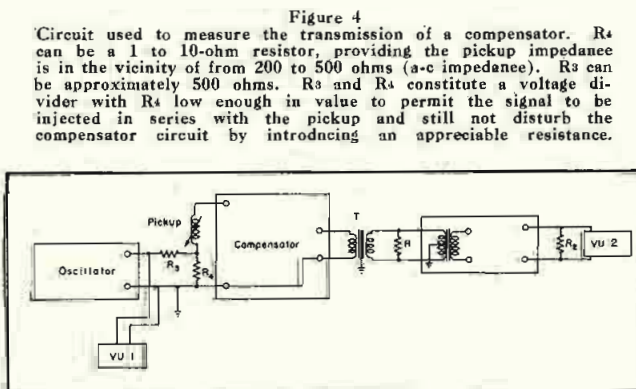


Figure 4

Circuit used to measure the transmission of a compensator. R_4 can be a 1 to 10-ohm resistor, providing the pickup impedance is in the vicinity of from 200 to 500 ohms (a-c impedance). R_3 can be approximately 500 ohms. R_3 and R_4 constitute a voltage divider with R_4 low enough in value to permit the signal to be injected in series with the pickup and still not disturb the compensator circuit by introducing an appreciable resistance.

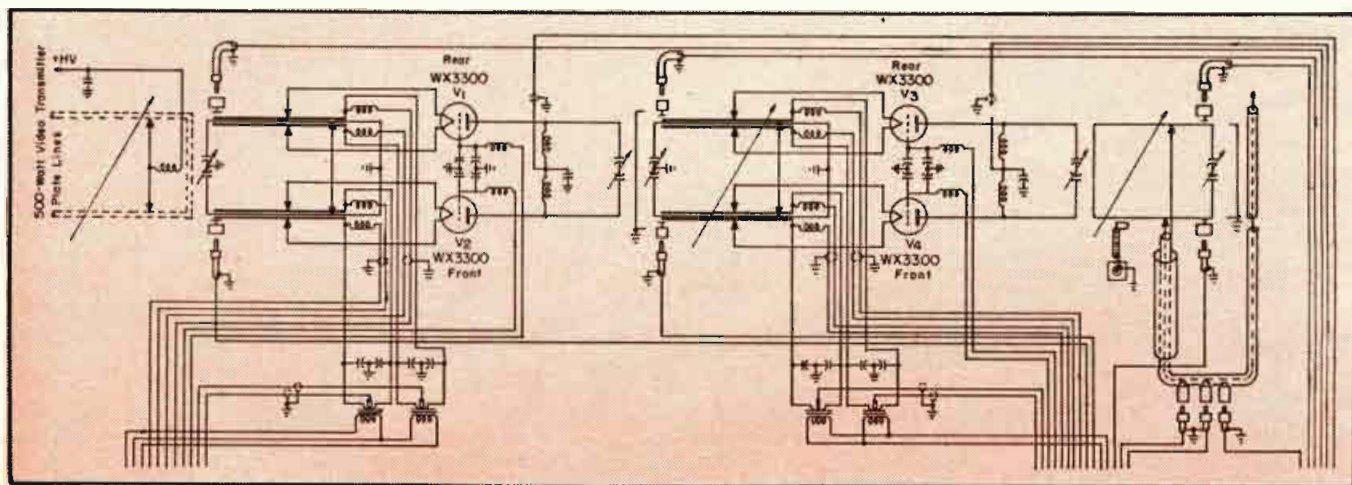

TV Transmitter Design

IN OUR ANALYSIS of class *B* linear amplifiers last month, the four primary conditions which linear amplifiers must meet were detailed as satisfactory bandwidth, adequate power output, linear output between the limits of 100% and 15% modulation, and suppression of lower sideband. Circuitry evolved to achieve these results were reviewed.

In this installment, linear amplifier design features are probed further.

Figure 1 shows the circuit breakdown of the two class *B* linear amplifier stages in which coupling and loading may be varied to produce a response characteristic satisfactory for the wide band of frequencies required for tv service. Secondary loading is increased by moving the cathode leads (filament) toward the open end of the resonant line. A fine adjustment of this variable is provided by a shorting bar near the shorted end of the line.

Variable coupling is provided by changing the physical position of the secondary with respect to the primary by means of a worm drive gearing system. This design, showing this physical positioning of the various elements, is illustrated in the six views shown in Figure 2. It will be noted that half wave lines are used. This allows for greater line length outside the tube to the quarter wave point, and in addition provides greater coupling efficiency between the stages. It is desirable to make the tuned circuits *only* broad enough to deliver high-definition television picture elements to realize a satisfactory plate circuit efficiency, since circuit efficiency is a function of bandwidth. A further

criteria for plate-circuit efficiency is that the tube output circuit be designed around a tube with relative low plate resistance, with respect to the plate-load resistance, in order that maximum voltage will be developed across the load impedance.

The modulated amplifier and class *B* linear stages are so tuned that the upper sideband of the television information is included in the passband characteristic of the tuned circuits, i.e., the carrier is positioned on the edge of the low-frequency end of the passband, and the circuits are adjusted to give a smooth frequency response characteristic over approximately F_c to $(F_c + 4)$ mc. This adjustment produces a single-sideband transmission system, since the tuned circuits reject the lower sideband—each tuned circuit contributing to the overall attenuation. In addition to the inherent selectivity of the tuned circuit, a notching filter is coupled to the cathode input circuit of the intermediate power amplifier. This filter is adjusted to 1.25 mc lower than the carrier frequency and results in narrowing the low frequency *skirt* of the passband characteristic.

Operation Setup of Amplifiers

Initial operation setup of the class *B* linear amplifiers is essentially the same as previously described for the modulated amplifier, except that in this case the video signal and r-f drive parameters are fixed. Bias should be main-

tained such that approximately 10% normal plate current flows with no excitation. This condition assumes that the grid plate transfer characteristic will be linear from this value up to the maximum excitation required to produce full rated output. For a *dripping condition* as described for the modulated amplifier, the output voltage will be directly proportional to the exciting voltage, and the modulation percentages will be maintained. Should the bias be kept at too highly negative a value, and the modulated amplifier be adjusted for proper modulation percentages, the video information will saturate in the white direction. This is due to operation about the lower knee of the transfer characteristic. Obviously should the bias be too positive, the sync output will swing into the upper knee of the transfer characteristic resulting in sync compression, excessive plate dissipation, and poor efficiency. The condition of excessive negative bias may be *masked* by reducing the modulation percentages in the modulated amplifier. This setup will allow the class *B* linear amplifiers to saturate toward the zero modulation direction, which *may* result in the proper ratio of modulation envelope percentages. However, this condition should be avoided, since the angle of flow of plate current with respect to the r-f grid drive will be reduced, resulting in lower efficiency and poor utilization of the transfer characteristic.

Output Load Considerations

The transmitter output is essentially a balanced system since the power ani-

Figure 1 (above)
Intermediate and power amplifier single sideband class *B* linear amplifier section of transmitter.

Part III . . . Linear Amplifier Design Features . . . Output Load Considerations . . . Testing the TV Transmitter (Video Amplifier Modulator Frequency Response) . . . Testing D-C Restorer . . . R-F Pass-Band Characteristics.

by G. EDWARD HAMILTON

Head, Television R-F Development Section
Television Transmitter Department
Allen B. Du Mont Laboratories, Inc.

plifier is push pull. Provision may be made for either balanced or unbalanced output connection, depending upon the antenna system to be used. Balanced output may be accomplished by connecting two transmission lines to the output coupling network. The two inner conductors connect to the coupling line at a position that produces satisfactory loading and match to the plate tank circuit, and the two outer conductors are bonded to chassis thereby producing a balanced output. To proceed from a balanced output circuit to an unbalanced transmission line, it is necessary to insert a balance to unbalance converter unit. This consists of a so-called *bazooka* system, i.e., a quarter-wave isolation transformer which places the outer conductor of the output transmission line at a high impedance with respect to the chassis. Figure 1 shows the manner in which the unit is installed in the transmitter. The electrical length of the *bazooka* is made adjustable by means of capacitive end loading for channels 2 and 3, and stub shortening for channels 4, 5 and 6.

The antenna is of prime importance in any installation since it must present a constant resistive load, at the end of the transmission line, over the entire passband (at least 4 mc above the video carrier frequency). A standing-wave ratio of better than 1:1 must be maintained for satisfactory picture resolution. Every effort must be made to keep the characteristic impedance of the transmission line constant since irregularities reflect back into the output circuit resulting in such effects as multiple reflections. These mismatches may be observed by the following method: (1) The transmitter output line is connected to a resistive impedance equal to its characteristic impedance and the output charac-

teristic noted as traced on the wobbulator scope with the transmitter operating under conditions of wobblelation and (2), the terminating resistor is replaced with the transmission line and compared with step 1. It has been noted that long transmission line installations show considerable variation across the passband especially where irregularities exist along the transmission line. It is, therefore, desirable for the antenna and transmitter to be located as close together as building layout permits to reduce the foregoing conditions.

Testing the TV Transmitter

Video Amplifier Modulator Frequency Response: The video amplifier frequency characteristic must be capable of essentially flat response to 5 or 6 mc. The low frequencies may best be tested by the application of square waves to the input and observing the amount of tilt on a 'scope whose l-f characteristic is flat down to at least 10 cycles.¹ The tilt allowable in a video amplifier is of the order of two per cent maximum with a sixty cycle square wave. In the circuit of Figure 3 (May, COMMUNICATIONS) there appeared capacitors (C_2 , C_4 , C_5 , C_6 and C_7) which act as l-f compensation elements. Excessive compensation may be observed on a 'scope as a rise in the trailing edge, while under compensation may result in a rise of the leading edge. In every case, each stage should be flat by itself—staggering stages may result in objectionable phase shift and should be avoided wherever possible.

The h-f response of video amplifiers may be best tested by means of a beat-frequency *wobbulator* whose output is linear from about 200 kc to 8 mc, and a 'scope. The characteristic of this 'scope need not be too exacting

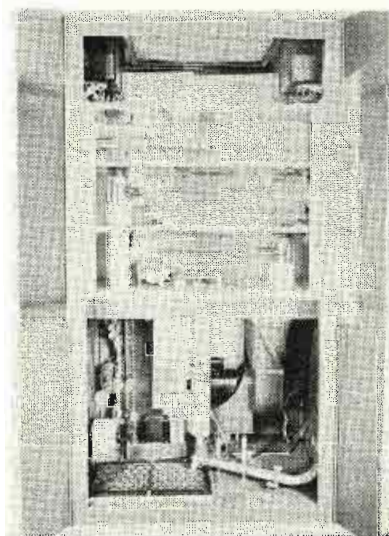


Figure 2

Top (a): Layout of final class B linear amplifier stages. Below (b): View showing manner in which the modulated amplifier drives the cathode to the intermediate power amplifier.


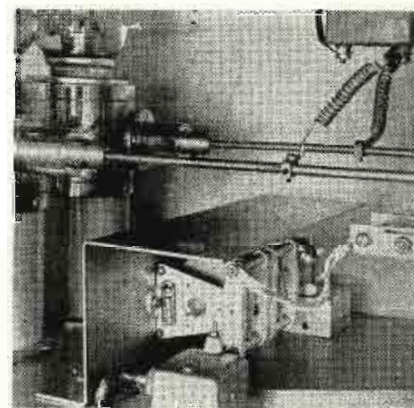


Figure 2

Above: Tuning and coupling system between intermediate power amplifier and power amplifier. Below: Another view of the tuning and coupling system between the intermediate power amplifier and power amplifier.

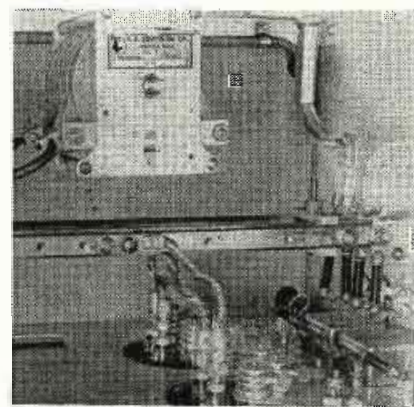

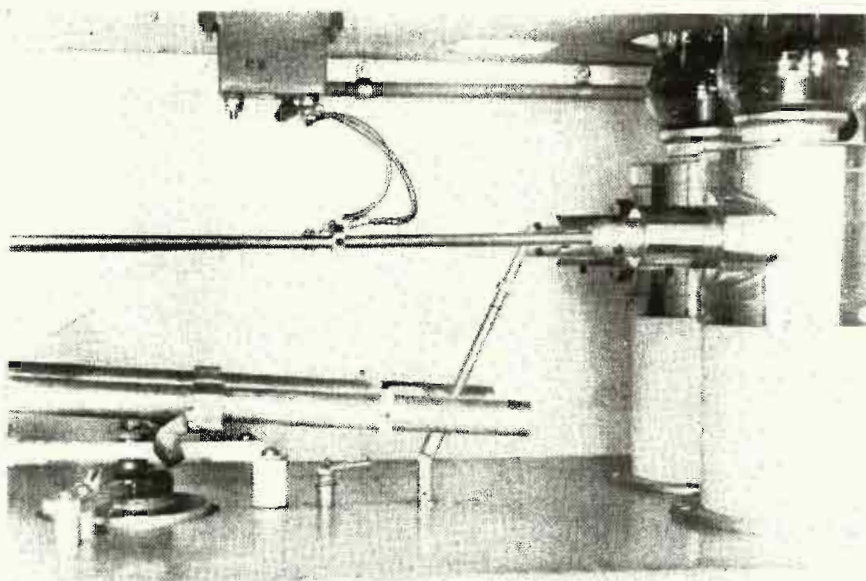


Figure 2
Position of the plate tank and output circuit of the power amplifier

since a $i-f$ wobulator sweep is used, and a high impedance linear detector is employed to measure the amplitude response. The May installment Figure 3 (video amplifier) shows that series and shunt peaking is employed with damping across the series elements. L_1 , L_2 , L_3 , L_4 , L_5 and L_6 comprise the $h-f$ compensation. Adjustment is accomplished by varying the powdered iron slugs so that flat frequency response obtains out to at least 5 mc.

As previously stated, each stage

should be flat by itself in order to keep phase shift to a minimum. Figure 3 shows a typical setup for this measurement.

Testing the D-C Restorer: The function of the d-c restorer is to refer all composite video information to the bias level of the modulator. Circuit discussion of this element was reviewed under the section on the *Video amplifier-modulator* in the May issue article. The restoring characteristic may be measured at two points:

namely: (1) at the grid of the modulator, or (2) at the plate of the modulator. Figure 4 shows how a 'scope may be connected for this measurement. Since the end result of the restorer is to keep the sync peak at a constant bias reference in the modulated $r-f$ amplifier, it has been found desirable to measure d-c restoration at the plate of the modulator (in effect at the grid of the modulated amplifier). Connection to the 'scope must be made directly to the deflection plate since the d-c component is the factor in question. With no video signal, the beam on the 'scope is adjusted for center position by means of the positioning control. Video signal is applied to the video amplifier and the peak sync position on the screen must remain at essentially the center position as adjusted above for proper operation. In case the beam is deflected off the face of the cathode-ray tube, an external positioning bias is required which will equalize the static potential. It is important to note that this removes the 'scope chassis from ground potential; therefore, no direct ground connection should be made where external positioning is required.

R-F Passband Characteristic: The $r-f$ passband characteristic is measured on the master² series transmitter by means of a built-in $r-f$ wobulator whose frequency range is ± 5 mc about the carrier frequency. Diode pickup sampling circuits are installed in the plate circuit of the modulated amplifier, cathode circuit of the intermediate power amplifier, cathode circuit of the power amplifier, plate circuit of the power amplifier, and in the transmission line output. A 'scope is provided to monitor any three of these pickup points simultaneously. Marker frequencies are provided by injecting the carrier frequency into the modulated amplifier grid circuit, and by inserting absorption type wave traps, tuned to high and low-frequency ends of the passband characteristic, in the plate circuit field of the modulated amplifier. Figure 3 (May article) shows how switch S_1 connects the modulated amplifier grids to either regular $r-f$ drive or wobulator drive by means of relay K .

Initial Adjustments

After initial adjustment of the $r-f$ stages is accomplished, only a few minutes are required to check performance or compensate for tube replacements, etc. Initial adjustment, however, requires a fundamental ap-

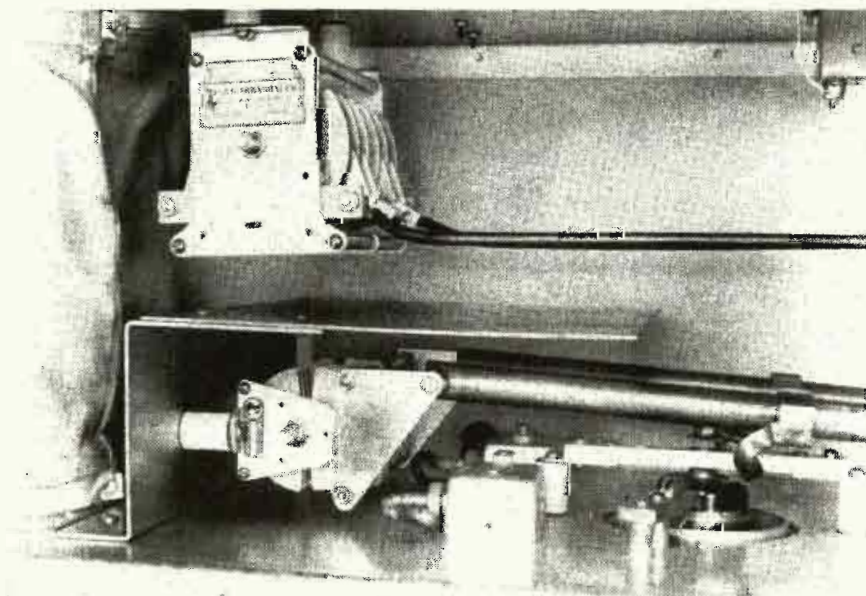


Figure 2
Another view of the plate tank and output circuit of the power amplifier.

² Du Mont 208 can be used for this application.

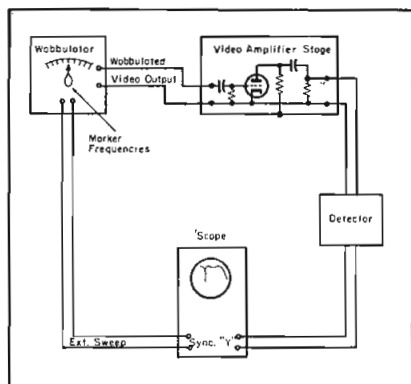


Figure 3

Setup of wobbulator and video amplifier used to determine frequency response.

proach to the problem as previously described. The coupling between stages is reduced to a minimum, and gradually increased until a double hump response is obtained with the low-frequency peak adjusted to carrier frequency and the high-frequency peak to approximately 3 mc higher than carrier frequency—these conditions being observed on the wobbulator 'scope at the various pickup points. The cathode loading and coupling determine the frequency separation and flatness of the response characteristic—frequency separation is predominately affected by coupling, while flatness is a function of loading. Loading is varied by adjusting the point of the cathode connection. Movement toward the open end of the resonant transmission line results in increased loading. A fine adjustment of this parameter is provided by the movable shorting bar—this factor also has an effect on coupling since the area of coupling is affected by its

movement. The foregoing procedure applies to the circuits between the modulated amplifier plate and intermediate power amplifier cathode, and *ipa* plate and *pa* cathode. The output circuit is tuned as indicated above, except that increased loading is accomplished by moving the transmission line connections toward the open end of the resonant line output circuit. Since three 'scopes are provided for observing three patterns simultaneously, any interaction between stages may be observed and corrected without the necessity for many retest checks. The diode samplers most useful for these adjustments are located in the *ipa* cathode circuit, *pa* cathode circuit, and transmission line output circuit. Figure 5 shows a typical passband characteristic for each of the three stages. The bandwidth was adjusted as shown in the first photograph. Curve *A* is the response of the input to the intermediate power amplifier. Curve *B* is the response into the power amplifier, and curve *C* is the response of the entire transmitter at the transmission line output circuit. The low frequency end of the sweep is at the left side. The marker shown up near the top of the bandpass characteristic represents 77.25 mc (for channel 5 operation). The second marker to the right represents 80 mc or a frequency deviation of 2.75 mc. The third marker to the right represents a frequency of 81.5 mc or a deviation of 4.25 mc from carrier. It will be noted that on the extreme left of each curve there is a vertical line. This is caused by the

"Du Mont.

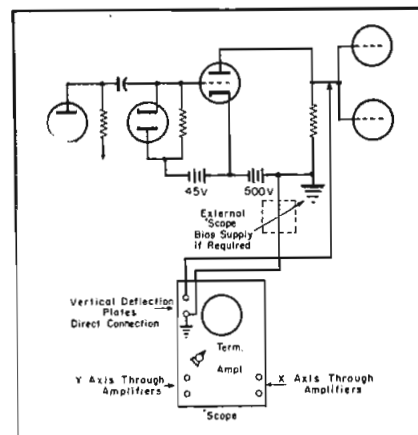


Figure 4

Typical measurement arrangement for determining d-c restorer operation.

lack of sweep over 75% of a revolution of the wobbulator motor. On the remaining 25%, the sweep is initiated and the indicated patterns result. It will be noted that the lower side of the response characteristic becomes more steep as it passes through the amplifiers resulting in adequate suppression of the lower sideband.


Plate-Bias Voltages

It has been desirable from theoretical and practical considerations to operate the class *B* linear amplifiers at a plate potential of 2500 volts with the bias adjusted to 140 volts. This setup allows for optimum transfer linearity, and low plate-to-plate impedance resulting in an efficiency of between 40 and 50% for a bandwidth of 3 mc across the top of the bandpass characteristic.

[To Be Continued]

Figure 5

Typical pass-band characteristics for each of three points of measurement. (In securing these curves, the transmitter was set up so that 5.04 peak kw was available at black level picture information). The curve at left (*A*) is the response of the input to the intermediate power amplifier. In the center (curve *B*) we have the response to the power amplifier, while the curve at the right (*C*) shows the response of the entire transmitter at the transmission-line output circuit. The low-frequency end of the sweep is at the left side. The marker (inked in) shown near the upper left of the bandpass characteristic represents carrier frequency. The second marker to the right represents a frequency deviation of 2.75 mc and the third marker to the right represents a deviation of 4.25 mc from the carrier. It will be noted that on the extreme left of each curve there is a vertical line; this is caused by the lack of sweep over $\frac{3}{4}$ of revolution of the wobbulator. On the remaining $\frac{1}{4}$ revolution, the sweep is initiated and the indicated patterns result.

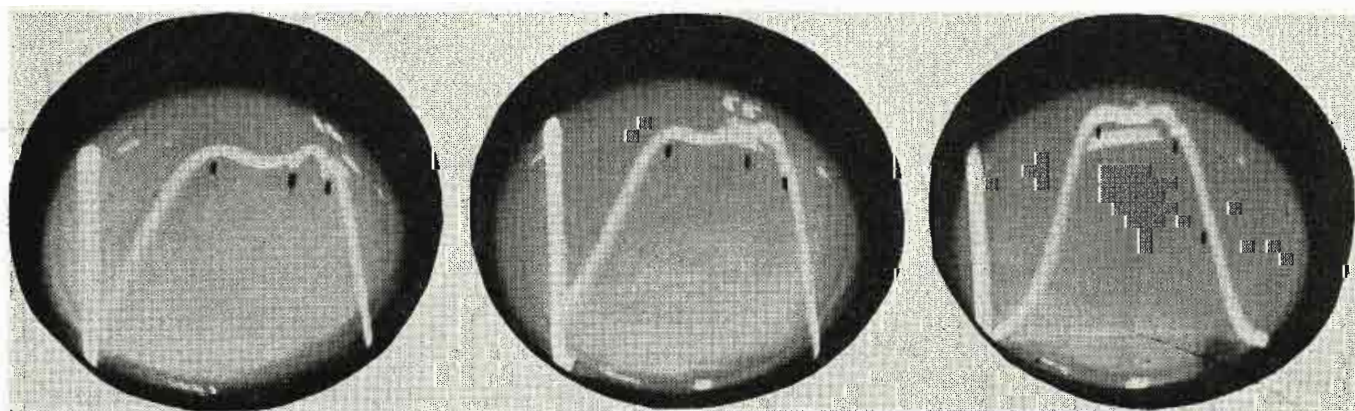

TUBE

Joint Army-Navy Electron Tube Committee Recommended
Subminiatures and Preferred Transmitting Tubes . . .
Vest Pocket Transmitter Using Subminiatures . . . Instant-
Heating Miniature Tubes

THE INCREASED USE OF PRINTED CIRCUIT techniques has emphasized the application possibilities of subminiatures, prompting the Joint Army Navy Electron Tube Committee to set up a recommended listing of these tubes for equipment design guidance.

In this listing we find the 6X512AX, with an E_c of .625, recommended as an audio pentode and for video and power work, and the 5644, also with an E_c of .625, recommended as a voltage regulator.

Eleven types with an E_d of 1.25 appear in another recommended group: The 5676 and 5677 as triodes; 2E31 and 5678 as sharp pentodes; 1Q6 and 2E41 for diode pentode application; CK503AN and CK506AN as audio pentodes; 1C8 as a converter, and VN21 and 5642 as rectifiers.

In the 6.3-volt category there are twelve recommended types: The 5N1006, 5645, 5718 and 5719 as tri-

odes; 5633 as a remote type pentode; 5634 as a sharp pentode; 5638, 5639 and 5640 as audio pentodes; 5X946 and 5X977 as rectifiers and the 5643 as a thyratron.

Subminiature Tube Transmitter

An interesting application of some of these tubes appears in a recently developed Bureau of Standards miniature crystal-controlled a-m transmitter with an output of 4 milliwatts; Figure 1.

Employing some of the latest miniaturization and printed circuit techniques, the transmitter, whose dimensions are 5 1/4" x 3" x 7/8", was designed for speech transmission on 6,575 kc.

The transmitter has a crystal oscillator, with a CK569AN operated as a triode driving a CK569AN pentode amplifier. The speech amplifier, with a gain of about 1,500, uses three resistance-capacitance coupled stages, with

two CK512 AX pentodes and a CK506 AX pentode.

The speech amplifier is printed on both sides of a 1/2" steatite plate 1 1/8" x 2 1/4". Power is obtained from a 30-volt dry battery and one of the new 1.4-volt mercuric oxide cells. One-third of the volume of the entire transmitter is occupied by the battery power supply.

The antenna which telescopes within the case can be extended 15". A two-position switch in the filament current is located on the edge of the unit for convenient thumb operation. Batteries are replaced by sliding them out of the metal end of the case. With new batteries the total B current drain is approximately 2.1 ma. Standard 30-volt hearing aid batteries yield about 12 hours of continuous service. Since the filament current of 150 ma for 5 tubes places a heavy load on the mercury oxide cell, useful A battery life is limited to 2 hours continuous operation.

The r-f output of 4 milliwatts provides reliable operation at distances up to 200 feet. This performance is obtained with the batteries operating at 80% of their nominal rated voltages. Greater distances of transmission may

(Continued on page 32)

Figure 1
Circuit of the Bureau of Standards vest pocket transmitter, using subminiature pentodes.



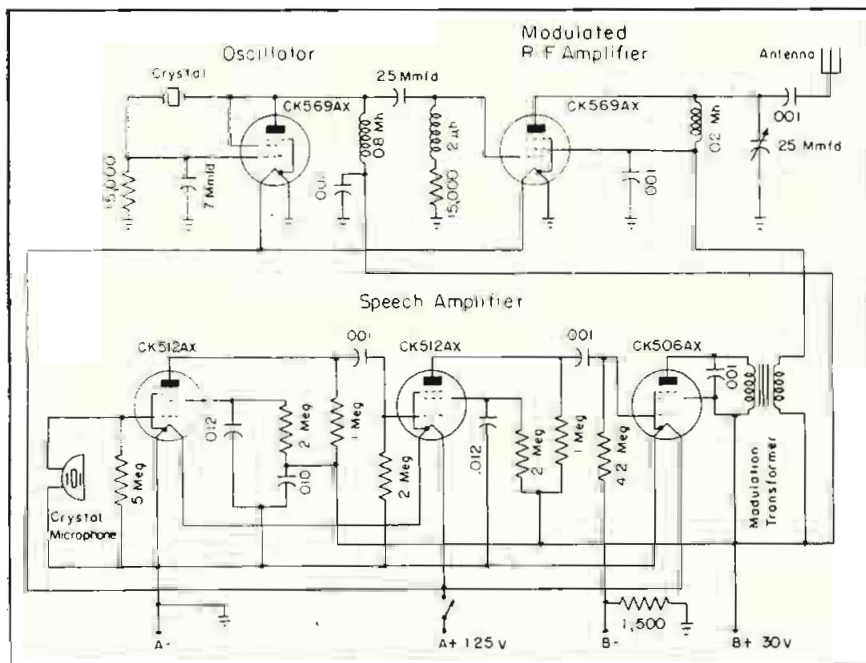


Figure 2
Front view of the 5-tube crystal-control miniature transmitter.

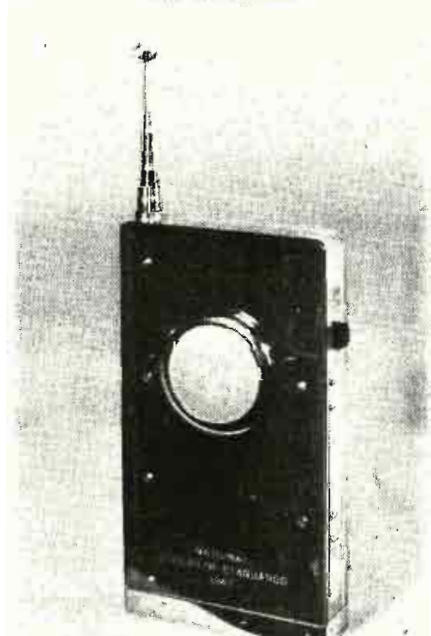

RCA Type WX-2A
540-1600 kc.
Price \$575*

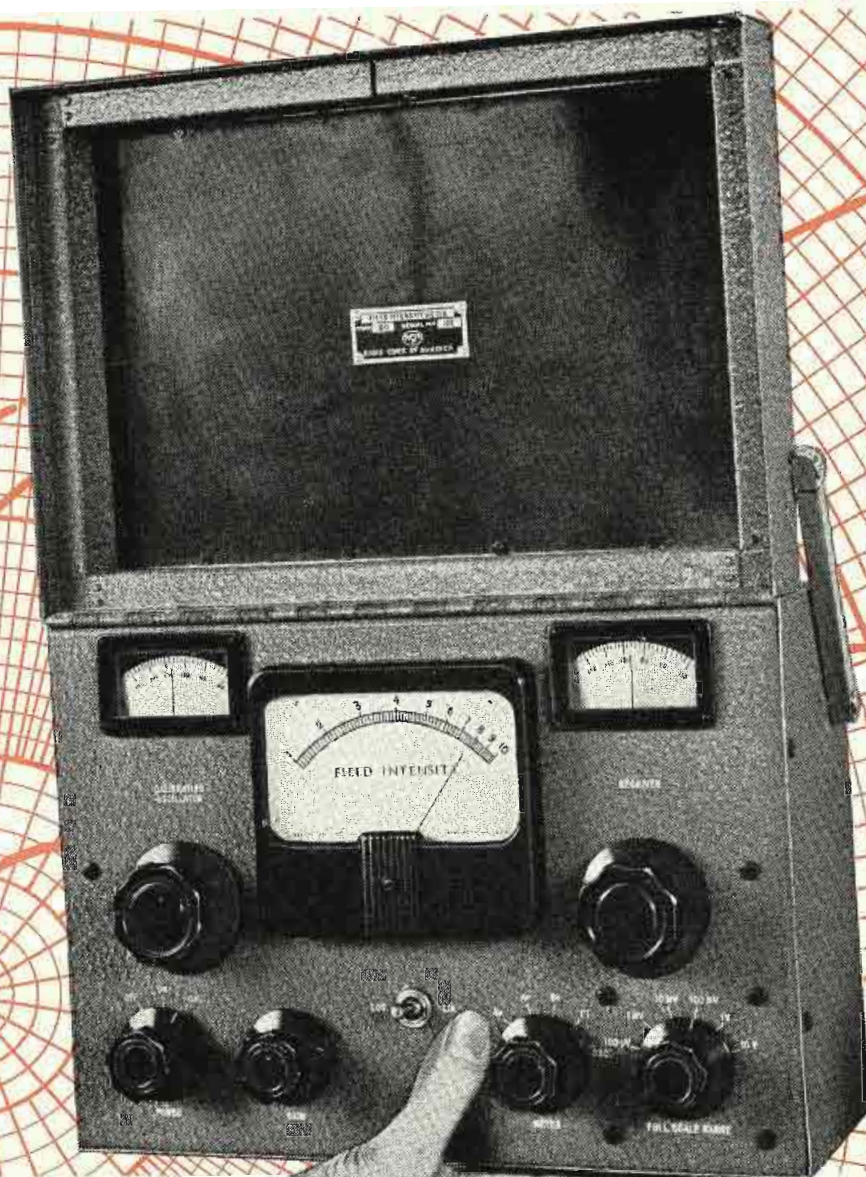

At Last—

The new Portable Field-Intensity Meter, RCA Type WX-2—shown one-third actual size. A loop antenna is built right into the lid!

a truly portable Field-Intensity Meter

● Weighing only 12½ pounds—including batteries, here's a small, compact field-intensity meter of high accuracy that carries around like a portable radio . . . and operates almost as simply. You tune in a signal, adjust a *built-in* calibrating oscillator and receiver gain . . . and *read signal intensity directly in microvolts-per-meter*. No charts, curves, or correction factors to worry about. No computations to make.

Designed with a wide sensitivity range of 10 microvolts/meter to 10 volts/meter, Type WX-2A enables you to make field-strength readings anywhere—from the very shadow of your transmitter, to the toughest location "down-in-the-

*Subject to change without notice.

noise." Plenty of front-end selectivity, too. Loop antenna Q is approximately 100 at one megacycle; An r-f amplifier stage provides a very high order of image rejection.

Power supply; Ordinary flashlight dry cells for the quick-heating tube filaments—and a 67-volt battery of the size used in camera-type radios for the B supply.

A lot easier now to get the facts on your coverage, service area, and antenna efficiency . . . with RCA's new portable WX-2A. Ask your RCA Broadcast Sales Engineer for the facts. Or write Department 23-G, RCA Engineering Products, Camden, New Jersey.



BROADCAST EQUIPMENT
RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.

V-H-F Railroad Radio Link

With Six-Channel Telephone Carrier System


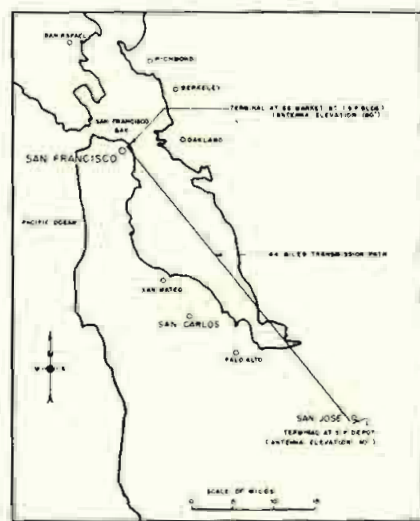


Figure 1

Map of San Francisco Bay area showing the 44-mile transmission path involved in the Southern Pacific Railroad carrier link.

Figure 2

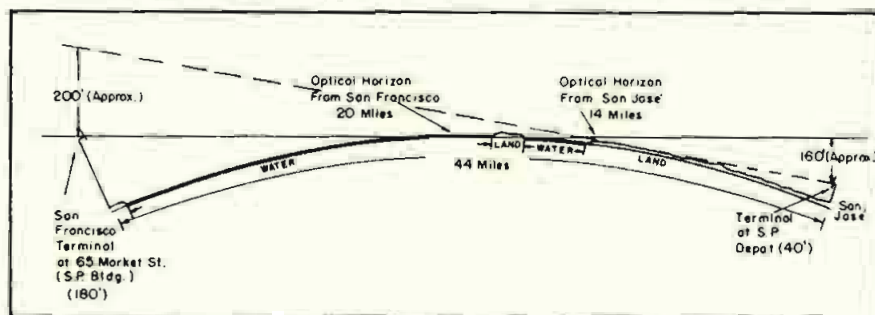Profile of the San Francisco to San Jose link used in the carrier multiplex tests.



LAND LINE OPERATORS in a number of industries are faced with a double problem:

They are handling growing traffic loads with limited facilities while confronted with sharply increased costs, both for new construction and maintenance of existing lines.

Thus railroads, petroleum pipe-line companies, airports, power utilities and telephone systems have had to seek additional methods of increasing their traffic-handling capacity. Many in these fields have already taken the step with multiplex carrier telephone and telegraph installations.

Now, a great deal of interest is being focussed on the possibility of creating superior, low-cost circuits with new forms of highly-directional point-to-point v-h-f radio links. An extremely successful test using such a link system was conducted recently by Southern Pacific between its office in San Francisco and San Jose, a distance of 44 miles, employing 160-mc equipment.

Equipment Used

An f-m setup¹ was used with bandwidth modifications to accommodate the 200-to-24,000-cps requirement of the carrier. Receiver was a crystal-controlled double conversion superhet with a sensitivity of 0.5 microvolt.

Simultaneous six-channel non-inter-

fering transmission was accomplished through the use of a single-sideband system.²

Five of six channels were used for telephone service and the sixth was utilized for transmission of five pulse signaling and two teletype channels operating on sub-channel carrier frequencies in the voice-frequency range. (Sixteen sub-channels can be impressed on one voice channel with this equipment.) Voice-frequency signaling channels are rated at transmission speeds up to 15 pps for dialing service, but in this case were arranged to provide ringdown signaling for the voice channels.

Telegraph transmitters and receivers used for teletype operation were operated at 1,625 and 1,775 cps. Signaling frequencies of 1,945, 2,125, 2,295, 2,465, and 2,635 cps were used for the five pulse signaling sub-channels.

Transmitting Setup

In the transmitting branch of the system, incoming voice-frequency currents enter the terminal and are amplified in a limiter amplifier. The output of this amplifier goes through the low-pass section of a transmitting-line filter to the transmitting-line circuit

and becomes the voice-frequency channel.

Other voice-frequency currents enter the terminal at channel-modulator input circuits for the particular channels and are converted to carrier frequencies by their associated modem (*modulator-demodulator*) panels. These panels function as inert frequency-translating devices and include filters, output-level adjusting pads, and varistor-type modulators actuated by carrier-frequency voltages from the carrier-supply panel.

Carrier-frequency output circuits of modem panels for all odd-numbered channels are wired in parallel and connected to one side of the center-tapped winding of the transmitting differential transformer. Similarly, all carrier-frequency output circuits for modem panels of even-numbered channels are wired in parallel to the other side of the same winding of the differential transformer.

This transformer is arranged as an unbalanced hybrid transformer to provide decoupling, for impedance reasons, between the two groups of modem panels. It serves to combine all the carrier currents in the input circuit to the transmitting h-f amplifier. This amplifier operates at a normal gain of 42 db and an output transmitting level of +4 dbm per channel.³ Amplified carrier currents go to the transmitting-line circuit through the

¹Sperry Gyroscope Co., RCU-1.

²System used in type 42 Lenkurt Carrier equipment.

³0 dbm equals .001 w in 600 ohms.

high-pass filter section of the transmitting-line filter.

Receiving

In the terminal receiving branch of the carrier equipment, incoming voice frequencies pass through a low-pass section of the receiving-line filter and are amplified by a voice-frequency amplifier. This amplifier operates at a normal gain of 20 db and has an output level of +4 dbm. The signal is then fed to channel 1 terminating equipment on a four-wire basis.

Incoming carrier frequencies go through the high-pass section of the receiving-line filter and to the receiving high-frequency amplifier at an input level of -38 dbm. This amplifier operates at a gain of 42 db and an output level of 4 dbm per channel. It passes the carrier currents to the primary of the receiving differential transformer which provides decoupling for the carrier-frequency sides of the modems used as channel demodulators.

Here the modems function in a manner opposite to those in the transmitting branch. They serve to select and convert the carrier frequencies for each channel to voice frequencies which next go to the terminal demodulator output circuit. En route they pass through a channel-level adjusting control and amplifier having 29-db gain. Again, the varistor-type demodulators

Southern Pacific San Francisco to San Jose 44-Mile Link Employs Duplex Radio (158.19 Mc and 154.57 Mc) and Six-Channel Setup for Intra-Company Telephone and Telegraph Service. Six-Channel System Provides Five for Telephone and the Sixth for Pulse Signalling and Teletype Work.

by **PHILIPS B. PATTON**

Engineer
Lenkurt Electric Company

are actuated by carrier-frequency voltages from the carrier-supply panel.

Frequencies

Frequency characteristics of an average transmitting channel are shown in Figure 5. This curve is representative of all channels, any variation usually being less than 1 db over the important part of the frequency range. Receiving-channel characteristics are approximately the same.



In Figure 6 appears the frequency allocation for a carrier system, showing the spectrum up to 35-channel

capacity. Channel 1 is a voice-frequency channel with frequencies from 200 to 3200 cps transmitted directly. The carrier-frequency band used for channel 2 is obtained by modulation with a 7.8-kc carrier, the lower sideband being used. The upper sideband of an 8.2-kc carrier is used for channel 3.

Two stages of modulation are used to obtain carrier currents for channels above the third. Channel 4, for instance, is derived through preliminary modulation of voice frequencies at 8.2 kc to produce an i-f band B, which is the upper sideband of 8.2 kc. This

Figures 3 (below) and 4 (right)

Figure 3: Carrier installation in the San Francisco communication headquarters of Southern Pacific. Entire terminal unit is in the right hand rack. The telegraph, measuring and auxiliary units are in the second rack. Figure 4: Block diagram of carrier terminal equipment.

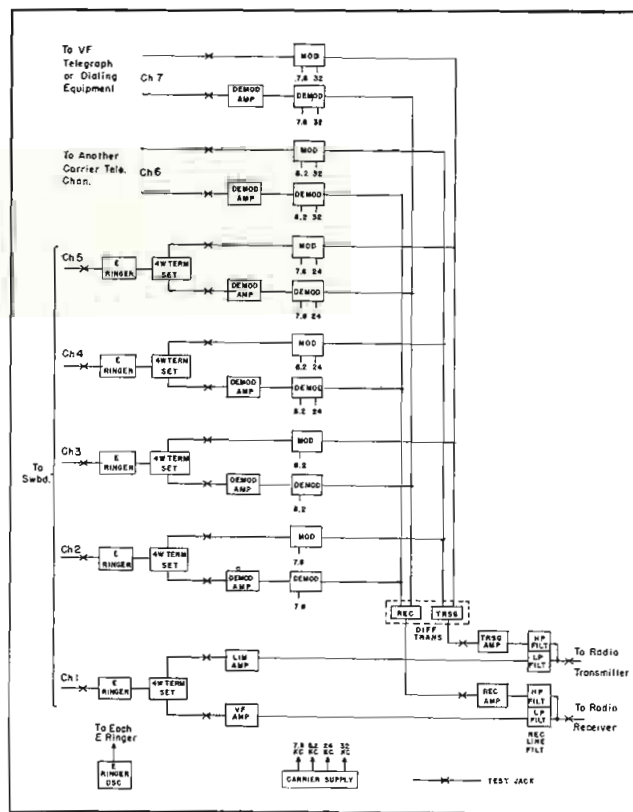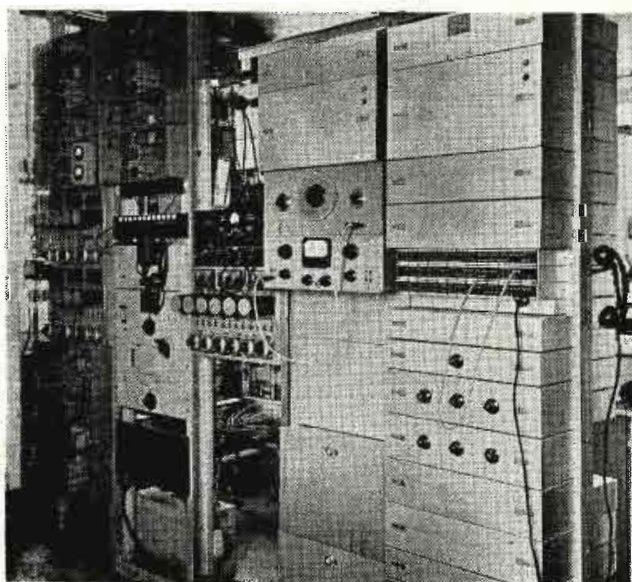




FEDERAL

BROADCAST EQUIPMENT

**... An Outstanding Line Offering
Finest Performance and Real Economy**

In standard AM and FM transmitters...TV transmitters for low or high band operation...square loop antenna...special new developments including Studio-to-Transmitter Links...Dummy Antenna...TV Monitors... High Power Transmitting and Rectifier Tubes.

You can count on Federal Broadcast Equipment—from a complete system to an individual installation. Federal Broadcast Equipment brings you the latest in engineering technique and practice... high quality of materials... precision craftsmanship of the highest order. There is real economy in both initial cost and operation. And you are assured of the finest performance, because Federal sees every job through. This Federal policy upholds a reputation established by more than 38 years of continuous achievement in the radio transmission field.

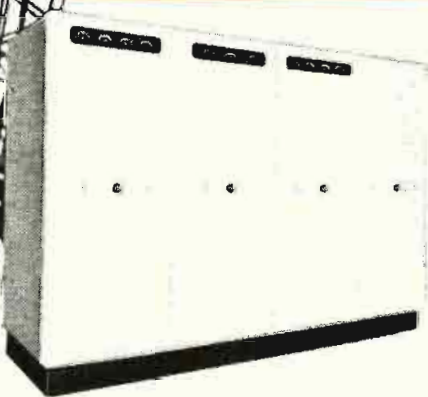


FEDERAL'S FM 10 KW Transmitter, officially approved by the FCC, has the exclusive "Frequency-Matic" FM Modulator. It reduces distortion and noise well below RMA specifications, and stabilizes mean carrier frequency within 0.001 per cent of assigned value. This transmitter combines outstanding fidelity with economy, accessibility and highly dependable performance.



FEDERAL'S Transmitting Tubes provide long service. They stand up under severe operating conditions, and maintain original characteristics for life.



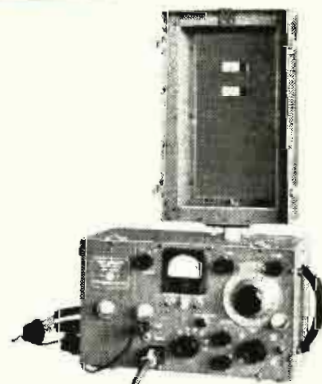FEDERAL'S TV Monitor meets all FCC requirements. Designed for long service life, it accurately measures video carrier frequency, and monitors sound carrier and modulation.




FEDERAL'S Field Intensity Meter accurately measures signal intensity of AM broadcasting stations whether in the standard band of 530-1600 Kc—200 to 400 Kc—1600 to 3600 Kc—or 3600 to 7000 Kc. This 29-lb. unit is portable.

HIGHEST GAIN IN THE FIELD WITH FEDERAL'S SQUARE LOOP ANTENNA. In many installations from coast to coast, this design is producing an effective radiated power of as much as twelve times the Kilowatt rating of the FM transmitter. This means new power and new range for better and wider service. Federal's Square Loop Antenna also brings you simplicity of mechanical and electrical design... greater accessibility for maintenance... no operational tuning... maximum lightning protection... immediate delivery and ease of installation.


Federal's Studio-to-Transmitter Link for High Fidelity Program Transmission

Here's the new Federal microwave system to eliminate S-T wire and cable circuits. Combining outstanding fidelity — distortion less than 1% over 50-15,000 cycles — low noise level, 65 db below 100% modulation — and a 35-mile "line of sight" range — this system complies with all applicable FCC regulations for good engineering practice. Link consists of a transmitter, receiver and two standard 6-foot parabolic reflectors (4- or 8-foot reflectors supplied on request).

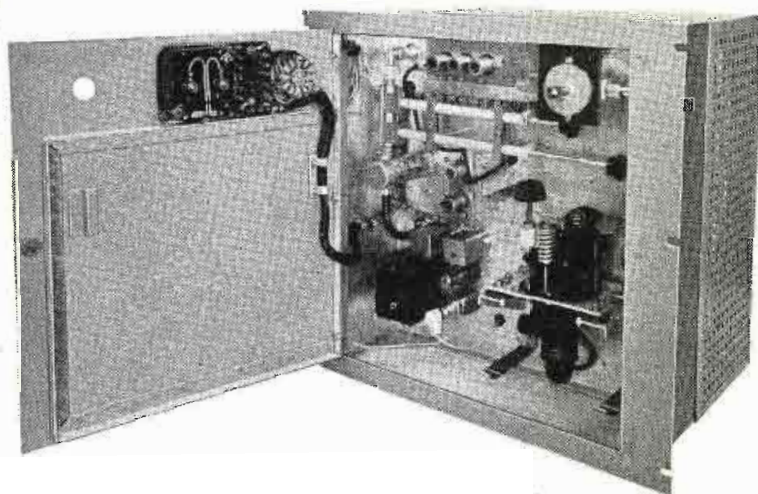**ONE OF MANY NEW DEVELOPMENTS BY
FEDERAL TELECOMMUNICATION LABORATORIES**



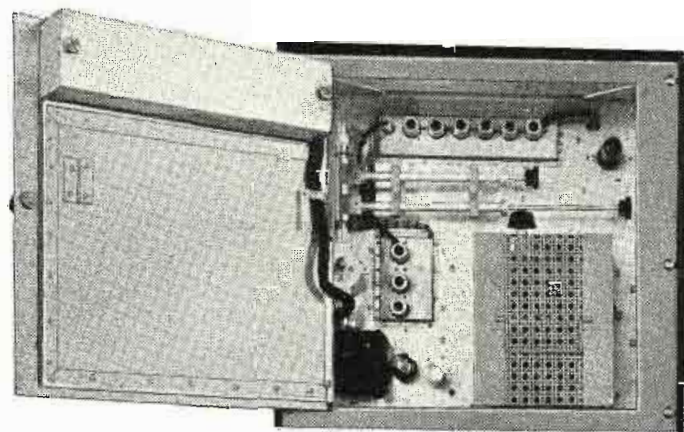
TRANSMITTER employs advanced-design direct frequency modulation and crystal-controlled klystron power oscillator. Complete monitoring facilities include frequency and power measurements, aural monitoring, and vacuum tube metering. Designed for mounting on standard 19" relay rack, it is only 35" high and 13" deep.




RECEIVER is a single superheterodyne which utilizes reflex-klystron local oscillator. It features pre-selection to reduce possibility of spurious interference. Relative stability is maintained within 0.01 per cent with automatic frequency control. Metering is provided for all vacuum tube circuits, carrier level, and crystal current. Same mounting and size as transmitter.



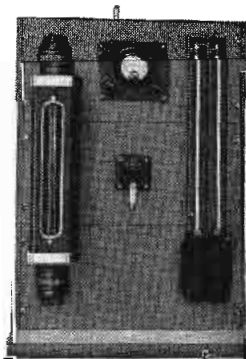FEDERAL'S De Luxe Studio Console combines control of all facilities of an FM transmitter into one unit—a "nerve center"—convenient, foolproof, and handsome in appearance.



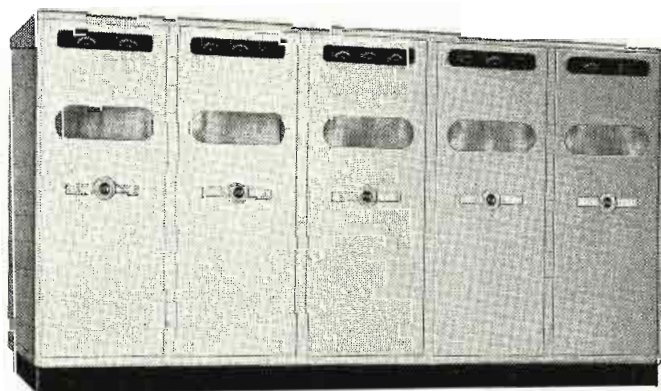FEDERAL'S All-Metol Dummy Antenna meets the need of the Broadcasting Industry for testing of high power, VHF and microwave (FM and TV) transmitters. No conventional resistors and insulators. Compact, light, water-cooled — determines RF power accurately.



FEDERAL'S Standard 5KW AM Broadcast Transmitter assures high fidelity performance and maximum operating efficiency. Nominal output of 5KW can be transferred instantaneously to 1 KW. Every component is conservatively operated. Every circuit is engineered for maximum life of its elements. A new simplified power supply reduces maintenance to a minimum. Standard operating band.




Federal Telephone and Radio Corporation

100 KINGSLAND ROAD, CLIFTON, NEW JERSEY

KEEPING FEDERAL YEARS AHEAD... is IT&T's world-wide research and engineering organization, of which the Federal Telecommunication Laboratories, Nutley, N. J., is a unit.

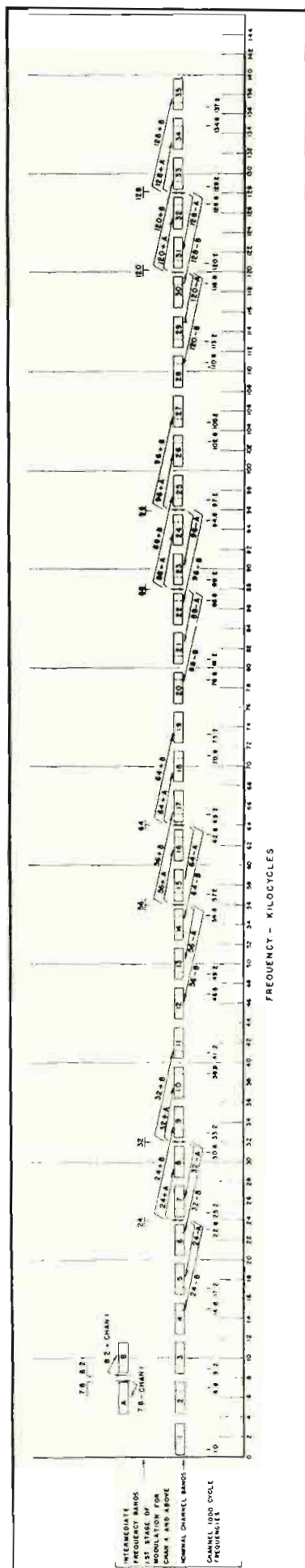In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp. 67 Broad St., N. Y.



group of intermediate frequencies is next modulated at a carrier frequency of 24 kc with the lower sideband selected for transmission in the frequency range from 12 to 16 kc.

All other carrier-frequency channels are obtained through preliminary modulation at 7.8 or 8.2 kc, to obtain i-f bands *A* or *B*, followed by modulation at higher carrier frequencies for final positioning. This procedure permits simplification of electrical wave filters used to separate the channel frequencies; reduces the number of different carrier frequencies required for modulation and demodulation; and allows uniform spacing of all channels at 4-kc intervals.

Radio Transmission

In the Southern Pacific installation, one of the duplex radio circuits operated on 158.19 mc, while the other was on 154.57 mc. The six channels called for uniform frequency response from 200 to 24,000 cps. Before the carrier was installed, tests were made on the 158.19-mc channel. A 1,000-cps tone was used to modulate the San Jose transmitter and graphic recorder⁴ was used to study the received-signal level. Higher noise levels at the San Francisco end suggested this procedure. Over a 100-hr period the signal-to-noise ratio was 40 db or more.

Investigations made with a wide range of antennas disclosed that the most effective design within the limits of practicality is a 16-element array consisting of eight half-wave elements in phase and eight reflectors, vertically polarized. Horizontal polarization

showed noise advantages, but more fading prevailed.

Noise at the San Jose terminal was primarily caused by the fact that trucks, buses, and automobiles entered directly into the station enclosure close by the antenna. At the San Francisco end the receiver was adjacent to elevator controls in the Southern Pacific Building where large and frequent arcs were being broken.

The radio equipment was modified in two ways to adapt it to carrier operation. Frequency response was widened to give a level variation less than 1 db within each 4-kc channel from 1 to 20 kc. Between 1 kc and 300 cps, response fell off 2 db, while a drop of 3 db appeared from 20 to 30 kc. To offset the increased noise level produced by the band widening, external r-f power amplifiers were added to the basic sets. These increased transmitting power to about 100 watts. They each used a pair of 4E27 pentodes and had 52-ohm coaxial input and output leads so the standard transmitter could be used as an exciter.

Two units were operated at each terminal, one as a transmitter and one as a receiver. Not only did this relieve the power supplies of an overload, which would have resulted from simultaneous operation of both the transmitter and the receiver in a single unit, but it also provided good shielding between units and avoided possible blocking of receivers in duplex service.

Operation

An input level of -10 dbm produced 100 per cent modulation of the transmitter. Accordingly the carrier equipment was adjusted to provide -15 dbm.

(Continued on page 33)


*Festerline Angus.

Figure 6

Frequency allocation chart of carrier equipment, detailing the assignments up to a 35-channel capacity.

Figure 5

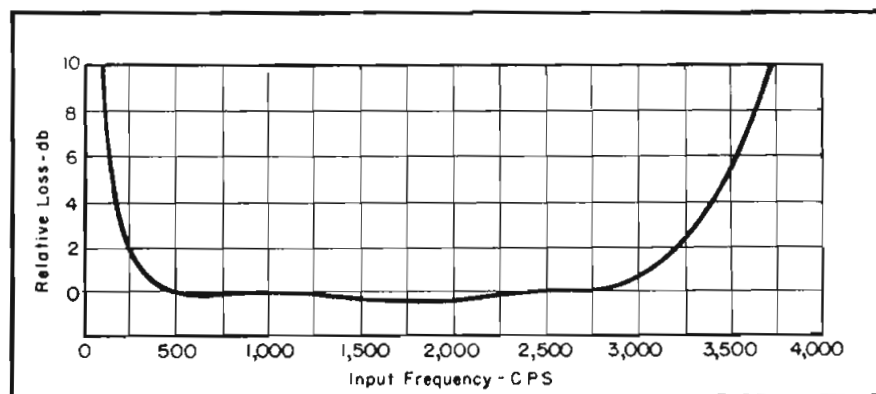Frequency curve of an average transmitting channel. This reverse type of plot is typical of the telephone type curves prepared to show attenuation characteristics.



NOISE Measurements

IN MAKING PRECISE measurements indoors the reflected sound energy has another aspect that may appreciably affect the results. The walls of any room will reflect more or less sound, depending on the sound absorptivity of the materials with which they are surfaced. Except in rooms especially treated with a highly sound-absorbent material, the reflected or reverberant sound is often quite high and will tend to obscure the direct sound radiated from a source. As mentioned before, the direct sound decreases in intensity approximately inversely as the square of the distance from the source, while the reverberant sound in a room is independent of the distance but decreases as the absorptivity of the room and its volume increases. Thus in small, live (reflective) rooms, the reverberant energy, at points well removed from the source, may be appreciably higher than the direct energy. This introduces an error in the measurement of direct sound which, under many conditions, may be serious.

Figure 1 shows the approximate relationship between the direct and reverberant sound in the specific room for which these curves were calculated. The diagonal line represents the direct sound, which is shown decreasing inversely as the square of the distance from the source; that is, as the distance of the microphone from the source is doubled, the direct sound energy falls to one-fourth of its original value, or drops 6 db in level. The reverberant sound, which when thoroughly diffuse, is constant, regardless of the position of the microphone in the room or its distance from the source, is represented by the dotted horizontal line across the middle of the drawing. The sum of the direct and reverberant sound, which is the intensity the sound meter would measure, is shown by the curved line asymptotic at both ends to the lines representing the direct and reverberant sound. These acoustic conditions are approximated in a room having an interior surface area of 3,000 square feet, with an average sound absorption coefficient of 50% over the audible frequency range.

It will be worth while to examine this drawing to see what would take

Concluding Installment¹ of Two-Part Paper Covers Measurements In Rooms, Studios and Plants, and Relationship of Direct and Reverberant Sounds.

by **ROBERT L. MORGAN**

Engineering Sales Manager
Norman B. Neely Enterprises

place in this room if noise measurements of some device, such as an electric fan, for example, were attempted. At a distance of one foot from the fan, the reverberant sound adds nothing and the sound meter would, therefore, read the correct level of direct sound. However, as the microphone is moved away from the source, the reverberant energy becomes a larger portion of the total and begins to introduce an error. For example, at 4', the total intensity is about 1 db above that of the direct sound only, which means a 1-db error in the measurement. At 7.7' from the source, the direct and reverberant sound energies are equal, so that their sum which the sound meter would measure, is 3 db higher than that of


the direct sound alone. At about 23', the error would be 10 db and would increase to greater values as the distance between microphone and source is increased.

It will be seen then, that in this particular room, it would be necessary to place the microphone not farther from the sound source than 4', to limit the error in measurement to 1 db. It would be inadvisable to attempt to eliminate this error by moving the microphone too close to the sound source. Such a procedure would only tend to favor one part of the noise-producing machine over another part and thus fail to give a good average reading.

It should be borne in mind that this distance of 4' and all of the information on Figure 1 applies only to this specific room, which has the area and average absorption given. If either

(Continued on page 35)

Figure 1
Approximate relationship between direct and reverberant sound.

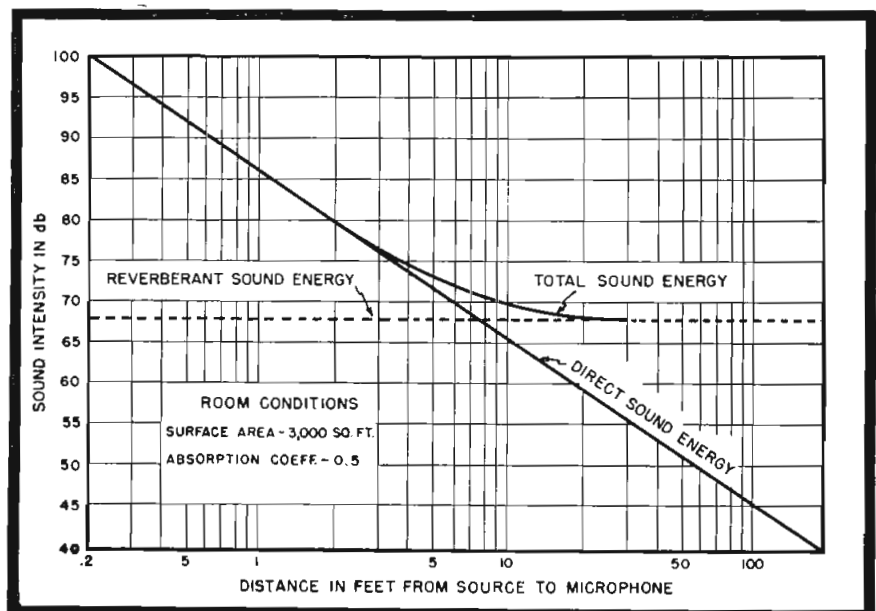

¹Initial installment appeared in the February, 1948, issue of COMMUNICATIONS.

Coaxial And Separate Two-Way Speaker System Design

Problems Encountered in Design and Production . . . Performance and Cost Considerations . . . Advantages and Disadvantages of Ring and Slab Magnets . . . Horn Flare Considerations . . . Horn Cells . . . Crossover Selection . . . H-F and L-F Units . . . Cabinetry.

by **HOWARD SOUTHER**

Stephens Manufacturing Corp.

IN THE FORMATIVE STAGES of any art, development is guided by theory. As the art progresses, direct application begins to mold the processes of production. An example of this phenomenon has been the genesis of the coaxial 2-way speaker from the well-known theater 2-way systems employed for well over a decade in motion pictures. This birth and development of the coaxial units from the separate systems has promoted advances benefiting the parent design. Costs of production have been reduced, promoting wide acceptance. Performance of both types of speakers has been improved.

Present Status Of Development

In standard type speakers the single diaphragm commonly used must attempt to reproduce faithfully a tone range of over 8 octaves or 30 to 16,000 cps.

This means that the voice coil attached to the single cone must try to move in and out through the dense flux area of the pole piece as far as $\frac{3}{8}$ of an inch on low tones. It must also attempt to vibrate very rapidly over short distances on high notes. To convert bass pulses to acoustic energy efficiently, the diaphragms should be large, and to vibrate rapidly and generate treble tones easily it should be small.

Accordingly a two-way system utilizing two driving units is extremely effective, since we have one unit large in size designed for the range of the first one-half of the audible spectrum, and another unit small in size, which generates the rapid pulses of the remaining tone range.

In addition, it should be noted that bass tones are easily heard throughout

the listening area. They act like the waves at the seashore, spreading around intervening objects and flowing out to the listeners on a broad angle. High tones speed like a bullet from a gun in a single direction straight from the axis to the speaker.

For this reason two-way speaker systems provide a nest of dispersing cellular horns as a complement of the high frequency unit. In this manner the higher frequencies are spread through a horizontal and a vertical angle, covering the listening area almost completely.

In Figure 1 appears an illustration of a typical two-way system with a peak-power handling capacity of 80 watts. Usual application will find the unit operating within a range of from 5 to 40 watts. In constructing this unit, the minimum area across the horn opening (70") was computed on the basis of one-fourth wavelength of the lowest frequency to be reproduced—30


cycles. The same holds true for the high-frequency speaker, the horn openings of which provide a cut off at 400 cycles on the same basis.

In average size theaters speaker power capacity is 40 watts peak, and normal levels resolve themselves into the region of 3 to 25 watts. Design is the same as that of the unit shown in Figure 1, but with one-half the number of components.

Figure 2 shows a smaller two-way system with one-half the power. Overall efficiency is 6 db less than for the theater system, an appreciable drop in acoustic conversion power. Space saved over the theater system is due in the main to use of the reflex baffle. Although these baffles are not peculiar only to two-way systems, they have been found necessary for optimum operation where vast amounts of space are not available. Design is such that the resonant period of the enclosure covers a broad band in the lower part of the spectrum, and a release port near the cone opening allows in-phase pulsations to reinforce the frontal wave. The high frequency horn cuts off at 800 cycles. This higher cut-off allows the horn configuration shown to be confined within an 11" height and 14" width.

In Figure 3 appears an example of a 20-watt coaxial type of two-way reproducer. The high-frequency unit feeds eight dispersing cells through the pole piece of the cone speaker. This unit is 3 db lower in efficiency than the Figure 2 separate two-way system.

Figure 1
An 80-watt separate two-way theatre system.

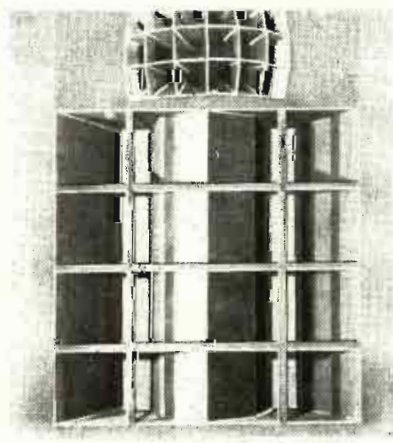

Performance And Cost Consideration In Coaxial Design

The physical design of a coaxial unit is illustrated in Figure 5. It will be noted that one magnet structure supplies flux for both gaps of the individual speakers. The diagram illustrates also the flux path and the use of a shunt around the high-frequency gap to more densely saturate the low end.

Ring And Slab Magnets

The use of ring magnets has been found technically more advantageous, because greater contact area is possible. From the practical standpoint,

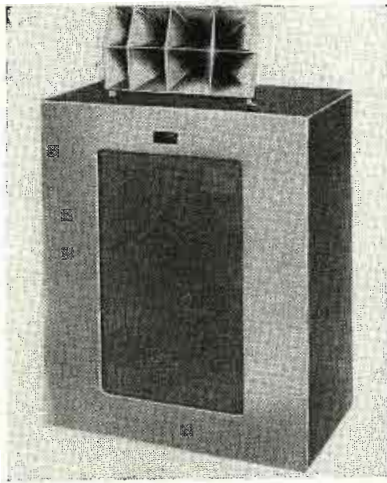


Figure 2

A 40-watt separate two-way system (43" x 23" x 15").

however, much less leakage results from the slab magnet construction due to the longer leakage path it is possible to incorporate. Present magnet production technique allows for less costly manufacture of slab structures. The use of Alnico five is, of course, mandatory; incontrovertible superiority of over three times that of the next best alloy is illustrated in Figure 6. We are excluding a platinum alloy from the argument as being totally impractical from the standpoint of cost.

Horn Flare Considerations

The exponential flare has for some time been considered the ideal design for coupling the acoustical energy from the generator at high impedance to the outside air which offers a considerably lower impedance. The formula governing the rate of flare discloses a startling feature. At frequencies above cut-off, velocity and pressure are exactly in phase, resulting in no movement of air in the horn, which in turn precludes the possibility of reflections. However, this is not strictly the case. We know that sound, even below theoretical cut-off frequency, is propagated along its length in appreciable quantity. This is due to approximations in the formula which includes no allowances for the varying speed of sound at different altitudes, the impossibility of present generators to be joined perfectly in an acoustic fashion to the horn throat, lack of control of back-pressures in a broad frequency band near the region of cut-off, and others.

Modified Exponential And Straight Exponential Flares

From the practical aspect, these facts would tend to minimize the importance

of adhering closely to the exact rate of flare called for by formula. If this point is conceded, an obvious advantage possible through a change in this flare rate presents itself. A broader flare at the mouth of the horns would allow for a more spherically emitted wave shape, resulting in cleaner response because of less discontinuity, and in a shorter horn than would otherwise be required. Horns have been designed for high-frequency units utilizing an exponential flare for three-fourths of their length, and making an easy transition into a much greater flare rate computed from a Bessel function for the remaining fourth. Measurements have revealed no loss of efficiency; in fact, a gain in efficiency has been found in several models produced.

Choice of Horn Cell Configuration

Because there exists a huge potential market for coaxial two-way loudspeakers in the receiver manufacturing field, a study has been made to determine the minimum number of cells required to effect adequate coverage under the conditions in which most receivers are used and placed in the home. It was found that coaxial speakers in widespread use were in the main limited to application in sets costing a thousand dollars. Such sets were of a size which precluded corner placement in the room, which would decrease dispersing requirements.

It has been found that a single cell covers an angle within the limits of 20°. One hundred per cent direct dispersion of high frequencies, therefore, would call for nine cells in the horizontal plane. But it is neither practical from a design consideration, nor necessary from the listener's viewpoint, to be able to hear direct high

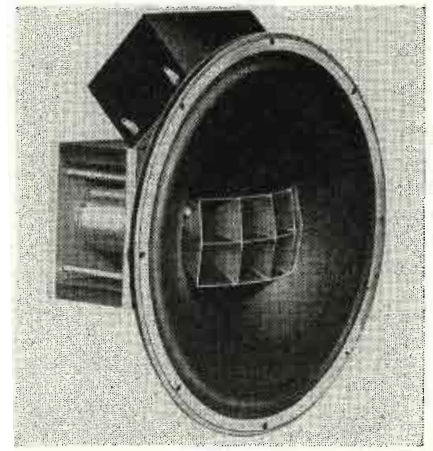


Figure 3


Coaxial type 20-watt speaker, frame diameter 15".

frequencies more than 60° off the axis. If the size of the cone opening would allow, it would be ideal to mount a horn nest with a 2 x 6 configuration. But within the limits of the size of the design, 2 x 4 is currently the maximum. This allows for 80° horizontal and 40° vertical dispersion, covering 90% of the normal listening area.

Crossover Selection

In Figure 10 appears a plot of the acoustic action of a cone radiator operating below 1500 cycles. At these frequencies the cone operates in the main as a piston; i.e., the motion is largely linear. In the diagram the cone is mounted on a straight baffle, and if we treat the cone interior as a pressure area, we find the formation of the spherical wave shape required for efficient coupling and minimum discontinuity. In Figure 11, illustrating the acoustic action of a cone radiator above 1500 cycles, we note that due to the large mass of the cone, consequent inertia prevents rapidly oscillating

Figure 4
Response characteristics of coaxial speakers.

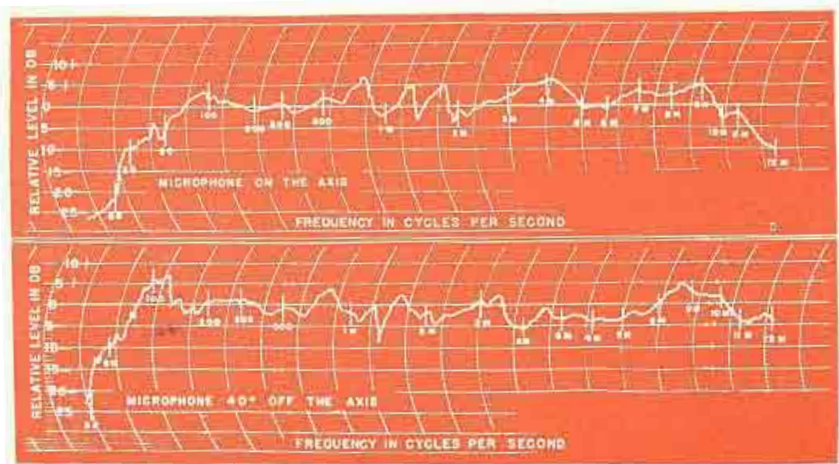

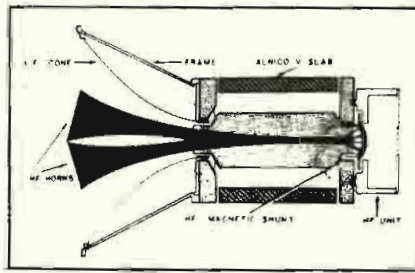


Figure 5
Coaxial unit design.

Figure 6
An illustration of the advantages and disadvantages of ring and slab magnets.

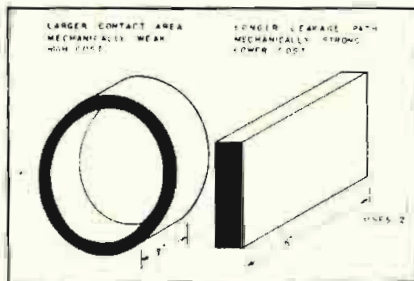


Figure 7
Demagnetization and external energy curves for permanent magnet steels: A , ampere turns per square inch (H) and B , energy in air gap per cubic inch of iron (joules) for Alnico 5 (A5), Alnico 4 (A4), cobalt steel 36% (CS-36) and Nipermag (NP).


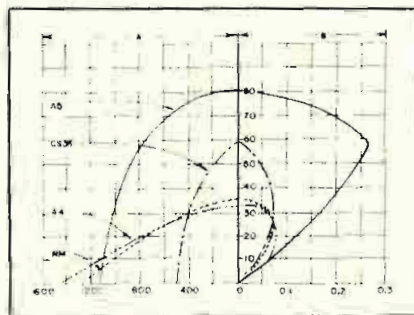


Figure 8
Comparison of modified exponential horn with a straight exponential flare

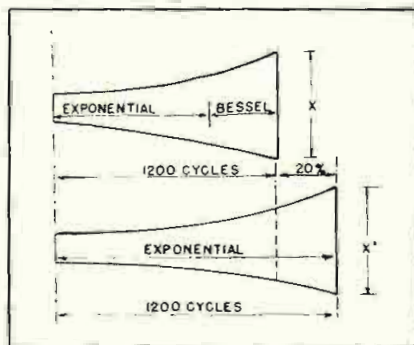

high frequencies from moving the entire cone. Extreme loss of efficiency, and, very important from the standpoint of quality, non-linear motion results causing phase cancellation, standing waves and a particularly bad form of quality impairment we may attribute to discontinuity of coupling. Stroboscopic observation has shown a gradual breakup in cones starting around 600 cycles indicating that in the region of 1500 cycles and above this matter becomes most serious.

Therefore, a crossover frequency of approximately 1200 cycles prescribes the upper limit of optimum design for present day speaker structures. In addition, the attenuation should be gradual. About 12 db per octave is considered good practice and is employed universally in the motion picture studies. Established practice suggests air-core coils to eliminate distortion. Metal cases and iron cores materially decrease the Q of such networks, causing the level to vary with frequency.

The High Frequency Unit

The high-frequency unit is a delicate mechanism. Tolerances are close. In order to be efficient, excursions as great as one-fourth inch must be allowed for in a unit as small as the 20-watt type. Full output at 1200 cycles puts a great strain on the leads from the voice coil attached to the diaphragm. Consequently lead failure has been the cause of 90% of all high-frequency troubles. In combating this problem, it has been found that $\frac{1}{8}$ " beryllium copper strips, soldered both with lead solder and aluminum solder, consecutively, have successfully eliminated this difficulty. The introduction of harmonics caused by lead vibration is prevented by dampening.

Diaphragms, which must be stiff and light, may be formed in two ways, by spinning and by drawing. Spinning is more economical and from some standpoints better. Stresses are held to a minimum and more accurate forming results. Drawing, though quicker, calls for high die cost amortization. Spinning limits compliances to designs of the annular type, whereas

(Continued on page 34)



Figure 9
An 800-cycle horn (16" w x 10" d x 11½" overall) with a 2 x 4 configuration, 40° x 80° dispersion.

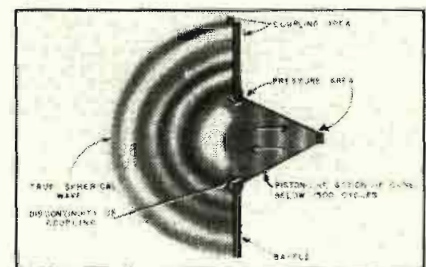


Figure 10
Acoustic action of a cone radiator below 1500 cycles.

Figure 11
Acoustic action of a cone radiator above 1500 cycles.

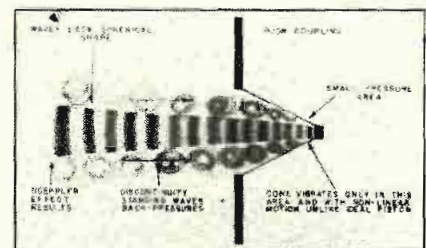


Figure 12
A high-frequency unit

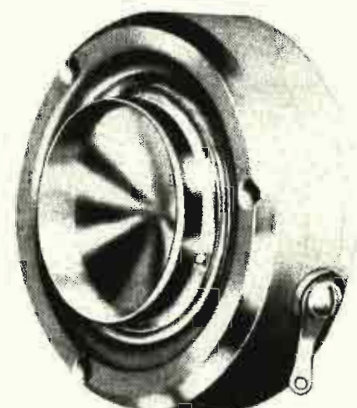


Figure 13
Exploded view of coaxial unit





Personals

VETERAN MEMBER Chas. E. Drew of Tuckahoe has sent in his renewal. . . . Oldtimer S. Specter has forwarded a note stating that he has changed his address to Mobile, Ala. Letter came from San Juan. Apparently S S is on his way to Mobile. . . . Lt. Col. M. Fernandez had been transferred from Chicopee Falls, Mass., to Washington, D. C., to Communications HQ M-ATS. . . . Johnny Lohman has become a member. Welcome J. L. John, as many seasoned veterans know, is with Mackay and lives out at College Point. . . . Life member Pete Boucheron's mail is piling up, returned due to lack of forwarding address. Anyone know his whereabouts? . . . Dewey Sturgell of Redwood City, Calif., has become a VWOA member. Perhaps Dewey can help the boys locate a few feet of redwood for that bungalow you would like to build. . . . Geo. E. Schell has advised that he is located at Guayama, P. R. Wonder what took him there. . . . Another new member is W. R. Kipp of RMCA, Baltimore, Md., who has recently been transferred to Norfolk, Va., as district superintendent. . . . H. E. Ballentine of New Brighton, S. I., and H. D. Taylor of West Hartford, Conn., became VWOA members earlier this year. Ballentine started his radio career in 1915 as an amateur, and received his Commercial First Class ticket in 1919. He has taken active part in Navy and Coast Guard radio affairs. Has also been a Reservist. Taylor's radio career began in 1917 with Marconi W. T. Co. as a seagoing operator. He joined RCA later and today is chief engineer and plant manager of WTIC, Hartford, Conn. . . . Joe Graham of Woburn (Wah'Ban), Mass., is doing a grand job monitoring for the FCC at their Millis station. . . . Al Dowd has moved from Union City, N. J., to Packanack Lake, N. J. . . . Charlie Pannell now has an office in the RCA Building. . . . C. R. Spicer has changed his address to Daly City, Calif. . . . Don De Neuf, who recently became chief engineer of the *Rural Radio Network*, Ithaca, N. Y., has forwarded some very interesting facts about the rural service.



VWOA old timers, Earl Nelson and Samuel Freedman at a recent VWOA get together in New York City.

The system consists of six f-m stations located in strategic points in the state of New York, providing coverage to about 40 counties. Profits of the organization will be used for research, education and public welfare. . . . James Devenport and Al Koehler are still enjoying life on the Bounding Main. . . . Robt. W. Hale of Ft. Wayne, Ind., reports that his dues were delayed due to illness. Hope all is well now. . . . Phil Partridge has recently been appointed radio supervisor of the Clark County, Nevada, Sheriff's Radio Communication system. Phil is also engaged in development work at the radio laboratory of the Nevada Electric Co., at Las Vegas. He's having a little trouble getting a number for his new home, but you can get him on c-w on 40 meters by calling W7UB. . . . Bill Stedman continues to keep busy doing conversion work on U. S. Maritime Commission ships at Atlantic Basin Iron Works Shipyard. . . . Peter Cuda advises he is still fighting heavy interference on 500 and 8280 kc. Pete failed to say what ship he was on. . . . H. D. Hayes, FCC engineer-in-charge at Chicago, has sent in his dues. . . . Charlie M. Hodge, whose home is in San Francisco, continues his assignment as radio technician with the Arabian American Oil Co., at Drahnan, Saudi Arabia. Gets his mail only by air. . . . Walter W. Hofmann of Kahuku, Oahu, T. H., sends his best 73's. . . . Oldtimer Sam Freedman is a busy writing man these days. He's preparing a book on transmitter design and operation, has written a couple of technical yarns for *Radio News* and *CQ*, writes a bi-weekly taxicab radio column for

a taxi paper and has completed a text on microwaves. . . . At a recent VWOA meeting Frank Orth of CBS told the boys that he just returned from a Florida vacation where he had one grand time. . . . George Duvall is as busy as ever at his television installation shop and particularly active in the installation of antennas. . . . Old timer Ben Beckerman told ye writer at an oldtimer's meeting that "the foundation and cornerstone of radio communications can be seen here tonight." . . . Among those who couldn't attend the Spring meeting were E. H. Price who reported that he wouldn't be able to attend since there was quite a Marine Show at the Grand Central Palace which required his attendance. . . . Anthony J. Brizzolau wrote in to say that he was up at his farm at Croydon, New Hampshire and couldn't make the meeting either. . . . Duty at the U. S. Navy prevented David S. Little from coming to the Spring meeting. . . . M. G. Carter was on watch on May 20 and unfortunately couldn't attend the get-together. . . . F. M. Quigley reported that Haraden Pratt was quite ill and wouldn't be able to attend our Spring meeting. . . . Jack Poppele was out in Los Angeles attending the NAB meeting and thus couldn't attend. . . . Mrs. M. Marshall dropped us a note to say that the OM would not be able to attend since he is now on his way to India and Japan. Good luck on your trip. . . . The birthday of Arthur Van Dyck and a subsequent celebration prevented attendance at the Spring meeting. A.D. said: "My bodily presence is demanded elsewhere. However I'll be with you in the Marine Room in spirit, and if my radar and loran are working late in the evening I might navigate through that watertight door after all. Best wishes for a grand evening." . . . Memo to everyone: Please send in news about heroic or meritorious deeds to Bill Simon. Include the name of the operator, name of ship and date of event. And please send in personal news notes, with photos where possible, reporting your present work, future plans, etc.

Impedance Matching Techniques

Analysis Reveals That Relationships Which Should Exist Between Source and Load Impedance for a Given Network Is Not Necessarily One Which Is Matched. Rather It Is One Which Is Determined Wholly by the Desired End in View and the Circuit Component That Is Variable or Under Control . . . Networks Containing Elements That Are Linear Are Considered.

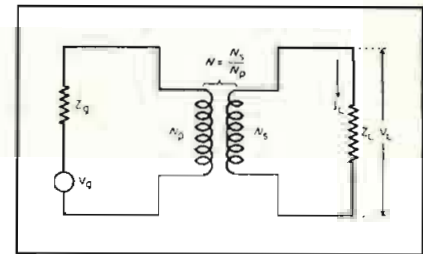


Figure 1
Generalized equivalent circuit.

by **WILLIAM J. KESSLER**

Assistant Research Engineer
Engineering and Industrial Experiment Station
University of Florida

MUCH HAS BEEN WRITTEN about the virtues of impedance matching. In fact, it seems to have become a popular misconception that an impedance match between source and load is the ideal condition to be realized wherever and whenever possible.

It is quite true, of course, that to obtain maximum power across a load when the load impedance is the only variable, that impedance must be the conjugate of the source impedance.¹ However, the load impedance is not always the *independent variable* and, furthermore, maximum power developed across the load is not always the *dependent variable*. Frequently it is desirable to obtain either maximum voltage across the load or maximum current through the load rather than maximum product across the resistive component, or power, for any one of three variables: (1) Generator or source impedance; (2) load impedance; or (3) degree of match existing between these two elements.

Method

The necessary network conditions for maximum voltage, current, or power may be readily determined by well known mathematical processes by treating the voltage, current, or power as the dependent variable, and the generator impedance, load impedance or transformation ratio N , (Figure 1) as the independent variable. Differentiating each dependent variable with respect to any one of the three independent variables, equating the result to zero, and solving for the independent variable will yield the value necessary for either a maximum or a minimum of the dependent variable. The maximum-minimum ambiguity

may be resolved by simply noting the sign of the second derivative upon substitution of the results of step one. If the sign of the second derivative is positive, the dependent variable is a minimum. The opposite, or negative, sign indicates a maximum for this quantity.

Maximum Voltage

Whenever maximum voltage across the load impedance is desired, the foregoing method can be applied only if an expression for V_L in terms of Z_g , Z_L and N can be found. Referring to the generalized equivalent circuit shown in Figure 1, such an expression for V_L can be written almost directly, that is,

$$V_L = \frac{V_g N Z_L}{Z_L + N^2 Z_g} \quad (1)$$

where it is assumed that the primary and secondary of the transformer are sufficiently closely coupled so that the expression $N^2 = Z_p/Z_s$ will not be seriously invalidated. Should the load impedance be the only variable with the ratio of transformation and the generator impedance remaining constant, the maximum (or minimum) voltage, V_L , will exist for some value of Z_L determined as follows:

$$\frac{dV_L}{dZ_L} = \frac{N^2 Z_g V_g}{(Z_L + N^2 Z_g)^2} = 0 \quad (2)$$

Solving for Z_L by inspection, it is seen that $Z_L = \infty$. To determine if this represents a maximum or minimum

voltage across the load, by observing the sign of the second derivative, results in

$$\frac{d^2 V_L}{dZ_L^2} = \frac{-2N^2 Z_g V_g}{(Z_L + N^2 Z_g)^3} \quad (3)$$

The minus sign indicates that V_L will be a maximum when Z_L is infinite, or, in an engineering sense, when Z_L is made as large as is practical or is open circuited. The value of V_L under these conditions can be determined by taking the limit of equation (1) as Z_L approaches infinity, that is,

$$\lim_{Z_L \rightarrow (\infty)} V_L = \lim_{Z_L \rightarrow (\infty)} \frac{N}{1 + N^2 Z_g / Z_L} = N$$

$$\text{or } V_L = NV_g \quad (4)$$

By inspection of equation (1) it is found that V_L will be a maximum if Z_g is the only variable when $Z_g = 0$ and, as before, $V_L = NV_g$.

Should both Z_L and Z_g be constant and only the ratio of transformation N vary, the value of N is found to be equal to $(Z_L/Z_g)^{1/2}$ for maximum V_L . This will be recognized as being the ratio necessary to affect an impedance match between the source impedance and the load impedance.

It is thus evident that in order to secure maximum output voltage from a given network, the load impedance must not simply be made equal to the generator impedance, but as large as is practical. Then, should the ratio of transformation and the generator impedance also be variable, the generator impedance should be made as small as

(Continued on page 31)

¹W. L. Everett, *Communication Engineering*, second edition, pp. 49-50, McGraw-Hill Book Company, New York.

News Briefs

INDUSTRY ACTIVITIES

KDFC's F-M transmitter atop Mt. Beacon, near Sausalito in Marin County, California, will go on the air in August. KDFC will radiate a 33-kw watt signal designed to serve nearly 3,000,000 people in the greater San Francisco Bay area.

The Hewlett-Packard Company, Palo Alto, Calif., has completed construction of new plant facilities totaling 20,000 square feet.

James H. Kellogg, president of Kellogg Switchboard & Supply Co., Chicago, addressed the California Independent Telephone Association at Los Angeles recently.

Mr. Kellogg reported that all thoughts of a recession which may have been prevalent last December have been dispelled because of world conditions and their effect upon the enormous purchasing power of the American government available to the European Recovery Program.

Commenting on the fact that the nation is now in a period similar to the days of 1940 when the United States was girding itself for its defense program, Mr. Kellogg said:

"Approaches to our company have already been made by the Signal Corps and we are told that over 11,000 United States industrial plants are being surveyed by the Armed Services to determine their capacity to produce war products in an emergency. In Chicago we are again hearing the all-too-familiar words 'allocations,' 'priorities' and 'the draft.'"

The New York Chapter of APCO held a recent meeting at Syracuse, N. Y., as guests of G. E. Lieutenant M. Boland of the Syracuse Police Dept. made the arrangements.

Twenty-one Mariners Pathfinder 10-cm radars, made by Raytheon Manufacturing Company, Waltham, Mass., have been ordered by The Atlantic Refining Company, Philadelphia.

The Penn-Allen Broadcasting Company, controlled and operated by World War II veterans at Allentown, Pa., have arranged to purchase a 500-watt G. E. television transmitter.

Transmitter is to be installed on South Mountain four miles south of the city.

John F. Rider Laboratories have leased about 11,000 square feet at 480 Canal Street, New York City.

The 1948 Rochester Fall Meeting of the IRE and RMA Engineering Department will be held November 8, 9 and 10 at the Sheraton Hotel, Rochester, New York.

Frank A. Gunther, REL vice president, recently conducted a demonstration of high fidelity f-m relay broadcasting via WHOO-FM, Orlando, and WNDL-FM, Daytona, before the Florida Association of Broadcasters. The relay path involved was over 100 miles long.

The Buckeye Pipe Line Company of Lima, Ohio, plans to install a Motorola 30- to 40-mc f-m system.

The Buckeye, parent company of the Northern Pipe Line Company of Pennsylvania and the New York Transit Company, Inc., has lines extending through Indiana, Pennsylvania, Ohio and New York with branches in Illinois and Michigan. Central station installations will be made in offices and pumping stations at Lima, Cygnet and Toledo, Ohio, and at Samaria and Trenton, Michigan. Ultimately 2-way radio will cover the entire line. To start, 100 vehicles of the company will be radio equipped.

LITERATURE

Lenkurt Electric Co., 1126 County Road, San Carlos, Calif., have prepared an 8-page bulletin, No. CX39A, on Lenkurt type 32 carrier systems. Publication describes the overall system, shows the relationship between maximum performance and minimum maintenance, and displays some of the facilities behind the design, development, and manufacture of Lenkurt equipment.

The Instrument Division of Allen B. Du Mont Labs, Inc., 1006 Main Avenue, Clifton, N. J., have published a catalog covering cathode-ray tubes, oscillographs, allied equipment and accessories. Features a wide selection of standard tubes and instruments.

PERSONALS

General William H. Harrison, had been elected president and a director of International Telephone and Telegraph Corporation.

Colonel Behn, who with his brother Hernand founded the company in 1920, will continue as chairman and chief executive officer.

General Harrison was formerly vice president in charge of operations and engineering of A. T. & T.



Gen. W. H. Harrison

James F. White has been appointed eastern manager of the new Eastern sales office of Andrew Corp. at 421 Seventh Avenue, New York. Also assigned to the new office is Paul F. Walker, Andrew sales rep.



J. F. White

Rural Radio Network's sixth f-m station, located at Turin, New York, will go on the air in August. This station, like the other five, will operate on a relay network basis.

Donald K. de Neuf is chief engineer of the network; Walter A. Knight, assistant chief engineer; John Dinter, Wethersfield station supervisor; Bud Kordalewski, Bristol Center station supervisor; Les Connelly, Ithaca station supervisor; Lou Agresti, De Ruyter station supervisor; Jim Trewin, Cherry Valley station supervisor; Stan Hickinbottom, Turin station supervisor; Tom Humphrey, audio facilities supervisor; Bill Perkins and Joe Sanford, field engineers; and Bob Wolverton, field maintenance.

Network headquarters are at 118 North Tioga, Ithaca, N. Y.

P. L. Coggeshall has joined the sales staff of FTR representing its mobile radiotelephone division in Northern California and Northern Nevada.

Harry Tarbell is now with FTR, and will cover the State of Oregon and southern Idaho for Federal's mobile radiotelephone division.

Harvey W. Smith has joined the engineering staff of Lenkurt Electric Co., San Carlos, Calif., where he will be in full charge of design and construction of transformers both for carrier application and custom manufacture.

John M. Otter has been elected vice president and general sales manager of Philco Corporation.

Junius R. Clark, former vice president of the Fawick Airflex Company, Inc., has purchased the entire capital stock of the Sterling Manufacturing Company, 9205-9223 Detroit Ave., Cleveland, Ohio, from Walter M. Scott.

Company now produces instruments, a-c and d-c, for the automotive, electrical, industrial, radio and hearing aid fields, including ammeters, voltmeters, milliameters, battery cell testers, hearing-aid testers, etc.

E. H. Vogel has been appointed to a new manager of marketing post in the general sales division of the Electronics Department of General Electric.

A. A. Brandt, the department's general sales manager since 1943, will continue in that position and will manage the general sales division which now has full operating division status.

L. E. Pettit has been named manager of a new advertising division in the Electronics Department of G. E. Pettit will operate at staff level under the manager of marketing and will be responsible for general supervision of all the department's advertising and agency relationships.

Paul Chamberlain has been appointed manager of sales in the G. E. transmitter division, succeeding Philip G. Caldwell who has joined the American Broadcasting Company.

Walter M. Skillman succeeds Mr. Chamberlain as manager of sales in the receiver division. He was formerly sales manager of standard line radios.

William B. Lodge is now vice president in charge of general engineering for the Columbia Broadcasting System.

Lodge has been Columbia's director of general engineering since November, 1944.

D. C. Summerford has resigned as assistant technical director of WHAS to become technical director for the Mid-America Broadcasting Corporation of Louisville, Kentucky, now installing a new 5,000-watt 1080-kc station.

Mr. Summerford is also president of the Shawnee Broadcasting Company, operating radio station WBEX, Chillicothe, Ohio.

Joseph K. Rose has been appointed to head the Chicago office of John F. Rider, Publisher, Inc., 6240 North Francisco Avenue. Rose was formerly service manager for Wells Gardner and Co.

Dr. Robert D. Huntoon, assistant chief of the atomic physics division, National Bureau of Standards, was recently awarded a distinguished physical science achievement award by the Washington Academy of Sciences for 1947, for his research in "the advancement of electronics and its application to other sciences and to modern ordnance."

Dr. Huntoon joined the staff of the Bureau of Standards in 1941 and assisted in the early development of proximity fuses.

Donald E. Ward has been appointed sales manager for Reeves Soundcraft Corporation, 10 East 52nd Street, New York City.

Dr. Henry H. Hausner is now a member of the Metallurgical Research and Development Laboratories of Sylvania Electric Products, Inc.

Joseph H. Humble has been appointed general sales and advertising manager of the Kester Solder Company, Chicago.

Dr. J. Howard Dellinger, chief of the Central Radio Propagation Laboratory of the National Bureau of Standards, has retired, after 40 years of Government service.

Dr. Dellinger will act as a radio consultant and adviser, and continue his present work as chairman of the Radio Technical Committee for Aeronautics. He will spend the summer attending sessions of the International Radio Consultative Committee in Stockholm, Sweden, and of the Provisional Frequency Board in Geneva, Switzerland.

E. D. Cooper, formerly manager of the Radio Specialties Division of Isolantite Corp., has joined General Ceramics and Steatite Corporation, Keasbey, New Jersey, as sales engineer, handling their new line of coaxial cable and wave guide equipment.

Howard H. Weber has been named chief engineer of the wire and cable department of United States Rubber Company. A. S. Basil is now general sales manager.

Jack Sadowsky, manager of electronic components for the Equipment Sales Section of the RCA Tube Department at Harrison, N. J., died recently.

The Industry Offers



AMPEREX 5-KW AIR COOLED AND WATER COOLED TRIODES

High-frequency water-cooled and air-cooled 5-kw triode amplifier and oscillator tubes, types 492 and 492-R, have been announced by Amperex Electronic Corporation, 79 Washington Street, Brooklyn, N. Y. Maximum rating of 5 kw plate dissipation is said to apply up to a frequency of 150 mc.

The 492-R dissipates full power with an air flow of 170 cfm. The 492 anode is capable of dissipating 5 kw of power with a water flow of 3 to 5 gallons of water per minute. The water jacket is an integral part of the tube, and a separate adaptor is provided for connection to external water lines. For high-frequency coaxial circuits, the water jacket is readily adaptable for extension into standard 2" copper tubing of any length to permit adjustment for a particular frequency.

Has a thoriated filament. Plate voltage of both tubes, 7,500.

ELECTRO-VOICE TORQUE DRIVE CRYSTAL PICKUP CARTRIDGES

Crystal pickup cartridges employing torque-drive design have been produced by Electro-Voice, Inc., Buchanan, Michigan. Acts as a mechanical transformer and provides a gear ratio between record groove and the crystal.

Weights 1/5 ounce. Has low mass drive system, high lateral and vertical compliance, zero output for vertical movement, moisture-proof crystal and replaceable whisker needle (osmium tip or sapphire tip).

Size, 1 3/32" x 11/16" x 5/16".

Available in low, medium and high-voltage outputs.

For full information, write for torque-drive bulletin No. 141.



BOONTON SIGNAL GENERATOR

An a-m signal generator, type 211 A, designed for testing and calibrating of omnirange receiving equipment operating within 88 to 140 mc has been developed by Boonton Radio Corp., Boonton, N. J.

Instrument consists of an r-f assembly, modulator and oscillator assembly, panel and meter assembly, and external dual regulated power supply unit.

Master oscillator coverage of 88 to 140 mc in one range. Vernier frequency dial has 100 divisions and is coupled to the main tuning capacitor through a 120:1 gear drive.

Either of two crystals providing 110,100 mc and 114,900 mc may be selected by a switch for use individually or in combination with the master oscillator to standardize its output frequency.

Master oscillator stability is said to be $\pm 0.25\%$ from 88-140 mc; crystal oscillator, $\pm 0.0035\%$ at 110,100 mc and 114,900 mc, operating temperature range 10°C to 50°C .

Modulation capabilities: 0-100% with internal oscillator or an external oscillator capable of supplying 2 volts across 100,000 ohms.

Distortion said to be 5% or less at 95% amplitude modulation.

Modulation meter has two ranges, 0.30% and 0.100%. Two modulating frequencies, 400 and 1,000 cycles in internal audio oscillator.

Instrument contains a demodulator or detector which supplies to front panel terminals a portion of the demodulated carrier. At 60% amplitude modulation, this voltage is 3.8 volts with a source impedance of 3,600 ohms.

Output attenuator is of single ended piston type; range is 0.2 volt to 0.1 microvolt.



TESCO ROTARY TAP SWITCH

A Tesco Rotary Tap Switch has been developed by the Eastern Specialty Co., Phila., 40, Pa.

Each switch section with 7 active positions and one off position is rated at 50 amperes, continuous duty, with an overload capacity of 75 amperes. As many as 12 switch sections in tandem may be operated in parallel to handle a maximum current of 600 amperes.

A current interrupter consisting of one or two microswitches, rated at 10 amperes, and operated by detent action, opens the source of power when the switch is rotated toward a new position, so that no arcing occurs at the switch contacts.

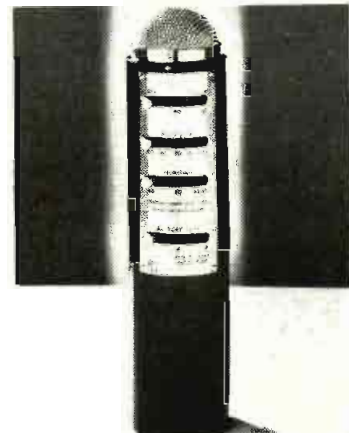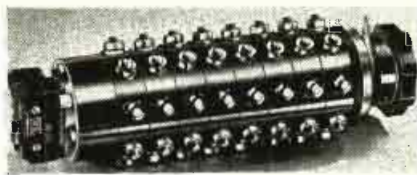Individual switch sections measure 2 3/4" diameter over the housing, 3 1/4" over the terminal studs, length 5 1/2". Bulletin No. 57 provides complete operating data.



SCOTT SOUND LEVEL METER

A sound level meter using subminiatures and covering the range from 34 to 140 db above the standard ASA reference level, has been developed by Hermon Hosmer Scott, Inc., 385 Putnam Avenue, Dept. C, Cambridge 39, Mass. Instrument, type 410-A, includes all three standard ASA weighting characteristics to duplicate the response of the ear at various levels, has a two-speed meter, provision for using extension cable, optional types of microphones, vibration pickups, etc., and analyzers or filters. The unit is 10 1/2" long, 2 1/2" in diameter, and weighs slightly over two pounds including batteries.

RAYTHEON SUBMINIATURES


Subminiatures, type CK5703/CK608CX, have been developed by the Special Tube Section of Raytheon Manufacturing Company, Newton, Mass.

Tubes are heater-cathode triodes with rated mutual conductance of 5,000 micromhos and amplification factor of 25. Tubes have a 3-watt plate dissipation and capable of an output of nearly 1 watt at 500 mc.

CLARE PLUG-IN RELAY ASSEMBLY

A dust-tight plug-in relay base and cover has been developed by C. P. Clare & Co., 4719 West Sunnyside Avenue, Chicago 30, Illinois.

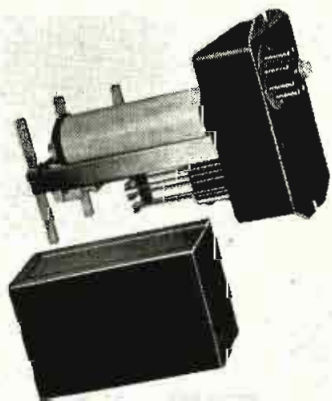
Assembly consists of an a-c or d-c relay mounted on a dust-tight base, the terminals brought through a Neoprene gasket, closely fitted. The steel cover, secured to the base by a thumb nut, can be readily removed for inspection of the relay. Either a standard radio-type plug as illustrated, or a 15-point plug of different design complete the installation.



HEWLETT-PACKARD VTVM

A vacuum-tube voltmeter, the 400C, which provides readings from .1 millivolt to 300 volts, throughout a range of 20 cycles to 2 mc, has been developed by Hewlett-Packard Company, 395 Page Mill Road, Palo Alto, Calif.

Calibrated linear scale reads directly in rms volts or in db based on 1 milliwatt into 600 ohms. Special output terminal permits use of the 400C as a wide-band stabilized amplifier, for increasing gain of oscilloscopes, recorders and measuring devices. Maximum gain is 54 db. In service as a voltmeter, instrument may be used for direct hum or noise readings, to determine transmitter and receiver voltages, audio, carrier or supersonic voltages, power gain or network response.

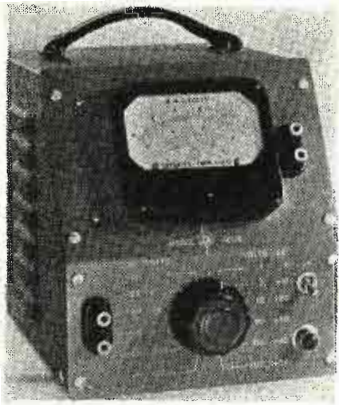


PHILCO F-M/TV VISUAL ALIGNMENT GENERATOR

A visual alignment generator, model 7008, which includes a crystal-diode h-f probe for use in examining the response curve of individual stages and the 4.5 video trap, has been developed by Philco.

Has a crystal calibrator which provides check points every 5 mc; an a-m (marker) generator, operating over a frequency range of 3.2-250 mc; an f-m generator, covering a range of approximately 4-120 mc and 145-260 mc with a variable sweep width of 15 mc maximum deviation; an a-f generator, operating at 400 cycles; scope; and a common power supply.

The cathode ray tube is a 3MP1 type employing electrostatic deflection, and is said to have a deflection sensitivity of better than 25 millivolts per inch at maximum vertical-amplifier gain. The screen is a medium-persistence, green-fluorescent type and is supplied with a removable crosshatch screen. Screen is constructed of laminated sheets of plastic so that the scribed markings are sandwiched in between two sheets, and cannot be damaged by handling. The cathode-ray tube is mounted in a separate swiveled housing which can be folded into the main housing.

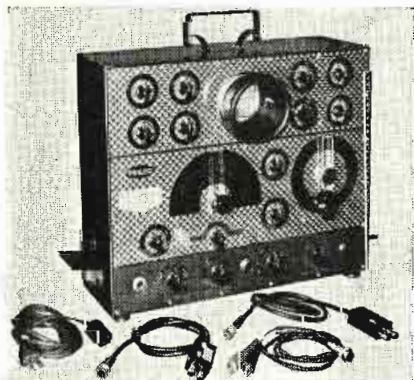

G.E. GAS-FILLED THYRATRON


An inert-gas filled midjet thyatron, type GL-5663, has been announced by the tube division of G. E.

The tube, 1½" high, has a typical heating time of ten seconds, and a peak inverse and peak forward voltage rating of 500. The anode current ratings are 60 ma instantaneous and 20 ma average.

BROWNING F-M/A-M TUNER

An f-m/a-m tuner, model RJ-12A, has been announced by Browning Laboratories, Inc., 750 Main St., Winchester, Mass. An r-f amplifier is used in both f-m and a-m sections. The a-f response of the f-m section is said to be flat from 10 to 15,000 cycles $\pm 1\frac{1}{2}$ db. A drift compensating network is said to eliminate drift after a two minute warmup period. Less than 10 microvolts required to produce 30 db noise reduction, through use of dual limiters in the Armstrong circuit. The a-m section employs recently developed triple-tuned i-f transformers and a high frequency extending network so that the audio response is flat from 20 to 6600 cycles ± 3 db. Sensitivity is 5 microvolts.

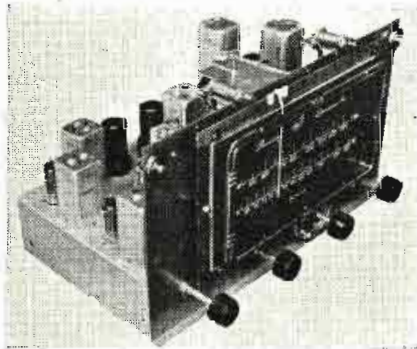A connector in the rear of the chassis for phono input allows the volume control to be employed when playing records. The f-m antenna input is 300 ohms balanced to ground and connected so that the entire f-m antenna and feeder system also functions as the a-m antenna.



TRIPLETT VOLT-OHM-MIL-AMMETER

A volt-ohm-mil-ammeter, type 630, featuring six d-c volt ranges from 0-6,000, at 20,000 ohms/volt and six a-c ranges to 6,000, at 5,000 ohms/volt has been announced by the Triplett Electrical Instrument Co., Bluffton, Ohio.

Available also are five d-c ranges from 0-60 microamperes to 0-12 amps; resistance ranges to 100 megohms; db from -30 to +70.



BROOK ELECTRONICS AMPLIFIER

A remote-control model amplifier, designed essentially for custom-built radio-phonographs, has been introduced by Brook Electronics, Inc., 34 DeHart Place, Elizabeth 2, New Jersey.


Designated model 10C3, the amplifier consists of two separate units. The smaller of two chassis contains preamp stages, input jacks, and all operating controls. The larger chassis contains a 30-watt power amplifier and power supply. Four input channels are provided, one of which is high-gain with internal equalization for use with low-level magnetic-type pickups. Low- μ u triodes are used throughout. Frequency response is said to be flat within .2 db from 20 to 20,000 cycles.

PICKERING MICROGROOVE CARTRIDGE REPRODUCER

A pickup, model D-140S, designed for the microgroove, fine-line slow-speed, recordings, has been announced by Pickering and Co., Inc., Oceanside, Long Island, N. Y. Sharp diamond stylus radius is .001".

Cartridge tracks the recordings with a stylus pressure of 5 grams, or approximately 1/6 of an ounce.

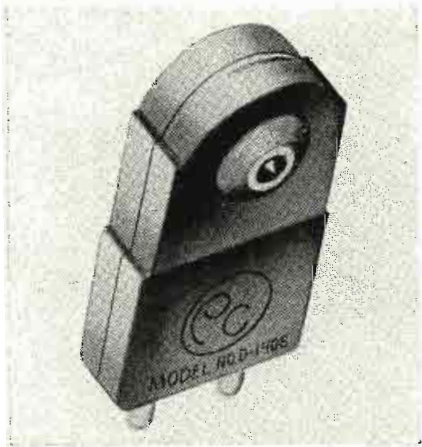
Has a *Keystone Clip Mounting* which permits conversion from the standard cartridge to model D-140S.



BENDIX FRACTIONAL H-P D-C MOTORS

A line of fractional horse-power, d-c motors designed for trim-tab actuators, stall-warning systems, bank-change switching and other applications, has been announced by the Red Bank Division, Bendix Aviation Corporation, Red Bank, New Jersey.

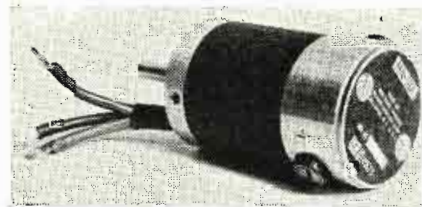These motors, designed to meet the requirements of AN specifications are available in various voltage ratings, clock, counter-clock or reversible rotation, and with pinions, worms or plain shafts. Motor diameter is 1½", length (less shaft) 2 9/16" and weight 12 ounces.




INDUSTRIAL DEVICES HI-VOLT NEON-INDICATOR VOLTMETER

A voltmeter, covering a range from 1,600 to 15,000 volts a-c, the Hi-Volt model 500, has been announced by Industrial Devices, Inc., Edgewater, N. J. Device is intended for testing high-voltage transformers. It is not recommended for use on high-power supplies other than those of the current-limiting type, except by those familiar with the technique of high-voltage measurements and the precautions necessary.

The unit utilizes a neon lamp indicator. A knob is turned until the neon lamp extinguishes, when the voltage is read directly off the dial. This device is designed for use only with transformers having one side grounded. A 15-megohm multiplier is incorporated in a 7" long prod which is integral with the meter. The current drawn is less than 1 ma.

(Continued on page 36)

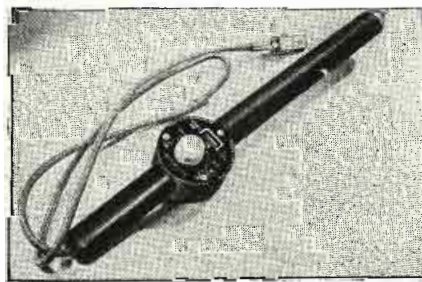

NEW 15/16" CONTROLS



ACTUAL SIZE!

★ Yes sir, a brand new member of the well-known Clarostat family of controls. Type 47 or 15/16" diameter miniature control is smaller, handier, yet just as tough as its bigger brother, Type 37 composition-element control.

It's a beauty. Note the trim lines. It includes the famous Clarostat stabilized element you can bank on. Nothing sacrificed by way of electrical and mechanical sturdiness in attaining smaller size. Available with (factory-equipped) or without switch. Available with one tap. Choice of tapers.

CLAROSTAT



Write for literature. Let us quote on your requirements.

Controls and Resistors

CLAROSTAT MFG. CO., Inc. - 285-7 N. 6th St., Brooklyn, N. Y.

In Canada: CANADIAN MARCONI CO., Ltd. Montreal, P.Q., and branches

Preamp Maintenance

(Continued from page 9)

be used, the terminating resistance shown in the circuit should be chosen to properly terminate the attenuator used. If the preamp has a given input impedance, which is of proper value to terminate the attenuator, no terminating resistor need be used. The isolation transformer should provide the required impedance ratio to match the oscillator to the attenuator which should have an impedance corresponding to the given value.

The input of the preamp may be balanced to ground or single-ended. The attenuator chosen should be of the corresponding type and should provide a maximum loss at least equal to the gain of the preamp. The ground connection to the input circuit of the preamp should be made as recommended by the manufacturer. The output circuit of the preamp should be terminated by a non-inductive resistor equal to the output impedance of the preamp. The Figure 1 circuit is used with balanced circuits. In Figure 2 we have a setup with unbalanced circuits.

The oscillator and preamp should be permitted a sufficient warm-up period to assure stability. The oscillator should be set to 1,000 cps and the output adjusted until the No. 1 vu meter (input) reads +4 vu. Sufficient attenuation should be inserted so that the output level as indicated by vu meter No. 2 is approximately +4 vu.

An alternate method is to insert an additional amplifier, having* sufficient gain for the purpose, ahead of the volume indicator. The frequency response of this amplifier should be determined and used to correct any readings taken.

Adjustment of Level

To determine the correct output level, preamp operating instructions should be studied carefully. The appropriate test circuit from Figures 1 and 2 should be selected and the foregoing suggestions applied if the preamp output is insufficient to operate a standard volume indicator. The audio oscillator should be set on 1,000 cycles and the output level adjusted until the No. 1 volume indicator (oscillator output) reads either +4 vu or ± 0 db, de-

If the preamp output level is substantially below +4 vu, the vu meter across the output load resistance may be replaced by a vvm of greater sensitivity, provided the output of the preamp is single-ended. The ground terminal of the vvm should be connected to the grounded output lead. If the preamp output transformer contains a center-tap ground, then a properly terminated isolation transformer must be inserted, since vacuum-tube voltmeters require a ground on one leg for stability purposes.



JOHNSON

a famous name in radio

BROADCAST EQUIPMENT

Adjustable phase sampling loops

Isolation filters

Sampling lines

FM and AM concentric lines

Fixed capacitors

Variable capacitors

Phase sampling transformers

FM iso-couplers

Standing wave indicators

Tower lighting filters

Supports for open wire transmission lines

Pressurized capacitors

Neutralizing capacitors

Fixed inductors

Variable inductors

Write for specific information directly or through your consulting engineer.

E. F. JOHNSON CO.

WASECA, MINNESOTA

pending on the type of volume indicator used.

The attenuator should be adjusted until a convenient reading is obtained on the No. 2 volume indicator.

Determining Overload Point

The output of the audio oscillator should be kept constant at +4 vu; the attenuation ahead of the preamp decreased in 4 db steps or the oscillator output alternately increased and the output volume indicator observed. A point will be reached where the output level increase is less than the corre-

sponding increase in input level due to the amplifier overload. When the overload point has been found for 1,000 cycles, the audio oscillator should be adjusted to 30 cycles, 10,000 and 15,000 cycles and the overload point at these frequencies determined. It may be helpful to plot the input level versus output level to determine the amplitude characteristics of the amplifier.

The highest value of output level before overloading is detected should be noted. *All subsequent frequency response measurements are to be made at an output level of approximately 10 db below this point.*

Frequency Response of the Preamp

A frequency run should be taken with the preamp input level adjusted as indicated previously, so that the resulting output level at the 1,000-cycle reference frequency is at least 10 db below the overload point as determined above. The frequency response runs should be made at output levels of 5 db above and below the original value. If the runs are in agreement within ± 2.5 db, it can be assumed that the preamp is operating within the linear range.

If the frequency response of the preamp is within ± 1 db from 50 cycles to at least 10 kc it may be considered satisfactory for use. If it should depart from the above, the manufacturer's bulletin should be consulted and suitable steps taken to correct any deficiencies.

Stabilization

(Continued from page 8)

can readily be seen by comparing Figure 1 with Figures 5 and 6. One disadvantage, however, should be pointed out. The feedback stabilization system must be calibrated; that is, it does not permit the frequency to be known directly as is the case where the source of the oscillation is an accurately known quartz crystal. Once the calibration of the unit has been made, however, its simplicity and ease of operation far surpasses the frequency multiplier units.

References

- ¹Microwave Instrument Blind Landing System, Electronic Industries; February, 1946.
- ²Dahl, Ernest A., 2660 Mc Train Communication System, Electronics; January, 1946.
- ³George, W. D.; Lyons, H.; Freeman, J. J., and Shaull, J. M., The Microwave Frequency Standard at the Central Radio Propagation Laboratory, Report CRPL-8-1, 9-4, U. S. Department of Commerce, National Bureau of Standards, Central Radio Propagation Laboratory, Washington, D. C.
- ⁴Straus, H. A.; Rueger, L. J.; Wert, C. A.; Reisman, S. J.; Taylor, M.; Davis, R. J., and Taylor, J. H., Fire-Control Radar MPGL, Electronics; December, 1945.
- ⁵Holdam, J. V.; McGrath, S., and Cole, A. D., Radar for Blind Bombing, Electronics; May and June, 1946.

Impedance Matching Techniques

(Continued from page 26)

practical, after which the value of N should be adjusted to match these two impedances.

Maximum Current

The conditions for maximum current through the load impedance, if Z_g or Z_L is the variable, is most easily determined by inspection after dividing equation (1) by Z_L . It is seen that I_L is a maximum when either Z_L or Z_g (or both) is equal to zero or is a minimum. If the transformation ratio N is the variable, the criterion is

$$\frac{dI_L}{dN} = 0$$

The value of N is found to be $(Z_L/Z_g)^{1/2}$, demonstrating that N should be adjusted to match the fixed impedances. It is again easily seen that to obtain maximum I_L , when all three network elements are variable, both the load impedance and its generator impedance should be made as low as practical after which these two impedances should be matched by adjusting the value of N .

Maximum Product of Voltage And Current, or Power

Taking the resistive components and the transformation ratio as the variables, while the reactive components are equal and opposite, the output power will be a maximum, when

$$\frac{dP_L}{dR_g} = 0, \frac{dP_L}{dR_L} = 0 \text{ and } \frac{dP_L}{dN} = 0$$

where

$$P_L = \frac{V_g^2 N^2 R_L}{(R_L + N^2 R_g)^2} \quad (5)$$

In the first case ($dP_L/dR_g = 0$) it is found that the output power is a maximum, if

$$R_g = -R_L/N^2$$

This indicates that R_g should be a negative resistance which cannot be realized physically. However, it is readily seen by inspection of equation (5) that P_L is a maximum and finite when R_g is a minimum or equal to zero.

For the two remaining cases it is found that for maximum output power the load resistance, if the transforma-

tion ratio N is the only variable, or the two resistances should be matched by means of the transformer, should be made equal to the generator resistance. If the load and generator impedances are complex and have fixed angles, the above results are also valid when considering only their absolute values.²

Conclusion

The foregoing results serve to stress the fact that the relationship existing between source impedance, load impedance, and degree of match, is determined entirely by which network components are variable, and whether it is desirable to obtain maximum voltage, current, or power across the load impedance.

Variable	Maximum Voltage	Maximum Current	Maximum Power
Z_g	$Z_g = 0$	$Z_g = 0$	$Z_g = 0$
Z_L	$Z_L = \infty$	$Z_L = 0$	$Z_L = Z_g$
N	$N^2 = \frac{Z_L}{Z_g}$	$N^2 = \frac{Z_L}{Z_g}$	$N^2 = \frac{Z_L}{Z_g}$

Figure 2

Tabulation of the results arrived at through application of procedures discussed in this paper. It may be seen that if all three circuit components are variable, an impedance match should be affected only after the source and load impedances are adjusted for optimum values.


²L. A. Ware and H. R. Reed, *Communication Circuits*, second edition, pp. 37-38, John Wiley & Sons, Inc., New York.

PORTABLE FIELD INTENSITY METER



Portable field intensity meter recently developed by RCA, weighing 12½ pounds with batteries and measuring 12" x 8½" x 5½". The meter (type WX-2A) provides direct readings.

Designed for Application

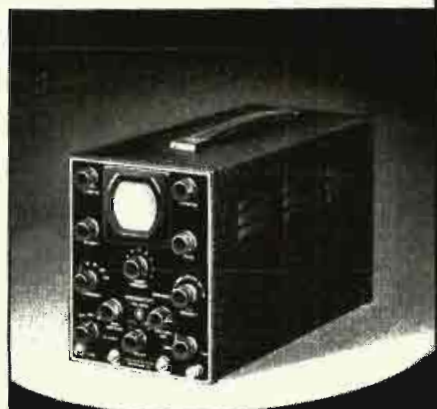

90952

The No. 90952 MINIATURE SYNCHROSCOPE For Field Service

The compact design of the No. 90952, measuring only 7 1/2" x 5 3/8" x 13", and weighing only 17 lbs., makes available for the first time a truly **DESIGNED FOR APPLICATION** "field service" Synchroscope.

JAMES MILLEN MFG. CO., INC.

MAIN OFFICE AND FACTORY
MALDEN
MASSACHUSETTS



Tube News

(Continued from page 14)

be obtained by increasing the *B* voltage.

JANETC Preferred Transmitting Tubes

A PREFERRED LIST of transmitting tubes has also been prepared by the Army-Navy committee.

There are ten classifications: Triodes, tetrodes, twin tetrodes, pulse modulation, magnetrons, vacuum, gas rectifiers, grid control, clipper tubes and gas switching.

In the triode group are the 2C39A, 2C43, 6C22, 9C21, 9C22, 100TH, 250TH, 450TH, 811, 880, 889RA, 893A and 893AR. Tetrodes include the 4D21, 5D22, 807W and 4X150A. The 829B and 832A are recommended as twin tetrodes. For pulse modulation seven types are specified: 3D21A, 3C45, 3E29, 4C35, 5C22, 6C21 and 715C.

The magnetron group includes the 2J30-34, 2J48, 2J51, 2J58, 2J60, 2J61A-62A, 3J21, 4J50, 4J51, 4J52, 4J54-59, 4J78, 5J26, 5586 and 5657. In the vacuum group we have the 2X2A, 3B24W, 371B, 5R4GY, 836, 1616 and 8020. Gas rectifiers include the 0Z4A, 3B28, 4B26, 4B32, 6C, 16B, 857B, 869B, 1005, 1006 and 5517. For grid control we have the 2D21, 6J1, 6D4, 393A, 394A and 884. Clipper tubes include the 3B29, 4B31 and 719A.

Two classifications are used for the gas switching approved types, the ATR and TR. In the ATR group we have nine tubes: 1B35, 1B36, 1B37, 1B44, 1B51, 1B52, 1B53, 1B56 and 1B57. There are five types in the TR group: 1B26, 1B27, 1B32, 1B50 and 1B60.

The 3B4

A MINIATURE instant-heating filamentary type r-f beam-power pentode for use in v-h-f portable mobile equipment as a class C oscillator, frequency multiplier and r-f amplifier, was recently announced by Hytron. Typed the 3B4, it utilizes a 1.25/2.5-volt filament, with current ratings of 330 and 165 ma, respectively.

Can be used as an r-f power amplifier and oscillator in class C telegraphy and f-m with d-c plate voltage of 150, d-c screen-grid voltage of 135 and d-c control-grid voltage of -75.

Useful power output, when the tube is used as a class C oscillator at 100 mc is about .45 watt with 90 volts plate and 1.25 watt with 150 volts on the plate, with 2.5 volts on the filament.

HERE'S BIG HELP IN TERMINAL WIRING!

The New JONES FANNING STRIP

Connections are made through Fanning Strip, on bench or anywhere apart from barrier strip, and quickly slipped into assembly.



Use with Jones Barrier Terminal Strips, Nos. 141 and 142, for 1 to 20 terminals.

Simplifies soldering. Insures correct connections. Saves time. Ideal for harness or cable assembly. Brass terminals, cadmium plated. Bakelite mounting. Send for complete data.

HOWARD B. JONES DIVISION
Cinch Mfg. Corp.
2460 W. GEORGE ST. CHICAGO 18, ILL.

ZOPHAR WAXES COMPOUNDS and EMULSIONS

FOR
INSULATING and WATERPROOFING
of ELECTRICAL and
RADIO COMPONENTS

Also for
CONTAINERS and PAPER
IMPREGNATION

FUNGUS RESISTANT WAXES

ZOPHAR WAXES and COMPOUNDS

Meet all army and navy
specifications if required

Inquiries Invited

ZOPHAR MILLS, INC.
FOUNDED 1846
122-26th ST., BROOKLYN, N. Y.

V-H-F Link

(Continued from page 20)

per channel for a 1,000-cps zero-dbm input signal to the two-wire hybrid. A 30-db *T* pad in the receiver output line reduced the 20-dbm output to a -10 dbm input level for the carrier terminal.

Carrier equipment⁵ used in this test normally operates with a level of -13 dbm at the modulator input and +4 dbm at the demodulator output. Two-wire terminations are obtained with four-wire terminating sets which include attenuation pads to reduce the incoming level from the switchboard to -13 dbm. Pads are also provided to reduce the receiving level at the switchboard to the desired value.

The carrier equipment can be adjusted for any desired transmitting level toward the radio transmitter over a range from about +3 dbm to -43 dbm and for operation on incoming signal levels in the range of -21 dbm to +10 dbm. The equipment operates at 600-ohm impedance on both the voice- and carrier-frequency sides.

First operating tests on this installation revealed such quiet circuits that listeners thought the equipment was dead. Signal-to-noise ratio was 60 db or more. At all other times ratios better than 30 db have been maintained.

Satisfactory conversations have been held over the complete 88-mile circuit produced by patching together two of the channels at San Jose and talking between two stations in the San Francisco offices of Southern Pacific.

One of the two telegraph sub-channels was used to replace a wire circuit between San Francisco and San Jose. The other was repeated at San Jose for wire connection to a teletype at Watsonville, 100 miles from San Francisco. The teletype circuit to San Jose gave a range of 80 points from San Francisco to San Jose and 75 points in the return direction.


⁵Lenkhurt type 42.

WLWT TV TRUCK



Thirty-two passenger bus converted for mobile tv work at WLWT, Cincinnati. Bus accommodates 2 cameras, over 1,500' of cable, portable microwave transmitter, sound equipment, monitoring and switching apparatus and in addition, seats for 22. Features of the bus include air conditioning and fluorescent lighting.

PICKERING REPRODUCERS

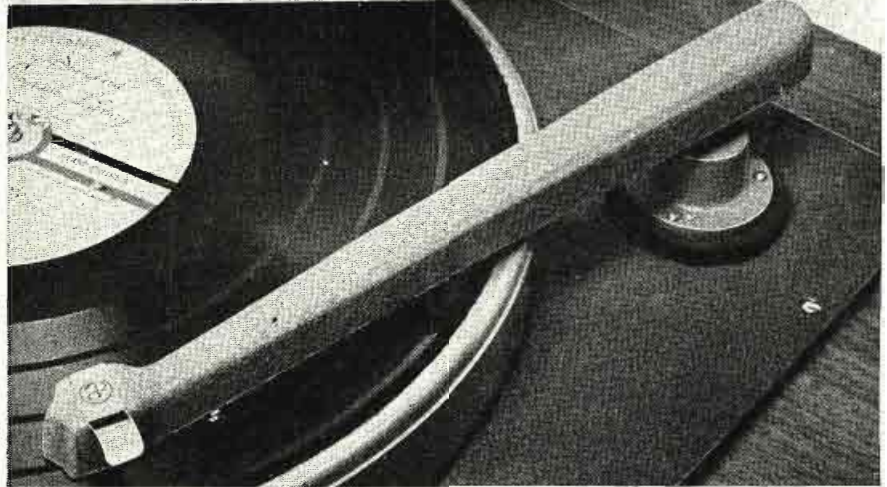

THE PICKERING MODEL 161M PICKUP incorporates all of the requirements for the finest possible reproduction of lateral records and transcriptions. It is extremely rugged and absolutely stable, ensuring long trouble-free service with minimum record wear. **TECHNICAL SPECIFICATIONS** include: Perfectly polished diamond stylus with .0025" radius; other radii available on special order at no extra cost ★ ★ Correctly offset head gives negligible tracking error ★ ★ Extremely rugged, may be scraped across records or dropped from full height without damage to pickup ★ ★ Tracking pressure adjusted at factory to 14-18 grams ★ ★ No measurable effect of temperature, humidity or age ★ ★ Equalized output level—60 dbm ★ ★ Frequency response flat within 1 db from 30 to 15,000 cycles per second ★ ★ Backtracking will not affect either pickup or record ★ ★ Convenient finger grip permits rapid accurate cueing ★ ★ Optimum combination of counterweight and spring permits excellent performance on warped records ★ ★ Convenient to mount, occupies least space of any transcription reproducer ★ ★ No measurable intermodulation or harmonic distortion ★ ★ Adaptable for turntables from 1" to 2½" high ★ ★ UNCONDITIONALLY GUARANTEED.

THE PICKERING Model 163A EQUALIZER

- positions**
1. Flat high frequency response to over 15,000 cycles per second. Low frequency rise to give full compensation from 500 to 400 cycles.
 2. Flat high frequency response. Low frequency response approximately 5 db below position 1.
 3. For NAB or Orthocoustic transcriptions.
 4. Low frequencies same as position 2. High frequencies sharply attenuated to reduce surface noise. Attenuation starts at 4000 cycles.
 5. Low frequencies same as position 1. High frequencies same as position 4.



MADE to a tolerance of ± 1 db, provides five different lateral characteristics to equalize properly all types of records and transcriptions. It is designed for use with 250 to 600 ohm input circuits at a level of -60 dbm. Hum pickup is less than -120 dbm. The model 161M PICKERING PICKUP with a 163A EQUALIZER is so free from distortion of all kinds that it may be used as a standard for measurement.

THE PICKERING Model 125H

EQUALIZER-AMPLIFIER for use with model 120M PICKERING CARTRIDGE REPRODUCER—it compensates for average recording characteristic, raises output voltage to as high as obtainable from crystal pickups, operates from the power supply of amplifier or radio set, saving cost of separate power supply, very simple to install.



THE PICKERING

Model 120M


CARTRIDGE REPRODUCER

A compact version of the PICKERING PICKUP for high quality reproduction, it fits into any arm which will accommodate a standard cartridge and affords the cleanest and smoothest response ever achieved. Its Frequency Response is ± 2 db, 40-10,000 cps ... its Waveform Distortion is 1 percent maximum ... its Output Level is 70 millivolts ± 2 db ... its Tracking Pressure is 15 grams maximum at 40 and 10,000 cps. NO OTHER PICKUP CAN MATCH THE PERFORMANCE OF THE PICKERING MODEL 120M



**Pickering
& Company, Inc.**


Oceanside, Long Island, N. Y.

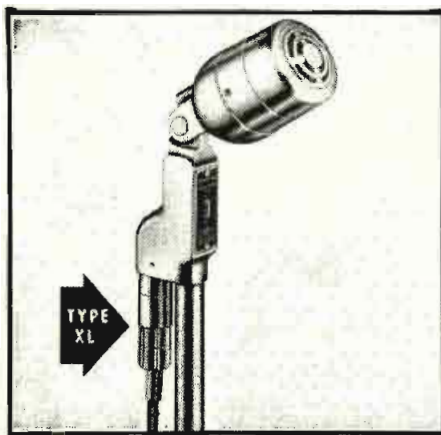

HIGH FIDELITY EV-635 MICROPHONE USES "XL" PLUG

Electro-Voice has equipped the new EV-635 High Fidelity Dynamic Microphone for studio and remote broadcasting, with the Cannon Type XL-3-11 Plug—a quality plug for a quality microphone.

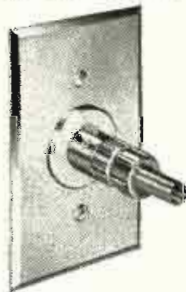Shown at left is the new XL-3-36 Wall Receptacle (pin insert) engaged with an XL-3-11 Plug. XL-3-36 is priced at \$5.45 List; and XL-3-35 (socket insert) \$4.95 List.



For a practical, low cost but high quality connector series having three 15-amp. contacts, choose the "XL". Four plug types and six receptacles with 3 adapter receptacles are available. Min. flashover voltage 1500 Volts.



Above are the two zinc plugs (Left) XL-3-12, List \$1.20 and (Right) XL-3-11, List \$1.25

No other small electric connector has all the features of the XL, including the safety latch lock.

XL Connectors are available from more than 250 radio supply houses throughout the U.S.A.

For complete information on the XL, write for Bulletins XL-347 and XL-PRI. Address Department G-121.

CANNON
ELECTRIC

Development Company

3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.

IN CANADA & BRITISH EMPIRE:
CANNON ELECTRIC CO., LTD., TORONTO 13, ONT.

WORLD EXPORT (Excepting British Empire):
FRAZER & HANSEN, 301 CLAY ST., SAN FRANCISCO

Speaker Systems

(Continued from page 24)

compliance of the tangential type may be employed where drawing is used. The greater excursion possible is offset, perhaps, by the fact that linear movement is accompanied under torsion, which may in turn affect response. Subjective tests indicate no great disparity in operation.

Mounting the diaphragm should be fast, accurate and easy. In the unit illustrated mounting is accomplished with no special skill or centering devices. Annular recesses center the unit positively and the diaphragm assembly is secured by only three screws.

The Low-Frequency Assembly

The low-frequency assembly consists of the frame, cone and voice coil with compliance. The frame must be strong and not subject to warping. Tolerances must be close to eliminate adjustments which would slow up production. For this reason no stampings are used, and the frame is accurately machined from non-warping aluminum castings of thick section.

A curvilinear designed cone is employed in our models to allow more driving area within the 15" diameter allowable. It was recognized when this choice was made that a straight-sided cone might theoretically supply more stiffness. Tests proved no discernible weave or cone breakup, and increased efficiency was apparent from the additional driving area, totaling over 125 sq. in.

The low-frequency voice coil in our speakers is copper wound. Conductivity is higher than for aluminum, though mass is greater. The use of aluminum in the voice coil is limited to the high-frequency unit, where mass increase would seriously affect the upper limit of response.

Quality Improvement

Perhaps because the listening audience has been easily satisfied, or more likely because the audience has not known how to articulate its dissatisfaction, and perhaps because acoustic design must be treated subjectively and this violates the objectivity of the engineer, speaker research and design have been neglected.

Surveying the art, we find many questions still unanswered. Why, for instance, have we seized upon flimsy paper cones and heavy metal diaphragms as the basis for our ultimate design, which to date have fallen far short of their goal?

What happened to the Klystron condenser speaker? Why was this design not pursued to the ultimate?

MICO— 2- & 3-DIMENSIONAL ENGRAVER



Permits accurate reproduction of three-dimensional master on any of four reduction ratios.

Prompt delivery. Catalogue on request.

Mico Instrument Co.
88A TROWBRIDGE STREET
CAMBRIDGE, MASS.

Where are the ideal piston type designs, and the infinite cellular unit designs?

Even in theater woofers today we are content with a folded horn or a short straight horn that violates even our present acoustic knowledge.

Yes, the problems are many. Acoustic engineers have quite a development and research program facing them.

SOUND MOVIE PROJECTOR FOR TV



RCA's 35-mm sound motion projector, which features electronically-triggered, high-intensity gap-lamp which is said to be virtually free of heat and eliminates the need for a moving shutter. The periodic flashes of the lamp, coupled with a specially-designed film drive mechanism, make it possible to use standard 35-mm film, which normally operates at 24 frames per second, to provide the 60 interlaced fields, or 30 frames per second required for tv. Operator is shown at the monitor and changeover control rack, which contains the switches for the remote starting and stopping of the projector, as well as the remote controls for operating a slide projector.

Noise Measurements

(Continued from page 21)

of these factors is varied, the plot would no longer hold and the distance from source to microphone for a 1-db error would have a different value. However, knowing the room conditions, a set of curves similar to those of Figure 1 can always be drawn up, using the following approximate formula:

$$\frac{E_R}{E_D} = \frac{16 \pi D^2 (1 - \alpha)}{S \alpha}, \text{ where } E_R \text{ and } E_D$$

E_D are the reverberant and direct sound energies respectively, D is the distance in feet from source to microphone, S the interior surface area of the room in square feet and α is the average sound-absorption coefficient of the room surface. A reasonable approximation of alpha may be calculated from published tables of the sound absorption coefficients of building materials, by multiplying the area of each surface material by its absorption coefficient to obtain absorption units, totaling the units and then dividing by the total surface area. Alpha may also be more accurately obtained by calculation from a measurement of the reverberation time of the room.

The value of D , when E_R equals E_D and their ratio is unity, is the point where the curves cross to give a total 3 db higher than either curve. Other points on the total energy curve can be obtained by converting the plotted decibel values of E_R and E_D to relative energies, adding and reconvert to decibels.

A drawing such as this should be available in acoustic test rooms where precise sound measurements are made, as with it, one can readily determine the microphone distance that will give an accuracy consistent with the precision of other factors affecting the measurements.

Noise measurements are sometimes made in power houses, transformer sub-stations and other locations where high magnetic fields are present. Such fields may often be picked up by low-level, high-impedance portions of the equipment to give erroneous noise readings. To guard against this, it is advisable to use as short a microphone cable as possible, and to check the minimum reading by covering the microphone tightly. Often orienting the microphone or substituting a crystal for a dynamic microphone will reduce the pickup to a satisfactorily low value.

A review of the foregoing will disclose many possibilities for results

(Continued on page 36)

DESIGNED TO MEET EVERY REQUIREMENT

The Complete Quality-Engineered

LINE OF FM & TV ANTENNAS

(44 to 216 MC) by

BRACH

MASS PRODUCERS OF ANTENNAS
SINCE THE START OF BROADCASTING

EST. 1906

Be assured of maximum reception and trouble-free operation with Brach FM & TV antennas. They are recommended for their simplicity, ease of installation and durability by service-men, installation engineers and dealers. Brach features a complete line, engineered for maximum performance and to meet all individual problems and requirements.


All antenna kits are complete, containing a five foot steel mast, non-corrosive aluminum elements, ample down-lead, all necessary hardware and the Brach Universal Base Mount which permits a 360° rotation of the mast to any position on any type of building after the mount has been secured. Guy wires are also included and give complete protection and stability to the installation.

Brach antennas feature a low standing wave ratio for peak reception and can be obtained to cover all channels from 44 to 216 MC. Each type of antenna has been tested to give a uniform pattern over the frequency range specified.


ATTENTION, USERS OF PRIVATE BRANDS

L. S. Brach Mfg. Corp., experienced in the development and manufacture of all types of receiving antennas, offers engineering and mass production facilities for the design and production of antennas to individual specifications.


SEND FOR CATALOG SHEETS

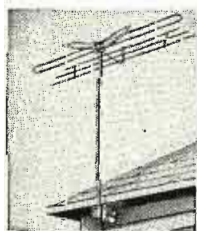

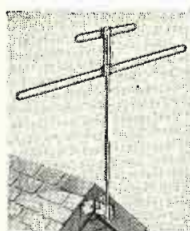BRACH MULTI BAND
FOR FM & TV #344
44-108 MC 174-216 MC
[Accessory Reflector Kit
#344-R as illustrated]



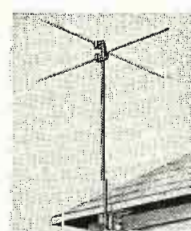
BRACH BROAD BAND
FOR FM & TV #338
44-108 MC
174-216 MC




BRACH CROSS DIPOLE
FOR FM #346
88-108 MC



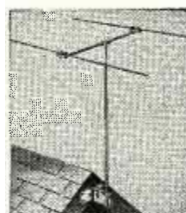
BRACH STRAIGHT DIPOLE
FOR FM #334 88-108 MC
FOR TV #333 44-88 MC
Accessory Reflector Kit—
For FM #334-R
Accessory Reflector Kit—
For TV #333-R



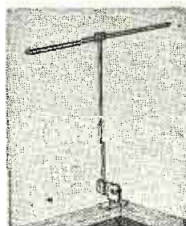BRACH STRAIGHT DIPOLE
SHOWN WITH REFLECTOR



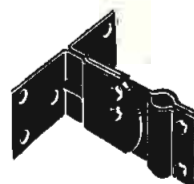BRACH FOLDED DIPOLE
FOR FM #335 88-108 MC
FOR TV #337 44-88 MC
Accessory Reflector Kit—
For FM #335-R
Accessory Reflector Kit—
For TV #337-R



BRACH
UNIVERSAL
BASE MOUNT

L. S. BRACH MFG. CORP.

200 CENTRAL AVE., NEWARK 4, N. J.

WORLD'S OLDEST AND LARGEST MANUFACTURERS OF RADIO ANTENNAS AND ACCESSORIES

AN
IMPORTANT
TECH LAB
DEVELOPMENT


New Type 1250 R. F. SWITCH

High r. f. current carrying capacity
50 amps. max. intermittent load; 30
amps. steady load. Low loss factor.

Sturdy mechanical design . . .

Mycalex insulation.

Furnished in any
number of
decks.

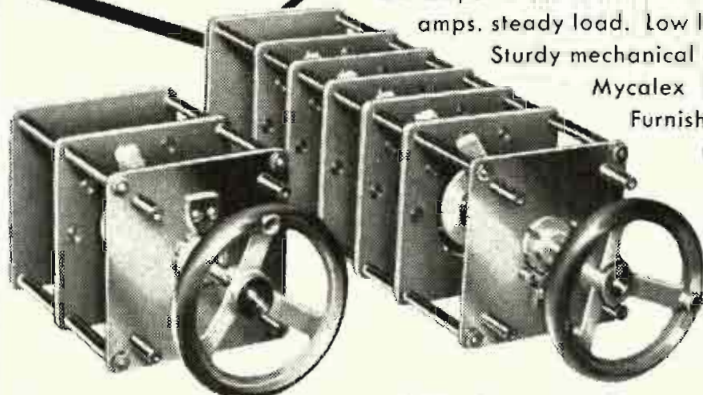

Write for Bulletin No. 472

TECH
LABORATORIES, INC.

Manufacturers of Precision Electrical Resistance Instruments

335 CENTRAL AVE. • JERSEY CITY, N. J.

(Continued from page 35)

that, to the uninitiated, might seem incomprehensible or inconsistent. However, with attention to the points brought out, the engineer making noise measurements for the first time can avoid many of the more common errors, and can save himself from the embarrassing position of distrusting his own equipment. A close scrutiny of the results of acoustic measurements is always profitable, but the sound-measuring equipment usually deserves questioning last of all. Most modern sound meters are well built, care having been taken to make them dependable, stable, and accurate. When one considers the other more probable causes of an inconsistent reading he will be more inclined to place the meter in the position of Caesar's wife—"above suspicion."


The Industry Offers

(Continued from page 29)

FISHER-PIERCE PHOTOELECTRIC LIGHT CONTROL

Photoelectric controls, for the control of aircraft obstruction lights on towers, have been announced by the Fisher-Pierce Company, 72 Ceylon Street, Boston 21, Mass.

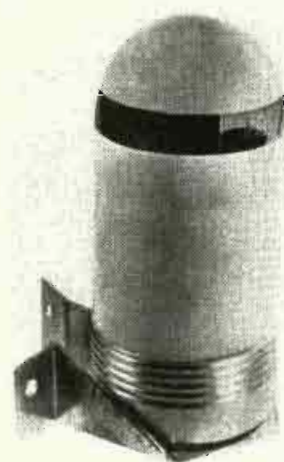Controls turn on automatically at 35 foot-candles and turn off at 55 foot-candles. One model, 61305, is rated to control 500 watts of incandescent lamp load, and another model, 61306, is rated to control 3,000 watts. Both operate at 120 volts, 50 to 60 cycles.



KAY ELECTRIC MEGALYZER

A wide spectrum analyzer, the Megalyzer, has been announced by Kay Electric Company, Pine Brook, N. J.

Unit can be used as a monitoring instrument for communication systems studies and analysis, and observe simultaneously all signals within a frequency sweep band 30 mc wide within the 30 to 300 mc range. Sensitivity said to be better than 200 microvolts. Narrow frequency resolution of 100 kc.

Megalyzer may also be used as a sweeping oscillator for conventional alignment work.

KURMAN SPLIT ARMATURE RELAY

A relay with a split armature, type 24, developed for automatic controls, keying, antenna changeover, burglar alarms, and closed circuit

AMPERITE Studio Microphones at P.A. Prices

Ideal for BROADCASTING

- RECORDING
- PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- The only type microphone that is not affected by any climatic conditions.
- Guaranteed to withstand more "knocking around" than any other type mike.

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.



Models

RBLG—200 ohms

RBHG—Hi-imp.

List \$42.00



"Kontak" Mikes

Model SKH, list \$12.00

Model KKH, list \$18.00

AMPERITE Company, Inc.

561 BROADWAY • NEW YORK 12, N. Y.

In Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto

applications, has been announced by the Kurman Electric Co., Inc., 35-18 37th St., Long Island City 1, N. Y.

Rated sensitivity, .014 watt d-c; .3 va a-c. Adjusts to operate at .005 watt, and from .01 to 115 volts d-c or a-c.



G.E. SINGLE SIDEBAND SELECTOR

A single sideband selector, type YRS-1, has been developed by the Specialty Division of G. E.

Device is said to afford a reduction of distortion due to selective fading for long distance reception of a-m signals. According to George F. Devine, commercial engineer for the division, a complete single sideband system, transmitter and receiver, would permit twice as many signals or stations in a band and would increase transmitter efficiency by up to 75%.

Carrier drift, within limits, is followed by means of a locked oscillator eliminating any need to follow small variations in transmitter frequency or drift in the receiver's local oscillator.

There are four pushbuttons on the device, one for dual sideband reception with reinforced carrier, one for normal reception and one for selection of each sideband. Designed for use with receivers having an i-f of about 455 kc.

TURNER MIKES

A bi-directional velocity type microphone and improved cardioid microphone have been developed by The Turner Company, Cedar Rapids, Iowa.

Velocity microphone, model 87, has a single element ribbon generator supported in an Alnico V magnet. Has shielded output transformers to exclude hum pickup. Response is said to be held to within ± 5 db from 80 to 10,000; level, 62 db below 1 volt/dyne/sq cm at high impedance. Has a 4-position output switch permitting use with 50, 200, 500 ohms, or high impedance inputs.

Cardioid microphone, model 77, features a wide-range pickup at the front and a sharply attenuated output at the rear. Discrimination between front and rear is said to be approximately 15 db at all frequencies; response is within ± 5 db from 70 to 10,000; level, 62 db below 1 volt/dyne/sq cm at high impedance. Equipped with 4-position output switch giving 50, 200, 500 ohms, or high impedance output; tilting head, and quick-disconnect cable.



Turner type 77.

W. E. REPRODUCER ARM GUARD


A guard, type 706A, for the 5A reproducer arm has been announced by Western Electric.

The guard serves as an automatic latch type support for the reproducer arm and reproducer during intervals between the playing of records.

Guard consists of two main assemblies, a guide housing which mounts on the reproducer panel and a follower assembly which is attached to the reproducer arm.

(Continued on page 38)

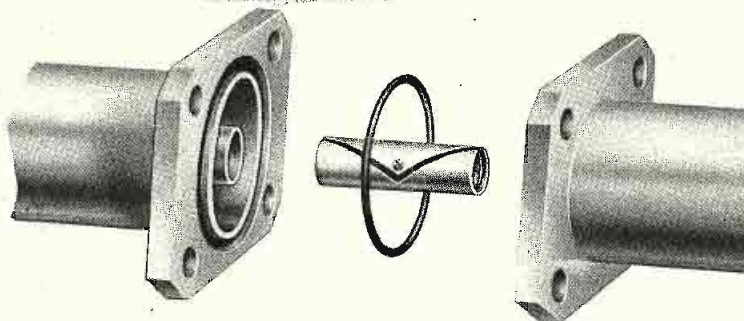WGN-TV SELECTS ANDREW TELEVISION TRANSMISSION LINE *and* ANDREW INSTALLATION SERVICE



Many of America's new television stations are selecting Andrew equipment because of the efficiency of Andrew's flanged coaxial transmission line and the added advantage of having Andrew consulting engineers install it.

Because each television installation poses its own different, individual problem, those stations selecting Andrew have two big advantages: 1) they obtain transmission line and accessories *specially designed for television*, and 2) specialized Andrew consulting engineers are available to direct the installation. These engineers have both the special instruments and the experience to engineer all or any part of the construction of a television station. **NO OTHER TRANSMISSION LINE MANUFACTURER OFFERS YOU THIS COMPLETE INSTALLATION SERVICE!**

Andrew TV transmission line meets official RMA standards and is specially designed for television. Mechanically, it's held to close television tolerances assuring an essentially "flat" transmission line system.

Fabricated in twenty foot lengths with brass connector flanges silver brazed to the ends, sections can be easily bolted together with only a couple of small wrenches. Flanges are fitted with gaskets so that a completely solderless, gas-tight installation results. Markings on the outer conductor indicate where twenty foot sections may be cut to maintain the characteristic 51.5 ohm impedance.

WANT A TELEVISION STATION DESIGNED AND BUILT—FROM THE GROUND UP? LET ANDREW DO IT!

Write today for full details. Andrew will get you on the air.

Television antenna of WGN-TV — Chicago's newest and most powerful television station—showing Andrew 1-5/8" flanged television transmission line.

ANDREW
Andrew
CORPORATION

363 EAST 75th STREET • CHICAGO 19

TRANSMISSION LINES FOR AM, FM, TV • DIRECTIONAL ANTENNA EQUIPMENT • ANTENNA TUNING UNITS • TOWER LIGHTING EQUIPMENT • CONSULTING ENGINEERING SERVICE

KEEP POSTED ON ELECTRON TUBES

Use this convenient coupon
for obtaining the RCA tube
reference data you need.

RCA, Commercial Engineering,
Section GW38, Harrison, N. J.
Send me the RCA publications checked below. I
am enclosing \$..... to cover cost of the books
for which there is a charge.

Name _____

Address _____

City _____ Zone _____ State _____

- ☐ Quick-Reference Chart, Miniature Tubes (Free). [A]
☐ HB-3 Tube Handbook (\$10.00)*. [B]
☐ RC-15 Receiving Tube Manual (35 cents). [C]
☐ Receiving Tubes for AM, FM, and Television Broad-
 cast (10 cents). [D]
☐ Radiotron Designers Handbook (\$1.25). [E]
☐ Quick Selection Guide, Non-Receiving Types (Free). [F]
☐ Power and Gas Tubes for Radio and Industry (10 cents). [G]
☐ Phototubes, Cathode-Ray and Special Types (10 cents). [H]
☐ RCA Preferred Types List (Free). [I]
☐ Headliners for Hams (Free). [J]

*Price applies to U. S. and possessions only.

TUBE DEPARTMENT

RADIO CORPORATION of AMERICA
HARRISON, N. J.



The Industry Offers

(Continued from page 37)

ROLLIN V-H-F/U-H-F SIGNAL GENERATOR

A power type standard signal generator, model 30, with 5 watts nominal r.f. output, 50 ohm impedance with a 160-db range of attenuation (15 volts to 10 μ v), and provision for cw, am or pulse operation, has been announced by the Rollin Company, 3570 N. Fair Oaks Ave., Pasadena 3, Calif. Signal generator can be tuned from 40 to 400 mc. and has a spiral dial scale nearly 4' long, calibrated at intervals of 1% in frequency.



ROBINSON RECORDING MACHINE

A lathe type recorder for professional work in stations and recording studios, has been announced by the Robinson Recording Laboratories, 2022 Sansom Street, Philadelphia 3, Pa. Improved belt drive and dynamically balanced parts are said to reduce the wow factor to .01% on both 78 and 33 1/3 speeds.

Five pitches are available with either inside or outside start: 88, 96, 112, 120 and 128 lines per inch. Quick feed or spiral is obtained by a large hand wheel. Provision is made for eccentric tries and safety groove cutting.



TRIG TOWERS

Trig Towers in self-supporting and guyed types have been announced by the Rostan Corp., 203 East 44th Street, New York 17, New York.

Of triangular design and fabricated of 61 ST-6 aluminum alloy. Ladder with 15" rung spacing, is integral with one side of tower.

Produced in 10' sections, the free standing type comes in heights of 10', 20', 30' and 40' and the guyed type in heights from 10' to 100'.

Designed to withstand 90 miles per hour winds, Guy towers support 200 pounds with a projected area of 10 square feet of round members of a 2 1/8 square feet of flat surface. The self-supporting towers will support 200 pounds with a projected area of 7 1/8 square feet of round members.

PEERLESS ELECTRICAL AUDIO TRANSFORMERS

A 20-20 line of audio transformers, which are said to be flat within 1 db from 20 to 20,000 cycles has been developed by the Peerless Electrical Products Division of Altec Lansing Corporation, 6930 McKinley Ave., Los Angeles 4, Calif.

REVOLUTIONARY SOLDERING IRON **1 Transvision Soldetron**

Tr. Mark Reg. - Pat. Pend.

For Easier, Better Soldering—on Any Job!

- Weighs only 3 ozs., yet can do the job of a 200 watt iron.
- Heats up in 20 seconds from a cold start; saves time.
- Fingertip control; permits soldering without fatigue.



Ready for attachment
and operation on 110
V A.C., 50-60 cycles,
through transformer
supplied with iron, or
6-8 volt A.C. or D.C. without transformer (from
an automobile battery).

Overall size of iron 9 1/4" x 15 1/16"; shipping
weight approx. 4 lbs.

- Ideal for fine precision work in "hard-to-reach" places.
- Readily interchangeable tip-heads; no cleaning or filing.
- Retains heat with switch off up to 1 minute; efficient.
- Bakelite handle, cork covering, for comfortable cool grip.

PRICE: including transformer and Tip-Head "A", \$13.95

5% higher west of Mississippi; fan-rated

Ask your distributor, or for further information write to:

TRANSVISION, INC., Dept. C, NEW ROCHELLE, N. Y.

IN CALIF.: Transvision of Cal., 8572 Santa Monica Blvd., Hollywood 46




MEASUREMENTS CORP. BROAD-BAND TRANSFORMER

A broad-band transformer, type M-286, designed for matching 72-ohm coaxial to 300-ohm balanced line in the range from 40 to 220 mc, has been announced by Measurements Corp., Boonton, New Jersey.

While the unit was developed primarily for use with Measurements type 80 standard signal generator, in conjunction with a 72-ohm matching pad, it is adaptable to other signal generators in the frequency range of the transformer. It may also be used for matching coaxial 72-ohm lines to receivers having an input impedance of 300 ohms. The transformer yields a voltage step-up of 1:2.

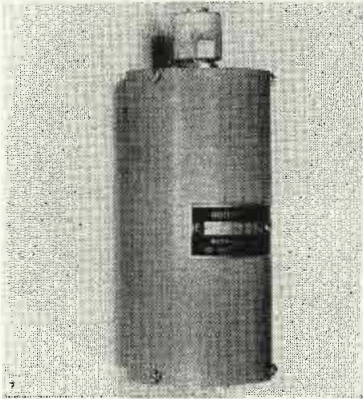The 72-ohm termination of the transformer has AN type UG-21/U (Navy type 49268) coaxial fitting; soldering lugs are provided for connections to the 300-ohm termination.



REK-O-KUT RECORDER

A 12" disc recorder, the *Challenger*, has been announced by the Rek-O-Kut Company, Inc., 38-01 Queens Boulevard, New York.

Features include a *Master-Pro* patented overhead feed mechanism, dual speed 12" turntable and chassis constructed of aluminum castings, instantaneous, speed change to 78 or 33 1/3 rpm, and a high-fidelity amplifier for recording and play back. Has a 16" pickup arm.



CANNON ELECTRIC UTILITY PILOT LIGHT

Electric utility colored pilot lights for signal applications, warning, decoration, and general illumination, have been developed by Cannon Electric Development Company, 3209 Humboldt Street, Los Angeles 31, California.

Available in one type of 8-prism lens to four separate lens or more, mounted on a plate 4 1/2" wide, the depth varying with the number of lens. Lens come in five colors of unbreakable plastic, and are lighted by 93S8 lamps for single contact bayonet base of 12 v. 15 cp. or 6S6 candelabra lamps for screw base in 115 v types.

A variation of the pilot light, the DPF9 uses a 9" 6 w fluorescent lamp for illumination purposes only.

Bulletin No. UPL-1 contains further data.



for Radio and Television receivers . . .

punched, threaded, notched or grooved to meet individual specifications with nominal tooling costs.

These spirally laminated paper base phenolic coil forms and tubes give exceptional performance with the added advantage of lower material costs. Note: We also have available numerous stock punching dies.

Partial list of Radio and Television Receivers in which Cosmalite is used:

Admiral
Arvin
Belmont
Bendix Radio
Colonial
Farnsworth
General Electric
Howard
Magnavox
Motorola
Sentinel
Stewart Warner
Warwick
Wells Gardner
Zenith

Your inquiry will receive immediate and intelligent attention.

Ask also about other Cosmalite types . . . No. 96 COSMALITE for coil forms in all standard broadcast receiving sets. SLF COSMALITE for permeability tuners. COSMALITE deflection yoke shells, cores and rings.

* * *

Spirally wound kraft and fish paper Coil Forms and Condenser Tubes.


* Trade Mark Registered.

The CLEVELAND CONTAINER Co.

6201 BARBERTON AVE. CLEVELAND 2, OHIO

- All-Fibre Cans • Combination Metal and Paper Cans
- Spiroly Wound Tubes and Cores for all Purposes
- Plastic and Combination Paper and Plastic Items

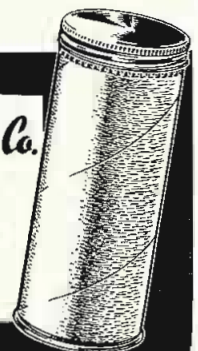PRODUCTION PLANTS also at Plymouth, Wisc., Ogdensburg, N.Y., Chicago, Ill., Detroit, Mich., Jamesburg, N.J.
PLASTICS DIVISION at Plymouth, Wisc. • ABRASIVE DIVISION at Cleveland, Ohio
SALES OFFICES: Room 5632, Grand Central Term. Bldg., New York 17, N.Y., also 647 Main St., Hartford, Conn.
CANADIAN PLANT: The Cleveland Container Canada, Ltd., Prescott, Ontario



*A Blanket
did the trick*



*Today...
the COIL'S the thing*

It's a far cry from smoke signals to electronic communications. And at the heart of electronics lies the coil. We wind coils of great variety for many uses and our 30 years of experience is at your service. Send us your specifications. We shall be glad to quote.



COTO-COIL CO., INC.
COIL SPECIALISTS SINCE 1917
65 Pavilion Ave., Providence 5, R. I.


ADVERTISERS IN THIS ISSUE

COMMUNICATIONS INDEX

JULY, 1948

AMPERITE CO. Agency: H. J. Gold Co.	36
ANDREW CO. Agency: Burton-Brown Advertising	37
BELL TELEPHONE LABORATORIES Agency: N. W. Ayer & Son, Inc.	Back Cover
L. S. BRACH MFG. CORP. Agency: A. W. Levin Co.	35
CANNON ELECTRIC DEVELOPMENT CO. Agency: Dana Jones Co.	34
CLAROSTAT MFG. CO., INC. Agency: Austin C. Leachman & Staff	30
THE CLEVELAND CONTAINER CO. Agency: The Nestor Service Co.	39
COTO-COIL CO., INC. Agency: Frank E. Dodge & Co., Inc.	40
ALLEN B. DUMONT LABS., INC. Agency: Austin C. Leachman & Staff	1
FEDERAL TELEPHONE & RADIO CORP. Agency: J. M. Mathes, Inc.	18, 19
GENERAL RADIO CO.	Inside Back Cover
E. F. JOHNSON CO. Agency: Randolph Bartz Advertising	10
HOWARD B. JONES DIV. CINCH MFG. CORP. Agency: Merrill Simonds Advertising	32
MICO INSTRUMENT CO.	34
JAMES MILLEN MFG. CO., INC.	32
MOTOROLA INC. Agency: Gourham Cobb, Adl. Agency	3
PICKERING & CO., INC. Agency: Sam J. Galtay	33
RADIO CORPORATION OF AMERICA Agency: J. Walter Thompson Co.	15, 38
SORENSEN & CO. INC. Agency: Lindsay Advertising	Inside Front Cover
TECH LABORATORIES Agency: Lewis A. B. Agency	36
TRANSVISION, INC. Agency: H. J. Gold Co.	38
U. S. TREASURY DEPARTMENT	4
ZOPHAR MILLS, INC. Agency: Gunn Mears Adl. Agency	32

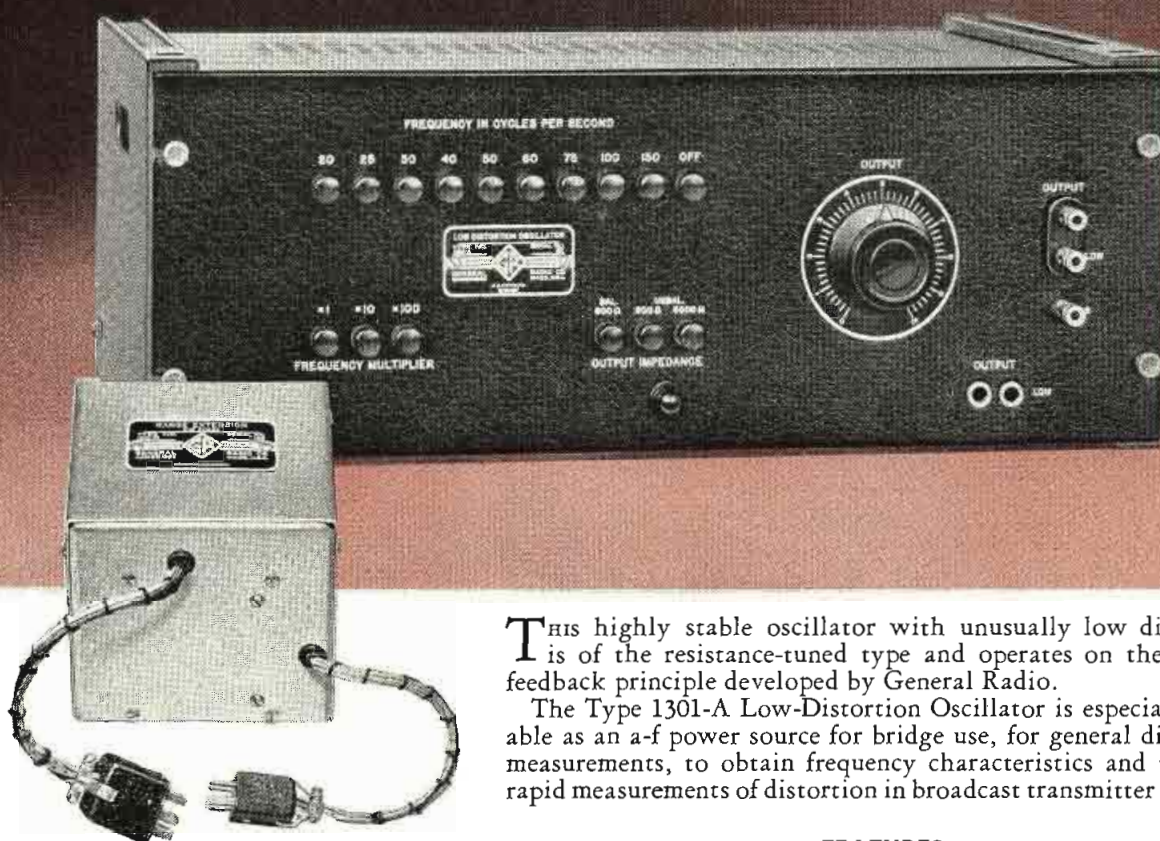for DISTORTION and BRIDGE MEASUREMENTS at 2 to 15,000 CYCLES



This highly stable oscillator with unusually low distortion is of the resistance-tuned type and operates on the inverse feedback principle developed by General Radio.

The Type 1301-A Low-Distortion Oscillator is especially suitable as an a-f power source for bridge use, for general distortion measurements, to obtain frequency characteristics and to make rapid measurements of distortion in broadcast transmitter systems.

FEATURES

● The normal range of this oscillator is 20 to 15,000 cycles. The Range Extension Unit (above) lowers this range by a full decade to 2 to 15 cycles, greatly extending its usefulness to frequencies considerably below those heretofore practicable.

With its very high stability, unusually low distortion and many operating conveniences, the Type 1301-A Low-Distortion Oscillator fills a universal need in distortion and bridge measurements.

TYPE 1301-P1 RANGE EXTENSION UNIT \$70.00

- **WIDE FREQUENCY RANGE** — 20 to 15,000 cycles (with Range Extension Unit, 2 to 15,000 cycles)
- **CONVENIENT TO USE** — 27 fixed frequencies, selected by two push-button switches in logarithmic steps — any desired frequency between steps obtained by plugging in external resistors
- **THREE OUTPUT IMPEDANCES** — 600-ohm balanced to ground; 600-ohm unbalanced; 5,000 ohm unbalanced
- **EXCEPTIONALLY PURE WAVEFORM** — Distortion not more than the following percentages: with 5,000-ohm output 0.1% from 40 to 7,500 cycles; 0.15% at other frequencies. With 600-ohm output 0.1% from 40 to 7,500 cycles; 0.25% from 20 to 40 cycles and 0.15% above 7,500 cycles
- **HIGH STABILITY** — Frequency is not affected by changes in load or plate supply voltage. Drift less than 0.02% per hour after a few minutes operation
- **ACCURATE FREQUENCY CALIBRATION** — Adjusted to within $1\frac{1}{2}\% \pm 0.1$ cycle
- **NO TEMPERATURE OR HUMIDITY EFFECTS** — In ordinary climatic changes, operation is unaffected

TYPE 1301-A LOW-DISTORTION OSCILLATOR \$395.00

GENERAL RADIO COMPANY

Cambridge 39,
Massachusetts

90 West St., New York 6

920 S. Michigan Ave., Chicago 5

950 N. Highland Ave., Los Angeles 38

RUBBER RECIPE

Rubber compounds to the tune of some 35 million pounds a year go into Bell System plant. Each compound must meet many requirements for resistance to humidity, oxygen, ozone, light and abrasion. The right properties depend on skillful selection and compounding of ingredients; this is one of the jobs of Bell Laboratories.

Sulphur, one essential ingredient of rubber, can also be corrosive. That seemed to rule out rubber on telephone cords. But Bell chemists found that if they held sulphur to the bare minimum, corrosion ceased. Now your handset cord has long life, is less susceptible to moisture as, for example, from a wet umbrella.

Connecting your home to the telephone wire on the street is a "drop" — one hundred feet or more of rubber-insulated wire. Once this wire was protected from ozone, light and abrasion by an impregnated cotton braid; but water leached the impregnant, and the braid rotted. Bell chemists tested scores of synthetics, and selected neoprene as an exterior covering with many times the life of braid.

Rubber is only one of many types of insulation developed by the Laboratories for the Bell System; insulation is only one of the Laboratories' problems in providing a quick, economical path for your voice.




BELL TELEPHONE LABORATORIES

EXPLORING AND INVENTING, DEVISING AND PERFECTING FOR CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE



COMMUNICATIONS

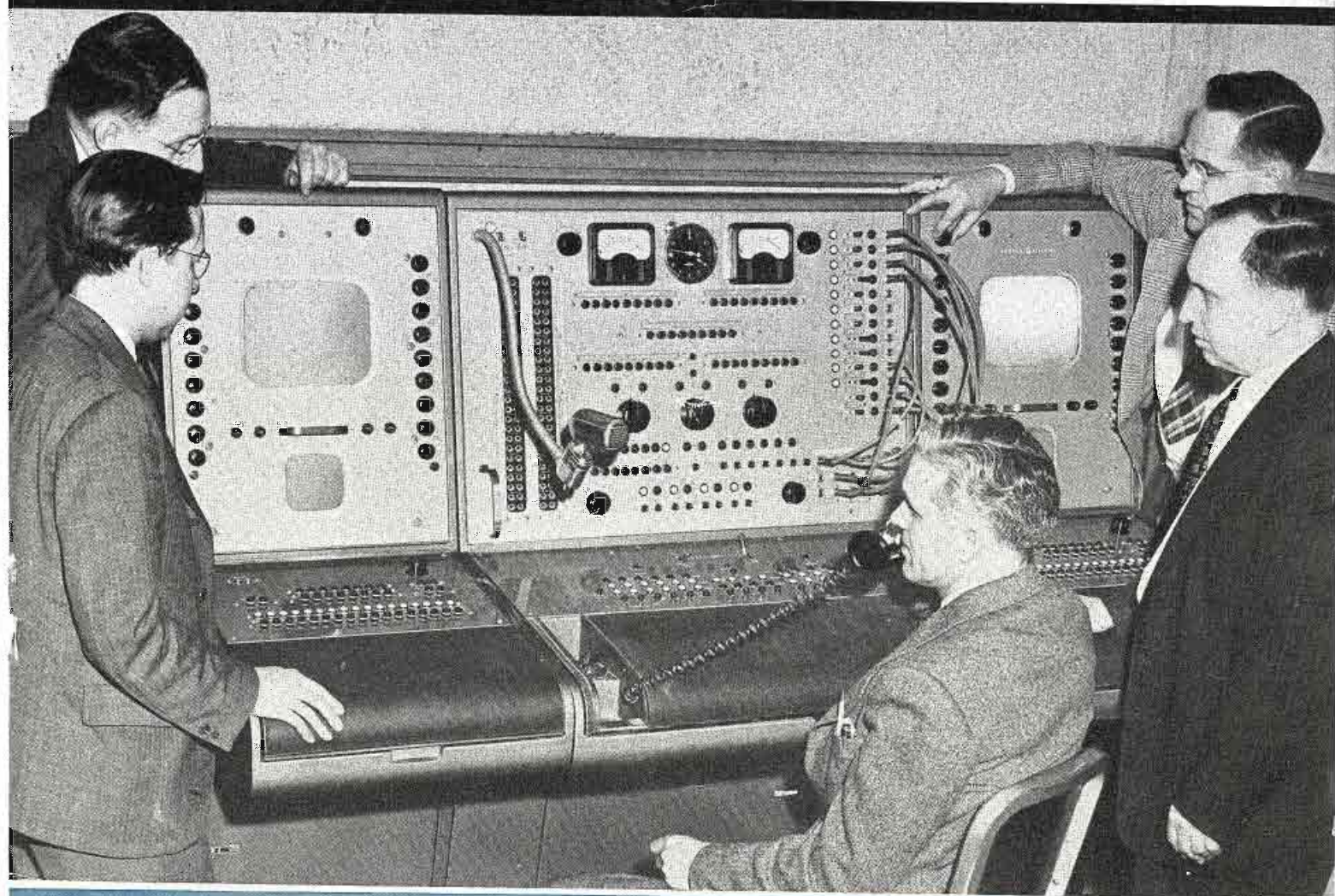INCLUDING "RADIO ENGINEERING" AND "TELEVISION ENGINEERING"



★ TV ANTENNA DESIGN

★ A-M, F-M AND TV ANTENNA INSTALLATIONS

1948


JUNE

Self Control

Here's how
the **CONTROLLER** answers
typical regulation problems


Q. An AC requirement. Can you stabilize
the output of a transformer?

ANSWER

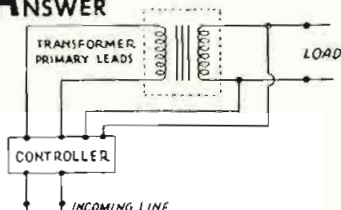


Q. Can you selectively regulate a number
of DC voltages and currents?


ANSWER

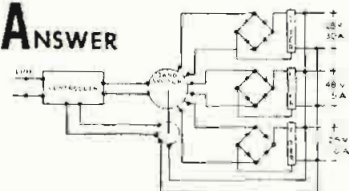


Q. Can the CONTROLLER stabilize a gen-
erator field to regulate its output?

ANSWER

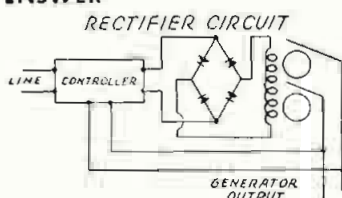

—of AC, DC or RF outputs in any
one circuit, selectively stabilized
over wide ranges of line and load
with the new  **SORENSEN**
ELECTRONIC CONTROLLER

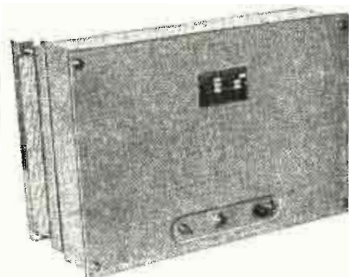The AC output of the CONTROL-
LER will swing between 85-145
VAC, AUTOMATICALLY adjust-
ing the output of your unit
against line and load variations.
By referencing this output back
to the CONTROLLER you get
output regulation.



TECHNICAL SPECIFICATIONS

The controlled circuit must make available at least one watt of power
to the CONTROLLER.

Input voltage range: 95-125 volts AC
(50 or 60 cycles)

Load range: 200 to 2000 VA

Regulation accuracy: 0.5% at the controlled point

write today for more information on the new CONTROLLER. Arrange
to have a Sorensen Engineer analyze voltage regulation requirements
in your plant. He can select a Sorensen unit or suggest a special
design to fit your unusual application.


Represented in all principal domestic and foreign cities.



The FIRST line of standard ELECTRONIC Voltage Regulators

SORENSEN

& COMPANY, INC. • STAMFORD, CONNECTICUT

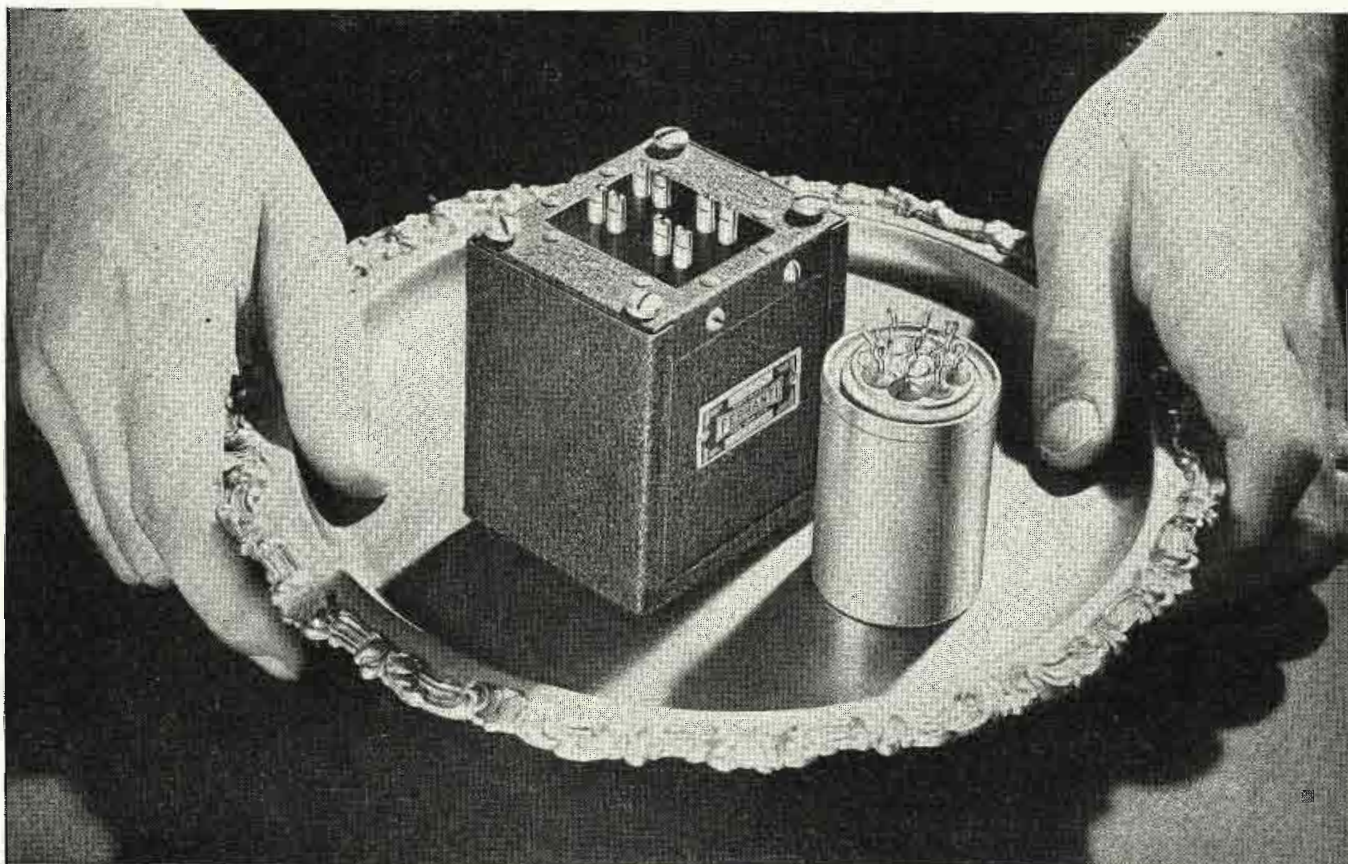

For quality and service

choose **FERRANTI** transformers

From our more than 20 years' experience as transformer specialists, come precision transformers of every type—custom-made for YOUR new applications. FERRANTI facilities permit unusual service to each customer, whether large or small, and insure prompt deliveries.


**AUDIO TRANSFORMERS
POWER TRANSFORMERS**

**AUDIO FILTERS
REACTORS**

HERMETICALLY SEALED WHEN SPECIFIED

We also build power supply units and electronic assemblies to specifications at prices comparable to those of stock assemblies. We invite your inquiries.

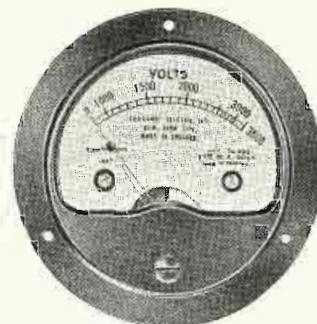ALSO FOR MODERN
HIGH VOLTAGE DEVELOPMENTS
WHERE ZERO CURRENT DRAIN IS
IMPERATIVE



THE FERRANTI ELECTROSTATIC
VOLTMETER

Types available for maximum readings from 150 to 3500 volts. 2½ in. dial, flush mounting, projecting and portable models. Write for informative literature.

● *Ferranti Electric, Inc.* ● **RCA BUILDING** ●

30 Rockefeller Plaza • New York 20, N. Y.

COMMUNICATIONS

Including Television Engineering, Radio Engineering, Communication & Broadcast Engineering, The Broadcast Engineer, Registered U. S. Patent Office.

LEWIS WINNER

Editor

F. WALEN

Assistant Editor

Bryan S. Davis, President

Paul S. Weil, Vice Pres.-Gen. Mgr

F. Walen, Secretary

A. Goebel, Circulation Manager

Cleveland Representative:

James C. Munn
2259 Delaware Dr., Cleveland 6, Ohio
Telephone: Erieview 4726

Pacific Coast Representative:

Brand & Brand
1032 W. Sixth St., Los Angeles 14, Calif.
Telephone Michigan 4732
315 Montgomery St., San Francisco 4, Calif.
Telephone Douglas 4475

Wellington, New Zealand: Te Aro Book Depot,
Melbourne, Australia: McGill's Agency.

Entered as second-class matter Oct. 1, 1937 at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price, \$2.00 per year in the United States of America and Canada, 35 cents per copy, \$3.00 per year in foreign countries, 35 cents per copy.

COMMUNICATIONS is indexed in the Industrial Arts Index.

COVER ILLUSTRATION

G.E. master tv console recently installed at WNAC-TV. At the console, left to right: I. R. Robinson (back); C. W. Stone, Thomas Foster at phone; Laird Whitledge and H. W. Whittemore (back) of the WNAC and WNAC-TV engineering departments.

BROADCAST ANTENNAS

V-F, F-M and TV Antenna Installations 10

Antenna Systems Recently Completed and Now Being Installed Throughout the Country with Square Loop, CloverLeaf, Batwing and Pylon Antennas.

TELEVISION ENGINEERING

Wide-Range Dual-Band TV Antenna Design Lester L. Libby 12

Antenna for 54 to 88 and 174 to 216 Mc. Provides Substantial Uniform Directivity Pattern and Constant Input Impedance.

TV Transmitter Design G. Edward Hamilton 20

Modulated Amplifier Characteristics, Adjustment of Video Signal Amplitude, Equipment Used for Adjustment of Class B Power Amplifiers.

BROADCAST STATION MAINTENANCE

Equipment Failure-Control System for Broadcast Stations F. E. Butterfield 16

Inspection, Maintenance and Trouble-Data-Recording Procedures.

TV/F-M STATION DESIGN

NBC TV/F-M in Washington, D. C. 28

Antenna Equipment Setup and Antenna-Line Systems at WNBW and WRC-FM.

TRANSMITTING TUBES

Tube Engineering News 32

Wide-Range Tuning System for Magnetrons, Flying Spot CRTs, Notes on Interchangeability of 5516 and 2L24.

MONTHLY FEATURES

News and Views Lewis Winner 9

Veteran Wireless Operators' Association News 25

News Briefs of the Month 26

The Industry Offers 38

Advertising Index 40

Entire contents Copyright 1948, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone Murray Hill 4-0170




Trolley Service restored in a jiffy!

CINCINNATI STREET RAILWAY SPEEDS EMERGENCY WORK WITH 2-WAY *Motorola* RADIO and SYLVANIA LOCK-IN TUBES

NO time lost in restoring service on the lines of the Cincinnati Street Railway Company! 2-way Motorola equipment maintains constant communication between headquarters and mobile equipment—5 tower trucks, 2 wreckers, 2 general-purpose trucks, 7 official and 5 supervisors' cars. Needed repairs are under way usually in a matter of seconds!

For a job as vital as this, Motorola has found it can depend on Sylvania Lock-In Tubes. These sturdy tubes stay firmly in place—unaffected by jolting and jarring—offer outstanding electrical advantages too. Connections are short and direct . . . there are no soldered joints, few welded ones. Getter located on top . . . leakage reduced by separating getter material from leads. See Sylvania Distributors, or write Radio Tube Division, Emporium, Pa.

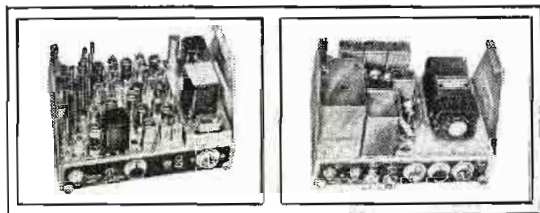


Transmitter and Receiving Unit used in Cincinnati Street Railway Company's mobile equipment, manufactured by Motorola, Inc., Chicago.


The famous Lock-In Tube's superiority makes it the ideal choice for equipment on the road, in the air, on the rails, marine radar, FM and television.



SYLVANIA ELECTRIC

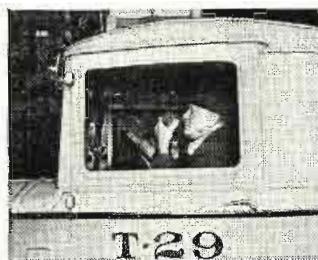

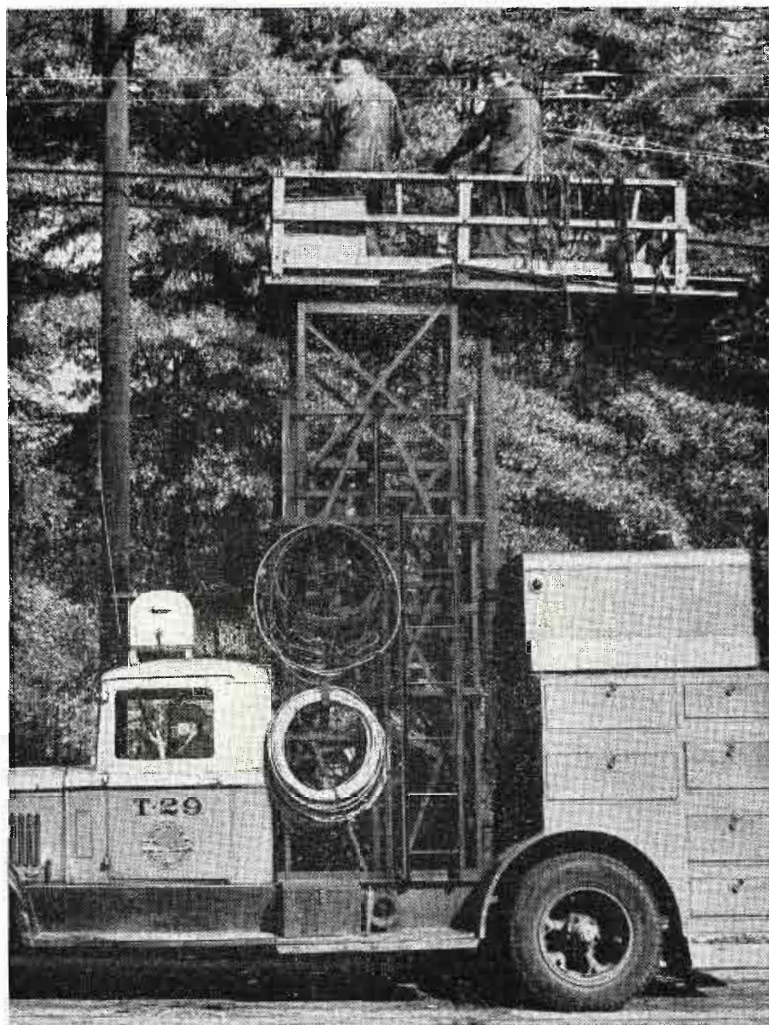Service restoration gets under way without delay as equipment responds to dispatcher's instructions.



Headquarters can quickly direct the needed equipment to the scene of a tie-up.



FOR

FM AND Television

PHILCO VISUAL ALIGNMENT GENERATOR

PHILCO 7008. The only instrument of its kind, combining all functions for complete, accurate visual alignments on Television and FM receivers. Includes 5 different signal generators and their associated controls; a complete oscilloscope with centering, gain, focus, intensity, phasing and blanking controls, and power supplies. Separate RF probe permits measurements of sensitive circuits without disturbance. Removable crosshatch screen for special ultra-short 3" cathode-ray tube. Compartment for storage of all cables, including RF probe.



PHILCO MAKES TEST EQUIPMENT HISTORY

In creating precision instruments for radio measurements, in compact, portable, inexpensive form . . . Philco engineers have repeatedly achieved results considered impossible by experts. Especially so, in the new Philco 7008 Visual Alignment Generator for FM and Television . . . which combines in one economical instrument functions that can be approached only by a cumbersome, costly collection of conventional devices. The 7008 alone performs complete, accurate visual alignments . . . saves the test engineer's time . . . makes the job easier. In every unit of today's Philco Test Equipment line you will find equally important advantages.

WRITE FOR TECHNICAL LITERATURE TO: PHILCO CORP., PHILADELPHIA 34, PA.


NO. 7008 PHILCO VISUAL ALIGNMENT GENERATOR
NO. 7001 PHILCO ELECTRONIC CIRCUIT MASTER
NO. 7070 PHILCO R.F. SIGNAL GENERATOR

NO. 5072 PHILCO CROSSHATCH GENERATOR
NO. 7030 PHILCO DYNAMIC TESTER
NO. 7019 PHILCO JUNIOR SCOPE




PHILCO SIGNAL GENERATOR

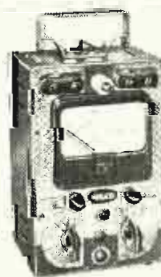MODEL 7070. Range from 100 kc to 110 mc—all fundamentals! No switching trouble at any frequency. Residual output less than 5 micro-volts! Model 7170 for FM also available.



PHILCO ELECTRONIC CIRCUIT MASTER

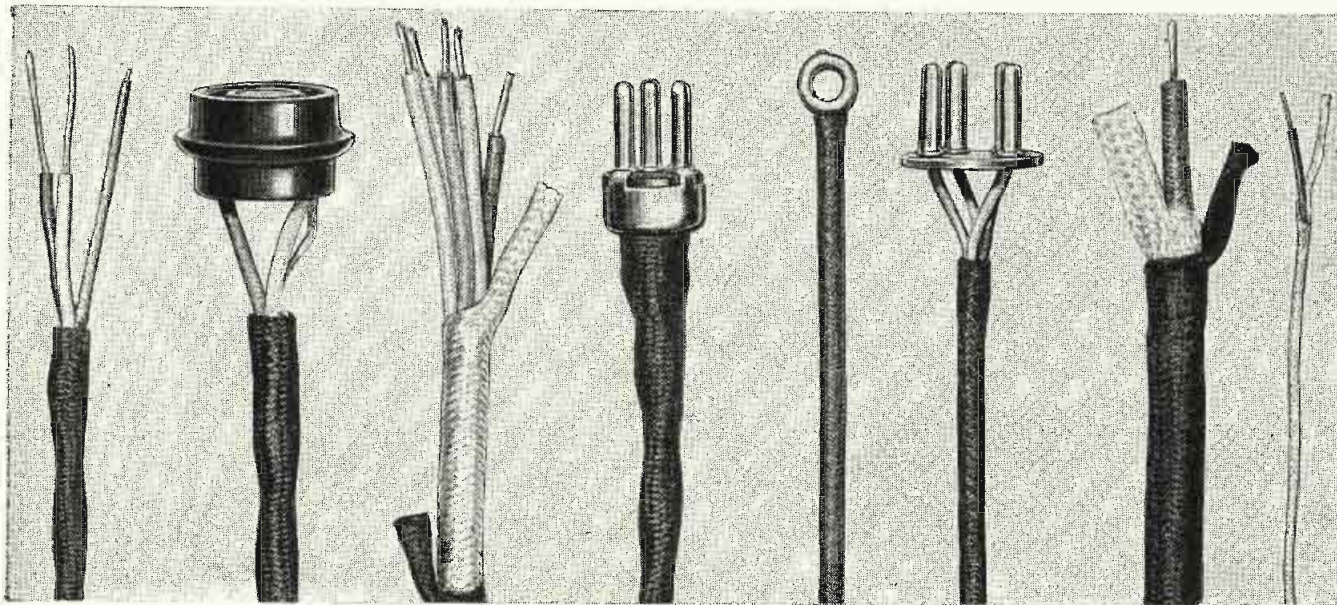MODEL 7001. Uses exclusive vacuum tube voltmeter and electronic bridge circuit. All ranges and functions including 10,000 volts AC or DC. Probe available for RF measurements.



WIRES and CABLES

THE *lifeline* OF ELECTRONIC EQUIPMENT

When you list the qualities most desirable in a supplier of wires and cables for your electronic equipment, you will find that Lenz most nearly answers your description of a dependable source.

First, this company has the engineering background and experience, the knowledge of your requirements in wires and cables that are needed to help draft your specifications.

Second, it has the facilities to produce these wires


and cables in volume exactly to specifications, economically and promptly.


Third, it is a reliable organization with over 40 years background of dependable service to the communications industry.

Make Lenz your principal source for wires and cables. A Lenz wire engineer will gladly consult with you regarding your special requirements. Correspondence is invited.

"IN BUSINESS SINCE 1904"

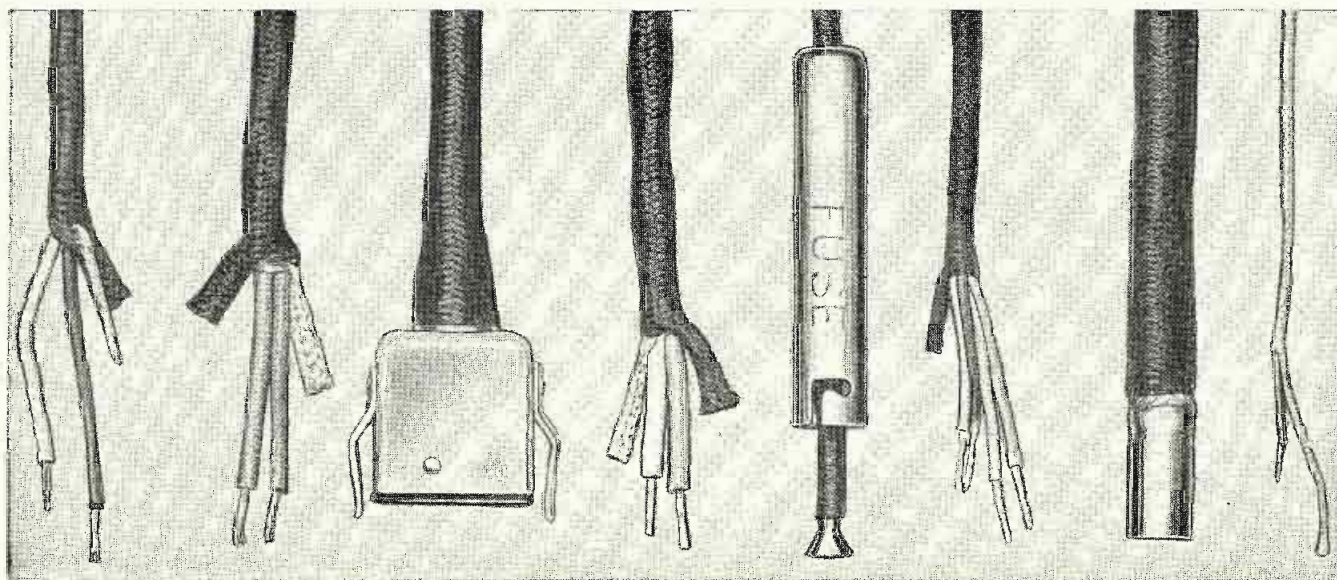LENZ ELECTRIC MANUFACTURING CO. • 1751 No. Western Avenue, Chicago 47, Illinois



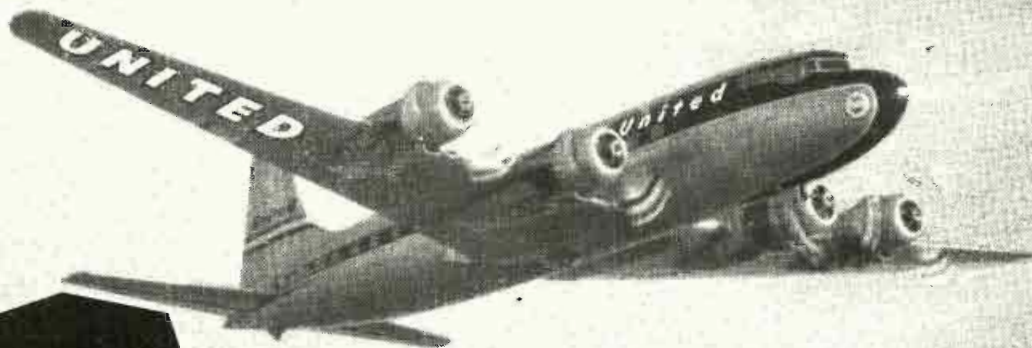

WILCOX..
First Choice
 OF THE
MAIN LINE
AIRWAY


UNITED AIR LINES Selects New WILCOX VHF Receiver For Ground Installations

*New Fixed Frequency Receiver
 Offers New Performance Features
 in the 118-136 Mc. Band*

- Selectivity Permits 100 Kc. Adjacent Channel Operation
- No Interference from Spurious Frequency Responses
- Simplicity of Circuit Design Means Easy Maintenance
- New Noise Limiter Means Better Reception
- Single Unit Construction Saves Space



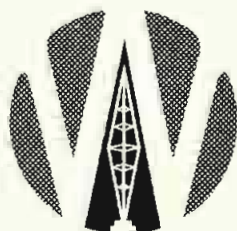*Write Today For Complete
 Information on the
 WILCOX 305A RECEIVER*



THE NAME

WILCOX MEANS
Dependable Communication

WILCOX ELECTRIC COMPANY • Kansas City 1, Missouri

A QUIET REVOLUTION IN CAPACITOR DESIGN

THE SMALLEST MOLDED
TUBULAR EVER MANU-
FACTURED! . . .
and rated up to 125° C!

A PROVEN PRODUCT NOW
IN MASS PRODUCTION!

ACTUAL SIZE
ILLUSTRATION
TYPE 65P

UNIQUE, MINERAL-
FILLED MOLDING MA-
TERIAL! . . . Provides
unequalled protection
against moisture absorp-
tion even under condi-
tions of extreme humidity!

Seven Physical Sizes
Color-Coded and Available in 20%, 10% and 5% Decade Values
TABLE OF MAXIMUM NOMINAL CAPACITIES

	Mold Size	100V @ 125° C.	200V @ 85° C.*	400V @ 85° C.	600V @ 85° C.
65 P	.175" D. x 1-1/16"	.015	.01	.0068	.0022
	.195" D. x 1-1/16"	.022	.015	.01	.0033
	.250" D. x 1-1/16"	.047	.033	.022	.0068
	.375" D. x 1-1/16"	.15	.1	.068	—
75 P	.175" D. x 3/4"	.0068	.0047	.0033	.001
	.200" D. x 3/4"	.01	.0068	.0047	.0015
	.250" D. x 3/4"	.022	.015	.01	.0033

* alternate rating 150V @ 125° C.

NEW SPRAGUE MOLDED PROKARS*

... dependable capacitors for sub-miniature assemblies

SUB-MINIATURE PAPER CAPACITORS IN METAL CANS WITH HERMETIC, GLASS-TO-METAL SEAL

for the most severe applications

Yes, this little can houses a high quality hermetically sealed Paper Capacitor! Rated at 100 volts, D C Working, this .5 mfd. unit measures .4" x 1 1/8". Presently being manufactured in quantity, variations of this sub-miniature type can be made to your specifications. Write for complete information about this and even smaller hermetically sealed units now in production as shown below.

These new molded Prokars were designed specifically to satisfy stringent military requirements. Types 65P & 75P are now in mass production and are available in a wide range of capacities—from .00047 mfd. to .15 mfd! Though higher in price than standard units, they easily justify the term "premium" in performance. Rated for —50° C to 125° C operation, these small but rugged units are ideally suited for any electrical or electronic application in which size, temperature, humidity and physical stress are dominant considerations.

Write for Engineering Bulletin No. 205 A

*T. M. Reg. U. S. Pat. Off.

SPRAGUE

SPRAGUE ELECTRIC COMPANY,
NORTH ADAMS, MASS.

PIONEERS OF

ELECTRIC AND ELECTRONIC PROGRESS



These "sound jurors" record their preferences as they listen over test circuits.

Trial by "Sound Jury"



The engineer in the foreground talks over the test circuits which the other engineer sets up on a "circuit simulator."

AFTER Bell Laboratories engineers have designed a new talking circuit, they measure its characteristics by oscilloscopes and meters.

But a talker and a listener are part of every telephone call, and to satisfy them is the primary Bell System aim.

So, before the circuit is put into

operation, a "sound jury" listens in. An actual performance test is set up with the trained ears of the jurors to supplement the meters.

As syllables, words, and sentences come in over the telephones, pencils are busy over score sheets, recording the judgment of the listeners on

behalf of you and millions of other telephone users.

Targets of the transmission engineer are: your easy understanding of the talker, the naturalness of his voice, and your all-around satisfaction. To score high is one of the feats of Bell System engineering.

BELL TELEPHONE LABORATORIES

Exploring and inventing, devising and perfecting for continued improvements and economies in telephone service



COMMUNICATIONS

LEWIS WINNER, Editor

JUNE, 1948

Still Going Up

STATION CONSTRUCTION continues to race on. As of June 1, 350 had received CP's for a-m stations and 788 had received construction permits for f-m stations, while 118 had been granted conditional grants. The total authorization scoreboard for a-m and f-m stations now reads 2028 for a-m and 1035 for f-m. FCC reports that there are currently 543 f-m and 24 tv stations on the air. Incidentally, as of June, 95 had received tv construction permits, which adds up to a total of 102 authorizations for tv.

Field reports from FCC and industry indicate that we will see quite a jump in on-the-air operation and CP grants before the year is over, particularly in f-m and tv, with f-m possibly climbing to 2,000 authorizations and tv to at least 150.

Fax Goes Commercial

THE GREEN LIGHT for commercial facsimile has been turned on by the FCC and on July 15, eleven f-m stations now operating experimentally will go commercial.

According to FCC either the simplex or multiplex methods will be permitted. The simplex system interrupts the aural program during facsimile transmission, while in multiplex simultaneous transmission is effected. Accordingly, simplex transmissions will be limited to one hour between 7 A.M. and midnight, with no limit for the hours between midnight and 7 A.M., while multiplex transmission will be permitted for a maximum of three hours between 7 A.M. and midnight as well as any time between midnight and 7 A.M.

The recording width of 8.2" for 105 lines-per-inch scanning has been adopted a standard, although other paper widths will be permitted with the appropriate number of lines per inch.

Good luck to fax!

Directional Antenna Performance

IN DESIGNING A COMPLETE BROADCAST station installation, the directional antenna system must receive priority attention and many factors

judged. Since the field gain of a directional array is a function of the tower spacing, field ratios and field phases, we have a number of variables to consider such as types of arrays, constants of transmission lines, coupling equipment, ground system, guying, etc.

An excellent interpretation of this problem was presented at the recent NAB Conference at Los Angeles, by A. Earl Cullum, Jr. Discussing guy wires, he showed how they can seriously affect the pattern shape. This effect can be minimized by installing the guys so that they are symmetrical with respect to the line of towers and by breaking them up with insulators near the tower and near the ground as well as throughout their length. It is also necessary, he said, that the tower section be bonded at all legs so that the current in the tower is equally distributed. Cullum pointed out that even the ladders must receive careful attention, requiring sectionalizing so as to carry a minimum of current or secure bonding so as to carry a proportional amount of the tower current.

Analyzing the features of current and phase-monitor antenna systems Cullum said that this type of system provides a reliable indication of the magnitude and phase relationship of the fields radiated by the elements of a directional array. Describing the location of a sampling loop with this equipment, he pointed out that excellent results have been attained by locating the loop in one leg of a tower so as to sample the current at that point, although in a wide base tower, each leg can and does act independently. A loop which samples a single leg of a well-bonded thin tower often provides the best indication. To be sure that the sample current is accurately indicated by the monitor, Cullum said that all sampling lines from the loops through the isolation coils and to the monitor, must be identical as to length and characteristic impedance, must be properly terminated at the monitor and should be maintained near the same temperature throughout the system.

S-T F-M U-H-F Relays

WITH F-M ANTENNA SYSTEMS being located in remote high-altitude areas, the need for u-h-f high-fidelity studio-to-transmitter links has grown, prompting intensive activity in the development and production of suitable equipment. As a result of one s-t-l research program, a 10-watt transmitter featuring a radial cavity in the plate output circuit, operating on the fundamental mode, has been developed. Describing this transmitter at the recent NAB Engineering Meeting, D. J. Nigg and W. G. Broughton of G. E. pointed out that the system uses ± 75 kc deviation for 100% modulation and direct f-m. The last three stages in the transmitter employ 4X150A tetrodes as frequency doublers. Open transmission line circuits are used for these doublers except for the plate circuit of the output stage.

Antennas are of the 40" parabolic-reflector type, with dipole feed. Receiver is a double conversion superhet. Frequency range of transmitter and receiver are in the s-t-l band of 920 to 960 mc.

U-H-F TV

WITH TV ALLOCATION REQUESTS pouring into Washington, and the need for additional channels imminent, the channels upstairs in the 475 to 890-mc bands are receiving quite a probing. Out in San Francisco, former FCC chief engineer, George P. Adair, now a consultant, put a 600-mc 700-watt tv setup on the air recently (W6XJD) to explore propagation characteristics at these frequencies.



In Washington, a 510-mc 25-kw station will be installed in the Wardman Park Hotel by RCA to study u-h-f tv. The transmissions of WNBW on 67 mc will be duplicated on the 510-mc transmitter during these tests.

To conduct field test comparisons, observers will use converters on standard tv receivers for u-h-f pickup.


Results of these and other tests will be detailed at the FCC hearings in Washington on September 20.

A complete report on these sessions will appear in COMMUNICATIONS. Watch for it.—L. W.


A-M, F-M And TV

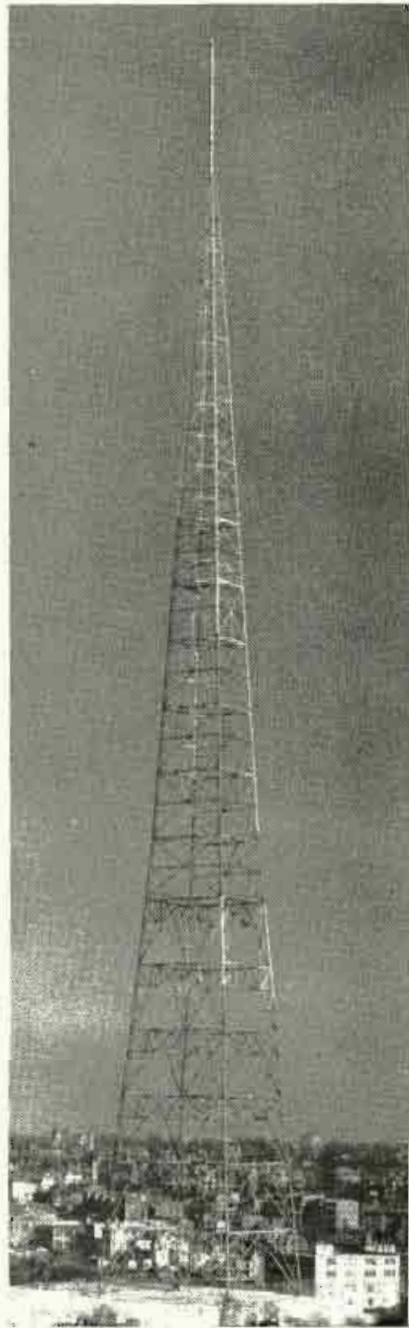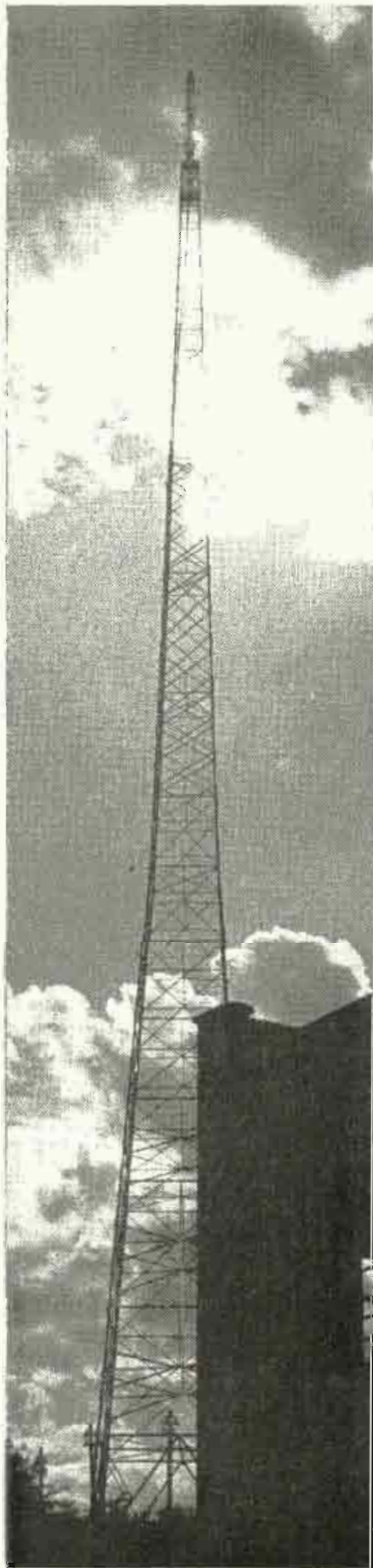


Left: Modified a-m Blaw-Knox tower supporting a 4-bay W.E. Clover leaf f-m antenna at WSTV, Steubenville, Ohio, providing simultaneous a-m and f-m broadcasts. (Courtesy Westinghouse). Top: A four section RCA pylon f-m antenna atop a Blaw-Knox tower at WCTS, Cincinnati, Ohio. Right: The f-m antenna of WHOO, Orlando, Fla., with an 8-bay FTR square loop antenna mounted atop a 414' Truscon guyed pipe tower.

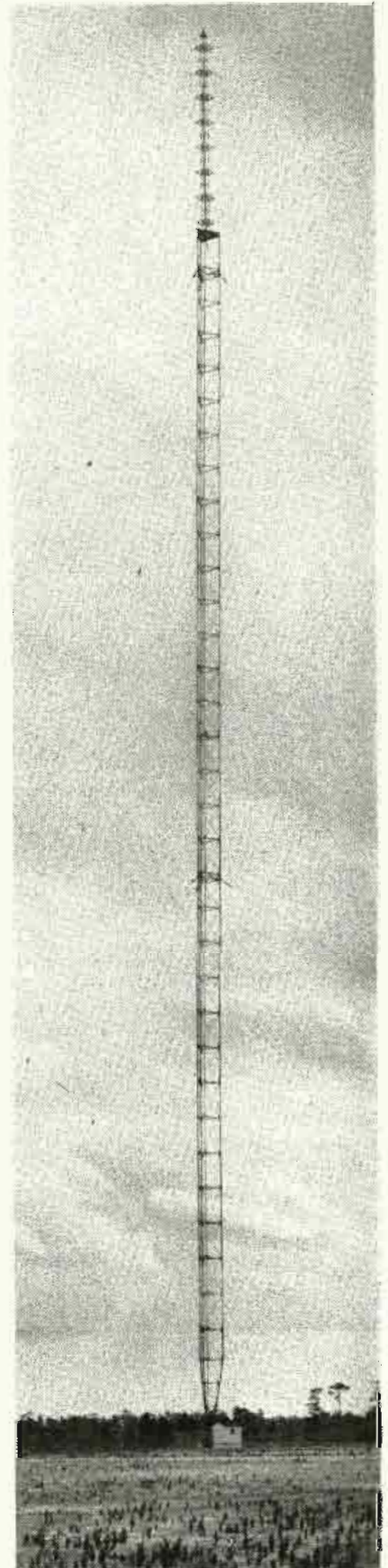


Antenna Installations

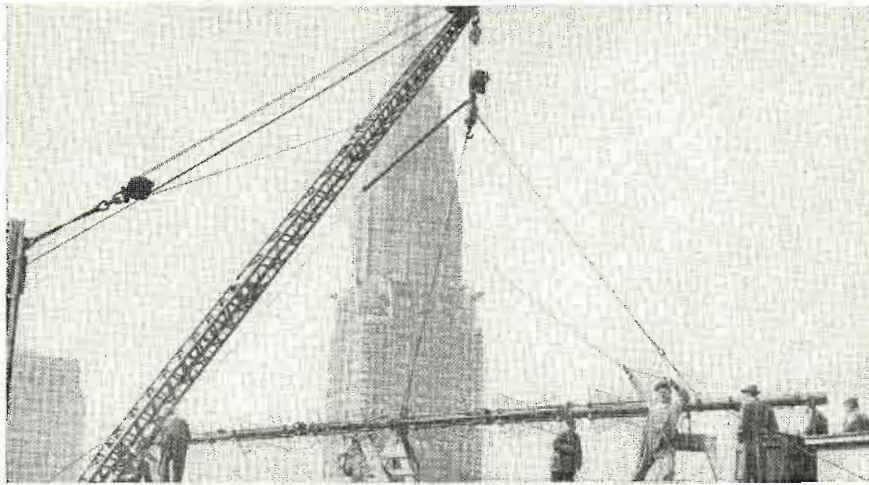

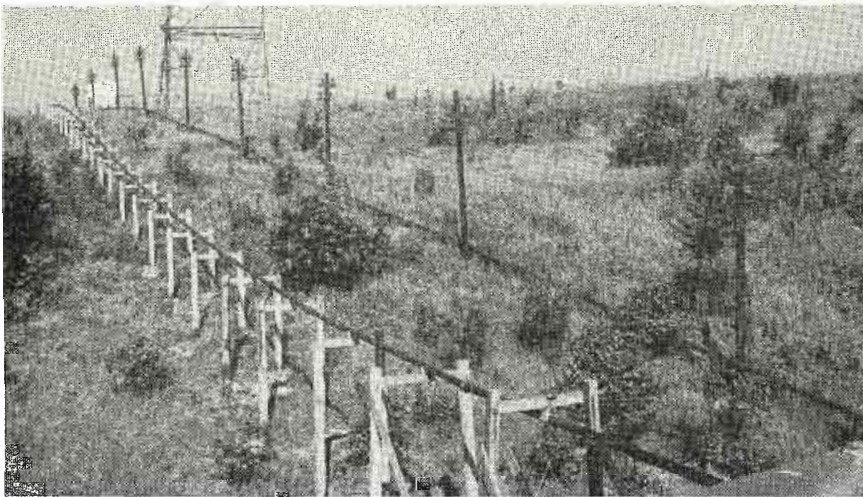Top: Six-bay RCA super turnstile antenna being hoisted to the roof of the 36-story News Building in New York City for WPIX, the *Daily News* tv station which went on the air on June 15 on channel 11. Below: Coaxial transmission line (3¼" Andrew type) at WSTV, Steubenville.



Below: View of the 300' microwave tower recently completed for the Federal Telecommunication Laboratories at Nutley, N. J. The tower houses experimental antennas and equipment for research and development work in television, aviation communications, multiplexing, microwave antennas, point-to-point communications, etc. Right: Three-bay RCA super turnstile tv antenna being mounted atop an RCA pylon i-m antenna for WBZ-TV near Harvard Stadium, Mass. Tower is 656' high and designed to service an area of 40 miles radius of Boston.

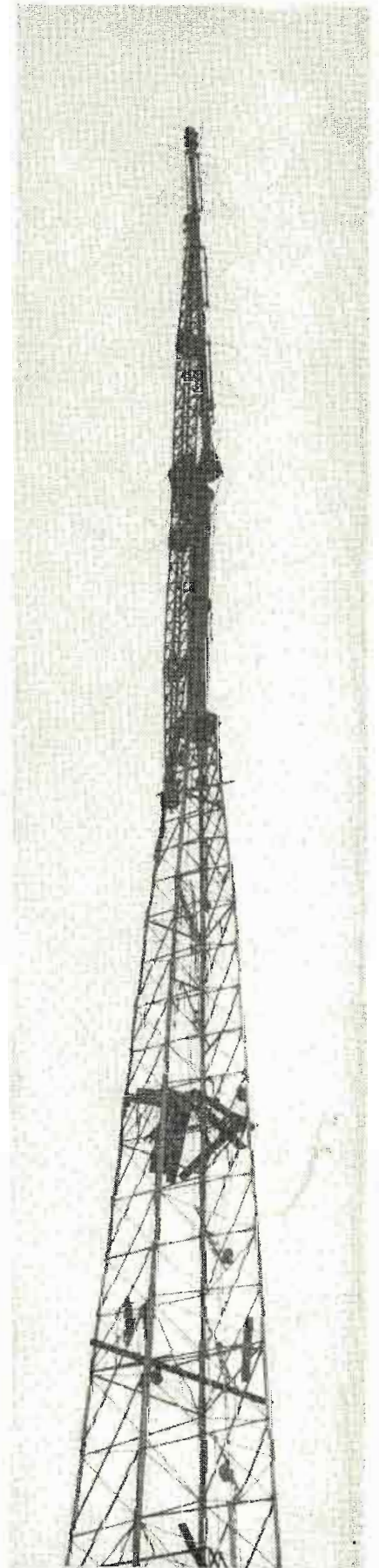

Wide-Range Dual-Band TV Antenna Design

THE DIPOLE ANTENNA in one form or another is perhaps the most commonly employed type of antenna for operation in the v-h-f range. The half-wave mode of operation of the dipole is frequently used as a standard of reference for describing the gain of an antenna array or system, and the impedance and directivity characteristics of the half-wave dipole have been evaluated and discussed in many papers¹ and books.²

In general, the values of feed-point resistance and reactance of a dipole antenna versus frequency will be a function of the geometric shape of its conductors. For cylindrical conductors of length l and diameter d , such as shown in the antenna of Figure 2, Schelkunoff³ ascribes an average characteristic impedance parameter, K_a , given by the expression

$$K_a = 276 \log_{10} \frac{l}{d} - 120 \quad (1)$$

and also shows families of curves relating the resistance and reactance of such antennas to their electrical length for various values of K_a , ranging from 500 to 1,200.

From a practical consideration of strength, weight and cost of a tv receiving antenna it becomes evident that a conductor diameter of the order of $\frac{1}{2}$ " is a very desirable size, and a dipole length cut to be resonant at 65 mc (the approximate center frequency of the lower television band) is the best compromise for good overall response and service in this range. The dipole length for half-wave resonance at 65 mc is very closely 7', so that the resultant K_a is approximately 600 for a conductor diameter of $\frac{1}{2}$ ".

The curves of feed-point resistance and reactance of this dipole versus frequency are accordingly those shown in Figure 3, and labeled R and X , respectively. The complex feed-point impedance at any frequency is $R + jX$, taking due note of the sign of X as given in the curve of Figure 3. Hence at 65 mc the antenna impedance is $58 + j0$ ohms. At 55 mc, the antenna impedance is $38 - j120$ ohms and at 80 mc, the antenna impedance is $113 + j140$ ohms, etc. It is evident from examination of the curves that, although the resistive component of the antenna impedance varies appreciably with frequency, the reactive component in the

Versatile, Sturdy Antenna Designed to Cover the 54 to 88 and 174 to 216-MC TV Bands, Provides a Substantially Uniform Directivity Pattern and Constant Input Impedance. Can Be Operated in Conjunction with Either Balanced (Twin Lead) or Coaxial Transmission Lines. Antenna Can Be Grounded for Lightning Protection.

by **LESTER L. LIBBY**

Chief Engineer
Ohmega Laboratories, Inc.

region of half-wave resonance varies much more rapidly, hence making it difficult to match the antenna to a transmission line within more than a narrow band of frequencies immediately surrounding the resonance frequency.

Broad-Banding the Dipole

Let us consider now the possible methods whereby the useful range of operable frequencies, i.e., the bandwidth, of the foregoing antenna may be increased. One expedient which suggests itself is to connect in series with

the antenna and its transmission line a reactance of equal magnitude and opposite sign to that which the antenna exhibits at all frequencies. This would then result in an antenna whose impedance was purely resistive at all frequencies and equal in value to the R curve shown in Figure 3. If this hypothetical antenna were operated with a 73-ohm transmission line, it would match this line to a reflection factor of less than 0.5 (corresponding to a voltage standing-wave ratio of less than 3:1) between the frequency limits of 45 and 90 mc. However, a series-compensating reactance having the complementary characteristics described is not readily realizable nor available, so that such a completely compensated antenna remains purely hypothetical. It is possible, however, to obtain partial reactive compensation of the antenna by means of a shunt reactance of proper magnitude and opposite sign to that of the antenna reactance. Such a reactance is realizable by shunting a shorted parallel-wire transmission line stub, of effective electrical length equal to a quarter-wave at a frequency slightly above the resonant frequency of the antenna, across the antenna feed-point terminals, and choosing the characteristic impedance of this transmission line stub to be in the range from 50 to 100 ohms. Figure 4 illustrates an antenna system of this type while the dotted curve of Figure 3 shows the reactance characteristic of the shorted stub for a Z_0 of 50 ohms, and a stub resonant frequency of 70 mc. It is apparent from examination of Figure 3 that the stub reactance tends to tune out the antenna reactance in the neighborhoods of 54 and 82 mc. At the same time, the high impedance of the

¹For example, S. A. Schelkunoff, *Theory of Antennas of Arbitrary Size and Shape*, Proc. I.R.E.; September, 1941.

²For example, N. Marchand, *Ultrahigh Frequency Transmission & Radiation*; John Wiley & Sons, Inc., New York, N. Y.; 1947.


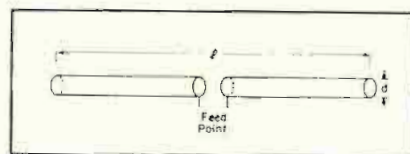


Figure 2

Dipole antenna with cylindrical conductors.

Figure 4
Cylindrical dipole with a compensating stub for broad-banding.

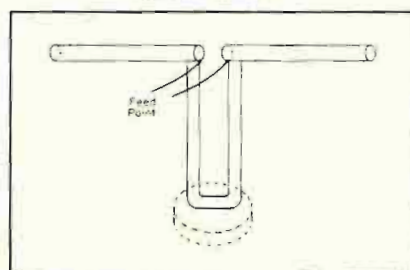

stub in the 65-mc region (where the antenna reactance component is low) results in negligible shunting effect on the antenna, so that the antenna system now has *three* frequency regions where the reactive component is small instead of the *one* frequency region possessed by the simple dipole. This results in effective broadbanding of the dipole within the frequency range of about 50 to 85 mc, thus making this antenna system quite well-suited for tv use in the complete low-frequency band.

A feature of this type of antenna system is that the combined dipole and stub conductor assembly may be fabricated from a single piece of metal rod or tubing, thus eliminating joints which might otherwise be subject to trouble from corrosion, structural weakness and the like. In addition, it is possible to attach a metallic base flange to the stub as shown in Figure 4, the flange serving the two-fold purpose of acting as a mounting base for the antenna as well as improving the nature of the electrical *short* on the end of the transmission-line stub. Under these conditions the stub itself serves as a very effective mounting support for the dipole, and the need for strong dielectric-type supporting insulators for the antenna is eliminated. The base flange may be mounted to any type of surface whatsoever without impairing the impedance properties of the antenna system.

Dual-Band Arrangement

For operation in the upper television band, the 65-mc antenna system begins to exhibit unfavorable characteristics with regard to both impedance and directivity pattern. As an example, the resistive component of antenna impedance at 195 mc (where the dipole goes through its $3/2$ wave resonance mode) is of the order of 125 ohms, and the directivity pattern breaks up from its 65 mc *figure-of-eight* shape into a *six-leaf clover* shape. This is depicted in Figure 5, where is shown one-half of the normally symmetrical pattern. The *clover* pattern is generally undesirable for tv reception since it has null response points in directions other than off the ends of the dipole.

To overcome the deficiencies of the single dipole a dual-band antenna system* has been devised (Figures 1 and 6). In this antenna system a second dipole antenna unit, resonant at 195 mc (i.e., at exactly three times the frequency of the 65-mc dipole unit), has been attached to the broadbanding stub at a distance one-third of the way up from the bottom of the stub (or two-thirds of the way down the stub from

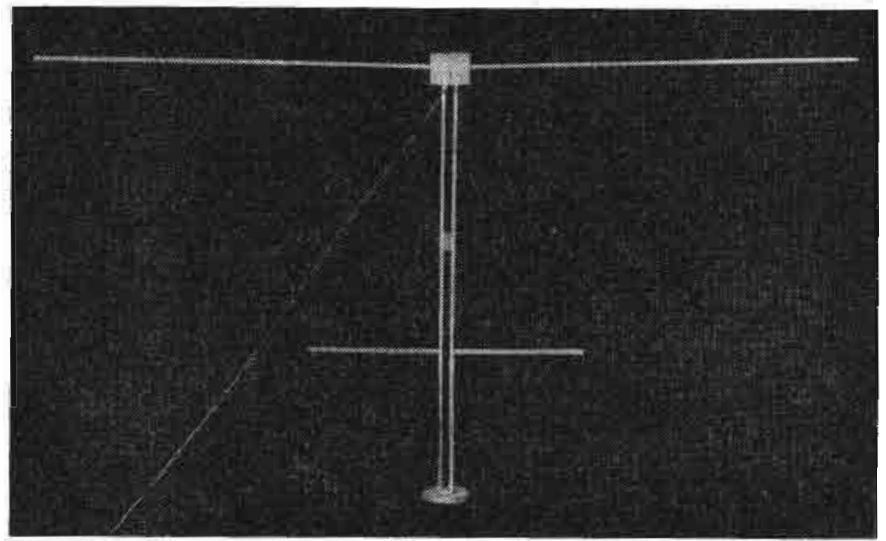



Figure 1
Experimental model of the dual-band antenna system.

the feed point). The presence of this 195-mc dipole unit has a substantially negligible effect on the operation of the antenna system in the 65-mc region, since it represents but a small shunt capacitive discontinuity 30° up from the shorted end of the stub at this frequency. However, at 195 mc, the small dipole is now a quarter wavelength up from the shorted end of the

*Megatenna.

stub and a half wavelength down from the top or *feed-point* end of the stub. Accordingly, the lower one-third of the stub now acts as a *broad-banding* reactance for the 195-mc dipole, while the upper two-thirds of the stub acts as a half-wave length of transmission line which serves to connect the broadbanded 195-mc dipole assembly directly across the feed-point terminals, putting it in parallel with the 65-mc dipole in the upper television band. Now, since

Figure 3
Plot of resistance and reactance versus frequency of a 65-mc dipole section of the dual-band antenna system.

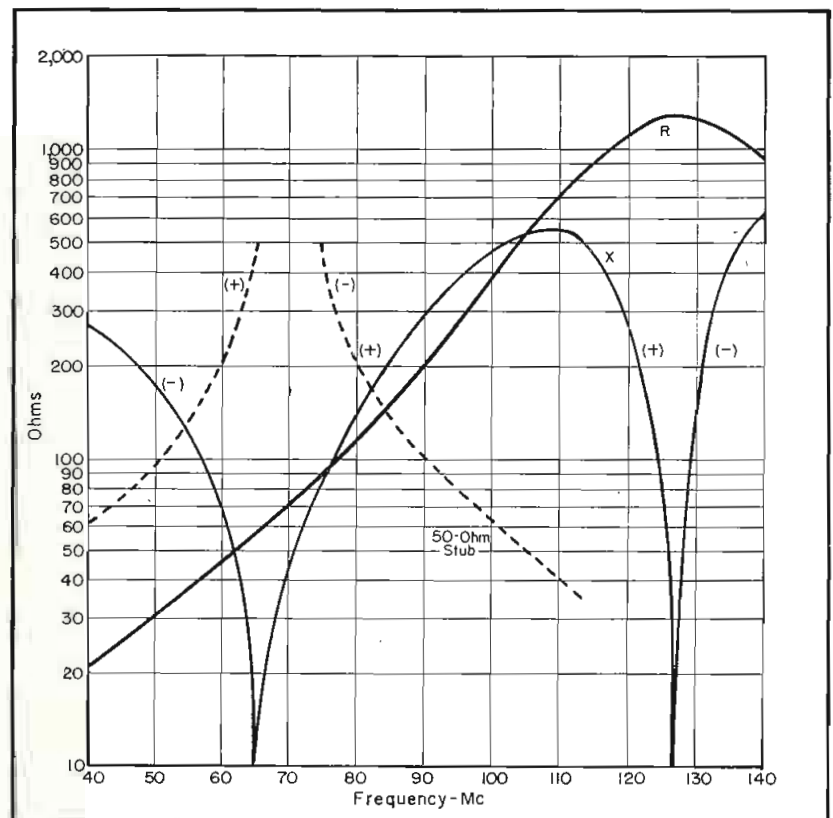

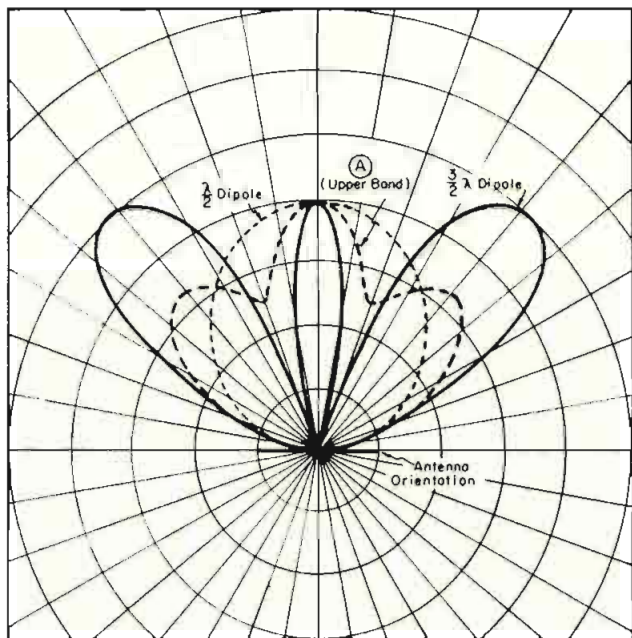


Figure 5
Antenna directivity patterns (two quadrants): plot at A is for the dual-band antenna.

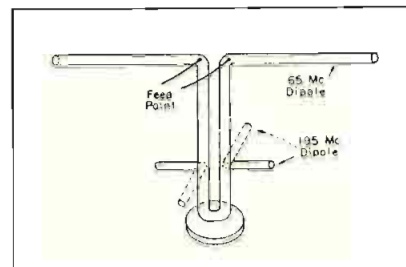


Figure 6 (Above)

Makeup of the dual-band antenna system, illustrating two possible orientations of the high-band dipole with respect to the low-band dipole.

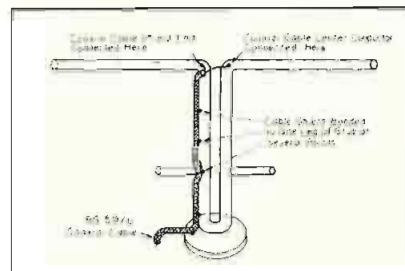


Figure 7

A coaxial feed arrangement for the dual-band antenna. The outer insulating jacket of coaxial cable is removed for length of stub.

the resistance of the large dipole is about 125 ohms at 195 mc, while the resistance of the small dipole is about 60 or 70 ohms, the small dipole tends to take over in this frequency region and contribute the major amount of the received energy to the transmission line system connecting the antenna to the tv receiver. Because the small dipole contributes the greater amount to the total received energy of the antenna system, its figure-of-eight directivity pattern will predominate over

the clover pattern of the large dipole, and the resultant directivity pattern will be a composite shape of the form shown in Figure 4 by the long-dashed line. Since this resultant upper band directivity pattern now has no sharp null responses other than those off the ends of the dipole, it is hence well suited for regular tv use.

Coaxial Cable Feeder Arrangement

Up to this point the transmission line feeder for the antenna has been de-

picted and discussed on the basis of a balanced line. However, the dual-band antenna can be used with equal effectiveness in conjunction with coaxial type transmission line, since it contains within its structure the elements of a balanced-to-unbalanced transformation device. Thus, referring to Figure 7, the coaxial cable is positioned against one leg of the broad-
(Continued on page 30)

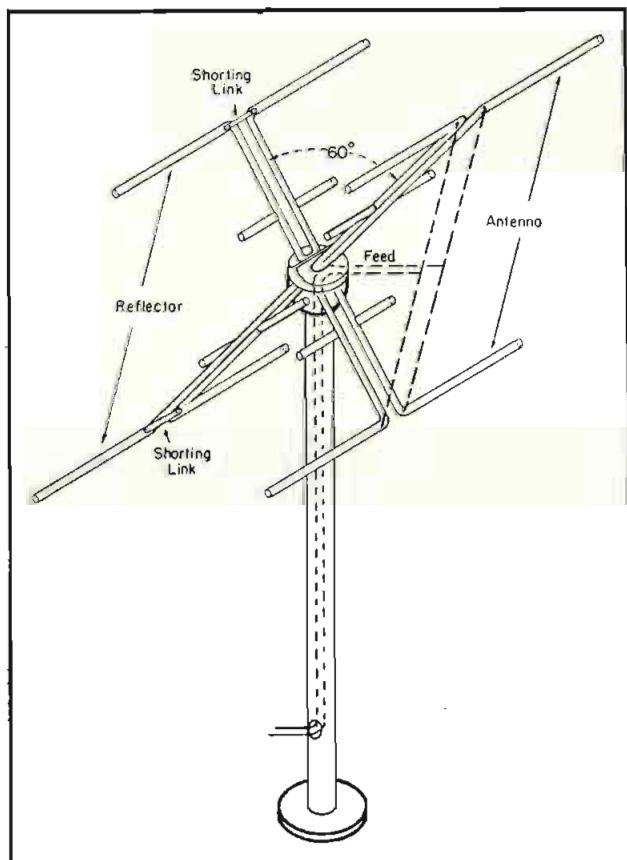


Figure 8 (Below)

Method of mounting two dual-band antenna assemblies to obtain a dual-band antenna-plus-reflector system.

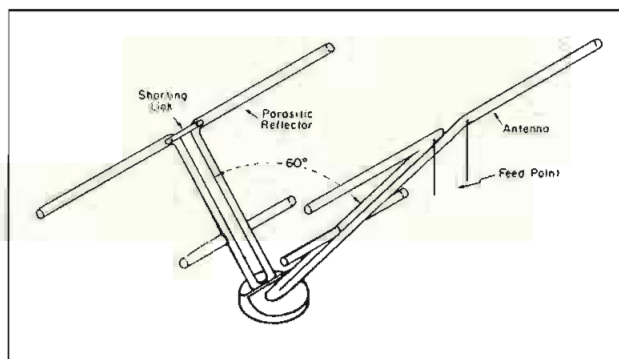


Figure 9 (Left)

An X type of array using four dual-band assemblies.

Always room for something **NEW** and **BETTER**


NEW ▶ ▶ ▶ **Presto 8D-G Recorder**

Extreme accuracy... designed for the finest instantaneous and master recordings. A special feature is the direct gear drive with separate motors for 33 $\frac{1}{3}$ and for 78.26 rpm. Overhead driven independently of the turntable and has a choice of seven different feed pitches in each direction.



NEW ▶ ▶ ▶ **Presto 92-A Recording Amplifier**

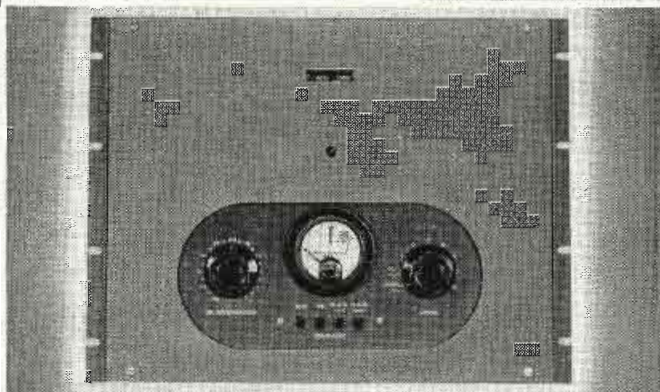Sixty-watt amplifier especially designed for high-fidelity recording. Vertically mounted chassis. Removal of front panel gives access to all circuits. Output stage has four 807's in push-pull parallel. Selector switch and meter provide both output level indicator and plate current readings for all tubes. Response: 20-17,000 cps.




NEW ▶ ▶ ▶ **Presto 64-A Transcription Unit**

Directly gear-driven at both 33 $\frac{1}{3}$ and 78.26 rpm, with two separate motors, one for each speed. Instantaneous speed selection by turning mercury switch, without damage to mechanism. Speed: Total speed error is zero. Noise: At least 50 db below program. Starting: Table on speed in less than $\frac{1}{8}$ revolution at 33 $\frac{1}{3}$ rpm.



NEW ▶ ▶ ▶ **Presto 90-A**

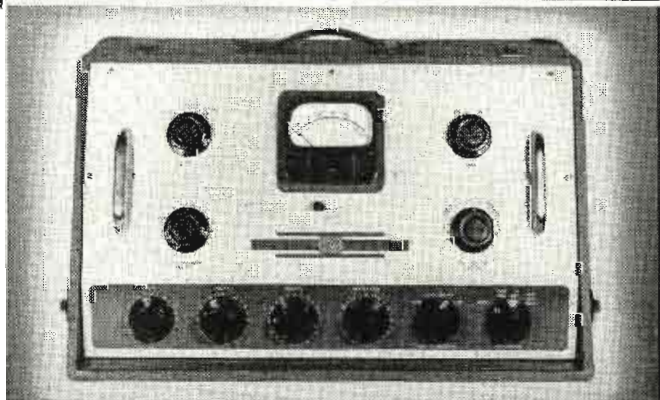Complete portable recording console. Three low-level input channels with mixers, master gain control and variable high and low frequency equalizers. Four fixed characteristics: Flat between 30 and 15,000 cps, NAB recording, 78 rpm recording, and playback complementing NAB recording.



*For further information about any of this new equipment,
write or wire*



RECORDING CORPORATION, Paramus, New Jersey
Mailing Address: P. O. Box 500, Hackensack, New Jersey

WORLD'S LARGEST MANUFACTURER OF INSTANTANEOUS SOUND RECORDING EQUIPMENT & DISCS

Equipment Failure-Control System For Broadcast Stations

Inspection, Maintenance and Trouble Data-Recording Procedure, Which Reveals Types of Failures to Be Expected, The Relative Rates of Occurrence and Effectiveness of Repair Work.

by F. E. BUTTERFIELD

Engineering Department
The Andrew Company

THE APPLICATION OF analytical systems has streamlined maintenance procedures, providing an effective balance of control expense and results.

A three-point procedure has been found very productive:

(1) *Inspection*: Equipment test procedure, with standards of performance, applied periodically to locate the maximum number of faults before they render equipment inoperative.

(2) *Maintenance*: Equipment maintenance procedure, applied when equipment fails in service or fails inspection, and having its own set of performance standards; developed to keep equipment in operation for the longest possible periods.

(3) *Analysis*: Trouble-analysis procedure which presents data for evaluating (1) and (2), for estimating the efficiencies of personnel and training and for finding costs associated with particular maintenance operations.

Since the analysis of faults has to be based on the statistics of failures in service, accurate analysis can be obtained only with large groups of

identically constructed and operated equipment, say fifty units or more. This is not true about test and maintenance procedures. The tests which are most suitable for large-scale operations may be of great help in determining the condition of some isolated unit. However, effective test procedures can be determined only by actual trial and analysis on large numbers of units.

Test and maintenance procedures, recommended and published by technical societies and manufacturers and prepared after considerable trial and analysis are general in nature and not necessarily adapted to particular operations. They do not ordinarily form completely satisfactory procedures without a good deal of addition in some details, elimination in others.

Inspection Procedures

An inspection procedure, ideal for the purpose of preventing failures of equipment in service, would be simple, easy and quick to complete, and would determine the point and time at which the unit would fail if continued in operation. Unfortunately, the most that an inspection actually can indicate is the effectiveness of a unit at the moment the test is applied. In the case of some units, mainly mechanical in nature, this information, gathered at regular intervals can be related to the life of the units and will then show

EQUIPMENT REPAIR RECORD		
EQUIPMENT TYPE _____, NO. _____		
DATE	WORK DONE	BY

Figure 2
Equipment repair record card.

the remaining service which can be expected from them. The performance of most electrical components is such, however, that failures are erratic and relatively unpredictable. Thus for the electrical unit, the inspection will answer the question "What will this unit do now?"; if that answer is not good enough, the unit must be repaired.

Typical Inspection Procedure

In one test procedure applied once a month to a large group of commun-

(Continued on page 34)

Figure 4
Equipment failure analysis sheet:
summarization of data on 1, 2 and 3 forms.

	JAN.	FEB.	MARCH	APRIL	MAY

- EQUIPMENT TYPE
- PERIOD
- NUMBER OF UNITS IN SERVICE
- FAILURES IN SERVICE
- (BREAKDOWN)
- SERVICE INTERRUPTION (UNIT HRS.)
- REPAIR TIME (MAN HRS.)
- FAILURES IN SERVICE/UNIT
- SERVICE INTERRUPTION/UNIT
- INSPECTION REJECTIONS
- (BREAKDOWN)
- INSP. AND MAINT. TIME (NOT INCLUDING TIME IN LINE 7)
- INSPECT. REJECTIONS/UNIT
- FAILURES IN SERVICE/INSP AND MAINT TIME
- TOTAL FAILURES/INSP AND MAINT TIME
- TOTAL TIME SPENT (MAN HRS)

Time Reported	Equipment Type and Number	Failure Reported	Action Taken	Trouble Found	Time Repaired	Repairs Made	Repaired By

Figure 1 (Above)
Form which can be used to record failures in service.

Figure 3 (Below)
Inspection report.

Date	Equipment & Number	Inspection Procedure	Failure	Inspected By	Repairs Made	Time Required	Repaired By	Date
1	2	3	4	5	6	7	8	9



*Save Time and Money...
Increase Operating Efficiency*

with **PHILCO**


2-WAY F-M MOBILE RADIOPHONE COMMUNICATIONS SYSTEMS

30 to 44 Mc. and 152 to 162 Mc. Sensational new developments . . . advanced engineering . . . proven reliability . . . new operating efficiency and economy for F-M Radiophone Communications Systems, permitting clear, crisp, two-way voice communications under all conditions.


PHILCO
INDUSTRIAL DIVISION
PHILADELPHIA 34 • PENNSYLVANIA




POLICE

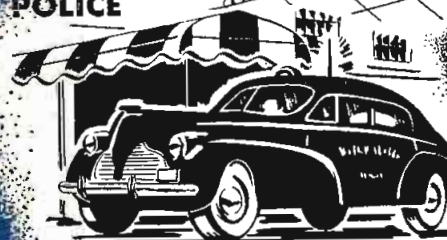

TAXICABS

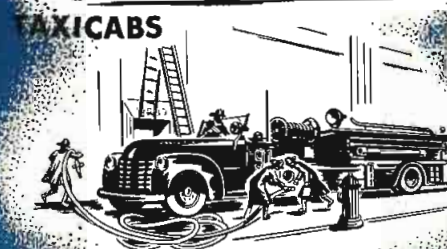

FIRE

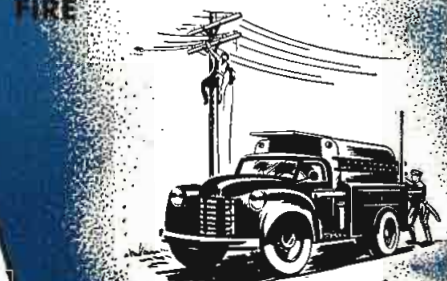

UTILITIES



BUSES



TRUCKING

Philco Industrial Division Dep't JN9
Tioga and C Sts., Philadelphia 34, Pa.

Gentlemen:


Please send me information about the
new PHILCO F-M Radiophone Com-
munications Systems

NAME


ADDRESS

CITY


Simple switching for your

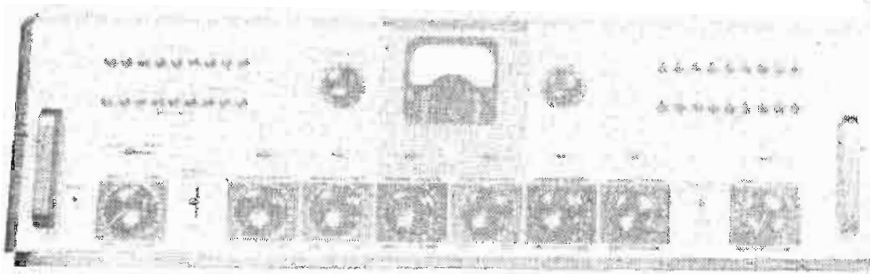

RCA 76-B5 Consolelette

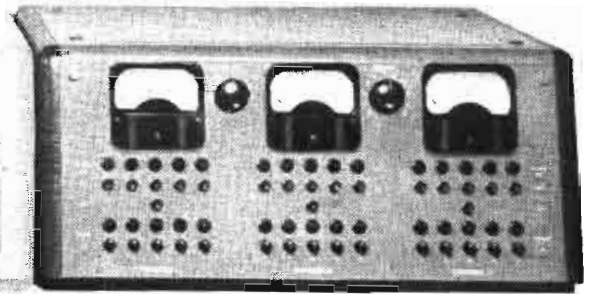

**Type BCS-1A
Master Switching Unit**

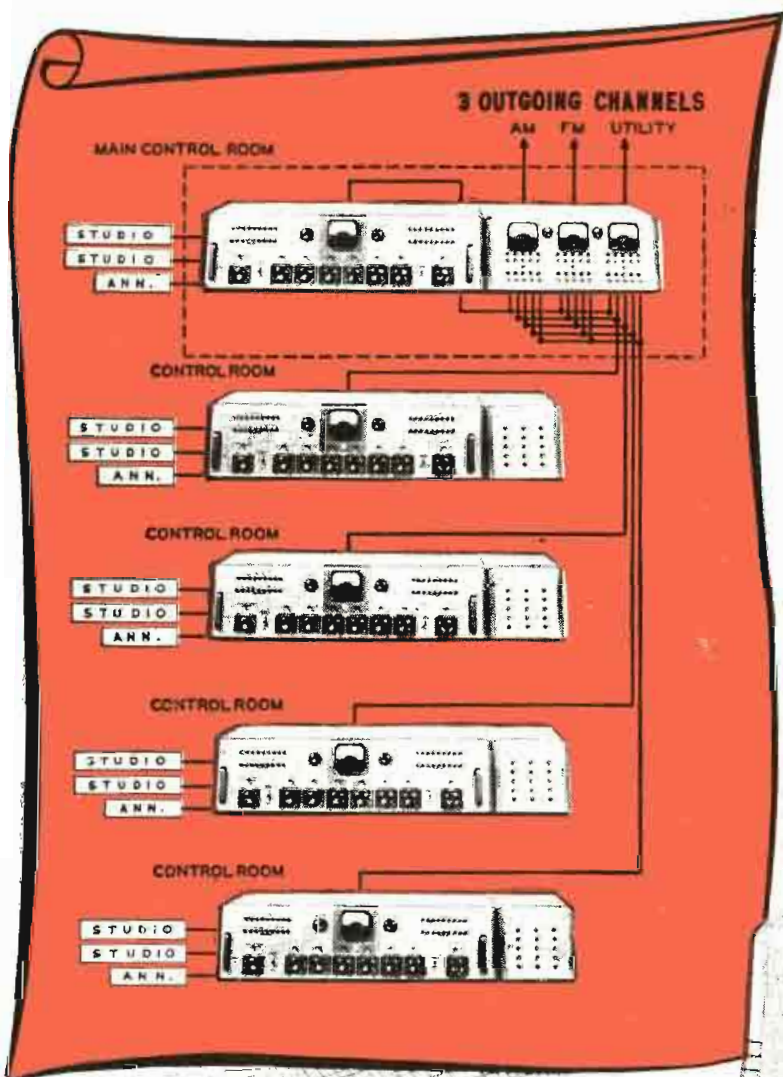


Type BCS-1A Master Switching System

This system consists of one Master Switching Console (above, right—shown with an RCA 76-B5 Consolelette), and one or more sub-control units (below). It contains all the relays needed for any combination of switching functions.

Up to five sub-control rooms can be used with the master console, each of which can handle from one to three studios.

Status lights give accurate picture of "On Air," "In Use," "Ready," and "On-Off" conditions in all control rooms for each outgoing line. Unique design features prevent feeding more than one program to any one line, although supporting program material can be handled as remotes from the originating studio. Sub-control units act as relay control stations between studios and master control unit.

Type BCS-1A Studio Sub-Control

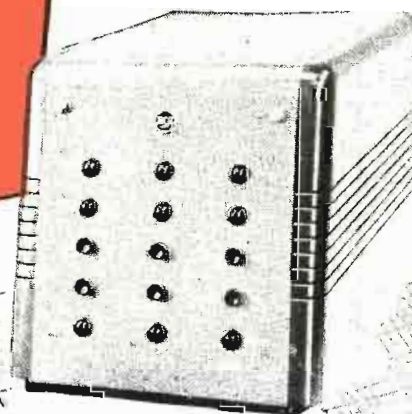

AM-FM Programming

RCA consolette switching systems co-ordinate all studio-station functions

● Here's another example of RCA's program of providing "packaged" broadcast equipments having the flexibility and performance of custom-built jobs.

The two Switching Consoles shown, in connection with standard RCA Consolettes of identical styling, give you sufficient latitude to perform intricate AM, FM and network programming operations—easily, precisely and quickly. Choice of model depends upon the complexity of your station's operating requirements.

The BCS-1A Console is designed for


the more elaborate station . . . switching the outputs of as many as five control consolettes to three outgoing lines. Many combinations are practicable. Inputs from studios, network, recording rooms or frequent remotes can be monitored and switched to transmitters or network lines. Electrically interlocking controls have reduced the possibility of switching error to the vanishing point.

Managers of stations requiring only two consolettes will find the RCA Type BCS-2A Console the ideal switching system. Used with two RCA 76-B5

Consolettes, program material from as many as four studios and two announce booths is routed to desired outgoing lines (AM and FM, or either transmitter and a network line).

• • •

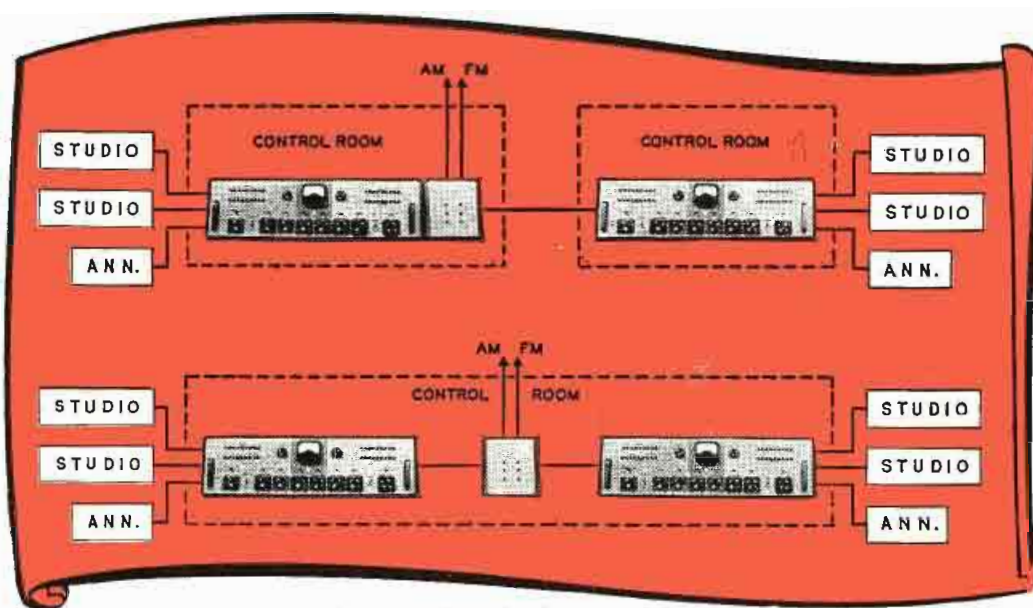Both types of RCA Switching Systems are designed for long-range station planning. They have sufficient flexibility to take care of future expansion. Complete details may be obtained from Engineering Products Dept., Section 23-F, Radio Corporation of America, Camden, N. J.




Type BCS-2A Switching System

Two studio inputs may be switched independently to either of two outgoing lines. Mechanical interlocking prevents feeding two inputs to the

same line. This system handles up to four studios and two announce booths. Two examples of the layouts possible are shown above.

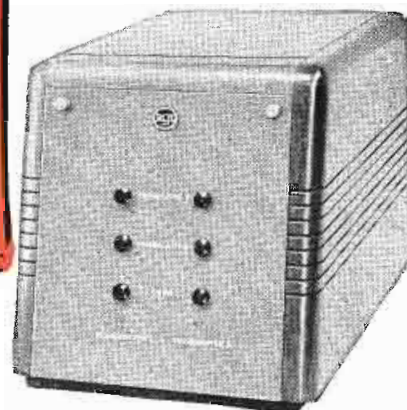Studio Switching Console for Small Studios



BROADCAST EQUIPMENT
RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.

In Canada: RCA VICTOR Company Limited, Montreal

TV Transmitter Design

IN THE INITIAL installment of this series appeared a discussion of the general design problems encountered in tv transmitter systems, with special consideration of the exciter and video modulator units, and d-c restorers.

In the analysis of d-c restorers, a series of wave forms were presented, the concluding figure showing various wave shapes and the manner in which equal areas are established about the zero a-c reference axis.

Continuing with our d-c restorer study, we find that if the time constant is sufficiently large, a voltage will be generated across the diode load resistor about equal to the peak value above or below the axis dependent upon the polarity of diode connection. Figure 1 shows a simplified circuit breakdown of a typical video amplifier, d-c restorer and modulator.

The restorer operates in a manner such that an additional biasing potential is applied to the modulator; in this case opposite to that supplied by the bias supply. For the wave shapes shown last month in Figure 9, the bias differential will be equal to the peaks appearing below the average a-c axis. This is shown graphically in Figure 2.

assuming an adequate time constant.

From Figure 2, it will be noted that the effect of the d-c restorer is to refer the peak of the applied signal to the quiescent bias level. In the case of (d) and (e), the sync tips are held at the reference level of the quiescent bias and any signal excursion toward *white level* results in a reduced grid voltage, with a consequent increase in plate current. This produces a signal voltage across the plate load resistor, and since this point is conductively coupled to the grids of the modulated amplifier, produces negative modulation from the condition of no video signal. In effect, this states that a white picture drives the modulated amplifier toward cutoff or minimizes output, while a black picture drives the amplifier toward maximum output. Figure 3 shows a typical transfer characteristic for the two conditions outlined.

Modulated Amplifier Considerations

Three conditions for one setting of r-f drive are shown in Figure 4: (1) no video modulation, (2) white picture modulation, and (3) black picture


modulation. For proper operation of a grid-modulated amplifier, the parameters should be adjusted to provide the results illustrated. Obviously, a balance between r-f drive, video signal amplitude, and bias is essential.

Fundamentally, a television grid-bias-modulated stage operates under conditions similar to class B, i.e., the tubes are biased in the vicinity of cutoff. In Figure 4, we find the ideal case where the bias is adjusted so that signal excursions about this point maintain the output waveform over a linear portion of the grid plate transfer characteristic. Should the bias be excessive, operation will be about the lower knee of the transfer curve and the resulting non-linearity will cause compression in the signal representing the white picture area. This condition is most easily noticed as amplitude distortion of a linear gray scale. When the bias is not as great as the tube linearity allows, full advantage of the grid base is not realized, and sync compression may take place. Sync compression is the result of operating on the upper knee of the transfer characteristic, and is evidenced by changing the ratio of sync to video-plus-sync;

MAY, 1948, COMMUNICATIONS.

Figure 2

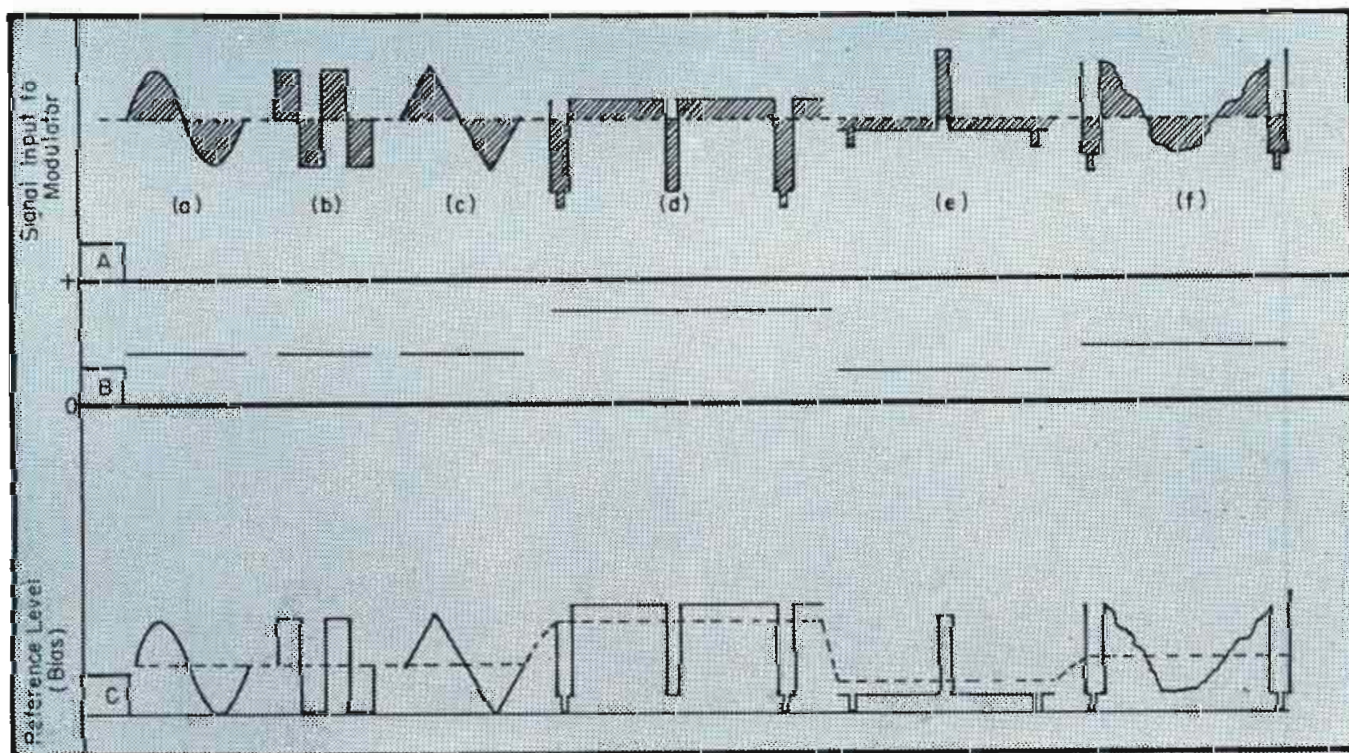At A (top), graphical representation of various wave forms about the zero axis. B (center) shows the d-c restored voltages for the wave forms above. At C (bottom), the signal is shown referred to the fixed bias potential; it consists of the summation of the bias, the restoration voltage and the signal input. Note how the a-c axis shifts by action of the d-c restorer.



Modulated Amplifier Considerations . . . Adjustment of Video Signal Amplitude . . . Equipment Used for Adjustment of Class B Linear Amplifiers.

by G. EDWARD HAMILTON

Head, Television R-F Development Section
Television Transmitter Department
Allen B. Du Mont Laboratories, Inc.

instead of being 25% it may decrease to a value of 20% for example.

The r-f drive (without video signal) must be sufficient to drive the plate current up to the upper knee of the transfer characteristic; above this level the plate current is no longer a linear function of grid excitation. With modulation, the sync plate current tips extend upward and any excursion into the upper knee will result in limiting or sync compression.

Adjustment of video signal amplitude is also of prime importance since upon this factor depends the modulation percentage levels for tv picture information, i.e., the FCC has decreed that the synchronizing impulses must occupy 25% of the total r-f signal amplitude, and that the transmitter be modulated down to at least 15% of the peak level on white picture detail. These limits are shown in Figure 5 for a black picture with a white line, with respect to relative r-f signal amplitude. To operate within these prescribed limits, which permit an effective modulation capability of only 85%, it is necessary to drive the transmitter with an augmented sync to picture ratio. Analysis of the proportions of Figure 5 shows that the input video signal must consist of 29.5% sync, referred to the peak-to-peak value of the input video signal (100%), the video comprising the remaining 70.5%. There are numerous methods of adjusting the three factors for satisfactory initial operation. One found to be practical (assuming correct bandwidth, amplitude response, modulation capability, etc.) is:

- (1) With no video signal and no r-f drive, the modulated amplifier bias is adjusted to almost plate current cutoff.
- (2) The r-f drive is increased to a point about half that required for maximum plate current.
- (3) With a white picture (approximately 30% sync, 70% video), the video gain is advanced until the r-f modulation envelope conforms to current FCC regulations, as observed on a modula-

tion indicator² which will show relative percentage values.

- (4) Should the transmission-line voltage be low (indicating insufficient power output), the r-f drive is raised to the modulated amplifier and the video signal increased until satisfactory modulation and transmission line voltage is attained. To determine the peak power output of the transmitter, the video modulating signal must be reduced to black (maintaining the previous input sync level) which will result in a standard black signal transmission comprising 25% of the total r-f amplitude as r-f synchronizing signal. The average power output should be measured under this condition of black signal. A water-cooled load terminating the transmitter output circuit, with means for determining the water inlet and outlet temperature differential and rate of flow, provides the most accurate measurement of this factor. The average power output thus

²DuMont 5034-A r-f waveform monitor.

*Care must be continually exercised so that neither sync compression nor white saturation take place. The discussion of Figure 4 explains how these various discrepancies may exist and how corrective measures may be applied.

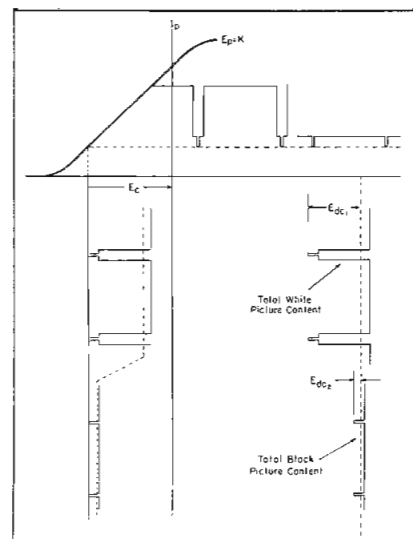


Figure 3

Curve illustrating a typical transfer characteristic of a video modulator for conditions of total black and white picture. E_{dc1} is the restorer potential for the white picture and E_{dc2} is the restorer potential for the black picture.

determined is converted to peak power by obtaining the product of average power output and 1.68, the factor derived from consideration of the duty cycle of the sync pulse for conditions outlined above.*

Proper adjustment of the foregoing three parameters above may be augmented by use of the following types of equipment:

- (1) An r-f waveform oscilloscope which consists of provision for observing the modulation envelope and a beam deflection circuit for determining modulation percentages which is read on the meter. Such an instrument is shown in Figure 6.
- (2) A diode pickup coupled to the transmission line whose output is connected to an ordinary h-f 'scope employing a scale calibrated in percentage. The input of the 'scope may be intermit-

Figure 1

Simplified circuit of a typical video amplifier, d-c restorer and video modulator.

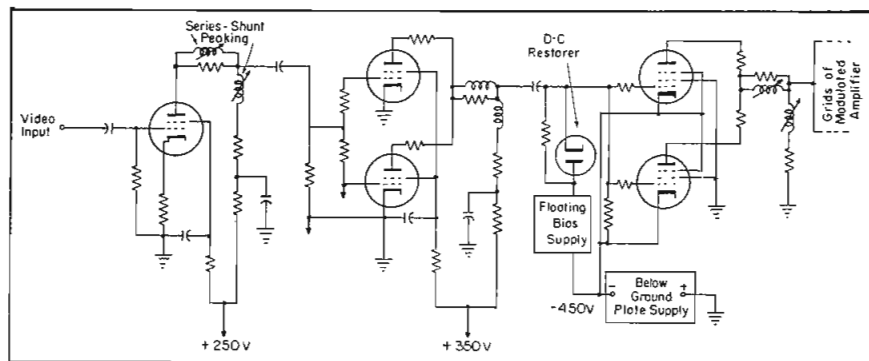


Figure 4

Transfer characteristics showing how (1) no picture, (2) white picture, and (3) total black picture modulates the r-f voltage applied to the modulated amplifier grid circuit, and the resulting plate current flow.

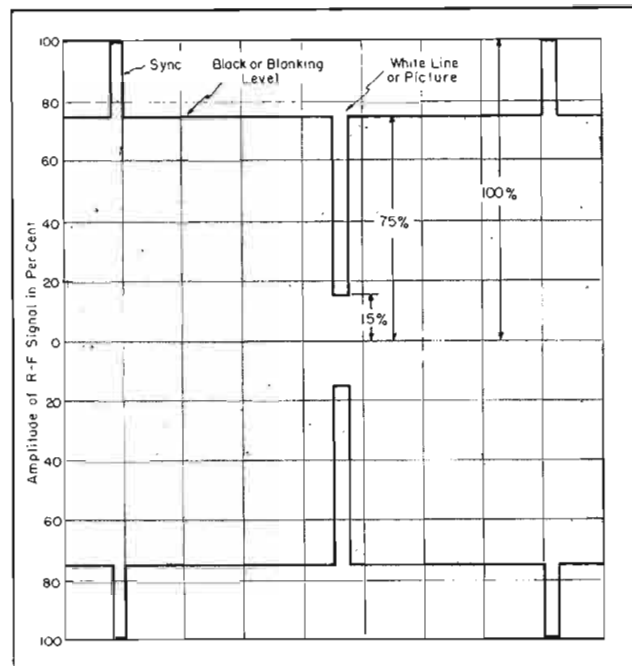
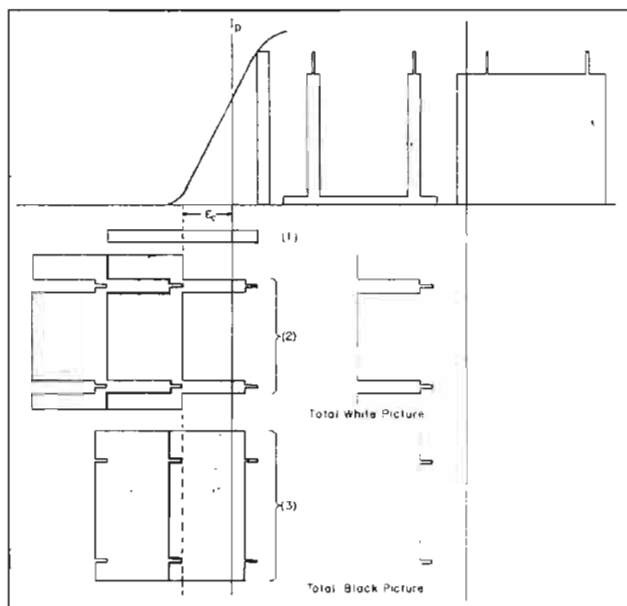


Figure 5
The r-f signal amplitude distribution for a black picture with a white line, as specified by the FCC.

tently keyed or shorted by means of a vibrator, to reclaim the zero reference axis, the total excursion being referred to this value. In any detecting system, there are two signal components, namely the d-c level, and the signal information. Periodic shorting of the input to the scope results in producing a zero reference level which represents *no signal*. This system allows measurement of the various modulation percentages. It is only necessary to adjust the scope gain for full excursion (with vibrator intermittently shorting the input). Relative amplitudes of modulation com-

ponents are then measured directly.

Class B Linear Amplifiers

In the master² series transmitter, the modulated amplifier supplies driving power to a pair of WL-3300 tubes operating in class B (*intermediate-power amplifier*), followed by a second pair of WL-3300 (*power amplifier*) tubes. Grounded-grid circuits are used in both stages, which results in freedom from neutralization problems and a direct transfer of energy from the out-

²For a complete discussion of this subject see C. B. Aiken, *Two Mesh Tuned Coupled Circuit Theory*, Proc. IRE, p. 230, February, 1947 and p. 672, June, 1947.
DuMont

put of the *ipa* to the output of the *pa* providing a higher apparent final efficiency. The circuits are cathode driven which automatically loads the preceding circuit precluding the necessity for *bandwidth* resistive loading.

Linear amplifiers must be adjusted to satisfy four primary conditions:

- (1) Satisfactory bandwidth.
- (2) Adequate power output.
- (3) Linear output between the limits of 100% and 15% modulation.
- (4) Suppression of lower sideband.

Adequate bandwidth for tv, of the order of 4 mc, is attained by coupled circuits which consist of resonant primary and secondary, variable coupling, and variable secondary loading; a fundamental circuit is shown in Figure 7(a).^{3,4}

A rapid review of coupled circuit theory shows that when two circuits which resonate at the same frequency are coupled together, the resulting behavior depends largely upon the coupling and secondary loading as shown in Figure 7. When the coefficient of coupling is small, the secondary response is low and varies with frequency according to a curve having a shape approximating typical resonance curves with only one peak. As the coupling is increased, the response increases in amplitude and simultaneously broadens. This trend continues until the coupling is such that the resistance, that the secondary circuit

(Continued on page 29)



Figure 6
Front panel view of the r-f wave-form monitor

Bendix **REGULATED** **DYNAMOTORS**



MAKE A BIG DIFFERENCE IN RELIABILITY . . . ECONOMY . . . WEIGHT

Under the most severe conditions in which your electronic installations are expected to operate, Bendix* regulated dynamotors will deliver dependable, uniform voltage. You can count on them to last longer, too, because they are manufactured with the same painstaking care which has made Bendix Aviation equipment famous for quality all over the world. Before you design, write our engineering department for detailed information on Bendix regulated dynamotors.


Dynamotors • Inverters • Convertors • D.C. Motors • Carbon Pile Voltage Regulators

RED BANK DIVISION of
RED BANK, N. J.



- Output voltage constant within plus or minus 2.5% at rated load, with as much as 30% input voltage variation.
- Consistent efficiency of associated equipment under extremes of temperature, humidity, altitude and vibration.
- Allows the use of smaller, lighter, less expensive components in design of electronic equipment.
- Tube life materially lengthened due to narrow voltage tolerances.

*TRADEMARK

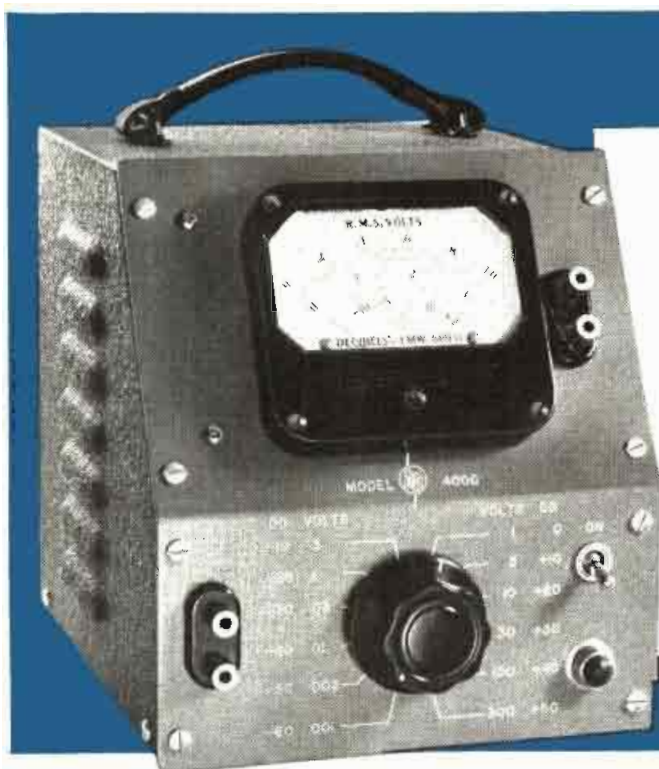

VOLTAGE RANGE:

3,000,000 to 1

READINGS:

.1 mv to 300 v

FREQUENCIES:

20 cps to 2 mc

THE NEW *-hp-* 400C VACUUM TUBE VOLTMETER

Increased sensitivity. Wider range. Easy-to-read linear scale. Space-saving, time-saving versatility! Those are but a few of the many advantages of the new *-hp-* 400C Vacuum Tube Voltmeter.

30 times more sensitive than the *-hp-* 400A voltmeter, the new *-hp-* 400C accurately determines voltages from .1 mv to 300 v. Its measuring range is broad and new—3,000,000 to 1. And with it you can make split-hair measurements all the way from 20 cps to 2 mc!

The big, clearly-calibrated linear scale reads directly in RMS volts or db based on 1 mw into 600 ohms. Generous overlap makes possible more readings at mid or maximum scale, where accuracy is highest. A new output terminal lets you use the *-hp-* 400C as a wide-band stabilized amplifier, for increasing gain of oscilloscopes, recorders and measuring devices. As a voltmeter, the new instrument has still wider applicability—for direct hum or noise readings, transmitter and receiver voltages, audio, carrier or supersonic voltages, power gain or network response.

Naturally the new *-hp-* 400C includes the familiar advantages of the *-hp-* 400A voltmeter. Range switch is calibrated in 10 db intervals providing direct readings from -70 dbm to +52 dbm. Overall accuracy

is $\pm 3\%$ full scale to 100 kc. High input impedance of 1 megohm means circuits under test are not disturbed. And the rugged meter movement is built to safely withstand occasional overloads 100 times normal.

In every respect, the convenient, durable *-hp-* 400C is the ideal new voltmeter for precision work in laboratory, plant or repair shop. Complete details are available at no obligation. Write today!

Hewlett-Packard Company

1556E Page Mill Road • Palo Alto, Calif.

CHECK THESE SPECIFICATIONS

VOLTAGE RANGES:

12 ranges. Full-scale readings.

.001 v	.100 v	10.0 v
.003 v	.300 v	30.0 v
.010 v	1.00 v	100. v
.030 v	3.00 v	300. v

FREQUENCY RANGE: 20 cps to 2 mc

ACCURACY:

$\pm 3\%$ full scale 20 cps to 100 kc
 $\pm 5\%$ full scale 100 kc to 2 mc

INPUT IMPEDANCE:

1 megohm shunted by 15 uuf, on .01 v to 300 v ranges.
1 megohm shunted by 25 uuf, on .001 v to .003 v ranges.

METER SCALE:

3" linear. Voltage ranges related by 10 db steps. Db calibrated -12 to +2 db. Zero level 1 mw into 600 ohms.

OUTPUT CIRCUIT:

Maximum 0.5 v full scale. Internal impedance 1000 ohms.

POWER SUPPLY:

115 v, 50/60 cps, 45 watts.

CABINET SIZE:

8" high, 7 1/2" wide, 9" deep.



Power Supplies Frequency Standards Amplifiers Electronic Tachometers Frequency Meters
UHF Signal Generators Square Wave Generators Audio Frequency Oscillators Attenuators
Audio Signal Generators Noise and Distortion Analyzers Wave Analyzers Vacuum Tube Voltmeters



VWOA Memorial Awards

THE MARCONI MEMORIAL SCROLLS OF HONOR were awarded by VWOA to seven Army Transport Service radio operators who aided in rescues at sea during special ceremonies at the New York Port of Embarkation in Brooklyn, N. Y.

Ye prexy, W. J. McGonigle, presented the awards. Lt. Col. John D. Fleming of the New York Port of Embarkation was master of ceremonies and Maj. Gen. Ewart G. Plank, Commanding Officer of the Port, delivered the keynote address.

Four of the heroes were at the ceremonies to receive their awards while three others, who were at sea, were informed of their awards. At the ceremonies were Lt. Dale Clason, operator on the Army transport Belle Isle, who relayed a call for help from the Portuguese schooner, Maria Carlotta; Ensign Jack Chiamonte, operator on the transport, Charles Stafford, who also relayed the call from the Maria Carlotta; Ensign Edward Nahan, another operator aboard the Charles Stafford, and Ensign Walter Fleming, who sent distress calls from the burning transport, Joseph Connelly, which was carrying war dead. The three radio men at sea who received awards were Winslow Lewandowski of the Charles Stafford and A. Donnary and Richard Astraukas of the Belle Isle.

VWOA was quite proud to make these awards to these outstanding wireless men of the year.

At the Spring Meeting

THERE WAS QUITE A TURNOUT at the Spring meeting of the VWOA which was held in the Marine Room of the Fireplace Inn in New York City on May 20.

VWOA honorary member, George Bailey, was guest speaker for the evening and told the boys about the United Nations' ham station at Lake Success. As prexy of the American Radio Relay League, George played a major role in setting up a coordinated plan for the amateurs of the world. He disclosed how the hams were united in this global plan to maintain



W. J. McGonigle, VWOA prexy, presenting Marconi Memorial Scrolls to Ensigns Walter Fleming, Edward Nahan, Jack Chiamonte and Lt. Dale Clason for their parts in rescues at sea. Major Gen. Ewart Plank, Commanding General, New York Port of Embarkation, is at extreme left.

contact with United Nations' head-quarter amateur station K2UN and spread U.N. gospel.

The station, a one kilowatt affair, was placed in operation several weeks ago with many U.N. dignitaries in attendance. Honorary member Brig. Gen. Frank E. Stoner, who is chief of communications at United Nations, is directing the activities of this unusual good-will station.

Among those at the meeting were Ken Richardson, who reported that he was an operator way back in 1908 when he served with the United Wireless Company. . . . Ray Morehouse pulled out his old time records which showed that his brass pounding days began in 1917 with the United States Navy. After a two-year hitch with the Navy he became a commercial operator with the Panama Railroad Steamship Company. After three years at this post he decided that he'd like to sell the keys he had been banging and became a dealer on radio row in Cortlandt Street, New York City. He joined Allen D. Cardwell in 1924 and served them in various capacities until 1946. During the 1936 to 1946 period, he was the Cardwell sales manager. At present Ray is a sales rep for Adolph Schwartz handling Eimac tubes, Electro-Voice microphones, Cardwell condensers, R.M.E. receivers, Ward antennas, Petersen

crystals and Sonar ham equipment. . . . Old timer Anthony Tamburino was also at the Spring meeting. A.T. had been a VWOA member for many years, dropped out for a spell and is now back with us again. His brass-pounding days go back to the S.S. America era. He was on the original staff of the S.S. Leviathan and also served with Prof. Wm. Beebe during the Galapagos scientific expedition in 1923. A.T. is now with the United States Navy at the Naval Shipyard in New York. . . . Old timer R. J. Iversen reported that the New York Times Radio station WHD has been moved into the new addition at the New York Times Building. All the equipment has been modernized and station facilities air-conditioned. The Times news summaries which are transmitted at 1900 GMT on 16,720 kc and 0500 GMT on 8360 kc have been received throughout the world.

Henry T. Hayden, Jr. was chairman of the meeting. Others at the meeting included C. D. Guthrie . . . V. Villandre . . . Sam Schneider . . . Joseph L. Sarick . . . W. McDermott . . . H. H. Parker . . . E. M. Krause . . . R. H. Frey . . . ye prexy, W. J. McGonigle . . . E. P. Nelson . . . Lester Reiss . . . G. N. Mathers . . . R. H. Phesey . . . ye secretary, Wm. C. Simon . . . G. H. Clark . . . and ye editor.



**WUXTRY!
GET THE XL-347!**

THE CONNECTORS WITH TECHNICAL SUPERIORITY...

favorite of sound technicians in night clubs, radio stations, motion picture studios—and also used extensively by "hams". Cannon Connectors require



XL-3-12 PLUG
LIST \$1.20

XL-3-11 PLUG
LIST \$1.25

a minimum of servicing—that's why sound men prefer Cannon.

Latch-lock keeps plug *positively* connected—no scratchy connections with loose coupling nuts. It stays connected!

Available from more than 300 distributors: In NEW YORK, Harvey and Newark Radio. In CHICAGO, Allied. Newark and Walker-Jimieson.

We'll send the XL-347 and the KJC-2 for the asking. Address: Department E-121

SINCE 1915

**CANNON
ELECTRIC**

Development Company

3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.

IN CANADA & BRITISH EMPIRE:
CANNON ELECTRIC CO., LTD., TORONTO 13, ONT

WORLD EXPORT (Excepting British Empire):
RAZAR & HANSEN, 301 CLAY ST., SAN FRANCISCO

News Briefs

INDUSTRY ACTIVITIES

WTVJ, Miami, Fla., is scheduled to go on the air by the end of July, with a 5 kw G.E. transmitter on channel 4.

Presto Recording Corporation is now located at Paramus, New Jersey, seven miles from New York City on Route 4, via the George Washington Bridge. Mail address: P. O. Box 300, Hackensack, N. J.

Four divisions and subsidiaries of Raytheon Manufacturing Company are now located at 50 Broadway telephone, Whitehall 3-1890: Equipment Sales Div., International Div., Russell Electric Co. and Submarine Signal Co.

Raytheon's publicity department and Broadcast Equipment Sales remain at 60 East 42nd Street. The New York office of Belmont Radio Corp. is at 520 Fifth Avenue.

Crown Capacitor Corp., 70 Stuart Street, Boston, Mass., has been formed to produce a line of air-dielectric paper capacitors.

J. H. McInloche, previously with the Canadian Marconi Company, is chief engineer, and Joseph D. Blumenthal is general manager.

A 500-foot Blaw-Knox tower is being installed at WDTN, DuMont station in Pittsburgh. Station will operate on channel 5, 60 to 66 mc.

The Baltimore Police and Fire Departments will soon have a 215 mobile-unit PTK two-way system for its police cars, fire department vehicles, fire boats and harbor police patrol boats.

Central station transmitting antenna will be located on a tower on top of the City Hall building, some 80 feet above the ground. Two 25-watt transmitters are being installed in the central station, one for continuous duty and another for standby.

A two-way G.E. fm system, KNDE (146.2 mc), is now in use at the Grand Coulee Dam in Washington.

Now installed aboard barges and tugs and in a ground station, equipment will soon be located on a mammoth floating caisson. Movement of this caisson, 115' long by 97' high steel structure, will be directed by fm as it is maneuvered along the spillway to permit workers to make repairs.

A symposium on cathode-ray equipment and techniques, was presented recently by the Instrument Division of Du Mont at the Wardman Park Hotel, Washington, D. C.

Purpose of the symposium was to acquaint qualified government personnel of the Washington area with the latest advances in the cathode-ray art.

Speakers were Dr. P. S. Christaldi, W. A. Knap, E. G. Nichols, M. G. Scheraga, and A. W. Jones, all of Du Mont.

WCIL-FM, Carbondale, Ill., is now on the air with a 1 kw W.E. transmitter. Antenna is a four bay cloverleaf. Paul McKee is general manager and Marion Sawyer, chief engineer.

WJR-FM, Detroit, will soon be on the air with a 1 kw W.E. fm transmitter. Transmitter is being built into the wall of the master control room located on the twenty-first floor of the Fisher Building.

G. E. Leydett is chief engineer.

A new television division has been set up in the G.E. Research Laboratory.

Clifford C. Pick, until recently division engineer of the receiver division, will head the new division.

PERSONALS

E. H. Vogel, manager of the radio sales division of G.E. from 1946 to 1949, has returned to the company as a member of the staff of Dr. W. R. G. Baker, vice president and general manager of G.E.'s Electronics Department.

R. J. Hartung is now controller of the radio tube division of Sylvania Electric Products Inc.

G. Robert Wannen, manager of Sylvania Electric's eastern radio tube sales division, died recently. He had been associated with the company for fifteen years.

Milton S. Roth has been appointed sales manager for Radiot Corp., Cleveland, Ohio.

PREMAX

Adjustable V Dipole Antennas For FM

*Insure Better
Reception!*

Actual operation proves the Premax FM-130 Adjustable Dipole Antenna with its exclusive 3d dimensional adjustment materially reduces man-made electrical noise in FM reception.

This Antenna has been found to be the dealer's and service man's solution to poor reception because he can adjust this antenna to cope with local conditions and cancel out noise and reflected signals.

Send for special Bulletin FM-130, telling why an adjustable 1 antenna is best for FM and TV reception.

Premax Products

Div. Chisholm-Ryder Co., Inc.

4809 Highland Av., Niagara Falls, N. Y.

Murray G. Crosby has started the firm of Crosby Laboratories, 126 Old Country Road, Mineola, N. Y., where he will conduct a radio-electronic consulting practice. He was formerly with Paul Godfrey Co.



M. G. Crosby

N. F. Shofstall has been placed in charge of all engineering for the G.E. receiver division, with headquarters at Electronics Park. His new title is division engineer.

Shofstall succeeds C. G. Pick.

C. R. Schmidt has joined the staff of the Avatron Engineering Company, P. O. Box 131, Caldwell, N. J., as assistant chief engineer.

Sidney Davidson has been named WPIX studio supervisor; William J. Kelly, transmitter supervisor; and Joseph Strackbine, supervisor in charge of transmitter maintenance.

Davidson and Kelly were formerly with NBC and Strackbine was with RCA.

Other engineers who have joined WPIX include Charles Anthony Voso, John F. Castello and Kenneth Petersen, formerly of WABD; Stanley Paul Palasek from CBS-TV; Michael Vardaky, formerly of Stewart Warner; Robert Lansing Mabot from WGN-FM; John R. Rieger, Jr. of the radio staff of the United Nations; Ephraim M. Abramson, a recent Carnegie Tech graduate; C. Russell Lea, Jr., formerly of WBBW, New Orleans and Armed Forces Network, Newark; Dominick Bernas, Michael Freier and Harold V. Smith.

F. D. Meadows is now merchandise manager of the Broadcast Audio Group of the RCA Engineering Products Department.

Meadows will supervise the merchandising of broadcast audio equipment.

R. B. Rennaker has been appointed sales manager of the mobile radiotelephone division of FTR.

Rennaker joined Federal in 1945 as broadcast equipment sales engineer, subsequently became associated with Collins Radio and rejoined FTR recently.



R. B. Rennaker

J. C. Farley has been named general manager of the Radio Division, Sylvania Electric Products Inc.

Farley was formerly controller of the Radio Division.



J. C. Farley

Sanford H. Levey has been appointed sales manager of Allied Radio Corporation, Chicago.

LITERATURE

The Cannon Electric Development Co., Humboldt St. and Avenue 33, Los Angeles 31, Calif., have issued a new 32-page edition of its condensed catalog, the C-47 edition, covering the thirteen major type series of multi-contact electric connectors for radio, aircraft, communications, etc.

Also included in the catalog are data on d-c solenoids and signal equipment, etc.

Karp Metal Products Co., Inc., 129 30th Street, Brooklyn, N. Y., has published a 16-page catalog describing facilities for fabricating sheet metal cabinets, housings, enclosures, metal boxes, etc., and illustrating cabinets and housings for broadcasting transmitters, television equipment and electronic test equipment.

Utah Radio Products, Division of International Detrola, Huntington, Indiana, have released a 1948 radio replacement speaker catalog, No. 100.

Electrical and physical specs for speakers are listed in tables.

L. S. Brach Manufacturing Corporation, Newark, N. J., have published a 16-page catalog (No. 48-A) describing lightning arresters, gas relays, terminal strip, potheads, etc.

Standard Transformer Corp., Dept. B. Elston, Kedzie and Addison Streets, Chicago 18, Ill., have prepared a 24-page catalog (140-H). Listed are over 400 stock items, including audio and power transformers and reactors, power packs, volt adjusters, radio transmitter kits and television components. Also included are charts on transmitting tubes, driver-modulator combinations and matched power supplies.


Clarostat Mfg. Co., Inc., 130 Clinton St., Brooklyn 2, N. Y., have prepared a wall chart with type designations, brief specs, photographs and detailed drawings of standard controls, attenuators, fixed and adjustable resistors, flexible glass-insulated resistors, midjet power resistors, ballasts and line-voltage-dropping resistors, power resistance decade box, television-tube beam-bender, and synchronous motors.

Radio City Products Co., 152 West 25th St., New York 1, N. Y., have published a bulletin, No. 133, describing ni-neg multimeters, the model 450 series, which includes six different units in open face models and in portable boxes.

Unit operates without batteries and tubes in the high ohmmeter circuit; provides resistance measurements of 50 to 1,000 megohms. Low-ohm range uses a single cell battery.

Electro-Voice, Inc., Buchanan, Michigan, have released a bulletin (No. 140), on *mobilmikes* for commercial and emergency 2-way communications.

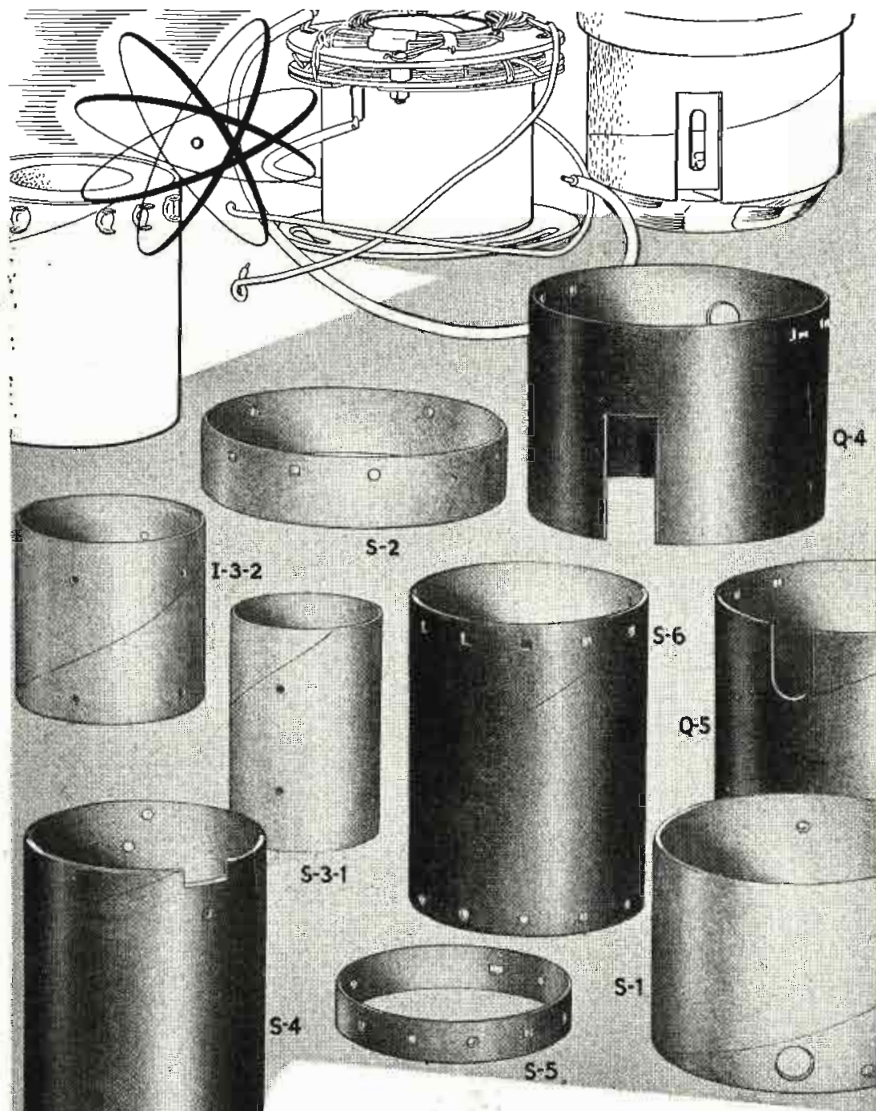Data covers carbon, dynamic and differential carbon *mobilmikes* for aircraft, police, fire, taxi, marine, utility, forestry, and similar services. Includes listing of carbon *mobilmikes* for exact replacement in current Motorola, RCA, G.E. and similar mobile equipment.



COSMALITE* TUBES

For Television deflection yokes

These spirally laminated paper base, phenolic tubes are obtainable in sizes and with punching and notching that meet each customer's individual needs.

Quality performance at prices that appeal.

OTHER COSMALITE TYPES INCLUDE . . .

#96 Cosmalite for coil forms in all standard broadcast receiving sets. SLF Cosmalite for Permeability Tuners.

Spirally wound Kraft and fish paper Coil Forms and Condenser Tubes.

Partial List of Radio & Television Receivers in which COSMALITE is used:

Admiral
Arvin
Belmont
Bendix Radio
Colonial
Farnsworth
General Electric
Howard

Magnavox
Motorola
Sentinel
Stewart Warner
Warwick
Wells Gardner
Zenith

DEFLECTION YOKE SHELLS		
	Inside Diameter	Length
S-1	3"	2 9/16"
S-4	2 3/8"	3 7/16"
Q-3	3"	2 3/32"
Q-4	3"	2 1/32"
Q-5	3"	2 1/32"
S-6	2 3/8"	3 7/16"
DEFLECTION YOKE CORES		
S-3-1	1 3/32"	2 15/32"
S-3-2	1 3/32"	2 1/32"
S-3-3	1 3/32"	2 15/32"
I-3-1	1 1/32"	2 3/8"
I-3-2	1 1/8"	2"
DEFLECTION YOKE RINGS		
S-2	3"	3/4"
S-5	2 3/8"	1 5/32"

* Trade Mark Registered

Inquiries given specialized attention.

The CLEVELAND CONTAINER Co.

6201 BARBERTON AVE. CLEVELAND 2, OHIO

- All-Fibre Cans • Combination Metal and Paper Cans
- Spirally Wound Tubes and Cores for all Purposes
- Plastic and Combination Paper and Plastic Items


PRODUCTION PLANTS also at Plymouth, Wisc., Ogdensburg, N.Y., Chicago, Ill., Detroit, Mich., Jamesburg, N.J.
PLASTICS DIVISION at Plymouth, Wisc. • ABRASIVE DIVISION at Cleveland, Ohio
SALES OFFICES: Room 5632, Grand Central Term. Bldg., New York 17, N.Y., also 647 Main St., Hartford, Conn.
CANADIAN PLANT: The Cleveland Container Canada, Ltd., Prescott, Ontario



Designed for



Application

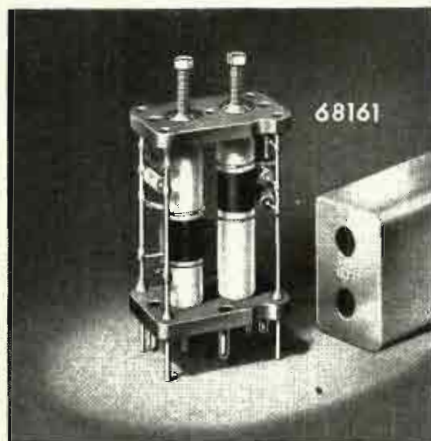

I. F. TRANSFORMERS

The Millen "Designed for Application" line of I. F. Transformers includes both variable air dielectric condenser and permeability tuned types for 5000 KC, 1600 KC, and 455 KC, as well as permeability tuned units for 50 KC-BFO, Interstage, Diode, Discriminator, Standard as well as DeLuxe Mechanical Design.

**JAMES MILLEN
MFG. CO., INC.**

MAIN OFFICE AND FACTORY
MALDEN
MASSACHUSETTS




NBC TV / F-M In Washington, D. C.



Above, control equipment setup at WNBW (66-72 mc)/WRC-FM (93.9 mc), Washington, D. C. In *a* appears the audio frequency preamp for f-m and tv. A jack feed is at *b*. At *c* we have a volume indicator and at *d* input controls. A limiting amplifier is shown at *e* and the volume indicators are at *f*. At *g* is the transmitter input control which permits switching of the entire spare a-f chain to either transmitter. Monitor amplifiers are at *h* and repeaters of percentage modulation are shown at *i*. The monitor control panel with switching, which permits listening to tv sound, f-m, or off-the-line material is at *j*. At *k* is the master monitor and power supply and at *l*, the master monitor for NBC. Master monitor switching is at *m* and at *n*, the master monitor and power supply. At *o* is an RCA tv receiver.

In view below, at *a*, are the lines to the antennas. At *b* is the line to f-m and at *c* is a quarter-wave transmission line for the television system. At *d* is the line to the tv picture transmitter, while in *e* is the line to the tv sound transmitter. At *f* is the triplexer in which there is an extra quarter-wave setup for f-m. At *g* is the diplexer and at *h* the dummy load. The vestigial side-band

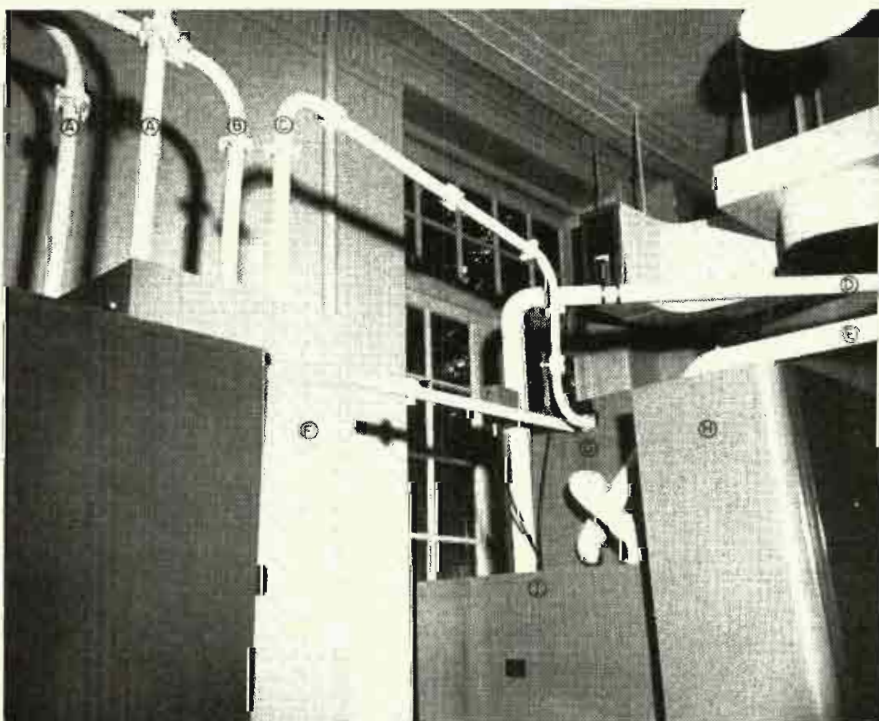

TV Transmitter Design


(Continued from page 22)

couples into the primary at resonance, is equal to the primary resistance. This coupling is called *critical coupling* and causes the secondary response characteristic to have the maximum possible value it can attain; Figure 7b. If the coupling is increased beyond critical coupling the secondary response begins to show double humps with the peaks becoming progressively more pronounced and further apart as the coefficient of coupling is increased. It is important to note, in the practical case, that when the loaded and unloaded circuit Q 's are not equal, the double humps do not appear in the secondary response until the coupling is somewhat greater than the critical value. A curve showing the effect of greater than critical coupling is illustrated in Figure 7c. Where the Q of the circuits is high, the double peaks will be quite sharp resulting in a pronounced valley between the peaks. This effect may be reduced by increasing the secondary load, which will lower the double peak response and make the overall characteristic more *flat topped*, as shown in Figure 7d.


[To Be Continued]

Figure 7

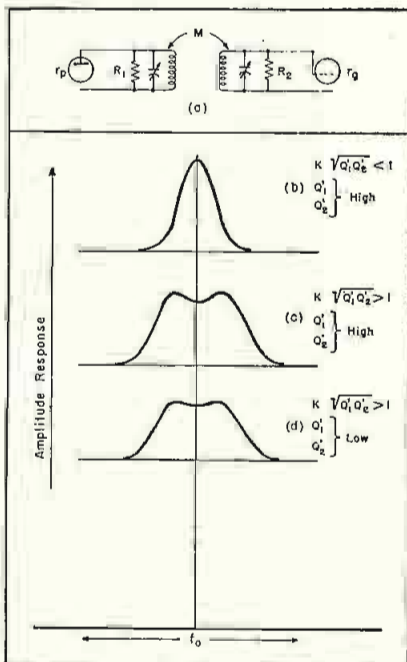At a appears a fundamental coupled circuit, and at b, c, d we have the effect of coupling and circuit loading.



Shallcross

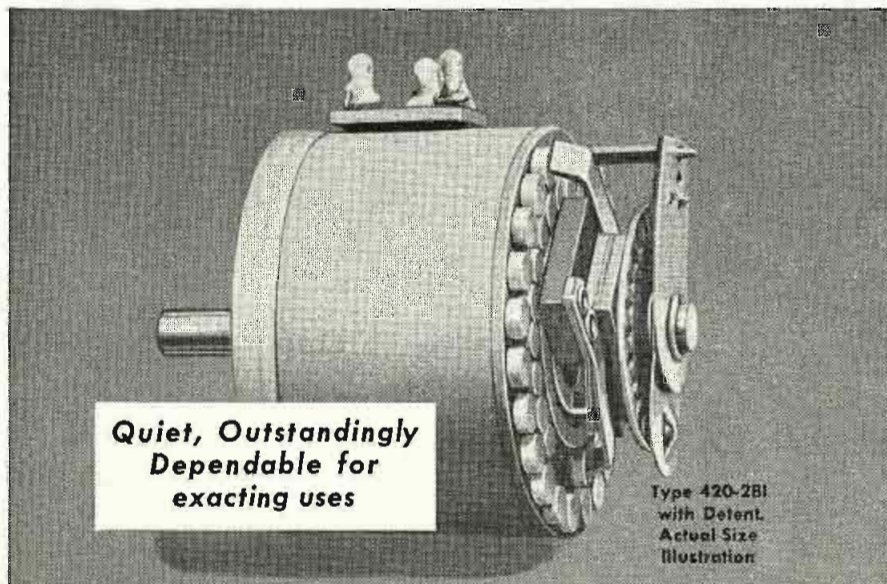

announces the 420-OBO series of bridged "T" ATTENUATORS

CHECK THESE IMPORTANT SPECIFICATIONS

ELECTRICAL CHARACTERISTICS —

Circuit — Bridged T

Attenuation — 1, 2, 3 db/step (odd values available on special order)

Number of steps — 20

Attenuation Characteristic — Available in linear, linear with off position or tapered on last 5 steps to off.

Impedance — 30, 60, 150, 200, 250, 500, 600 ohms, in or out. Other values on special order.

Insertion loss — Zero.

Resistors — All wound with low temperature coefficient wire.

MECHANICAL CHARACTERISTICS —

Diameter — 2 1/8"

Back of panel depth — 2" (with detent 2 5/16")

Mounting — Two 6-32 or 8-32 screws on 1 1/2" centers

Shaft Length — 15/16"

Contact Spacing — 15°

Good things continue to come in small packages! If you're looking for a small attenuator of highest quality — if you want all the quality features normally found in large units but still must save space — Shallcross has the answer.

Measuring only 2 1/8" in diameter, the new 420-OBO Series Bridged T Attenuators are destined to satisfy many important requirements for speech input engineers. The various characteristics available make these new units ideal for use as mixer or master gain controls. In addition to compact construction and the wide variation of ranges and tapers available to your specifications, consider these typical Shallcross quality features:

1. Attenuation characteristic essentially flat from 30 to 15,000 cycles.
2. Attenuation in "off" position 100 db or better.
3. All resistors non-inductively wound and sealed against moisture and shock.

A New Shallcross Cueing Attenuator

Any standard Shallcross ladder, bridged T, or straight T attenuator may be equipped for cueing action without any increase in the diameter of the unit. With it, the operator can listen for cue and transfer a program from cueing amplifier to the transmitter smoothly and efficiently merely by turning up the volume instead of reaching for a separate switch. Write for complete details.

Write for Attenuator Quotation Specification Sheet

SHALLCROSS MANUFACTURING COMPANY


Dept. C-68, Collingdale, Pa.



STANDARDIZED READY-TO-USE METAL EQUIPMENT

ADAPTABLE FOR EVERY REQUIREMENT

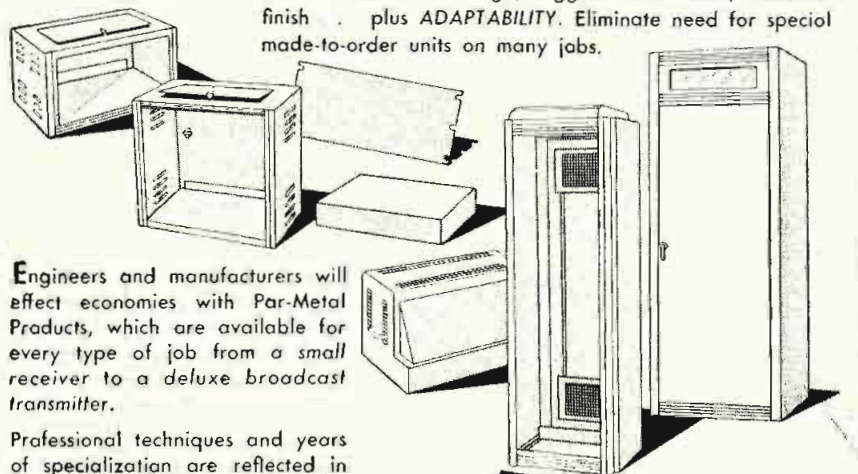Par-Metal Equipment offers many features, including functional streamlined design, rugged construction, beautiful finish . . . plus ADAPTABILITY. Eliminate need for special made-to-order units on many jobs.



Engineers and manufacturers will effect economies with Par-Metal Products, which are available for every type of job from a small receiver to a deluxe broadcast transmitter.

Professional techniques and years of specialization are reflected in the high quality of Par-Metal.

**CABINETS • CHASSIS
PANELS • RACKS**

Write for Catalog



TV Antenna

(Continued from page 14)

banding stub as shown, with the cable shield bonded to the leg at several points along its length. Under this condition the cable shield becomes an integral part of the stub conductor, but since the diameter of the shield is small compared to that of the stub conductor there is no serious alteration in either the Z_0 or the balance of the broad-banding stub. Hence, the signal delivered to the coaxial line from the antenna system is essentially only that energy which is derived from the dipole elements, with no extraneous contributions from any signal components which may be picked up on the outer surface of the coaxial-cable shield.

As an alternative coaxial-fed arrangement, the dual-band antenna conductors may be fabricated of tubing and the coaxial cable then inserted up through the center of one of the stub legs via a hole in the bottom head. It may then be brought out through another hole in the corresponding top head, and the shield and center conductor connected as before. Although this method is somewhat better electrically than the one described in the preceding paragraph, it may result in some sacrifice of mechanical strength occasioned by the use of tubing instead of solid rod.

Gain-Producing Arrays

To obtain a dual-band antenna array with greater directivity (and therefore higher gain) than that of a normal dipole, two or more antenna assemblies may be combined in various fashions. Figure 8 illustrates a T arrangement whereby one dual-band antenna assembly is used as a parasitic reflector element for another dual-band antenna. The assemblies are attached to a common mounting base and inclined 60° with respect to each other, each one being inclined 30° from vertical. The 60° inclination between antenna systems is the value required to produce a quarter-wave spacing both between the high-band dipole and its reflector element and between the low-band antenna and its reflector. The shorting link shown across the feed point of the reflector is the only short-circuiting device necessary, since it automatically reflects a short circuit across the high band parasitic element in the proper frequency range.

For still higher gain and directivity than described in the preceding paragraph, four assemblies may be combined in an X type of array, as

Wanted

- ★ **PHYSICISTS**
- ★ **RADAR ENGINEERS**
- ★ **SYSTEMS ENGINEERS**
- ★ **ELECTRONIC ENGINEERS**

To enable us to carry out our long-term engineering program on missiles, radar, communications, etc., we must add a considerable number of qualified graduate engineers with electronic, research design and/or development experience to our staff. Please furnish complete resume of education, experience and salary expected to: Personnel Manager

BENDIX RADIO DIVISION
Bendix Aviation Corporation
Baltimore 4, Maryland

sketched in Figure 9. Here the pair of assemblies described in the preceding paragraph is combined with a similar pair, inverted, with the entire combination supported from a central mast through which is fed the balanced transmission line which connects the array to the receiver. The upper and lower *V* assemblies are fed in parallel, as shown, although the impedance properties are not as favorable for this array as they were for the preceding antenna systems.

The dual-band antenna system has also been found to reject signals which occur in the neighborhood of 140 and 280 mc, i.e., at the frequencies where the broad-banding stub is an integral number of half-wavelengths long. This action takes place because the stub reflects a short-circuit across the feed point at these frequencies. This property is useful in rejecting interference from signals in these frequency bands, so that the image ratio of the overall receiver-plus-antenna system is hence improved.

Use With 300-Ohm Line

Another feature of this antenna system is that, although its impedance is nominally about 70 ohms, its use in conjunction with 300-ohm transmission line, properly terminated by the receiver input impedance, will generally result in an improvement of signal-to-noise ratio (or noise figure). This well-known effect takes place because the noise level (referred to the input circuit) of most tv receivers is from 10 to 18 db above thermal noise, whereas the noise from the antenna resistance is substantially at thermal level. Hence, mismatching the antenna to the receiver in the manner indicated will result in a measurable improvement of signal-to-noise ratio, while not seriously impairing the bandwidth of the system.

AT NAB MEETING



S. P. Taylor (left), manager distributor sales, W.E. Radio Division, discussing the W.E. 728 loudspeaker with Neal McNaughten and Royal V. Howard of the NAB engineering department, at the recent NAB Convention in Los Angeles.


KFI's NEW 50,000 WATT VERTICAL ANTENNA 750' high, tallest on the West Coast. Erected by IDECO, this tower is equipped with "Guardian" Tower and Obstruction Lights.

LOWER Maintenance Costs!

WITH H & P *Guardian* TOWER LIGHTS

"Guardian" 300 mm Tower Lights, Obstruction Lights and Code Flashers, furnished as standard equipment by leading tower manufacturers, are consistently specified by outstanding radio engineers because of dependable performance under every operating condition..

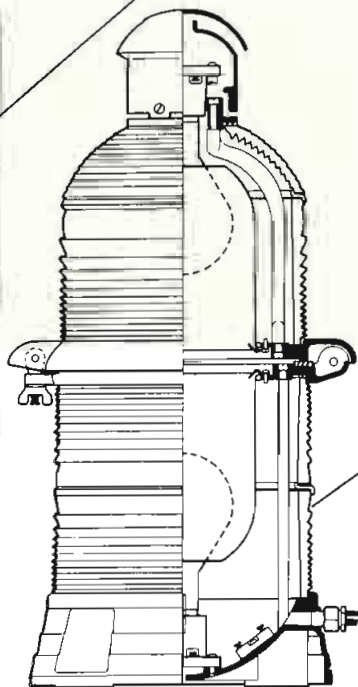**"Guardians" INCREASE Safety Factor
PROLONG Lamp Life . . . LOWER Maintenance Costs!**



Patented Ventilator Dome circulates the air—reduces internal temperature—increases lamp life. Water cannot enter vents even during most severe rainstorm.

Concave Base with drainage port at lowest point dissipates condensation moisture, prevents short-circuits.

Spun-Glass Shielding on color-screen supports provides glass-to-glass contact with color screens, equalizing contraction and expansion due to temperature changes. Color-screen breakage virtually eliminated.

Recessed Neoprene Gasket and completely concealed center hinge provides **positive protection** against dirt and moisture at this most vulnerable point. Neoprene gaskets used throughout in place of cork. Compounded to last indefinitely.

Improved Locking Device with butterfly clamp maintains secure center seal.

"Guardian" complete lighting kits can be furnished for conduit installation subject to availability, or exposed wiring installations in any quantity.

**FOR COMPLETE
INFORMATION
AND NAME OF
NEAREST DEALER
WRITE TO**

**SOLD ONLY THROUGH JOBBERS and
TOWER MANUFACTURERS**

HUGHEY & PHILLIPS

**326 NORTH LA CIENEGA BLVD.
LOS ANGELES 36, CALIFORNIA**

TUBE *Engineering News*

WITH THE ACCELERATED INTEREST IN commercial s-h-f work has come an increased demand for special types of s-h-f tubes, such as the magnetron, particularly in wide-range tuning systems. Many projects devoted to the development of such systems have been set up.

Describing one such research program at the recent IRE National Convention, E. Navin Kather, of Raytheon, pointed out that the ultimate design requirements of any wide-range tunable magnetron are linear tuning, uniform input current and voltage, constant power output and efficiency, and a high order of stability.

These are substantial requirements to meet. We find, for instance, that the electronic efficiency of a magnetron of fixed anode and cathode diameter and length will change as its resonant frequency is varied. If constant input voltage and current are to be obtained, the magnetron will require a varying magnetic field over the tuning range. However, a change of the magnetic field will aggravate the variation of the electronic efficiency which results from changing the resonant frequency of the magnetron. Introduction of a tuning element into the resonant circuit of the magnetron usually is accompanied by increased losses and lower circuit efficiencies, especially if the tuning element is resonant at any frequency through which the magnetron is tuned. These

losses are reflected in lower overall Q values.

Satisfactory magnetron performance is dependent on a proper separation of its resonant modes. The tuning element usually changes this mode separation, and if not restricted may prevent operation of the magnetron in the π mode at the required power input.

It is possible to secure wide-range tuning with mechanical systems where the resonant frequency of the magnetron is changed by moving some element in the associated resonant circuit. From the mechanical viewpoint, these systems may be divided into four groups: coupled reactive, capacitive, inductive, and combination capacitive-inductive systems. Any one of these groups may be symmetrical or unsymmetrical in relation to the magnetron resonant circuits. The circuit elements of a symmetrical system are varied in a manner that preserves angular symmetry about the magnetron. In the unsymmetrical system, this angular symmetry is not preserved.

Defining the coupled reactive system Kather said that in this system the resonant frequency of the magnetron is varied indirectly by a second resonant circuit coupled to the magnetron. Such a system offers an advantage, since the coupling circuit may be external to the magnetron and thus not confined to the limitations imposed by the magnetron geometry. The coupled

resonant circuit, however, introduces new modes in the magnetron mode spectrum and, because of the stored energy in the coupled circuits, increases the stabilization of the magnetron. The increased stabilization usually increases the tendency of the magnetron to operate in undesired modes and, therefore, must be limited if satisfactory operation over a wide tuning range is to be obtained. These inherent properties limit the useful tuning range of such systems to about 10%.

Capacitive-Tuning System

In the capacitive tuning system the capacity of the magnetron resonant circuit is varied directly. The most successful systems accomplish this variation by changing the strap or vane capacity. The strap capacity tuner or *cookie cutter* generally takes the form of a third ring inserted between the straps of the magnetron. In the vane type tuner we usually have a set of *fingers*, sometimes referred to as a *sprocket* or *crow's foot*, which is inserted between the vanes comprising the resonant cavities of the magnetron. These *fingers* are confined to the capacitive portion of the cavities and, since the greater part of the total capacity in the magnetron resonant circuit is usually contained in this region, greater tuning ranges are obtained by using the vane capacity system. A capacitive system requires close spacing for greatest tuning range and, therefore, is subjected to voltage breakdown limitations.


Inductive-Tuning System

In the inductive-tuning system, the inductance of the magnetron resonant circuit is varied directly. This system may take a form similar to the vane type capacitive tuner, excepting that the *fingers* are inserted into the inductive region of the magnetron resonant cavities, thus varying the inductance thereof. Such systems usually introduce greater losses and are, therefore, limited in application.

Kather disclosed that a combination of the capacitive and inductive systems yielded a system which would give the greatest tuning range. This combination system consists of capacitive fingers joined to inductive fingers, so proportioned with respect to the anode that proper movement of the tuner will result in maximum inductance, maxi-

Figure 1

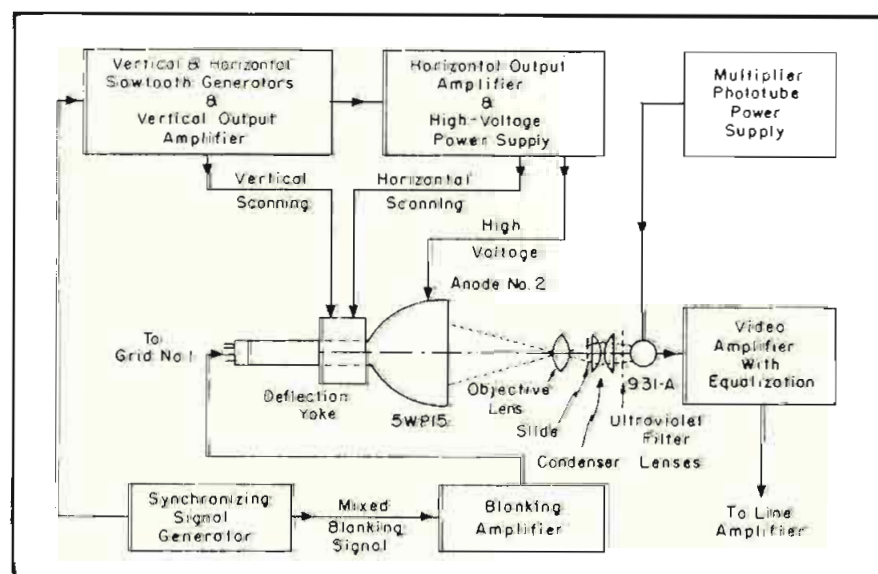Block diagram of flying-spot video-signal generator system for slide transparencies.



imum capacitance or minimum inductance, minimum capacitance, or all degrees in between.

The case of a 200-watt c-w magnetron, tunable from 3,500 to 5,500 mc, was used by Kather to illustrate how the problem of designing a wide-range tuning system was solved.

A vane-type capacity tuner of linear characteristics was chosen for use in this particular magnetron because the voltages were relatively low and close spacing between the tuner and vanes of the magnetron resonant cavities could be tolerated. The undesirable inductive effect of the tuning *fingers* was considerably reduced by cutting a *V* slot in the back of each finger, thus minimizing the disturbance to the r-f field and resulting in a 22% increase of the tuning range. A variation of the magnetic field required for constant-input voltage and current was accomplished by arranging one magnetic pole face so that it would move with the tuner system, noting that as the capacitive *fingers* were inserted, the resonant frequency was lowered and a higher magnetic field was required to maintain constant input voltage. This variation in magnetic field must be accomplished without producing excessive distortion in the interaction space of the magnetron.

As the magnetron is tuned, both the resonant frequency and magnetic field are changed, resulting in a wide variation of the electronic efficiency over the tuning range. Compensation for this variation was obtained by designing the output coupling circuit so as to vary the circuit efficiency inversely with respect to the electronic efficiency and yet maintain reasonable stability. Satisfactory circuit efficiencies over the entire tuning range could not be obtained until the resonant modes of the tuning system were determined and adjusted. Kather pointed out that, unfortunately, a tuning system designed to mesh with the resonant cavities of a magnetron is necessarily comparable in size and, since the tuner system resonates in much the same fashion as the magnetron cavities to which it is coupled, the natural resonant modes of the tuning system are normally close in frequency to those of the magnetron. The tuner assembly was, therefore, designed so as to move its family of resonant modes out of the magnetron tuning range and yet provide adequate dissipation of the r-f losses.

Performance tests on this magnetron showed that the tube had a tuning ratio of 1.57:1 with a power output variation of 12% and input voltage

Wide-Range Tuning System for Magnetrons . . . Flying Spot C-R Tube . . . Notes on Interchangeability of 5516 and 2E24.

variation of only 4% over the entire range.

Flying-Spot Cathode-Ray Tube

A FLYING-SPOT cathode-ray 5" tube, 5WP15, which permits the telecasting of individual station call letters and test patterns from interchangeable slide transparencies or from opaque surfaces, has been developed by RCA.

The tube, which has a metallized back, furnishes a small, rapidly moving spot of radiant energy for scanning a slide transparency or opaque object.

Featured in the 5WP15 is a new short persistence phosphor having a large component of its energy emission in the near ultraviolet region. The persistence of the ultraviolet radiation is so short that the amount of equalization needed in the video amplifier to minimize trailing in the reproduced picture is small and can be supplied by a single network.

Magnetic deflection and electrostatic focus are utilized to permit obtaining essentially uniform focus over the useful screen area. Other design features include an external conductive coating on the neck which, when grounded, prevents corona between yoke and neck, built-in capacitance between interior and exterior neck coatings to serve as a filter capacitor for the high-voltage power-supply unit, an external insulating coating on the bulb cone to minimize sparking over the glass bulb under high humidity conditions and a duodecal 7-pin base for high-voltage service.

Flying-Spot Video-Signal Generator

A flying-spot video-signal generator consists essentially of a flying-spot cathode-ray tube with associated power supplies, deflection yoke, and scanning circuits to provide a small, rapidly moving source of radiant energy, optical system arranged to project the raster on the subject to be scanned, subject which may be a slide transparency, motion picture film or an opaque object, multiplier phototube with associated power supply to intercept the radiation transmitted or reflected by the subject and convert it into video signals, and an amplifier to

increase the strength of the video signals.

A setup of such a system arranged for use with a slide transparency appears in Figure 1. For best results, the objective lens must be a high quality, enlarger type designed for low magnification and preferably corrected for use with ultraviolet radiation. The diameter of the objective lens should be adequate to cover the slide to be scanned. For use with 35-mm slides, the Kodak Enlarging Ektar f:4.5 lens with focal length of 100 mm, or equivalent, is suitable.

For absorbing the visible and passing the ultraviolet radiation of the screen the Eastman Wratten Nos. 18A, 34, and 35 as well as the Corning Nos. 9863 and 5970 filters can be used. The choice of filter for a particular generator design is affected by a compromise between the permissible loss of signal output through absorption by the filter on the one hand, and the amount of trailing which can be tolerated, or the extent of equalization needed, on the other hand.

Trailing results from the lag in buildup and decay of output from the screen. As the flying spot moves across a boundary from a light to a dark area of the subject being scanned, the persistence of energy output from the screen results in continued input to the phototube from the light area during the time the dark area is being scanned. Thus, the light area trails into the dark area in the reproduced picture. Similarly, as the flying spot moves from a dark area to a light area, the lag in buildup of the screen output causes the dark area to trail over into the light area. As a result of these effects, the reproduced picture has an appearance similar to that produced by a signal deficient in high frequencies. It is, therefore, necessary to enhance the high-frequency response of the video amplifier by introducing equalizing networks of the resistance-capacitance type with suitable time constants. Sufficient equalization should be provided to give the desired square-wave response.

The decay characteristics of most standard phosphors are such as to require considerable equalization provided by networks with different time constants in several stages of the video


(Continued on page 36)

STATION WHKC ...Selects TECH LABS VERTICAL ATTENUATORS

for new CONSOLE INSTALLATION



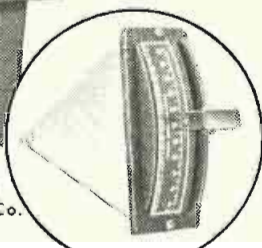The flick of a finger operates the patented "Gove" Vertical Attenuator. Representing the very latest in broadcast components, these units are suitable for every type of sound equipment from elaborate broadcast stations to the simplest P.A. system. Unit gives smooth easy operation and can be cleaned from front of panel by removing escutcheon. Completely shielded and dust proof.



Write
for
Descriptive
Bulletin


Courtesy of WHKC,
United Broadcasting Co.



Manufacturers of Precision Electrical Resistance Instruments
337 CENTRAL AVE. • JERSEY CITY 7, N. J.

TERMINAL'S SOUND STUDIO is now demonstrating the amazing recent developments in TRUE SOUND REPRODUCTION

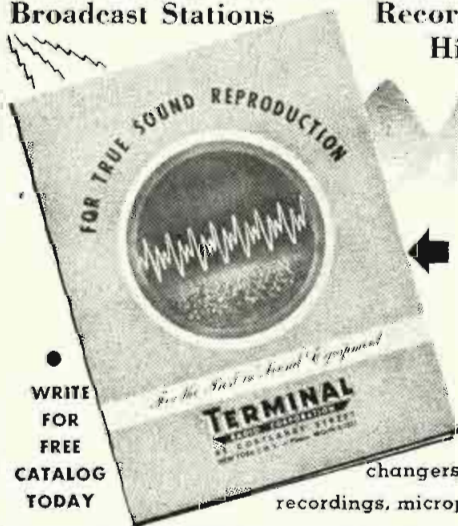FEATURING SOUND EQUIPMENT FOR
Broadcast Stations Recording Studios... Set Builders
High Fidelity Enthusiasts...



See and hear the finest and latest in sound equipment. New York's leading radio and electronic distributor invites you to Terminal's uniquely equipped sound studio.

Our well illustrated catalog is yours for the asking...featuring the latest amplifiers, tuners, speakers, record changers, cabinets, pick-ups, phono cartridges, recordings, microphones and essential sound accessories.

WRITE
FOR
FREE
CATALOG
TODAY

TERMINAL RADIO CORP.
85 CORTLANDT STREET, NEW YORK CITY, N. Y. • WO-4-3311

Maintenance

(Continued from page 16)

cations receivers, we first applied a 5-microvolt signal at 13 mc through 70 ohms to the input of the receiver, sensitivity maximum and ave on. We then recorded the output across a 600-ohm load for conditions of signal unmodulated and signal modulated 30% at 400 cps. A receiver in good condition might give an output in the latter instance of 20 db higher than in the former case. A borderline receiver, which is beginning to show noticeably decreased sensitivity during normal operation might give readings differing by only 10 db. Depending upon the conditions of operation, a limit might be set, such that any receiver giving a difference of less than 14 db is regarded as unsatisfactory and is removed for repair before it hampers operation.

Inspection procedures must be designed to reduce the number of failures during operation. The actual inspection may be as valuable as any part of the procedure. It is intended that if possible inspection procedures be carried out at such times as the equipment is normally idle so they do not require interruption of service. The same is true of replacement of equipment found defective by these inspections.

Maintenance Procedures

The purpose of maintenance procedures is to prolong the useful life of equipment, to reduce the total number of failures in operation and rejections by periodic inspection. These procedures will thus necessarily include their own inspection. They will be complete and include their own set of performance standards. The repair procedure for the aforementioned receivers might include six steps:

- (1) Inspection procedure, if it has not been done.
- (2) If trouble is mechanical, processing of necessary repairs.
- (3) If trouble is sensitivity, checking of tubes (testing sensitivity if replacements are made) and readjustment if required, plus an additional sensitivity test.
- (4) If trouble is failure of component, determining cause, correcting and replacing of part.
- (5) Cleaning and examining for signs of overheating and deterioration.
- (6) After 72 hours of operation, another inspection procedure.

In this example, the emphasis is on finding specific difficulties and correct-

ing them, then making sure the receiver is in good condition. Inspection is stressed rather than repair because unnecessary work is costly and sometimes introduces more difficulties than it eliminates. This imposes severe requirements on the tests applied at the completion of the repair work.

The test part of the inspection procedure is applied most successfully to r-f equipment. Mechanical equipment often responds best to visual inspection. Since this inspection may require partial dismantling of the equipment, it can conveniently be combined with cleaning and lubrication of the machines. The combined maintenance-inspection procedure must be undertaken at regular intervals.


Analysis Procedures

In order to arrive at effective inspection and maintenance procedures for any operational system, the results of a large number of experiments must be recorded and evaluated. The starting point will, of course, be the best accepted practices. After some weeks, shortcomings in these practices will be detectable and changes to be made in the procedures will suggest themselves, a step to be added here or a requirement to be relaxed there, the frequency of inspection on a certain unit to be changed. The value of these changes must, by some simple and accurate means, be made evident.

The information required for this evaluation is found in the record of failures in service and rejection during inspection. If servicing of all equipment is centralized in one location, a simple form such as that shown in Figure 1 may suffice for the record of failures in service. The *time reported* and *time repaired* entries disclose the length of time the unit is out of service. The *action taken* entry tells what the conditions of service were in the meantime. *Trouble reported* and *trouble found* are both recorded because they are not necessarily the same and they may indicate the need for instructing operating personnel. Finally, the repairman's name is required for evaluation of his competence.

The *equipment and number* column in the *trouble log* provides reference to an *equipment repair record card*, Figure 2. Each individual of a group of identical units must be numbered and a card kept for it. These cards are used as a current status report on individual items. They make it possible to spot individuals which are not conforming to the average of performance.

Proved in Millions of Applications!



RELAYS RESISTORS RHEOSTATS

Vast Variety of Stock Units ANSWERS EVERYDAY NEEDS ECONOMICALLY

Relays are available from stock in general-purpose, industrial, and radio amateur types for continuous or intermittent duty.

Vitrohm wire-wound Fixed Resistors are available in 8 stock sizes from 5 to 200 watts. Adjustohms in 7 stock sizes from 10 to 200 watts. Plaque Resistors in 3 sizes from 20 to 125 watts. Discohms in 18 watts. Stripohm in 5 stock sizes from 30 watts to 75 watts. Ring-type close control Rheostats in 4 stock sizes from 25 to 150 watts. (Plate Type Rheostats recommended for larger sizes.) Wide variety of Resistance Values.

**AUTHORIZED DISTRIBUTORS EVERYWHERE
WARD LEONARD ELECTRIC COMPANY**

Radio & Electronic Distributor Division
53-M West Jackson Blvd., Chicago 4, U. S. A.

SEND FOR HELPFUL CATALOGS
Catalog D-30 gives complete data and listings on stock units available in Resistors, Rheostats and Radio Amateur Relays. *Catalog D-20* lists Industrial and General-Purpose Relays. *Write for them today!*



WARD LEONARD

Basic 3R's in Current Control

The *inspection procedures* are, of course, outlined in such form that they are readily available to the people concerned. It is only necessary, then, that certification be made that the prescribed procedures have been carried out and the units found unacceptable listed on the *inspection report* of Figure 3. Here again we find it is possible to transcribe pertinent data to the *repair record card*. The designation number of name of the *inspection procedure* appears in column 3, and a description of the defects found in col-

umn 4. Names of inspector and workman are required as certification, and the time required for repair is needed for totalling repair costs.

The *inspection reports*, *trouble logs*, and certification of performance of *inspection procedures* for any period contain all data concerning equipment failures, and repairs over that period. It remains only to summarize the information and determine significant relationships. This is a simple clerical

(Continued on page 36)

Developed and Engineered for Better Television Reception

THE MEGA- TENNA


(Pat. Pending)

**NO INSULATING
SUPPORTS REQUIRED**

**HAS
DUAL BAND FEATURES...**

**LOW V.S.W.R. FOR
ALL CHANNELS...
UNVARYING DIREC-
TIVITY PATTERN...**

**RUGGED
CONSTRUCTION**

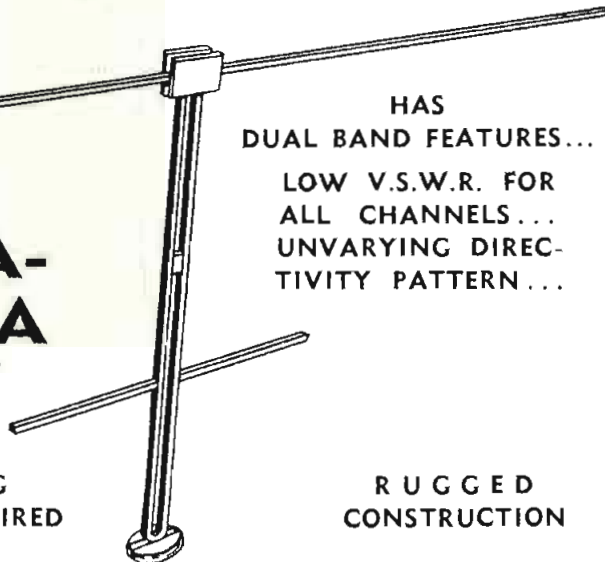

Exhibits a substantially constant figure-of-eight pattern in both lower and upper television bands.

Matches a 70 ohm transmission line to a reflection factor magnitude of less than 0.5 from 55 to 80 mc and 170 to 220 mc. At the same time, rejects signals in the 140 and 280 mc regions to improve effective image ratio.

Can be used with either balanced or co-axial transmission line.

Easily and firmly mounted. Requires

no separate supporting mast. May be grounded for lightning protection without affecting characteristics.

High frequency dipole may be mounted at angle to low frequency dipole where high band and low band stations are in different directions with respect to the receiving point.

By combining several assemblies, various arrays may be obtained to produce higher gain.

Write for further details.

OHMEGA LABORATORIES, INC.

23 MAPLE AVENUE
PINE BROOK, N. J.

(Continued from page 35)

task requiring only a slight acquaintance with the terms encountered in the records. Figure 4 illustrates a convenient form on which this summarization may be made.


As indicated by line 1, a sheet of this kind is kept for each type of equipment under consideration. A summarizing period of one month is shown because it is convenient for most purposes. The breakdown of failures in service and inspection rejections can be made as detailed as desired. Greater detail is likely to be required as the most common difficulties are eliminated and the factor entered on line 8 decreases. Care should be taken to enter on line 6 only the total time in unit hours (similar to man hours) that equipment was impeding operation.

The primary object of this whole program is to reduce the service interruption per unit, line 9, to as low a value as possible. A great deal can be done toward this end in some cases by providing spare units which can be put into service almost instantly. The secondary purpose is to reduce the entries on lines 3, 7, and 10, to values as low as practical. Here the inspection and maintenance time, line 12, comes into the picture. If the cost of failures in

service can be calculated, the problem simplifies to one of balancing failure cost against the cost of inspection and maintenance time. If the failure in service cost cannot be determined, a carefully considered decision must be made as to the permissible magnitude of the quotient in line 14. For example, one type of recording apparatus exhibited the failure characteristic shown in Figure 5 over a period of several months. This clearly defined characteristic was obtained only after some months of developing the inspection procedure and training the people who actually made the inspections. Knowing how many failures can be accepted, an engineer responsible for this equipment has little difficulty com-

Figure 5

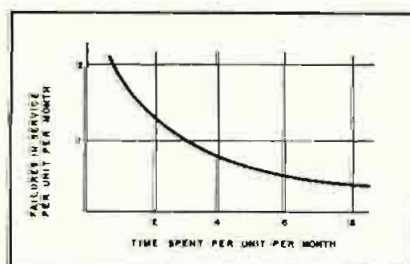Typical record of failure of equipment over a period of months; time spent in inspection and maintenance, not in repairing failures in service, being recorded.



cluding how much time has to be spent on the equipment.

Other equipment may not show such simple characteristics, especially when a program of this sort is first begun. Occasionally a type of equipment will be found which refuses to respond to inspection or to regular maintenance. If the trouble rate is low, the equipment is evidently well designed and constructed. If the trouble rate is high, the inspection and maintenance procedures should be examined with more than ordinary care; and finally, modification of the units should be undertaken. The record of troubles will point to the modifications required.

Tube News

(Continued from page 33)

amplifier. Their relatively long decay generally results in appreciable reduction of the useful signal-to-noise ratio. The persistence of the phosphor used in this tube, however, is comparatively so short that less equalization is needed. If the tube is used without an ultraviolet filter, less equalization is required than for other standard phosphors but a complex network is nevertheless needed because the decay characteristic is not a simple exponential curve but a curve of a complex function.

Grid 2 is incorporated in the 5WP15 to prevent interaction between the fields produced by grid 1 and anode 1. However, grid 2 may also be used to compensate for the normal variation to be expected in the grid 1 voltage for cutoff in individual tubes. By adjusting the voltage applied to grid 2, with due consideration to its maximum rated value, it is possible to fix the grid 1 bias at a desired value, and obtain almost the same anode-current characteristics for individual tubes having different cutoff voltages. Adjusting grid 1 cutoff in this way not only makes grid drive more uniform, but also reduces variations in anode 1 current. Since grid 2 draws at most only negligible leakage current, its voltage may be obtained from a potentiometer inserted in the anode 1 voltage divider.

The d-c power supplies for the 5WP15, which should be well filtered, consist of a high-voltage type (20,000-volt for recommended operation) preferably of the limited-peak-energy type, i.e., one in which the peak current even under short-circuit conditions is well below the value dangerous to life, for anode 2, and a negative supply of about 100 volts, depending on equip-

ment design, for grid 1. Voltage for anode 1 is obtained by means of a voltage divider across the high-voltage supply.

Soft x-rays are produced when the tube is operated with an anode 2 voltage above approximately 20,000 volts. These rays can constitute a health hazard unless the tube is adequately shielded. Relatively simple shielding should prove adequate, but the need for this precaution must be considered in equipment design.

Resolution of better than 700 lines at the center of the reproduced picture can be produced. To obtain such resolution in the horizontal direction, it is necessary to use a video amplifier having a bandwidth of about 10 mc.

The screen of the 5WP15 has radiation in the visible blue-green region and in the invisible near-ultraviolet region. The blue-green radiation decays hyperbolically to about 30 per cent of its initial value in 1.5 microseconds. The ultraviolet radiation has an equivalent exponential decay with a time constant less than 0.05 microsecond. The frequency response of the ultraviolet radiation is substantially constant for a range of 3 mc and then decreases exponentially toward zero at approximately 100 mc.

[Data based on copyrighted material supplied by RCA.]

Interchangeability Of 5516 With 2E24

THE 5516 is directly interchangeable with the 2E24, although when the tubes are interchanged without circuit changes the 5516 will be operating with less power input than the 2E24, because the 5516 normally requires a higher screen potential.

When a direct substitution is made without any circuit changes, there will be a corresponding reduction in power output, the efficiency remaining essentially the same, because of the lower plate power input.

To utilize the full capabilities of the 5516, it is generally necessary to increase the screen voltage of the 5516. In sets using a series screen dropping resistor, this is accomplished by decreasing the value of this resistor, or by shunting another resistor in parallel with the original one. As high as 250 volts may be applied to the screen of the 5516, this voltage being measured when the equipment is properly tuned and delivering power to the load. A change in the value of the control grid resistor may be required in some equipments. If this is necessary, a



"look for the
GREEN CORE"



... your
assurance of quality"

Panther and Dragon
friction and rubber tapes

lower value of control grid resistor will usually be needed.

When a set is modified for the use of the 5516 or designed to use a 5516, it is not generally possible to replace the 5516 directly with a 2E24. This is because the 5516 operates at a somewhat higher screen voltage (above the maximum rating for the 2E24) and because the 5516 carries higher ratings.

Typical modifications required for control grid and screen grid resistors when the 5516 is used in place of the 2E24 (when the 5516 or 2E24 is used as a doubler driver) are:

Resistor	2E24	5516
Control-grid resistor	100,000 ohms	50,000 ohms
Screen-dropping resistor	27,000 ohms	13,500 ohms (10 w)

The following data are applicable when two 5516 or 2E24 tubes are used as push-pull amplifiers:

Resistor	2E24	5516
Control-grid resistor	27,000 ohms	10,800 ohms
Screen-grid resistor	12,500 ohms (10 w)	8,500 ohms (10 w)

[Data courtesy Hytron.]

Breaking Strength tests HERE...



... assure strong splices

• The exceptionally high tensile strength of the fabric used in PANTHER and DRAGON Friction Tapes makes for stronger splices ... splices that last longer. This higher quality is guaranteed by constant checks on breaking strength, such as the one for ASTM specifications shown above.

PANTHER and DRAGON Friction Tapes also rate high in tests for adhesive and electrical properties ... work easily and stay spliced in cold as well as warm weather. Sold only through recognized independent wholesalers. The Okonite Company, Passaic, New Jersey.

6410



ANTENNA phasing equipment

Designed especially for your station, incorporating the recommendations of your consulting engineers, JOHNSON phasing equipment offers:

1. Optimum circuit design.
2. Heavier components, wider range of tuning adjustments.
3. Individually designed and built by E. F. JOHNSON for YOUR existing installation.
4. Automatic switching from directional to non-directional operation.

E. F. JOHNSON CO.
WASECA, MINNESOTA

OVER 10,000*

Broadcast
Communications
Radio-Television
Engineers & Executives
Subscribe to
COMMUNICATIONS

Advertising pays dividends!

ABC net paid

The Industry Offers

RCA MINIATURE BROADCAST MICROPHONE

A rugged 12-ounce microphone has been developed by the RCA engineering products department.

The microphone is said to have an output level comparable to that of conventional broadcast studio types.

GOTHARD MOBILE TRANSMITTER DYNAMOTOR

A dynamotor, designed especially for mobile transmitters, model GP-26, has been announced by the Gothard Manufacturing Company, 2110 Clear Lake Ave., Springfield, Illinois.

Dynamotor is available with power output ranging up to 80 watts continuous and 150 watts intermittent duty. Voltage regulation averages 99%, with unit efficiency about 61%. Weight is 8½ pounds, with the height of the unit 4½, frame diameter 3½, and the length 2½.

Further information may be obtained from M. A. Winkler, sales manager.

HEWLETT-PACKARD BATTERY- OPERATED VOLTMETER AND OSCILLATOR


Two battery-operated instruments, a vacuum tube voltmeter (404A) and audio oscillator (404B) have been announced by Hewlett-Packard Company, 355 Page Mill Road, Palo Alto, California.

The audio oscillator has a frequency range of 2 cps to 20 kc in decade ranges. Stability is said to be better than $\pm 3\%$ throughout frequency range. Output is 5 volts into a 10,000-ohm load, and frequency response is said to be flat within ± 1 db between 2 cps and 20 kc.

The instrument is tunable directly or by a 6 to 1 vernier micro-drive control. Five flash light and three standard 45 volt B batteries are accessible, mounted in rubber lined anti corrosive case, and balanced for over 60 hours life.

The battery-operated vacuum tube voltmeter is designed for ac measurements from 2 cps to 20 kc, with useful range extending to 50 kc. Voltages from 100 to 300 can be measured.

Input impedance is 10 megohms shunted by a capacity of approximately 20 mmfd. Accuracy is said to be $\pm 2\%$ over a range of 2 cps to 20 kc, $\pm 7\%$ from 20 kc to 50 kc or full scale including all error due to tube aging, warm-up, and battery voltage changes. The meter is calibrated to read rms value of a sine wave. Voltage scale is linear, and a db scale is also provided from -12 to +12. Each voltage scale is related to the next by exactly 10 db. Continuous db readings can be made from -52 to +52 db. (Zero level equals 1 mw in 600 ohms.) Eleven voltage ranges are selected with a single switch. For measurements below 10 cps, a damping capacitor is available to reduce meter point vibration.

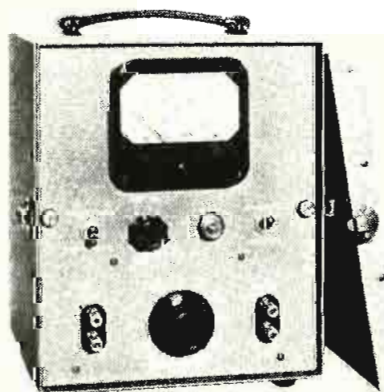


Hewlett-Packard 404A

CALIFONE PORTABLE TRANSCRIPTION PLAYER

A portable transcription unit, model 4-A, which plays up to 17½" transcriptions at 33 1/3 rpm and regular phone records at 78 rpm, has been developed by the Califone Corp., 6041 N. Sacramento Ave., Hollywood 38, Calif.

Unit features a 7½-ounce pickup, 30" turntable, wide-range amplifier. Models available for use on ac or dc operation.

—MICO— 2- & 3-DIMENSIONAL ENGRAVER

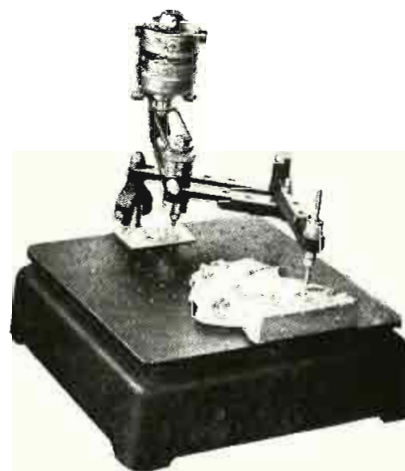

Permits accurate reproduction of three-dimensional master on any of four reduction ratios.

Prompt delivery. Catalogue on request.

Mico Instrument Co.
88A TROWBRIDGE STREET
CAMBRIDGE, MASS.

Ideal for
**ANTENNA CONNECTIONS
PHOTO-CELL WORK
MICROPHONE CONNECTIONS**

JONES SHIELDED TYPE PLUGS & SOCKETS

**LOW LOSS PLUGS AND
SOCKETS FOR HIGH
FREQUENCY CONNECTIONS.
SUPPLIED IN 1 AND 2
CONTACT TYPES:**



101 Series can be furnished with ¼", .290", 5/16", 3/8" or ½" ferrule for cable entrance. Knurled nut securely fastens unit together. Plugs have ceramic insulation and sockets have bakelite. Quality construction. Fine finish. Assembly meets Navy specifications.

For full details and engineering data ask for Jones Catalog No. 16.

**JONES MEANS
Proven QUALITY**

HOWARD B. JONES DIVISION
Cinch Mfg. Corp.
2460 W. GEORGE ST. CHICAGO 18, ILL.

Greatest Advance in V.O.M. History

TRIPLETT Model 630

\$3750

Dealer Net

Adapter Prod For TV High Voltage
Tests Extra

TECH DATA

D.C. VOLTS 0-3-12-60-300-1200-6000, at 20,000
Ohms Volts
A.C. VOLTS 0-3-12-60-300-1200-6000, at 5,000
Ohms Volts
D.C. MICROAMPERES 0-60, at 250 Millivolts
D.C. MILLIAMPERES 0-1-2-12-120, at 250 Millivolts
D.C. AMPERES 0-12, at 250 Millivolts
OHMS 0-1000-10,000; 4-4 Ohms at center scale on 1000
scale, 4-4 Ohms center scale on 10,000 range
MEGOHMS 0-1-100 (4400-440 000 at center scale)
DECIBELS 30 to -4 -16, +30, +44 +56 -70
OUTPUT Condenser in series with A.C. Volt ranges



Note These Sensational Improvements

- ★ Beautiful Streamlined Instrument
- ★ Large 5 1/2 Inch Meter In Special Molded Case Under Panel.
- ★ Resistance Scale Markings from 2 Ohms To 100 Megohms—Zero Ohms Control Flush With Panel.
- ★ Only One Switch—Has Extra Large Knob 2 1/2" Long—Easy To Turn—Flush With Panel Surface
- ★ New Molded Selector Switch—Contacts Are Fully Enclosed.
- ★ Unit Construction—Resistors, Shunts, Rectifier, Batteries All Are Housed In A Molded Base Built Right Over The Switch -- Provides Direct Connections Without Cabling—No Chance For Shorts.
- ★ All Resistors Are Precision Film Or Wire Wound Types—All Sealed For Permanent Accuracy.
- ★ Batteries Easily Replaced—New Double Suspended Contacts.

**A completely new Volt Ohm
Mil-Ammeter that does more...
has proved components... and
will give a lifetime of satisfaction.**

For complete information and technical data write

**TRIPLETT ELECTRICAL INSTRUMENT CO.
BLUFFTON, OHIO**

In Canada: Triplet Instruments of Canada, Georgetown, Ontario

WHEN YOU CHANGE YOUR ADDRESS


Be sure to notify the Subscription Department of COMMUNICATIONS, 52 Vanderbilt Avenue, New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

ELECTRICAL ENGINEER

Graduate engineer with several years experience in audio development work, preferably magnetic recording, wanted for design work. Unusual opportunity and permanent position for right person, with long-established company, vicinity New York City. Reply giving resume of personal data, educational background, experience and salary expected. Write Box C 1699, 113 West 42nd St., N. Y. 18.

JOHNSON INDUCTORS

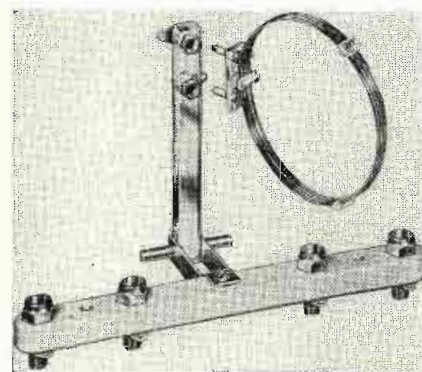A line of air-wound inductors and swinging-link assemblies has been announced by E. F. Johnson Co., of Waseca, Minnesota. Inductors are supported on polystyrene. Available in 150-, 500- and 1,000-watt ratings.



AEROVOX TUBULAR CAPACITORS

Durante cased tubular capacitors have been announced by Aerovox Corporation, New Bedford, Mass.

The casing material, developed by Aerovox is said to provide a permanent rock-hard seal heretofore expected only of metal-cased capacitors.

HYTRON 3B4 V-H-F BEAM PENTODE

A v h-f beam pentode power amplifier, the 3B4, developed to meet U. S. Signal Corps application requirements, has been announced by Hytron Radio & Electronics Corp., 76 Lafayette Street, Salem, Mass. A filamentary-type miniature, the tube is particularly suited to portable/mobile operation from R-M cells or ordinary dry cells.

Instant-heating feature of the 3B4's 1.25/2.5-volt filament is said to eliminate filament drain during standby. Full ratings are applicable up to 100 mc; as a class C amplifier, the 3B4 delivers approximately 1.25 watts.

The 3B4 can be used as an r-f oscillator/amplifier or frequency multiplier in transmitting equipment for civilian light aircraft.

The 3B4 is through its pilot run and is now in regular production. Engineering samples are being shipped from stock.

FURST REGULATED POWER SUPPLIES


An electronically-regulated power supply, designed to serve as a source of d-c power at high voltage and low current, has been announced by Furst Electronics, 800 West North Ave., Chicago 22, Ill.

Two or three independently regulated and independently adjustable outputs are available on models 710-2 and 710-3. Regulated output voltage is continuously adjustable over a range of less than 600 to over 1,500 d-c at 0.1 ma per channel.

ENGINEERING RESEARCH ASSOCIATES MINATURE VARIABLE CAPACITOR

A miniature variable capacitor, with a capacity of 9 to 585 mmfd per section has been announced by Engineering Research Associates, Inc., 1902 West Minnehaha Avenue, St. Paul, Minnesota.

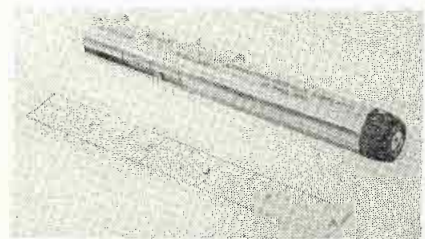Capacitor is said to have less than .002 dissipation factor at r-f. Has self-contained dial with micrometer action. May be temperature compensated, and made up in gauged or single section.




DAVEN MINATURE CONTROLS

A line of miniature attenuators has been announced by the Daven Company, 191 Central Avenue, Newark 4, N. J.

Types include a 1 1/4" ladder type (LA-130) with 30 steps; a 2 1/4" ladder (LA-745) with 45 steps; a tee type, 2 1/4" in diameter (T-730) with 30 steps; and a 2 1/4" tee type for 45 steps.

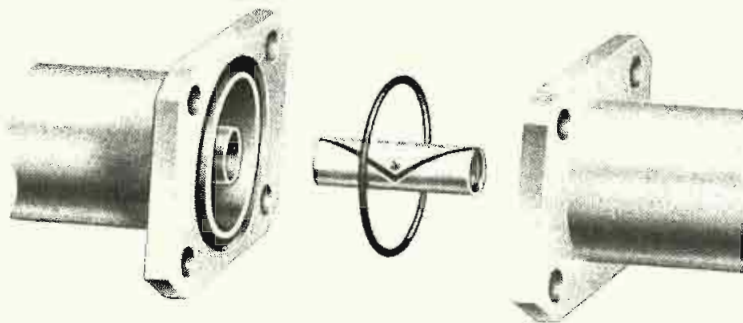WGN-TV SELECTS ANDREW TELEVISION TRANSMISSION LINE *and* ANDREW INSTALLATION SERVICE



Many of America's new television stations are selecting Andrew equipment because of the efficiency of Andrew's flanged coaxial transmission line and the added advantage of having Andrew consulting engineers install it.


Because each television installation poses its own different, individual problem, those stations selecting Andrew have two big advantages: 1) they obtain transmission line and accessories *specially designed for television*, and 2) specialized Andrew consulting engineers are available to direct the installation. These engineers have both the special instruments and the experience to engineer all or any part of the construction of a television station. **NO OTHER TRANSMISSION LINE MANUFACTURER OFFERS YOU THIS COMPLETE INSTALLATION SERVICE!**

Andrew TV transmission line meets official RMA standards and is specially designed for television. Mechanically, it's held to close television tolerances assuring an essentially "flat" transmission line system.

Fabricated in twenty foot lengths with brass connector flanges silver brazed to the ends, sections can be easily bolted together with only a couple of small wrenches. Flanges are fitted with gaskets so that a completely solderless, gas-tight installation results. Markings on the outer conductor indicate where twenty foot sections may be cut to maintain the characteristic 51.5 ohm impedance.

WANT A TELEVISION STATION DESIGNED AND BUILT—FROM THE GROUND UP? LET ANDREW DO IT!

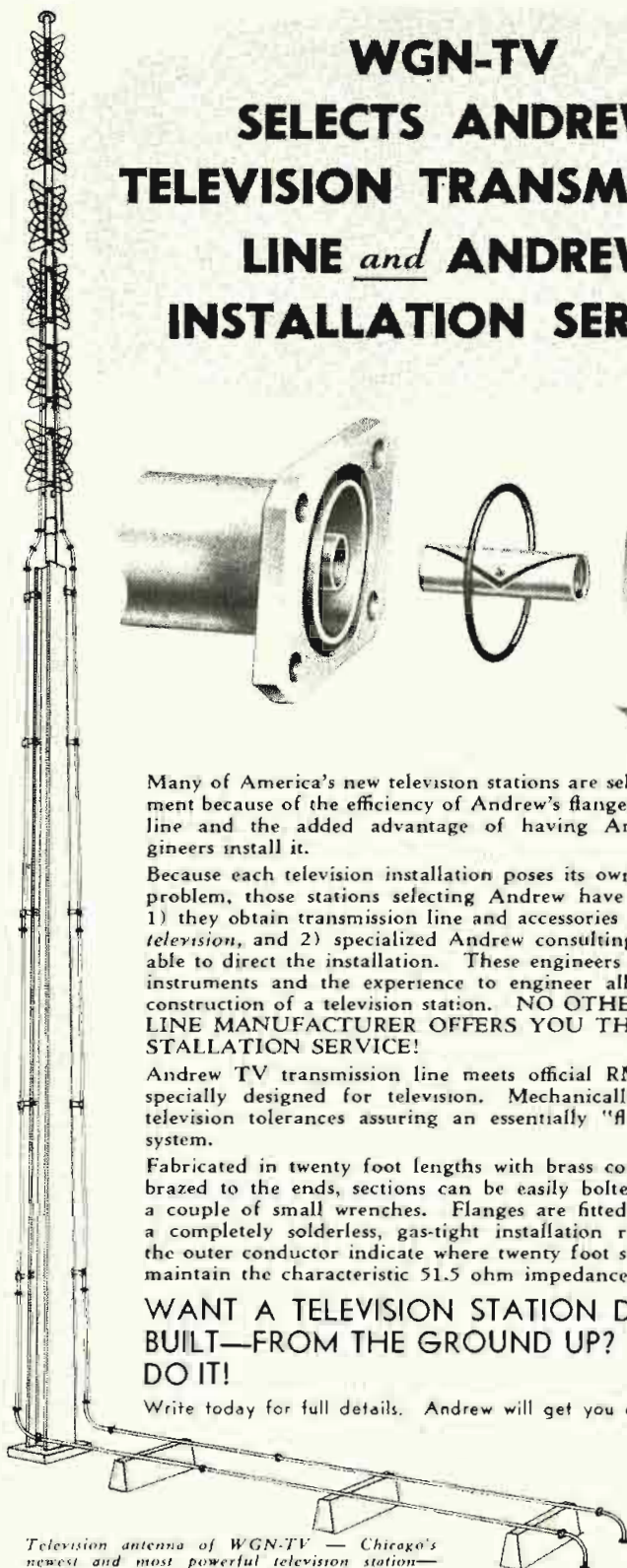Write today for full details. Andrew will get you on the air.



Television antenna of WGN-TV — Chicago's newest and most powerful television station—showing Andrew 1-5/8" flanged television transmission line.

Andrew
CORPORATION

363 EAST 75th STREET • CHICAGO 19


TRANSMISSION LINES FOR AM, FM, TV • DIRECTIONAL ANTENNA EQUIPMENT • ANTENNA TUNING UNITS • TOWER LIGHTING EQUIPMENT • CONSULTING ENGINEERING SERVICE

ADVERTISERS IN THIS ISSUE

COMMUNICATIONS INDEX

JUNE, 1948

ANDREW CO. Agency: Burton Brown Advertising	40
BELL TELEPHONE LABORATORIES Agency: N. W. Ayer & Son, Inc.	8
BENDIX AVIATION CORP. RED BANK DIV Agency: MacManus, John & Adams, Inc.	23
BENDIX RADIO DIV. BENDIX AVIATION CORP. Agency: MacManus, John & Adams, Inc.	30
CANNON ELECTRIC DEVELOPMENT CO. Agency: Dana Jones Co.	26
THE CLEVELAND CONTAINER CO. Agency: The Nesbitt Service Co.	27
EITEL-McCULLOUGH, INC. Agency: J. C. Cole Advertising	Back Cover
FERRANTI ELECTRIC INC. Agency: Root Martin, Inc.	1
GENERAL RADIO CO.	Inside Back Cover
HEWLETT-PACKARD CO. Agency: L. C. Cole Advertising	24
HUGHEY & PHILLIPS Agency: Welsh-Hollander Advertising	31
E. F. JOHNSON CO. Agency: Rudolph Bartz Advertising	39
HOWARD B. JONES DIV. CINCH MFG. CORP. Agency: Merrill Symonds Advertising	38
LENZ ELECTRIC MFG. CO. Agency: Triangle Adv. Agency	5
MICO INSTRUMENT CO.	38
JAMES MILLEN MFG. CO., INC.	28
OMEGA LABORATORIES, INC. Agency: George C. Felt	36
THE OKONITE CO. Agency: Doyle, Kitcher & McCormick, Inc.	37
PAR-METAL PRODUCTS CORP. Agency: H. J. Gold Co.	30
PHILCO CORPORATION Agency: Hutchins Adv. Co.	4
PHILCO CORPORATION Agency: Julian G. Pollock Co.	17
PREMAX PRODUCTS DIV. CHISHOLM-RYDER CO., INC. Agency: Norton Adv. Service	26
PRESTO RECORDING CORP. Agency: Roy S. Durstine, Inc.	15
RADIO CORPORATION OF AMERICA Agency: J. Walter Thompson Co.	18, 19
SHALLCROSS MFG. CO. Agency: The Harry P. Bridge Co.	29
SORENSEN & CO., INC. Agency: Henry A. Stephens, Inc.	Inside Front Cover
SPRAGUE ELECTRIC CO. Agency: The Harry P. Bridge Co.	7
SYLVANIA ELECTRIC PRODUCTS, INC. Agency: Newell Emmett Co.	3
TECH. LABORATORIES, INC. Agency: Lewis Adv. Agency	34
TERMINAL RADIO CORP. Agency: Berthman-Jarrett Co.	34
TRIPLETT ELECTRICAL INSTRU. CO. Agency: Western Adv. Agency, Inc.	39
WARD LEONARD ELECTRIC CO. Agency: Henry H. Tepitz, Adv.	35
WILCOX ELECTRIC CO. Agency: Arthur G. Rippey & Co.	6

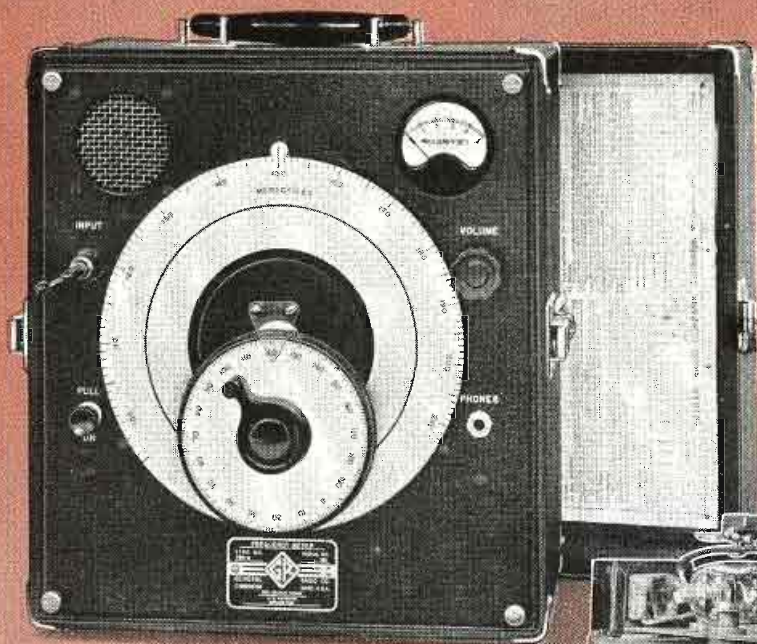

FREQUENCY MEASUREMENTS TO 3,000 Mc

FULL advantage of the simplicity of the heterodyne method of frequency measurement is taken in this frequency meter. With a fundamental range of 100 to 200 megacycles, accurate frequency measurements may be made between 10 and 3,000 megacycles.

The tuning circuit is our butterfly type with no sliding contacts, obviating many of the difficulties encountered in the usual tuning elements used in u-h-f equipment.


A standard plug-in silicon crystal is used as the detector, followed by a three-stage audio amplifier. The band width of the amplifier is 50 kc to permit visual beat indication even if the signal under measurement is unstable.

For very strong signals beat indication may be obtained either aurally from the built-in dynamic loud speaker or visually from the panel meter. For weak signals a telephone jack is provided for headset detection.

Normally no direct connection to the signal under measurement is required, the retractable 'antenna' providing the necessary coupling. On weak signals, terminals are provided for additional pick-up if necessary.

This instrument is finding wide application both in the laboratory and in the field where a portable, self-contained, stable and accurate heterodyne frequency meter is needed for measurements over a very wide range of high and ultra-high frequencies.

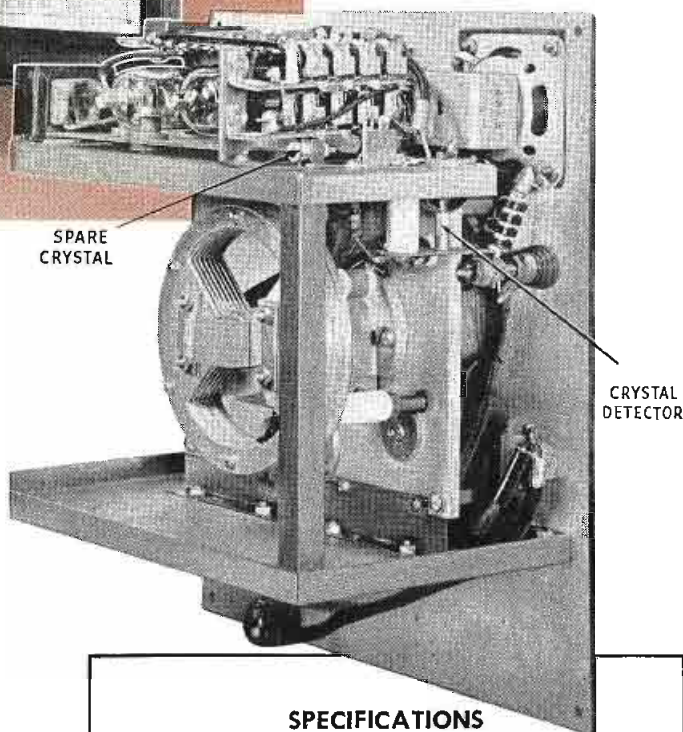TYPE 720-A HETERODYNE FREQUENCY METER \$340



SPECIFICATIONS

FREQUENCY RANGE — fundamental range of instrument is 100 to 200 Mc; by harmonic methods measurement range is 10 Mc to 3,000 Mc.

CIRCUIT — our butterfly tuning unit used in the oscillator; crystal detector (with spare); 3-stage audio-frequency amplifier.

BEAT INDICATORS — built-in dynamic loud speaker and panel meter for aural and visual beat indication; telephone jack for headset indication from weak signals.

ACCURACY — over-all accuracy is $\pm 0.1\%$

CALIBRATION — main dial calibrated in frequency, each division being 1 Mc; one-half turn of vernier dial corresponds to approximately 1% change in frequency over entire tuning range.

PORTABILITY — instrument weighs only 27½ pounds complete with batteries. Separate a-c power supply may be ordered for a-c operation.



GENERAL RADIO COMPANY

Cambridge 39,
Massachusetts

90 West St., New York 6

920 S. Michigan Ave., Chicago 5


950 N. Highland Ave., Los Angeles 38

15 WATTS AT 940.5-Mc. with the EIMAC 4X150A TETRODES

KSBR
STL Transmitter

FREQUENCY UP 6X, (156.75-Mc. to 940.5-Mc.)
POWER UP 7X (2 watts to 15 watts)

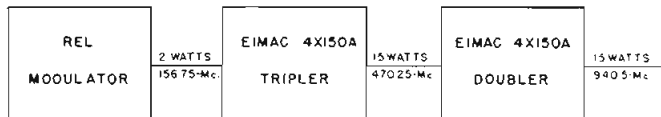Here's a STL transmitter that's in operation on the new 950-Mc. band, fulfilling all the FCC requirements and powered by Eimac 4X150A tetrodes. It's a part of the studio-transmitter-link between the San Bruno studios and the 250 Kw FM transmitter of station KSBR high atop 3849-foot Mt. Diablo some 33 miles away.




The R-F amplifier was specifically designed for the KSBR application by Eimac engineers. It is driven by an REL modulator delivering 2 watts output at 156.7-Mc. to one Eimac 4X150A in a tripler stage, which in turn drives a single 4X150A in a doubler stage, providing 15 watts useful output at 940.5-Mc.

The Eimac 4X150A is ideally suited for this application because of its high power gain at relatively low plate voltages, ability as a frequency multiplier without loss of amplification, low grid drive requirements, and a high ratio of transconductance to capacitance. It also has the advantage of being physically small and functionally designed for simple installation.

Complete data on the Eimac 4X150A for STL and other UHF applications is available by writing direct.

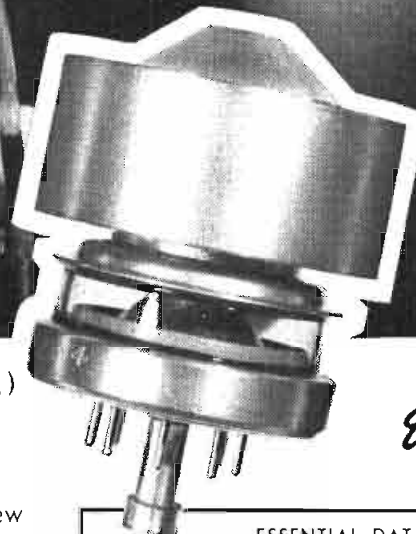EITEL-McCULLOUGH, INC.
197 San Mateo Avenue, San Bruno, California
EXPORT AGENTS: Frazer & Hansen—301 Clay St.—San Francisco, Calif.



Eimac
4X150A

ESSENTIAL DATA KSBR STL TRANSMITTER

REL MODULATOR, MODEL 694
EIMAC 4X150A, R-F AMPLIFIER

Useful Output Power - - - - - 15 watts
Frequency - - - - - 940.5 Mc.
Frequency Stability - - - - - .002%
Audio Frequency Response.
Substantially flat - - - - - 50 to 15,000 cycles
Distortion - - - - - .5% Max.
Noise Level - 70 db below 100% modulation
- - - - - ± 100 Kc. deviation

Eimac 4X150A General Characteristics

Heater voltage - - - - - 6.0 volts
Heater current - - - - - 2.8 amps.
Minimum heating time - - - - - 30 secs.
Grid Screen amplification factor - - - - - 4.5
Direct interelectrode capacitance (Average)
Grid-Plate - - - - - 0.02 μ f
Input - - - - - 14.1 μ f
Output - - - - - 4.7 μ f

Maximum Ratings

D-C Plate voltage - - - - - 1000 volts
D-C Plate current - - - - - 250 ma.
Plate dissipation - - - - - 150 watts
D-C Screen voltage - - - - - 300 volts

Follow the Leaders to

Eimac
TUBES
The Power for R-F