AUSTRALIA'S DYNAMIC ELECTRONICS MONTHLY!

LEHALDODO

Electronics



GUIDE TO CIRCUIT FAULT FINDING PROJECTS: MIDI MUSIC INTERFACE FORTH CONTROLLER INTELLIGENT MODEM POWER SUPPLY

eti

**\$2.75\*** NZ \$3.50

**MARCH 1986** 

## The critics have put it on a pedestal. (But it sounds better on a speaker stand.)



# Wharfedale

wharfedale/2

Distributed by: N.Z. MARKETING PTY. LTD. Phone (02) 938 4077

ETI READER SERVICE 126

#### EDITOR David Kelly B.Com.

ASSISTANT EDITOR Jon Fairall B.A.

EDITORIAL STAFF Mary Rennie B.A. S. K. Hui B.Sc. (Hons), M.Eng.Sc., MIEEE Neale Hancock B.E.

DRAUGHTING David Burrows

ART DIRECTOR Vickl Jones

ART STAFF Gary Gray Ray Einth

ADVERTISING MANAGER Peter Hayes B.Sc.

ADVERTISING PRODUCTION Wayne Hanley

READER SERVICES Pam Todd

**ACOUSTICAL CONSULTANTS** Louis Challis and Associates

PUBLISHER Michael Hannan

HEAD OFFICE 140 Joynton Avenue, (PO Box 227) Waterloo, NSW 2017. Phone: (02) 663-9999 Sydney. Telex: 74488, FEDPUB, Federal Facsimile: 662-1007.

ADVERTISING OFFICES AND AGENTS:

New South Wales: Peter Kilby, Mark Lewis, The Federal Publishing Company, 140 Joynton Avenue, Waterloo.

Victoria and Tasmania: Virginia Salmon, The Federal Publishing Company, 23rd Floor, 150 Lonsdale Steet, Melbourne, Vic. 3000. Phone: (03) 662-1222. Telex: 34340, FEDPUB.

South Australia and Northern Territory: Brendan Mahoney, John Fairfax & Sons, 101-105 Waymouth Street, Adelaide, 5000. Phone (08) 212-1212. Telex: 82930

Queensland: John Perry, The Federal Publishing Company, 25 Balaclava Street, Woolloongabba, Qid. 4102. Phone: (07) 391-8922. Telex; AA145520.

Western Australia: Tony Allen & Associates, 7 Fore St, Perth, WA 6000. Phone: (09) 328-9833.

New Zealand: Chris Horsley, 4A Symonds Court, Symonds Street, Auckland, Telex: NZ60753, TEXTURE, Phone: 39-6096, Auckland,





ELECTRONICS TODAY INTERNATIONAL is published monthly by the Electronics Division of the Federal Publishing Company Pty Limited, 140 Joynton Avenue, Waterloo, NSW 2017 under licence from Double Bay Newspapers Pty Limited, General Newspapers Pty Limited and Suburban Publications Pty Limited. Typeset and printed by SN-The Litho Centre, Sydney. Ostributed by Gordon and Gotch Limited, Sydney. 'Maximum and recommended Australian retail price only. Registered by Australia Post, Publication No NBP0407. ISSN No 0013-5216.


COPYRIGHT <sup>©</sup> 1985, Double Bay Newspapers Pty Limited, General Newspapers Pty Limited and Suburban Publications Pty Limited (trading as "Eastern Suburbs Newspapers").

# ectronics



	NIN IN	Questin Strates	
<b>T</b>	INVIE INVIE	FEAT	URES
Teaching the electronic Instilling the lessons with mic	brain	or development systems	1
Computer aided electro	the second se		
Hewlett-Packard's bid to lead	the field	orgin	40
Starting electronics: fir	ding the	ose faults	7
The spectrum analyser	expose	d	94
Looking for clearer freq While you search the dial, bro	uencies adcasters	s shift around too	111
Perpendicular Magnetic Could tape outshine compact	disk?	ling	72
		PROJ	ECTS
ETI-609: Midi thru box Provides ports for instruments	to output	MIDI data simultaneously	50
ETI-697: Simple Forth c			58
ETI-684: Intelligent mod			67
Getting the power supply toge	ether	And the second second	01
		REV	IEWS
8 mm VCR challenges to	p CD pl		22
Wharfedale woos the ma		1 Particular Inc.	30
The 708 loudspeakers offer so	mething n	iew	00
Low cost IBM compatibi	lity		89
Under analysis	111		101
A spectrum analyser from Anri	tsu put to	the test	
Micros join the measure	ment re	volution	108
f you thought your old CRO w	as safe, d	on't look now!	
		OF	FERS
Advertisers' index			108
TI mail order books			98,99
Energy Control offer			66
Subscriptions offer	_		106
		DEPARTMI	ENTS
Vews Digest	6	Ideas for Experimenters	48
etters	10	Idea of the Month	49
Sight and Sound News	19	Microbee Column	85
lew Components	38	Commodore Column	87
lew Equipment	42	Shoparound	96
Computing News	83	Minimart	96
Communications News	91	Dregs	114
	_		

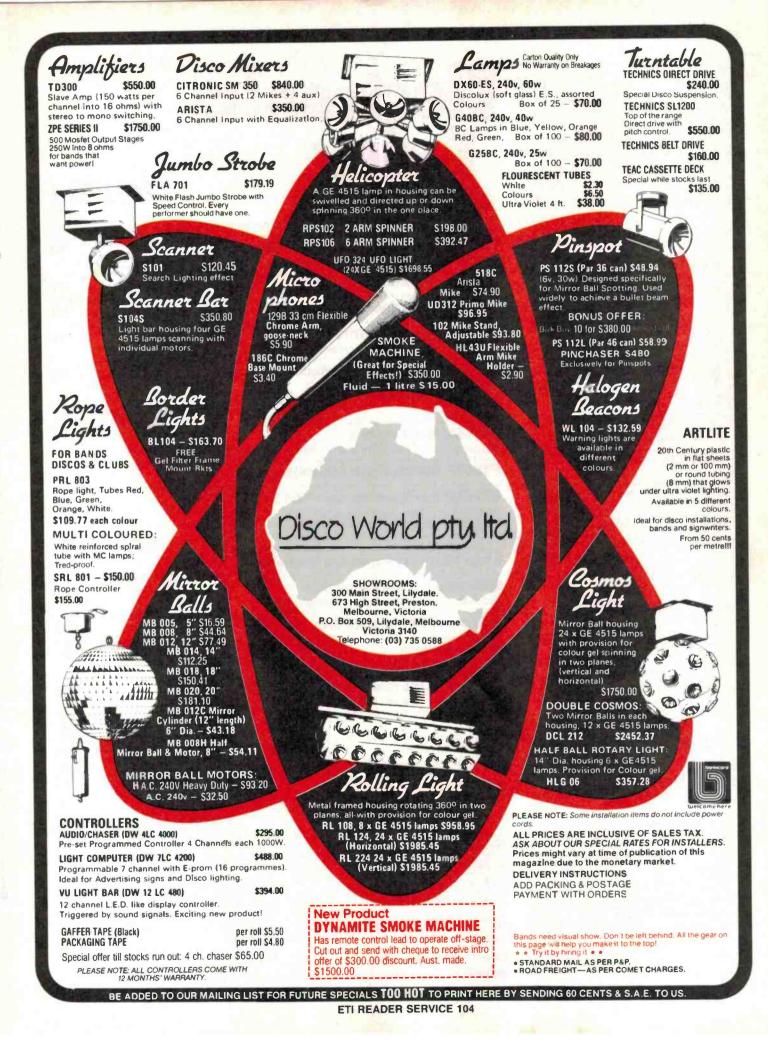COVER: Design by Vicki Jones, photographed by Mario Borg and Helmut Mueller.



## EDITORIAL

## SERVICES

TECHNICAL INQUIRIES: Technical inquiries by mail must be accompanied by a stamped self-addressed envelope. There is no charge, but we reserve the right to publish the inquiry and the reply in Electronics Today or any of its associated publications. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. Difficult questions may take some time to answer.

GENERAL INQUIRIES: For all inquiries about back issues, subscriptions, photocopies of articles, atwork or submitting articles, call (02) 663-9999 or write to: ETI Reader Services, 140 Joynton Avenue (PO Box 227), Waterloo, NSW 2017.

CONTRIBUTIONS: Submissions must be accompanied by a stamped, selfaddressed envelope. The publisher accepts no responsibility for unsolicited material.

COPYRIGHT: The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968). Copyright extends to all written material, photographs, drawings, circuit diagrams and printedcircuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by bands (for example) constructing one or more items for use in connection with their performances. Commercial organisations should note that no project or part project described In Electronics Today International or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publisher, The Federal Publishing Company, or from the copyright holders,


LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

IT COMES AS A SURPRISE to many Australians that the respected United Nations bodies, the World Bank and the International Monetary Fund, do not regard Australia as even a member of the first world, the world's developed countries.

Obviously we are not regarded as one of the underdeveloped countries described as the third world, but somewhere in the middle in a not so large group called developing. We are not regarded as developed because we have not been able to support a manufacturing industry with much of its sales in the export market.

As well, a very large part of Australia's commercial activities are in primary industry and very rudimentary manufacturing. While I certainly would not down play the importance of these more basic industries to the country's welfare, they are regarded in some circles as a sign of a 'not so advanced' nation.

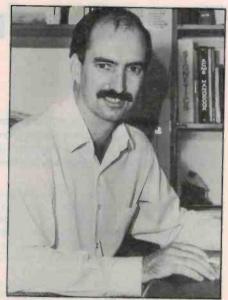As I said, all this will come as a great surprise to many, but for some it is not surpris-



ing at all. So it is that technology has become the flavour of the month, or year, or decade, in Australia.

Though rarely described in so ruthless a fashion there have been many valiant efforts to raise Australia's awareness and actions.

Some of the best efforts have come from schools, which, with virtually no resources, have embraced what part of technology they can. The result will be not just a lot of computer programmers but many accountants, doctors, market researchers, builders and plumbers who are comfortable using computers as work tools.

An admirable effort indeed, but just when many people in schools might be about to congratulate themselves, I would like to say they simply scraped the top of the technology iceberg. There are many areas of technology, some more general than others. Computers is a very generally applied area, slightly more specific and much harder to come to grips with is electronics hardware.

Electronics pervades many areas of the manufacturing industry in both products and the processes used to make products. In the future it will be a vital element in most successful manufacturing businesses.

We don't just need electronics engineers and technicians but a whole range of people in other disciplines who are comfortable in their understanding of the limitations and capabilities of electronics.

As a magazine we can play a small part. Our "1986 High Schools Electronics Competition" will hopefully raise the general level of interest in electronics among those who in not too many years will control Australian industry.

> David Kelly Editor

#### CAR AUDIO

ETI goes for a drive to check out what's been happening In car audio. The two new things on the scene are CD players and AM stereo. We look at their influence, offer a few tips on installing systems, mounting speakers and have words on some other exotic accoutrements.

## MICRO-MINIATURE FM BUG

When Slemens challenged us to build the 751 miniature FM transmitter with surface mounting components, we jumped. In the end, it was Philips that came through with the parts and the know-how (with an article on surface mounting) and with this help we made a few innovations; this time we're building a surface mount receiver as well, and changing the frequency to 27 megs.

## NEXT MONTH

## LAS VEGAS CES

The Winter CES in Las Vegas is very, very blg. All the new gear for 1986 Is polished up and displayed, visitors are dazzled. But it doesn't faze Louis Challis who marched up and down the rows and rows of CDs, videos, TVs, hi-fl and took in a few other things as well.

#### REVIEWS

Under scrutiny next month are the Yamaha YCD1000 car CD player, the Sony XR-A740 AM stereo receiver, the Amstrad CPC6128 PC and (not forgetting basic engineering skills) the Scope soldering workstation.

## **NEWS DIGEST**

# Results from comet

Scientists from the US, France, the United Kingdom and West Germany have released their findings from the rendezvous of the International Cometary Explorer (ICE) spacecraft with Comet Giacobini-Zinner (the world's first such rendezvous) on 11 September 1985.

The data was collected by NASA's Goddard Space Flight Centre, Greenbelt, Maryland. Perhaps the most unexpected result was detection of electrical wave (plasma) disturbances and high speed, molecular species coming from the comet more than a day before the rendezyous. Detection of the electrical waves was made while ICE was 1,429,200 miles away from the comet. Scientists had theorised that first detection might occur just a few hours before the spacecraft crossed the comet's tail.


A few hours after initial detection, but still one day prior to the intercept, two of the ICE's instruments discovered electrically-charged particles (ions) as far as 1,130,000 miles from Giacobini-Zinner.

According to Dr Robert Hynds, of Imperial College, London, who directed the energetic proton experiment, it is believed that the gas molecules escaping from the comet's nucleus were ionised by solar ultraviolet light and then picked up and accelerated back toward the comet by the solar wind, a constant outpouring of magnetised, electrified gas from the sun.

Discovery of the plasma waves and 'pick-up' of the ions at great distances from Comet Giacobino-Zinner prompted Dr John C. Brandt, ICE comet scientist at Goddard, to predict a possibly larger role for the spacecraft than earlier planned. Brandt reasoned that, "the results from the ICE encounter leads to the conclusion that ICE may directly detect Halley". The results also indicate that Halley measurements by other spacecraft should be initiated earlier than previously planned.

It had been expected earlier that ICE, while between Comet Halley and the sun in late March and early April 1986, would gather data only on variations in the solar wind to compare with the resulting disturbances caused in the comet's tail as photographed by ground telescopes.

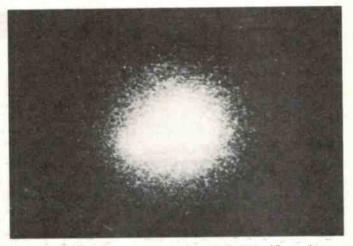In another finding, Dr Samuel I Bame, of the Los Alamos National Laboratory, reported that in contrast to the hot electrons on the outskirts of the comet, its tail consisted of a dense, parrow structure of cool plasma. This



The comet under most attention now: Comet Halley. The ICE expedition confirmed the 'dirty snowball' theory of comet composition.

finding was also made by the radio wave experiment of the Meudon Observatory in France.

The ICE's ion composition experiment, directed by Dr Keith Ogilvie of Goddard, made the first direct measurements of molecules in a comet. The experiment found mainly water vapour ions  $(H_2O+)$ , confirming the 'dirty snowball' model of comets.

A major prediction confirmed by the ICE data was that the magnetic structure of the comet's plasma tail consisted of two parallel lobes, each threaded by a magnetic field of opposite polarity. This structure, predicted by Nobel physicist Dr Hannes Alfven in 1957, was mapped by ICE's magnetometer experiment.

Putting conflicting scientific conjecture to rest, the ICE mission revealed that no clear-cut bow shock — a surface moving ahead of the comet like that through which a jet aircraft passes as it breaks the sound barrier — accompanied the comet. Instead, experimenters found a transition region around the head of the comet, in which the solar wind has been heated, compressed and slowed.

Neither the ICE spacecraft nor its instrument payload suffered any detectable damage as a result of the impact with the comet's dust. In the historic intercept mission, ICE sliced through the 14,000 mile wide tail of the comet, 4800 miles behind the cometary nucleus. Travelling at 46,000 miles an hour, ICE emerged from the tail approximately 20 minutes later.

The encounter was a high point of a seven year odyssey through space for ICE, launched in 1978 as the International Sun-Earth Explorer. The spacecraft was diverted to fulfil its comet rendezvous at the suggestion of Goddard engineer Dr Robert Farguhar. Farguhar, after thousands of computer simulations, engineered the ICE past the moon five times in 1983, using lunar gravitational help to give the spacecraft the additional thrust necessary for the intercept.

## Doh re me VDU

Bridging the chasm between the creative inspiration that produces a new piece of music and the laborious job of translating it into the thousands of crotchets and quavers of musical notation is a new pitch recognition system that writes each note as it is played, stores what it 'hears' and will play it back on command.

Developed at Cardiff University Industry Centre the system combines a microphone, signal

6 - ETI March 1986

processor and versatile graphics software. The first two programs are designed for the descant recorder. One is essentially an introduction to the instrument and lets very small children choose a cartoon character which jumps into position on the musical staff as they play each note. Simultaneously a simple diagram appears on the screen showing which holes to cover to produce the notes that make up the chosen tune. As the child's technique improves the prompt diagram cuts out, only reappearing when the same mistake is repeated.

More sophisticated is the tutorial program which takes the player from basic instruction on how to produce each note through to instant notation and playback of the composition. The finished piece can then be printed using a standard word processor printer.

The pitch processor also has obvious applications outside music such as a security device for industry — allowing access only on a recognized specific sequence of notes — or even geared to monitor the performance of machinery by signalling changes in the pitch of electrical motors.

## BRIEFS

## Australian cable in Telecom's fibre optics link

The first section of Telecom Australia's new optical fibre cable network is now being ploughed in at Gundaroo, 50 kms north of Canberra. The cable used in this initial link in the Sydney-Melbourne telecommunication trunk route is being manufactured by Austral Standard Cables Pty Ltd at its Clayton, Victoria, plant.

## Mel Ward to lead Telecom Australia

Telecom Australia's chief general manager, Mel Ward, has been appointed managing director of the organisation following the resignation of W.J.B. Pollock AM, to take effect in April.

## Fault diagnosis system uses laser probing

National Panasonic's parent company, Matsushita Electric Industrial Co of Japan, has announced that its semiconductor research centre has developed a laser probing technique for VLSI fault diagnosis. The system improves the fault diagnosis processes of VLSIs assembled in sub-micron rule, resulting in an efficient design evaluation and enhanced reliability.

## Rural telecommunications system for OS markets

Telecom and NEC Australia have signed an historic agreement for a joint enterprise to sell the Australian Digital Radio Concentrator System (DRCS) on the international market. The solar-powered DRCS system was conceived by Telecom's research engineers and is manufactured in Australia by NEC at its Mulgrave plant.

## Funding for IC fabricating machine

The Enhanced Discharge Silicon Wafer Dry Etching Project will receive government funding of \$370,000 over 10 months under the Australian Industrial Research and Development Incentives act. The project will be carried out by Unisearch Pty Ltd on behalf of the University of New South Wales where the enhanced discharge concept has been developed by Dr Chris Horwitz, in the university's electrical engineering department laboratories.

## New era in external uni education

Deakin University in Victoria is participating in an educational revolution that in the next 12 months will see the establishment of a telecommunications network linking tertiary institutions with students throughout the country.

## **Electronics 86 show**

Electronics 86, the fifth Australian international electronics and computer technology exhibition and conference, will be held from 7-9 October 1986 at the Royal Showground, Adelaide. The show is sponsored by the Electronics Association of South Australia (EASA) and this year will be organised by Australian Exhibition Services (AES) Pty Ltd. For further information contact AES on (03) 267-4500.

## Mazda's delivery van of tomorrow

Mazda Motor Corporation has unveiled a prototype of tomorrow's delivery van, the Mazda Telecom Delivery, which is intended to function as 'an office on wheels'. Combining innovative vehicle design with the latest telecommunications and computer technologies, it is equipped with a full-function computer terminal connected with the main head office computer.



## NASA suspects possible ancient civilisation

Using remote sensing technology, NASA's National Space Technology Laboratories (NSTL), and the University of Colorado at Boulder, have uncovered information that suggests a civilisation existed in the subtropical Peruvian jungles. prior to the Incas.

Tom Sever, NASA's principal investigator, and Tom Lennon, archaeologist and co-director of the university's Rio Abiseo National Park Project, jointly completed a five-day expedition into the jungles of Peru's Rio Abiseo National Park after remote sensing, by satellite and aircraft, permitted the explorers to map and select the field investigation sites.

Prior to the field exploration,

Cerro Central, the largest site including more than 250 buildings, was discovered by the remote sensing operation. The ancient site of Gran Pajaten, which included only 30 buildings, previously had been the major point of interest. Sever said, "We know now that Pajaten is probably the smallest and least important of the sites. We are fairly confident that we have approached the very edges of a new civilisation and we believe that the farther in we go, the higher and more complicated the elevation of architecture and civilisation will be"

Sever said some plant and animal species, thought to be extinct, were discovered. "That is the reason the expertise of more than 30 support people and interdisciplinary scientists was required on the expedition.

A materials dating process is currently under way to determine when the civilisation existed. Sever continued, "Our guess right now is that the civilisation was pre-Inca because the architecture is circular and statuary have very delicate motifs, in comparison with the Inca ruins which are long, narrow structures with corner bases. This civilisation built in a totally different and perhaps more advanced achitectural style than has been seen in the Inca civilisations".

NSTL was asked to collaborate in the investigation with the University's Anthropology Department because of the installation's expertise in satellite remote sensing and image analysis.

According to Sever, NSTL remote sensing specialist and archaeologist, the investigation represents the best example of remote sensing application and perhaps the only known means by which the objectives of this project could be obtained. "The job certainly could not be accomplished on foot or by ground survey. We are dependent upon remote sensing because the jungle-cloud-forest environment is treacherous and extensive. Thus, we needed to select where to send the field investigators."

## **NEWS DIGEST**

## IBM Australia at World Expo 88

IBM Australia has announced plans for a major technical pavilion at World Expo 88.

Its plans for a display, covering 1000 square metres on the Expo site, represent the largest corporate pavilion commitment to date.

The announcement of IBM Australia's participation in Expo 88 was made at a luncheon hosted by the Queensland Premier, Sir Joh Bjelke-Petersen, at Parliament House.

Sir Joh welcomed IBM Australia's decision to participate in the Expo. He said the decision underlined corporate recognition of the value of World Expo 88. He said it was another sign that Expo would be a major success.

The Expo Authority's chairman, Sir Llewellyn Edwards, said discussions were continuing between the Expo Authority and IBM Australia in relation to the Expo's computer and word processing requirements. Managing Director of IBM Australia, Mr Brian Finn, said the total investment by IBM Australia would be more than \$3 million, but this could increase during the run-up to Expo. "Although the contents of

"Although the contents of the IBM display have not yet been finalised, it will reflect IBM's position as a leader in the technology industry," Mr Finn said.

"Expo 88 is a major bicentennial project and the first Expo to be held in Australia this century. Obviously, it is an important and historic event and, as a leader in the information technology industry, IBM is pleased that it can make such a positive contribution."

More than 30 countries and 20 corporations are expected to exhibit under the Expo's theme 'Leisure in the Age of Technology'.

The corporate commitment to World Expo 88 is now worth more than \$23 million.

#### **CRO winners**

Congratulations to the winners of our ETI-Dick Smith Electronics CRO Competition (ETI, Nov 85). They were Wen Liang Soong of Fullarton, SA, and B.G. Sloss of Canterbury, Vic, whose entries were the first correct ones opened.

Both winners were recently presented with their prizes lightweight 6.5 MHz CROs from DSE, which bring the facility of a laboratory oscilloscope to the home workbench.

Condolences to the hundreds of entrants who weren't successful, but keep watching ETI for more great competitions. Better luck next time!

## International standards to help high-tech

Many Australian businesses, particularly manufacturers of high-technology products, will benefit from recent agreements between this country and both the UK and USA.

Science minister Barry Jones, announced that the CSIRO National Measurement Laboratory has exchanged statements with the corresponding UK and USA laboratories to recognise the equivalence of six of the most basic primary standards of measurement: length, time, temperature, voltage, capacitance and resistance.

"This mutual recognition of equivalence should assist many Australian businesses, particularly manufacturers of hightechnology products who are required to satisfy stringent technical specifications set by UK or US partners," Mr Jones said. The minister added that in the past it had sometimes been difficult to convince foreign companies that Australian based measurements would fully satisfy their requirements.

The new statements recognise

an extremely high degree of equivalence between the national standards. For example, the standards of electric resistance are equivalent to within two parts in one million, the standards of length to within two parts in one thousand million, and the standards of time and frequency to within two parts in ten million million.

The first of the agreements was reached in London on 28 October last year when Dr W. R. Blevin, CSIRO's chief standards scientist, signed and exchanged statements of recognition with the director of the UK National Physical Laboratory, Dr P. Dean. The second agreement was signed three days later when Dr Blevin exchanged similar documents with the director of the National Bureau of Standards, Dr E. Ambler in Washington.

Copies of the statements of equivalence are available from Dr Paul Hewitt, CSIRO Division of Applied Physics, National Measurement Laboratory, PO Box 218, Lindfield, NSW 2070.

## COMPANY NEWS


The Canadian video terminal manufacturer, Volker-Craig Ltd, is now represented in Australia by Databridge Electronic Communications of 604 North Rd, Ormond, Vic 3204. (03)578-0814. Parameters of Sydney has moved to larger, modern premises. The new address is Centrecourt, 25-27 Paul St Nth, North Ryde, NSW 2113. (02)888-8777.


## NOTES & ERRATA

Project 169, Low distortion audio oscillator Pt 2, November '85: Resistors, R38-R49, are labelled incorrectly on the overlay. The right ordering is reprinted herewith. Also on the overlay, the pc board track from pin 2 IC3 was shown leading to pin 16 IC5. Rather it should lead to pin 15 IC5. To correct this, cut the track from pin 2 IC3 at pin 16 IC5, and attach fly wire between the cut track and pin 15 of IC5. The correct layout is also reproduced.

Project 689, Bus sharing for the Commodore, January '86: Diode D3, on the overlay should read ZD1 as per the parts list.

Project 142, dc Power Supply, February 1979: The circuit and wiring diagrams for this project contain a mistake that all builders should be aware of — even at this late stage. Wires from the transformer T1 (PF4244 240V/32V 300 VA) are incorrectly labelled orange and white on the circuit. They should be transposed so that 'orange' should connect to the rectifier rather than 'white' as is shown, and 'white' should connect to the circuit board instead of 'orange'.

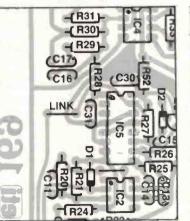

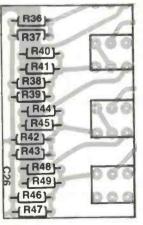

8 - ETI March 1986

Glover & Assoc. PM5810

All digital meters feature Easy to read LCD displays Overrange and low battery indicators 

Overload protected on all ranges • 10A current ranges 

Diode test Complete with case and probes 12 month no-nonsense warranty

1

### 1. 7040 31/2 digit DMM 33 ranges 0.1% DCV accuracy

\$99.00 2. 7080 31/2 digit DMM 37 ranges 0.1% DCV accuracy Capacitance measurement - HFE measurement \$128.80

# Test us

No matter what you're after in a multimeter, Parameters has it. Top value digitals and analogues, clamp meters and probe testers.

## 3. 8040 41/2 digit DMM

0 100 50

6

31 ranges 0.05% DCV accuracy HFE measurement Audible continuity test \$207.25

3

4. CM100 Capacitance Meter 6. 2010BZ multimeter 31/2 digit, 0.1% accuracy 8 ranges 0.1 pF-2000µF

\$171.35

#### 5. 260 Clamp meter AC current to 1000A

8

4

OHMS 0 50 30 20 7

AC 750V, DC 1000V Resistance to  $2M\Omega$ **Diode test** \$194.35 24 ranges, 20,000Ω/VDC

- Continuity buzzer \$39.68
- 7. 5050E FET multimeter 43 ranges including 0.1µA DC and 12A AC Input imp. approx.  $10M\Omega$ Polarity reversal switch \$85.68

5

8. 2447 Circuit tester A convenient probe-style multimeter. 12 ranges + continuity test DCV, ACV and resistance \$108.10

Parameters Pty Ltd. SYDNEY: 25-27 Paul St. North Ryde NSW 2113. (02) 888 8777. MELBOURNE: 1064 Centre Road, Oakleigh South, Vic. (03) 575 0222

ADELAIDE: Trio Electrix (08) 212 6235. BRISBANE: LE Boughen & Co. (07) 369 1277. HOBART: Imbros (002) 34 9899. NEWCASTLE: DGE Systems (049) 69 4242. PERTH: WJ. Moncrieff (09) 325 5722. TOWNSVILLE: Nortek (077) 79 8600. WOLLONGONG: Macelec (042) 29 1455. CAIRNS: Thompson Instrument Services (070) 51 2404.

PERFECTION IN MEASUREMENT

**PARAMETERS** 

Due to currency fluctuation prices are subject to change without notice. All prices are recommended only and include sales tax. Tax free prices on request.

## Letters to the Editor

## The great audio swindle

I WISH TO take issue with some of the claims made by the proponents of CD players.

The maximum peak sound level encountered in a live performance is approximately 120 dB SPL for a symphony orchestra, and can easily go higher in amplified music concerts. In a quiet hall, the background noise level is often lower than 20 dB SPL, when weighted correctly to account for the ear's frequency response at this volume. This amounts to a dynamic range of over 90 dB for live music.

Unfortunately, the two most popular forms of storing recorded music today, records and cassette tapes, have dynamic ranges much less than the 90 dB of live music. Conventional records generally have 45 to 50 dB dynamic range, while the more carefully prepared audiophile pressings have slightly over 60 dB dynamic range. Even the best metal tape cassettes do not reach 60 dB without a noise reduction system.

tem. In order to fit into this range an audio signal is subjected to compression and/or gain riding, wherein the loud passages are reduced in level, and the soft passages are increased in level, thereby reducing the overall dynamic range.

The new form of storing recorded music is the compact disc for which the manufacturers are claiming 100 dB dynamic range. This can be achieved, but is a great misrepresentation in that 80% of the discs released to date are from analogue masters and only 55 dB dynamic range is attainable, all things being correct.

Another misrepresentation of the compact disc is that it cannot be scratched or affected by dirt. This is incorrect. Once a disc has been scratched it will not be played by most players. Dirt on the disc will cause problems with the sound reproduction mainly in a surging effect.

The proponents of the CD player will point out the ease of operation, length of playing time and, of course, no surface noise.

On the other hand the proponents of the analogue system will advise that the disc lacks presence (ambience) appears to have lost harmonics and when comparing the disc to the record one finds that depth of sound is missing on the compact disc.

It would seem that the arguments for and against compact discs are going to go on for some time. But it is to the point to note that even with digital recording techniques there is still no substitute for the microphone.

With the Japanese marketing machine in top gear promoting the virtues of compact disc (whether they are actual or not) we have got the system here to stay. However, in my opinion a full orchestral piece reproduced from a record on a good turntable arm and pickup cartridge is more sonically correct and less harsh to listen to than the comparable piece reproduced on compact disc.

#### Gary Fitzsimmons,

**Consumer Electronics Suppliers Association** 

#### Wherefore the artwork?

DURING THE LAST several months I have noticed a disturbing trend by your magazine not to publish printed circuit board details. As a hobbyist reader, this represents nothing more than an effort by your organisation to extract more money from the readers of your publication, just one more 'nail in the coffin' and as such it will now put it out of my reach to even contemplate using your magazine as a source for projects.

Also, as I live some one hour's drive from the nearest kit stockist this adds further to the cost of the kit, not to mention time, involved in travelling to and from the city. As these kits are available off the shelf, I have no further use for your publication as a source of information for projects; all I have to do is look up the kits in a list from the supplier and use his construction details and information to verify if the kit is what I require.

Trevor Bartlett Nuriootpa, SA

Ouch! There is no conspiracy! It is our furthest intention to be squeezing money out of our readers, and we apologise profusely. Since we became aware of our oversight we have taken care to ensure space is left to include the artwork.

-Ed.

#### **Talking to Microbee**

REF MR BIRD'S letter to the editor (ETI Nov '85).

I took my sick 'Bee' to the West Australian branch of Applied Technology (Microbee Systems), explained how it was used by myself for library business and requested return in a reasonable time. After a week a few discreet calls were made. I finally ascertained that service on my unit had not even commenced; Microbee assured me it would "get around to it soon". I indicated that I would collect the unit and have it serviced elsewhere.

When collecting the unit, I ventured a mild complaint about the time taken and lack of repairs. The person in charge dared me to write to the manager.

The letter I despatched on 17 September was a modest statement of the event, ie, lack of service and abuse of a customer.

The manager obviously does not answer any complaints, this seems a very sensible way to avoid work and discourage Microbee users.

R. Wallace Perth, WA

#### **Microbee talks back**

THANKS FOR THE opportunity to comment on Mr Wallace's letter. To be honest I was surprised by Mr Wallace's allegations as our people staffing the Perth centre are particularly enthusiastic and customer orientated. In fairness to them, I immediately contacted our Perth Manager, Mr David Crossley, and asked for his comments.

It appears that Mr Wallace left his computer with our service department, but returned in only three or four days expecting repairs to have been completed. At the time, the service department was very busy (we have a great many machines installed in WA schools), and had not been able to attend to Mr Wallace's machine.

To me this does not sound unreasonable; we are a small company, and the economies of manufacturing computers in Australia mean that we cannot afford sufficient service people to completely obviate all temporary overloads and delays. In fact I believe most reasonable people would agree that delays of even three or four weeks are not unusual for repairs to equipment like video cassette recorders, even by much larger firms than ourselves. Normally MSL endeavours to achieve a service turnaround of less than two weeks, and frequently much less.

Apparently Mr Wallace took the advice to write to our Managing Director, and as I write this our MD, Mr Owen Hill, is currently looking into the matter personally during a trip to Perth.

Needless to say, if we are able to improve our level of service and customer support in Perth (or any other area, for that matter), we will certainly do so.

Jim Rowe Communications Manager Microbee Systems Limited North Ryde, NSW



You can come on an incredible journey, not to the future, but to a technology available today for innovative electronics users. Philips, custom design and manufacture right here in Australia, both hybrid circuits or custom I.C. chips, to suit your budget and product concept.

Access to reliable hi-technology at very competitive cost even in modest production quantities.

Tell the Philips Elcoma designers what you are trying to achieve and they will create for you a unique microcircuit solution. Perhaps you already have a design. That's where Philips 50 years of continuous production experience in Australia will ensure an efficient result. Naturally, your product design security is always assured and the resulting microcircuit is exclusively your own property.

Philips years of practical experience in computer aided design (CAD/CAM) will get you off to a good start. Your new electronics package will require little space, will improve reliability and the performance of your "new product." At the same time it will provide you with more features and added benefits for your customer, and protect your design against "copycats"!



Electronic Components & Materials

## Imagine the new business opportunities with Philips custom microcircuits

The time it takes, from engineers briefing to delivery of your first electronic microcircuit or micro subassembly, will pleasantly surprise you. Design sampling and testing may be as little as 8 to 10 weeks for hybrid circuits. More advanced custom "monolithic chip" designs will take longer, depending on the size of the chip and complexity of the design.

Send off the coupon today or call Philips Electronic Components & Materials to get the ball rolling on the improvements you'd like to make to your product. Sydney (02) 439 3322 Melbourne (03) 542 333

a product.	
dney	(02) 439 3322
lbourne	(03) 5423333
elaide	(08) 243 0155
rth	(09) 2774199
sbane	(07) 440191

PHILIPS

We make electronics in Australia

Ad

Pe

Bri

My area of Interest is	s of Philips microcircuits in my products.	
Name:		
Organisation:		
Address:		
Postcode:	Phone:	
Send to: Philips Elcoma, 11 W	altham Street, ARTARMON, N.S.W. 2064.	

**ETI READER SERVICE 107** 



# TEACH ELECTRONI

12 - ETI March 1986

ING THE C BRAIN

> Software development can mean a whole lot of problems, any help is welcome. Such help is usually from microprocessor development systems which can come as a powerful total package, but frighteningly expensive, or both modest in assistance and cost.

## **Jon Fairall**

TURNING AN IDEA into electronic hardware is fairly straightforward, at least conceptually, as long as you stick to hardware. You have an idea, draw up a schematic, put the bits together, and then get out the test instruments and ensure that everything happens when it's supposed to. If, as all too often happens, it doesn't work out quite that simply, in theory it's still not a very difficult job to find out why by making the appropriate electronic measurements.

With the development of microprocessors, machines with brains and software dependence, all this changed. It's impossible to see the mental activity of the machine, thus impossible to correct it if it's not doing what it's told. There are no electronic measurements to be made. Even when the faults do have hardware manifestations, problems remain. Because processors move so fast on an irregular basis, it's almost impossible to use conventional test instruments like oscilloscopes and multimeters to find faults.

So the requirement is a machine that allows a design engineer to develop microprocessor-based products with as much ease as his colleague develops analogue circuits. Such devices are called microprocessor development systems, and come in a huge variety of performances and prices.

## History

In the beginning the way one developed microprocessor projects was with a pencil,

## **MICROPROFESSOR MPF-1/88**

The MPF-I/88 from Multitech is typical of a low end development system. It is designed primarily as an educational tool for teaching machine language programming of the 8088 microprocessor. However, with expansion modules it can be turned into quite a powerful little development system. Naturally, it doesn't compete with devices like the Philips PEDS. On the other hand its cost isn't in the same league either.

However, it does share some features with more expensive machines. For instance, the MPF-I/88 is user expandable up to the level required by the user. The basic unit is all that is needed for instruction in machine code. It contains a keyboard, two line LCD display, the 8088 processor plus associated RAM (24K) and the monitor programme in ROM. There is also an editor assembler on board to allow the composition of programmes, debugging and running on the internal processor. Nonvolatile memory is provided by a cassette interface.

There are a number of expansion modules

available. A printer can be connected via a Centronics interface. A special interface module provides a number of slots into which 'option' cards can be inserted. One of these cards allows connection to the slots of an IBM-PC. Indeed the slots on the card are IBM-compatible, so you could use any IBM-compatible card in the system.

This Introduces a whole host of powerful features to the MPF-I/88. For instance, it can work as a remote terminal, in which case you can talk to the MPF-I/88 from the PC's keyboard and read out from the screen. Mass storage can be achieved via the PC's disk drives and you can access onboard RAM (up to 512K) for program space. You plug in an asynchronous communications adaptor, monochrome or colour display adaptor and so on. And, of course, you can manufacture your own boards and write software for them using all the programming editing and debugging tools on the host system.



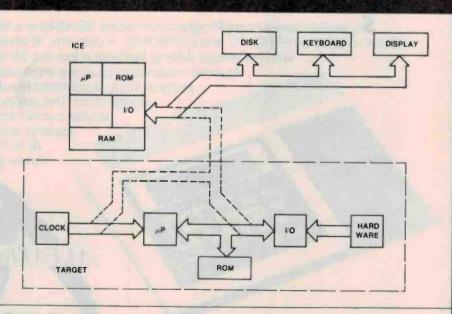


Figure 1. ICE to target system block diagram.



## PHILIPS' ENGINEERING AND DEVELOPMENT

Philips 'PEDS is a typical high end development system. It's universal, with emulation of 50 different types of processor. It's fully modular, expandable both in the number of users and the number of processors being emulated. It has software to cover all aspects of product development, from design to production. It has documentation, EPROM burning and service functions, In addition to the normal software and hardware development programmes.

To get PEDS up and running you need a basic master system that includes 256K of RAM and 64K of ROM, hard and floppy disks, a 68000 CPU, two RS232 ports and a printer interface. The whole thing is glued together by a multi tasking operating system. There is also a universal debug unit and 16K of fast static emulation memory, a micro adaptor box and an assembler and emulator processor.

This can be expanded in a number of different directions. PEDS handles all the different processors via microcomputer adaptor boxes, (MABs). The user buys MABs specific to the target micro, which plug into a universal debug unit. The MAB is responsible for translating the information from the micro into a universal format that can be understood by the rest of the system.

You can also buy a state trace facility when required to assist in debugging, additional

# "Easy to use Prom Programmer seen loitering at Alfatron."

Super-Ex's latest Prom Programmer model SE-4943 is a friendly tool for programming 16K bit to 512K bit EPROM'S and EEPROM'S. A dual line 16 character LCD display coupled with enhanced editing features make the SE-4943 very easy to use. No extra modules or plug-ins are needed and the latest programming algorithms result in a highly flexible and fast

programmer. The unit provides serial RS-232 for full remote control and Centronic ports for down loading and record keeping. At ALFATRON, we

know programmers.

ALFATRON

Alfatron Pty Ltd

1761 Ferntree Gully Road Ferntree Gully Victoria 3156

Telephone (03) 758 9000 Telex AA37795 Alftrn.

14 - ETI March 1986

**ETI READER SERVICE 108** 

## FEATURE

## SYSTEM

emulation memory, additional user terminals, a PROM programmer, compilers and so on.

Its cost is difficult to state, depending on the options you specify, exchange rates and so on. The minimum system would set you back about \$35,000. But you could easily spend \$100,000 without trying too hard, especially if you needed a number of terminals.

Programming in PEDS is done via Unix. However there are also options including C, Pascal, PL/M and Fortran. Any of these is turned into machine code by the assembler. This is displayed in the mnemonics of the target micro. The assembler has sufficient intelligence to refine the code as it is assembled. For instance it can choose between different instructions in certain circumstances and will always choose the short forms of operands.

There is great flexibility in the way one develops a project using PEDS. For instance, it has a simulation mode, appropriate when no hardware is available. This means that software can be developed even before the hardware. On the other hand, PEDS has an emulation mode, in which the program is run on the target system. In addition, any mixture of these two extremes is possible, so that one can run software on the half a target system that exists, while the other half is still being simulated by the PEDS.

paper, PROM burner and an awful lot of patience. One wrote out the program, burnt it into the EPROM, put the EPROM back into the board and hoped nothing blew up. If things went wrong, one went back to the paper and tried again.

Clearly, there were problems with this approach, so development systems were produced almost as soon as microprocessors themselves became commercial products in the early 1970s. Predictably, the first ones were developed by the processor manufacturers, noticeably Intel. These were essentially prototyping boards, and gave the user the freedom to enter machine code directly into the onboard RAM so that the effects of a particular sequence could be studied.

It didn't take long, however, to establish the technique of in-circuit emulation (ICE), which remains the fundamental principle behind all development systems to this day. To explain: we start with a piece of processor controlled hardware, called the target system. At a minimum it will contain the processor, its memory, input/output (I/O) stages and some other hardware to interface it to the outside world. The processor then reads its instructions from the ROM and controls the hardware via the I/O.

ICE takes over the functioning of the processor and the ROM. Usually what happens is that the ICE consists of a box with a lead coming out of it which is plugged into the processor socket on the target system (see Figure 1). The ICE itself is a computer, with its own processor, memory and I/O. The difference is that the ICE has a program already installed in it which allows it to do certain tricks.

It does all the usual house keeping you get in any computer, looking after the keyboard and screen for instance, arranging and controlling files and mass storage on disks or cassettes. In addition, it reserves a section of its own memory so that it can simulate the ROM on the target system. In other words, the I/O stage on the target system sees the ICE perform in exactly the same way as its own resident processor.


The result is that the operator can enter code directly into memory in the ICE, and then instruct the target to behave as if that code was located in its own onboard ROM. Execution of the program can be debugged by the ICE in exactly the same way as with BASIC in a domestic PC. You can step, or trace, insert break points, etc, etc, in fact use all the familiar tools of program analysis. And while all this is happening in the ICE, the target is behaving as if the particular program step has been executed in its own onboard ROM.

A refinement to this was the advent of software compilers and assemblers which allow one to write code for the processor, either in the form of mnemonic codes or in some high level language like BASIC. Actually, BASIC itself is not much favoured in this particular application. Most high level editors seem to use C or Pascal because of their inherent efficiency.

As time has passed, this basic vision of what an MDS should be has grown more sophisticated. During the late seventies and early eighties a number of leading companies like Hewlett-Packard and Tektronix began to look at design as a single process, all the way from the initial idea 'on the back of a fag packet' through to manufacture. This is only logical, as many practicing designers will attest, because of the enormous amount of time involved in documenting everything, or liaising between members of a design group and so on.
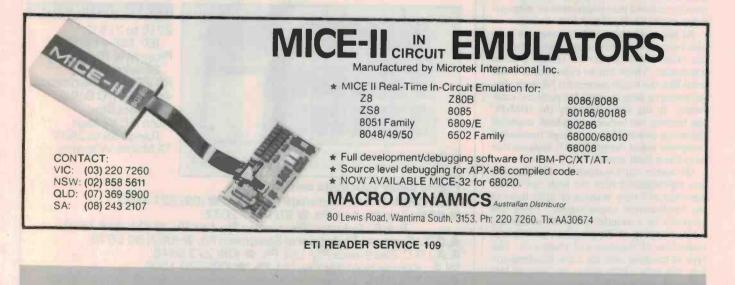
#### Range

And so the number and variety of systems has grown enormously. At one end of the scale, designers have piled on features and flexibility, using the increasing power of computers to do more and more and to integrate the design cycle into one discrete whole. At the other end of the scale, the same sophistication in computer design has



## FEATURE

been dedicated to squeezing the basic minimum functions into smaller and cheaper packages.

The modern high end system usually has multi-user capability, so that an entire design team can work on one machine, each user with an individual terminal. Work being created on one terminal is instantly accessible on any other so that interfacing problems between the various parts of a project are minimised. There will be text editors, and documentation subroutines, so that parts list and numbers are automatically inserted and updated as required. There is often an impressive graphics capacity to assist in conceptualising problems with flow charts and symbols.

Many modern machines have hardware emulation characteristics as well. In systems like this the structure of the hardware can be specified and the computer will then emulate its response to simulate a software program. In this way an entire project can be designed and debugged without even building a prototype.

However this hardware emulation is more fraught with danger than might at first appear. It depends for its accuracy on the extent to which the individual components are accurately modelled in the software of the emulator. Development models of this technology are full of bugs caused by unsuspected peculiarities of individual components, but it seems that most of these problems have been ironed out. Indeed, some companies are now starting to achieve notable successes in this area.

Further refinements permit the system to generate its own fault analysis for use in manufacturing and testing procedures or for quality control on an assembly line. In fact, some companies have products that allow results from the development system to be directly entered into production or management control computers.

At the same time, low end systems have also been developed that take advantage of the tremendous power of cheap modern computers. These can be either stand alone units like the highly successful Microprofessor series or plug in cards for personal computers. In the latter category the IBM-PC has become the industry standard, made all the more powerful by the large number of computer aided design (CAD) systems that have been built around it.

Of course, such systems are considerably less sophisticated than the high end machines, but still they manage to fulfil most of the fundamental requirements. There will certainly be a monitor program permitting single stepping of the program, editing and inspection of registers and memories. This type of machine sells for a few hundred dollars. For only a little more, you can get into the world of compilers and assemblers, allowing far more efficient programming.

#### **Universal v dedicated**

Another significant development in the marketplace has been the growth of universal systems. The distinction between universal and dedicated systems is that universal machines are able to handle a large number of processors, dedicated machines only one, or perhaps a single family. In some cases universal machines might be restricted in terms of the number of bits, so it might only take 8, or only 8 or 16, or some such restriction. However, the important point is that it is not restricted to the products of one manufacturer.

Dedicated devices, on the other hand, are restricted to one type or range of processor. For the most part these are made by the manufacturer of the device under question. As one can imagine, the big players in this market have names like Motorola and Intel.

The advantages of the universal machine are obvious enough: you can choose the processor that best fits the application instead of being limited to one company's product. On the other hand, makers of dedicated systems can bring some strong arguments to bear. They argue that the freedom given by the universal system is largely illusory for a start. The machine may be able to handle a dozen different micros, but can the engineer? In fact, most engineers are stuck to one, or possibly two different types.

Another advantage is that dedicated machines are far less complex than their equivalent universal machine, since emulating a single micro is a far less complex task. Low end machines all tend to be of this type for precisely that reason.

Most universal machines handle a multitude of processors with the use of separate modules, each dedicated to a single processor. This leads naturally to the idea of modular construction for the entire unit. So one of the major trends in development systems at the moment is to allow the user to determine how much, or how little, is needed to do any particular job. The Tektronix 856 family, or Philips PEDS are both systems of this type.

It's a trend that has one tremendous advantage: you only pay for what you need. It also means that the cost of developing software, although still breathtakingly high, is more and more within reach of small companies with creative ideas.



QUEENSLAND: Computer Components Pty. Ltd. Ph. 2 (07) 44 9559. TASMANIA: Hocking Electronics Ph. 2 (002) 23 4388.

**ETI READER SERVICE 110** 

# **RITRONICS WHOLESALE** "Your prime source for quality electronic components and hardware at the lowest prices!"



## ONG YFE-1030C

eatures; Large 31/2 digit display, 11/2 inch high) Autopolarity, "-" display for Negative Input. High over-load protection for all ranges. Over-load display highest figure "1" or "-1"

Power consumption 20mW approx.     Cat. Q126030	
1-99	100-
42.05	100

#### 43.95 Plus 20% Sales tax where applicable 34.00

#### TANTALUM CAPACITORS

Cat. No.	Description	10+	100+	
R16124	4.7uF 16V	\$0.24	\$0.18	
R16125	10uF16V	\$0,25	\$0.23	
R16126	15uF 16V	\$0.38	\$0.36	
R16128	22uF 16V	\$0,42	\$0.40	
R16132	47uF16V	\$1.55	\$1.20	
R16134	68uF 16V	\$1.80	\$1.50	
R16220	4.7uF 16V	\$0.35	\$0.33	
R16224	10uF 16V	\$0.38		
R16228	22uF 16V	\$1.20	\$1.00	
R16300	0.1uF 35V	\$0.13	\$0.12	
R16302	0.15uF 35V	\$0.13	\$0.12	
R16304	0.22uF35V	\$0.15	\$0.12	
R16306	0.33uF 35V	\$0.15	\$0.14	
R16308	0.47uF35V	\$0.15	\$0.14	
R16310	0.68uF 35V	\$0.16	\$0.15	
R16311	0.82uF 35V	\$0.18	\$0.15	
R16312	1uF35V	\$0.15	\$0.12	
R16314	1.5uF 35V	\$0.24	\$0.20	
R16316	2.2uF 35V	\$0.24	\$0.23	
R16318	3.3uF 35V	\$0.29	\$0.27	
R16320	4.7uF 35V	\$0.35	\$0.33	
30% Sale	es tax where a	oplica	ble	

## NICADS

Cat No. 1-99 100+ 250+ 500-\$15020 AA 1.60 1.50 1.40 1.10 \$15022 D4.0AH 7.90 7.50 7.20 6.90



		1.9	10+	100+
Cat. T12461		10.50	10.00	8.00
Cal. T12465		10.50	10.00	9.00
Cat. T12463		10.50	10.00	8.00
Cat. T12467	115V 31/2"	10.50	10.00	9.00
(Fan guard Plus 20% ti	s to suit als	o availa	biel	0.00

#### RAINBOW CABLE

Cat.No.	Description	1-29 mtr	30+ mtr
W12714	28AWG 14W per metre	\$0.90	\$0.70
W12716	28AWG 16W per metre	\$0.90	\$0.70
W12720	28AWG 20W per metre	\$1.20	\$1.10
W12726	28AWG 26W per metre		\$1.50
W12734	28AWG 34W per metre	\$1.90	\$1.80
W12740	28AWG 40W per metre	\$2.20	\$2.00
Plus 20%	tax where applicable		



#### ADD ON DISK DRIVE FOR 6502 SYSTEM APPLE\* COMPATIBLE 1-9 10-24 25+ \$150 \$140 \$130 \$150 \$140 ("Apple is a registered trademark) 25+

## IBM ADD ON HARD DISK O Mbyte Seagate hard disk Hard disk controller by Xebec Cat. X20010 Plus 20% tax where applicable

\$1295

## **MITSUBISHI DISK DRIVES**

	the second s	1.9	10+	25+	
4851	51/4" 500K	\$175	\$160	\$150	
4853	51/4" 1M	\$220	\$205	\$175	
4854	51/4" 1.6M	\$250	\$220	\$195	
2896	8" 1.6M		\$430	\$400	
Plus 2	0% tax where	applic	able		



RITRON II ivel base monitor in stylish case Green Cat. X14506 \$145 Amber Cat. X14508 \$150 Plus 20% tax where applic \$135 \$140 \$115

## MONITORS Cat No. X14500 Ritron 1 Greer X14502 Ritron 1 Ambe

Ritron 1 Green \$130 Ritron 1 Amber \$135 BACK IN STOCK \$125 Plus 20% tax where at



DATA CASSETTES ck our low prices on these quality tapes! 10-99 \$0.70 100+ \$0.75 \$0.65 Plus 20% tax where ann

## COMPUTER

RITRONICS

CONNECTOR	5		
Cat No. Description	1-99	100+	100
P10900 DB25 Plug	1.30	1,20	1.00
P10901 DB25 Socket	1.40	1.30	1.20
P12210 Centronics Solder	3.50	3.15	2.50
P12200 Centronics Crimp	6.00	5.50	5.00
P10880 DB9 Plug	1.30	1.20	0.90
P10881 DB9 Socket	1.40	1.30	1.00
P10890 DB15 Plug	1.30	1.20	0.90
P10891 DB15 Socket	1.40	1.30	1.00
P10902 DB25 Cover	.80	.65	.55
Plus 20% tax where applies	bla		

## VERBATIM DATA LIFE DISKETTES 10-99 100+ 500+ SS/DD MD525-01 2.50 2.35 2.25 DS/DD MD550-01 3.20 2.50 2.40 XIDEX DISKETTES SS/DD 2.50 2.50 2.25 DS/DD 3.40 3.05 2.85 Plus 20% tax where applicable



## **10W P.A. SPEAKERS**

1-9 10+ 100+ 300+ \$5.00 \$4.75 \$4.50 \$4.00 Plus 20% tax where applicable

## POLYESTER 100V

"GRI	EENC	AP"	TYP	E
Cat No.		1-99	100+	10004
R15131	.001uF	0.06	0.04	.036
R15137	.0012uF	0.06	0.04	.036
R15138	.0015uF	0.06	0.04	.036
R15140	.0022uF	0.06	0.04	.036
R15142	.0033uF	0.06	0.04	.036
R15143	.0039uF	0.06	0.04	.036
R15145	.0047UF	0.06	0.04	.036
R15146	.0056uF	0.06	0.04	036
R15147	.0082uF	0.06	0.04	.036
R15148	.01uF	0.07	0.05	.045
R15150	.015uF	0.07	0.05	.045
R15152	.022uF	0 07	0.05	.045
R15154	.033uF	0.07	0.05	.048
R15155	.039uF	0.07	0.05	.045
R15156	.047uF	0.08	0.06	.055
R15157	.056uF	0.08	0.06	.055
R15158	.068uF	0.08	0.06	.055
R15159	.082UF	0.08	0.07	.055
R15160	.1uF	0.09	0.08	.07
R15162	.15uF	0.11	0.10	.09
R15164	.22uF	0.15	0.14	.13
R15165	.27uF	0.16	0.15	.14
R15172	1uF	0.70	0.55	0.50
R15176	2.20	1.20	1.10	1.00
R15178	3.3uF	1.50	1.20	
Plus 30%	tax where	applica	ble	



CHOCA IUI	OLO HUTO	21 menne	Dry price	851	
	10-99	100+	1000+	10K+	
4164-15P	\$ 2.50	\$ 2.00	\$ 1.75	\$ 1.60	
41256	\$ 6.00	\$ 5.00	\$ 4.50	\$ 4.00	
5116P-3		\$ 2.90			
2716	\$ 4.90	\$ 4.50	\$ 4.25	\$ 4.00	
	\$ 5.00				
2532	\$ 7.50	\$ 6.50	\$ 6.40	\$ 6.30	
2732	\$ 6.50	\$ 6.10	\$ 5.90	\$ 5.50	
27256	\$29.00	\$27.00	\$22.00	19.00	
	\$ 5.50				
	\$ 6.00				
1. 1000 aul	and seath man	a secolita.			



	10+	100+	1000+	10K
8 Pin	.08	.07	.06	.05
14 Pin	.10	.09	.08	.07
16 Pin	.11	.10	.09	.08
18 Pin	.12	.11	.10	.09
20 Pin	.13	.12	.11	.10
22 Pin	.14	.13	.12	.11
24 Pin	.15	.14	.13	.12
28 Pin	.19	.17	.15	.14
40 Pin	.25	.24	22	.20



## PANEL METERS

		1.9	10+	100+
Q10500	MU450-1mA	6.95	6.75	6.50
Q10502	MU45 50-0-50uA	6.95	6.75	6.50
Q10504	MU450-100uA	6.95	6.75	6 50
Q10505	MU450-50uA	6.95	6.75	6.50
Q10510	MU450-5A	6.95	6.75	6.50
Q10518	MU450-1A	6.95	6.75	6.50
Q10520	MU45 0-20V	6.95	6.75	6.50
Q10535	MU45 VU	7.95	7.75	7.50
Q10530	MU52E 0-1mA	9.95	8.35	1.50
Q10533	MU52E 0-5mA	9.95	8.35	
Q10538	MU65 0-500A	9.35	8.95	8,75
Q10540	MU650-1mA	9.35	8.95	8.75
010550	MU650-100uA	9.35	6.95	B.75
010560	MU650 0-20v	9.35	6.95	8.75
	tax where applicab		0.35	0.75



## RESISTORS

1/4 WATT E12 CARBON BULK PACKED 5:25/1000 TAPED AND BOXED 55.25/1000 \$5.00/1000 10K LOTS 1/4 METAL FILM TAPED AND BOXED \$12.00/1000 \$111.00/1000/10K LOT SUPPLY E24 11.00/1000/10K LOT SUPPLY E24 VALUE Plus 30% tax where applicable

<b>750HM</b>	COA	XCA	BLE
Cat No.	100M	500M	1000M
W11222 3C2V	18.00	17.00	16.00
W11224 5C2V	27.00	25.00	24.00
(5C2V WHITE O	RBLACK	3	
100M ROLLS			
LINE LOSS PER	100' (33	M 200MHz	:)
W11222 6.2dB (	Approx)		
W11224 3.9dB (	Approx		

## Plus 20% tax where applicable

LEDS 5mm STANDARD 10+ 100+ 100+ Red \$0.10 \$0.09 \$0.08 Green \$0.15 \$0.10 \$0.09 Yellow\$0.15 \$0.10 \$0.09 Yellow\$0.15 \$0.10 \$0.09







Pty. Ltd Renver Road, CLAYTON, 3168, VICTORIA, AUSTRALIA. Phone (03) 543 2166 (3 lines) Telex: AA151938 Minimum account order is \$50, minimum cash sale is \$25. Minimum post/pack \$3.00. Minimum account post/pack \$5.00. Comet Road Freight, bulky items and/or over 10Kg is extra. **ETI READER SERVICE 111** Bankcard, Visa and Mastercard welcome Errors and Omissions Excepted

## Eliminate hot sites faster. HP's complete family of protocol analyzers. All compatible.

HP is the first company to offer you a complete family of protocol analyzers that are all data-compatible. Now, you can quickly identify and solve network problems — without having to recreate them for analysis at each organizational level.

## Clear lines of communication with remote capability

For the first time, you can have a clear line of communication from the customer's hot site to your district or regional service center — even to R&D if necessary.

All HP protocol analyzers permit remote transfer of data and test programs, so you have high-powered analysis wherever you need it. Captured data and test programs written on one HP analyzer can be transferred to any other remote unit.

Now your field service personnel have direct access to the technical resources they need to solve even the toughest problems



in the shortest possible time – no matter how dispersed the network is geographically.

Software extends flexibility With three HP protocol analyzers to choose from, you don't have to buy any more performance than you need. You are also assured continuing software support – a comprehensive package for X.25 certification and testing as well as powerful decode and simulation packages for SNA, X.21, CCITT #7, and the other protocols you need.

## Quick and easy measurements

All HP protocol analyzers feature a common human interface — menus, decoded displays, ASCII keyboards, and softkeys that quickly and easily guide you through your measurements. Learn how to use one HP protocol analyzer and you can use them all.

For details about the HP family of data-compatible protocol analyzers, call Hewlett-Packard.

Melbourne: 895-2895, Sydney: 888-4444, Adelaide: 272-5911, Perth: 383-2188, Brisbane: 30-4133, Canberra: 80-4244.



## **SIGHT & SOUND NEWS**

# Loudspeaker series from Jamo

Following three years of research and development work Jamo is launching a new range of speakers with the front baffle of a concrete-like material.


In 1982 Jamo started to experiment with loudspeaker cabinets in other materials and different shapes finally concluding that concrete was an excellent material for loudspeaker cabinets. This was not from a production point of view but from a sonic view. Unfortunately concrete has many disadvantages such as extremely high cost.

Jamo has settled on a technique of injection moulding a 1-inch thick concrete-like material between two layers of vacuum-formed polystyrene. By using vacuum formed polystyrene it was possible to give a finish and shape to the front baffle in the best possible way. As a result the loudspeaker drivers are mounted with the acoustic centre in line, thus assuring no time delay between the three drivers. The surface of the front baffle could also be incorporated with anti-diffraction pattern, an which gives the new digital monitor speakers a stereo image.

A new shaped cabinet has been developed in which none of the five sides are parallel. In this way Jamo has avoided the traditional standing waves in the cabinet and the new cabinet shape matches the front baffle. Incorporated in the cabinet is a solid loudspeaker stand which can be equipped with tip-toes or spikes. Jamo's Centre-Bass-Reflex System has also been incorporated in the new series. The CBR-system mounts the woofer in four rubber suspension points which initially isolates the worst vibration from ther woofer before being transferred into the front baffle. The port opening, which is an air gap surrounding the woofer, gives a symmetrical loading of the woofers' diaphragm. The tuning of the bassreflex cabinet is based on the American Schneider theories.

The speakers have electronic overload protection for the tweeter. The larger models have built-in attenuators for treble and mid-range.

The top of the range model is the CBR 200 which is a 3-way floor standing loudspeaker. The dome tweeter used in this system has a polymer diaphragm and has ferro-fluid injected in the voice coil air gap. This magnetic coil gives better damping of the tweeter and cooling of the voice coil which gives the speaker its high power handling capacity of 200 watt rms. The mid-range and woofer diaphragms are made of carbon fibre which is a light and very strong material with high internal stiffness. The 10" woofer has a specially developed dual magnet system for high efficiency and improved linearity. The prices are expected to be between \$700-\$2000 per pair.

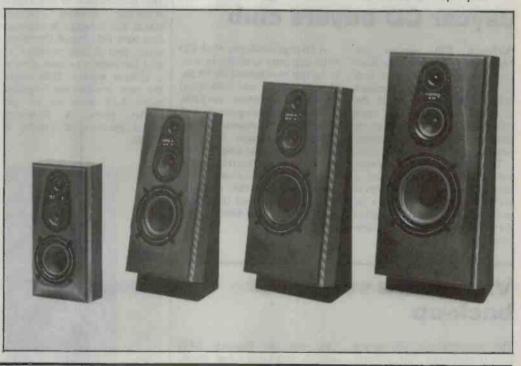

## JVC opts for midi-system

JVC has opted for the midi size in its range of hi-fi systems with the new MIDI-X5.

This system features a direct source selector. This computerised input selection system both selects and plays an input at the touch of a button. A 'Computer Shift Control' feature makes additional conveniences like blank search and blank skip possible by means of a special 'shift' control together with the tape controls.

The quartz locked digital synthesiser tuner (T-E30B) has presets for six FM and six AM stations, while the two-way speakers (S-E708) have passive radiators for rich lows. The graphic equaliser (SAE-E30B) has 10 frequency equaliser controls and gives the user total control.

Also included in the system are a stereo integrated amplifier (A-E40B) with 45 W DIN/channel and direct source selection; a programmable fully automatic turntable (L-E30B) with index scan and linear tracking tone arm; a double mechanism full logic cassette deck (D-W30) allowing random access of up to 10 selections, double speed tape dubbing, synchro recording, and Dolby noise reduction; plus an adjustable turntable stand (LK-E20B).

The cost of the JVC Midi-X5 system is about \$2699 RRP.

## SIGHT & SOUND NEWS

## **Speaker connectors**

A specially designed version of the AXR Series connectors, suitable for connecting a power amplifier to loudspeaker enclosures is available from STC-Cannon. The precision machined contacts ensure minimum power loss and improve performances when used in combination with high qualityaudio cable.

Features include rugged metal shells with satin nickel finish; positive quick action lock coupling: positive polarisation; highly conductive copper alloy machined contacts incorporating large solder bucket to accept up to 12 AWG cable (4 mm<sup>2</sup>); enlarged cable entry capable of accepting both high quality circular audio cable to 10 mm diameter and figure eight cable with a cross section of 7 mm x 12 mm. The flat section on the connector housing can be used for circuit identification purposes. When combined with the AXR range of optional coloured boots, this facility provides multiple combinations for rapid circuit identification. They also provide convenient grub screw cable clamping.

## **Jaycar CD buyers club**

Although CD players are becoming very popular in Australia, there is still a serious lack of readily available compact discs. Only about half of the country's record stores carry these discs, and those that do generally have a limited and expensive range.

To help overcome this problem, Jaycar has established a mail order compact disc buyers club. Discs can be ordered by phone or mail, and Jaycar gives a conditional 30-day satisfaction guarantee. A 56-page catalogue of all CD titles currently available in Australia can be obtained for \$4 (including postage and packaging) or free with any order over \$100. Jaycar has arrangements with fifteen record companies, ensuring a considerable range of titles. Cost of the discs will be less than the normal retail price. For more information contact Jaycar, PO Box 185, Concord, NSW 2137, or phone the Jaycar Hotline on (02)747-1888.

## **Slim cabinet loudspeakers**

With the new NAD 20 loudspeakers the approach has been to concentrate on aspects which contribute to sonic excellence and real performance while avoiding cosmetic 'features'.

ADS woofers were used for quick transient response and soft dome tweeters for crisp, airy, extended, peak-free highs.

The key to the performance of both drivers in the NAD 20 is a very high ratio of force to moving mass.

Special construction techniques are used so that the drivers have an exceptionally small voice coil gap. The intense field of the powerful barium ferrite magnet is focused on a voice coil of very fine wire which is double insulated and wound using special techniques.

The proprietary material used to form the cones and domes of the NAD 20 is exceptionally light yet stiff and resonant free. The cone of the woofer is progressively tapered in thickness which prevents 'cone break up' to eliminate colouration.

The cabinets are made to a slim, simple column design which occupies only 0.6 of a square foot of floor space. They are manufactured using MDS to tight tolerances, finished in a black ash with light grey snapon grille.

## **New 8-inch Dali woofers**

Dali has released its new Dali-8 reference monitor speaker which was designed in conjunction with Peerless of Denmark, using two 8-inch woofers to give the same size cone area as a 12-inch woofer. Dali claims the new woofers can together move 1.25 litres of air per stroke, giving a maximum sound pressure of 118 dB at 35 Hz. The woofers work in a bass reflex enclosure, along with a 4-inch mid range,  $1\frac{1}{2}$ -inch dome mid range and  $\frac{3}{4}$ -inch supertweeter.

The speakers are finished in polished walnut veneer with the woofers mounted in rubber suspensions. They sell for around \$2000 per pair.


## Visioncare service back-up

The inconvenience of having your television or video cassette recorder breakdown can be made a lot worse by the lack of expert service to repair the set quickly, at reasonable cost, and with a guarantee of quality workmanship.

A little over a year ago Visionhire (Australia) Pty Ltd established a servicing arm called Visioncare to meet the need for servicing electronic products such as televisions, video cassette recorders, sound systems and even personal computers. One of the first to offer Visioncare was the Gosford NSW branch, and Gold Coast stores. Eventually there will be a string of Visioncare service outlets throughout Visionhire's Australia-wide network.

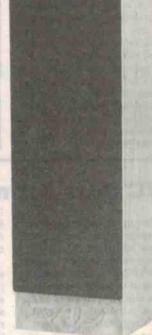
David Hall, Visionhire's managing director, says that the company has the expertise and resources to back up the Visioncare service, because it is an established rental specialist with some 30 branches and service centres, and also has the stability of being a multinational organisation.





ADD IN A STOLEN OF LONG TO SHARE IN

20 - ETh March 1986

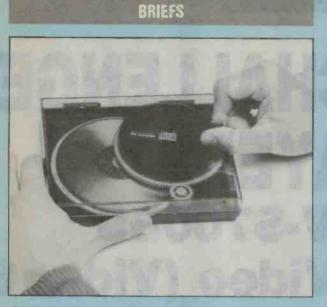

## **Compact disc cleaner**

The Discwasher Compact Disc Cleaner is a new product said to offer radial cleaning to protect against scratching the disc surface along the line of the recorded message, which can cause laser mistracking. The package includes the compact disc cleaning unit; CD-1 cleaning fluid; a cleaning pad grooming brush; and replacement cleaning pad. No power supplies or batteries are required. Detailed instructions are printed on the bottom of the compact disc cleaner. The Discwasher is available for \$49.90 from Arena Distributors, 642 Albany Hwy, Victoria Park, WA 6100. (09) 361-5422.

#### New speaker range from Visonlk

The new "David" speaker range from Visonik West Germany, was released at the International Funkausstellung Audio-Video Exhibition in Berlin last year. The new models reportedly feature improved technical performance in keeping with demand for CD compatible and high performance amplification requirements. Emphasis is on the Satellite System comprising one sub woofer and two David 6001 Mini High Performance Boxes. When placed in a room correctly, the end result is reportedly similar to the performance of a four speaker type quadro system, however using a relatively tiny amount of space. They are available from German Hi Fi, 61 Burns Bay Rd, Lane Cove, NSW 2066.

#### Stereo AM/FM radio-cassette from DSE

A new stereo-AM/FM-cassette deck (Cat A-6020) is available from DSE for \$279. It features LED digital frequency display, a five AM/FM station memory with auto scanning and automatic noise reduction. It has a 6 watt output and separate bass and treble controls to suit personal tastes. The front-rear fader is suitable for four speaker systems.

## Lloyds Bank chooses Laservision

Lloyds Bank, UK, has appointed Philips as project managers for the supply and installation of an interactive Laservision system for staff training. Lloyds requires Laservision systems to be installed in 1500 key branches and principal head office departments by the end of this year. These will provide individual self paced learning courses for Lloyds' 46,000 staff. This order for Philips in the UK follows the success in the development with the BBC of a laservision.

## And HBA uses videodisc

Recently, the finance department of the Hospital Benefits Association in Melbourne leased a Pioneer Electronics L-D V1000 LaserDisc player to train its staff in the Lotus 1-2-3 computer program. It is being used in conjunction with an IBM-PC. The instant random access facility of the laser beam 'stylus' locates any of 54,000 frames of vision on one side of a single disc, and specific points can be accurately and quickly accessed in a random or pre-programmed sequence. Pioneer LaserDisc systems are making a significant impact on communications technology. Current industry figures indicate that over 100,000 industrial videodisc players are now in use in the US, Europe, Japan and Australia. Companies using videodisc systems include General Motors and IBM.

#### **New Ross headphones**

Concept Audio Pty Ltd, importers and distributors of the popular British-made Ross headphones, has released two new models. The RE-2225 comes fitted with 2 metres of cable and a 6.4 mm stereo jack plug and has the added advantage of in-line left and right channel volume controls together with a stereo/mono switch. The RE-2285 has been designed specifically for TV and video listening and comes with a 5 metre cable. It is supplied with a 6.4 mm stereo jack socket to 3.5 mm mono jack plug adaptor for mono TV and video connection. These headphones are additionally supplied with in-line left and right channel volume controls and stereo/mono switch.

#### Compact disc cleaner II

The new Milty Products CD cleaner comes in the form of pre-saturated single use wipes which are ready for immediate use. They are packaged in a 70 wipe drum which sells for \$13.95. Further information can be obtained by calling Concept Audio on (02) 938-3700.

#### CD-100X CD player

A new CD player, the CD-100X from ADC is now available for \$499 from Concept Audio. It features a simple and easy to use motorised disc tray; three beam laser for better tracking; programmable memory for 16 tracks; single track repeat, programmed track repeat and all track repeat; linear digital-to-analogue converter for low distortion sound; and versatile multi function display. Further information is available from Concept Audio on (02) 938-3700.

#### JVC video cassette range

JVC is now offering its Dynarec range of video cassettes each with special characteristics suited to specific purposes such as professional video presentation, master recordings or time-shift viewing. The different tailoring includes a high resolution magnetic coating on the HR type, head cleaning and anti-static features on the HG Hi-Fi variety, and a new magnetic coating of emulsion on the Pro. Information on these and other variations is available from JVC, 5-7 Garema Ct, Kingsgrove, NSW 2208. (02) 750-3777.




# 8mm VCR CHALLENGES TOP CD PLAYERS — the Sony EV-S700ES Digital Audio Video (Video 8)

Apart from its excellent video features, Sony's new VCR can be used as a PCM audio recorder — with extraordinary results!

IN 1982 SONY and four other major manufacturers announced proposals for an 8 mm VCR format. Not long afterwards 122 different manufacturers gathered in Japan for the first 8 mm Video Conference which set up working groups. These groups quietly developed the standards which have now been ratified by the original conference members.

During my last visit to Japan at the end of 1984 I evaluated the multiple options available to the Japanese manufacturers for the new DASH format cassettes that would be used for the new DAV (digital audio video) equipment. In the ensuing period, the Japanese and European manufacturers have resolved the issues and have even submitted appropriate documentation to the International Electro-Technical Commission so that the formal standard requirements will soon be ratified.

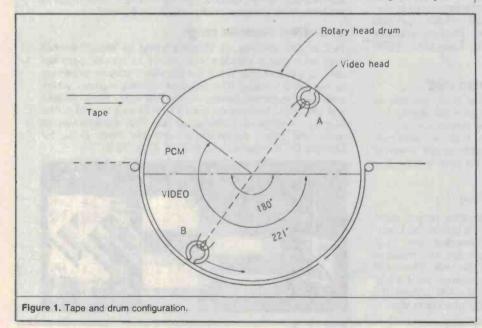When we reviewed the Sony CCD-V8 8 mm video camera/recorder (ETI, October 1985), I primarily evaluated the video characteristics of the system, as there was no direct means of evaluating the full poten-



tial of the audio section. I was, however, very much aware of that unit's potential as a PCM digital audio recorder. This review looks at this rather considerable potential.

#### **Design features**

The 8 mm video system has an energy density capacity which is 50% superior to the standard VCR cassette when used in the standard play (SP) mode and three times greater in the long play (LP) mode.

Although the Video 8 cassette is 12% larger than a standard audio compact cassette it is much more efficient because it uses a specially formulated tape with a base thickness of polyester only 9 microns thick, a backcoating 1 micron thick and an iron powder magnetic coating layer which is 3 microns thick. A superior tape will soon be available in which an evaporated metal coating only 0.15 microns thick will be used. This new coating will provide superlative high frequency performance and much higher mechanical stability.

The format of the recording system used with a Video 8 recorder is based on two video heads mounted on the opposite sides of a rotary head drum. Of each half drum rotation, 150° is devoted to the video signal and the remaining 30° is allocated for the pulse code modulated (PCM) audio signal component (see Figure 1). This arrangement is in sharp contrast to the conventional VHS or Beta format VCRs which use a separate stationary head for the monophonic FM sound track on one side of the tape.

The innovative tracking system used in the Video 8 system was developed by

### SONY EV-S700ES DIGITAL AUDIO VIDEO (VIDEO 8)

Dimensions:	355 mm (wide) x 95 mm (high) x 342 mm (deep)
Weight:	7.3 kg
Accessories:	Remote Commander type RMT-405 coaxial video cable
Manufacturer: RRP:	Sony Corporation, Japan \$1899 (anticipated)



## **Louis Challis**

Philips at Eindhoven and has been aptly named the Automatic Track Finding (ATF) system. It works on the basis of recording each one of the four pilot signals ( $f_1$  to  $f_4$ ) side by side on each video track. The  $f_1$  signal is recorded by the Channel 1 (CH1) head,  $f_2$  by CH2,  $f_3$  by CH1 and  $f_4$  by CH2 (see Figure 2). Thus  $f_1$  and  $f_3$  are recorded by the same head CH1, and  $f_2$  and  $f_4$  alternately by CH2. During playback the rotating video head detects the pilot signals on the adjacent track and compares the level of these signals.

There are several advantages of the ATF system. Firstly, because the conventional stationary CTL head is deleted, the need to provide highly accurate positioning of the CTL head relative to that of the rotating drum is avoided. Secondly, any expansion or contraction of the tape as a result of differential tensioning or thermal effects does not affect the tape tracking. Thirdly, the loading of the tape is simplified because the tape path mechanism is somewhat simpler. And, fourthly, the need for users to adjust tape tracking to take into account the differences between the playback machine and the recording machine are completely avoided.

Although the new hi-fi video (see ETI, November 1984) provides an excellent audio capability, the effective recording time is still limited to the basic video recording time. By contrast, the Video 8 system provides us with a brand new and dramatically expanded capability. We now have the option of either interleaving the PCM signal and a video signal with five-sixths of the time allocated to video and one-sixth to audio, or allocating all the recording time to the PCM audio, expanding audio recording time by six.

It can even be expanded by another 100% if you are prepared to use the LP (slow speed) mode. A P5-90 tape can provide an almost unbelievable 18 hours of stereo recording and playback in the LP mode or nine hours in the SP (standard play) mode. The only catch is that this requires six separate passes through the tape recorder (without turning the tape over) rather than being a continuous 18 hours non-stop recording. Obviously this may not be what you expected, but it isn't all that different from a multi-track recorder and the system can probably be expanded into a 12 track machine.

The CD system and earlier PCM adaptors used with VHS and Beta format VCRs incorporated 44.1 kHz sampling frequencies, however the designers of the 8 mm DAV system have elected to use a 31.25 kHz PCM sampling frequency. The resulting audio bandwidth capability of the Video 8 DAV PCM channels is consequently only 15 kHz. This limited bandwidth capability has been deliberately chosen to meet the primary audio requirements of TV. These conveniently place the audio bandwidth below the 16.25 kHz line sampling frequency, thereby avoiding interference problems. Notwithstanding its limitations, a 15 kHz bandwidth effectively covers more than 99% of the time-related usable audible bandwidth of classical or pop music and the perceived loss of audible content is almost inconsequential.

#### Appearance


The first impressions of the front panel of this unit are quite deceptive for, although it looks like a lamb, it is very much a 'wolf in sheep's clothing'.

The POWER ON/STANDBY switch is on the left hand side of the front panel. This surmounts a cassette EJECT button and a tiny headphone volume control. To the right is a very neat electronically activated, compact, loading cassette well. The cover requires the use of a very small eject button to open it. Immediately below the cassette well are five primary elongated control switches for REWIND, PLAY, FAST FORWARD, STOP and PAUSE. The pause button also provides a still picture during video playback. Each of these control switches is relatively small.

Adjacent to these are three very small pushbuttons. The first of these is STEP which provides a step-by-step playback picture in the playback pause mode. Next is a SLOW button which provides a one-fifth speed playback picture, and lastly a x2 button which provides a double speed playback picture.

At the top centre of the panel is the remote control sensor, below which is the record button which also activates a red indicator light to confirm that recording is taking place. On the extreme right hand side of the unit is the functional display panel which provides the following comprehensive data: whether or not multi-PCM recording is available and on which channel recording is taking place; the day of the week and time (in hours and minutes) as

ETI March 1986 - 23

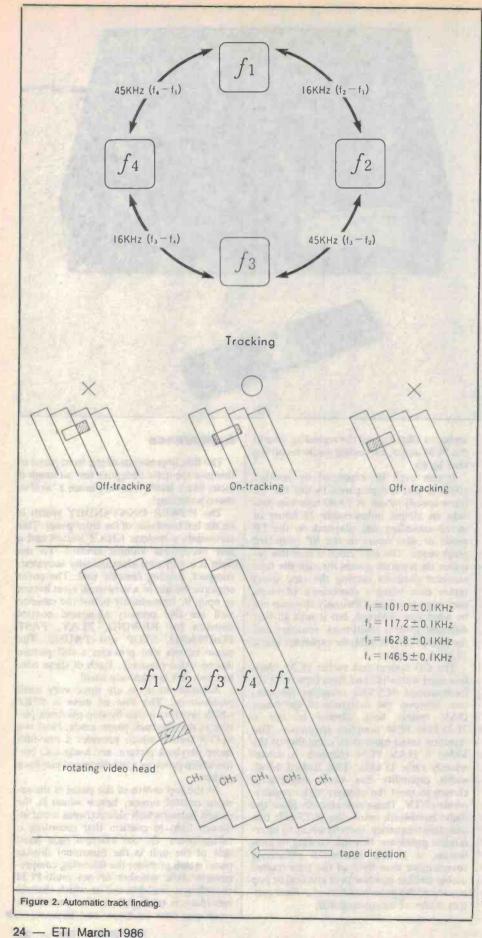

well as data on forward timing for turn-on and turn-off programming time, when requested; the peak level meter display for left and right channels covering -40 dB to +5 dB; information as to whether conventional stereo, bilingual or mono reception is taking place; which channel number has been selected; whether the input is from a tuner, line, simulcast or audio; and if the recording mode is standard play or long play.

The secondary controls include a FUNC-TION button which switches the display between COUNTER, TAPE REMAINING or CLOCK COUNTER, and other controls for the COUNTER RESET, for TV/VTR, and programming the channel number with switches labelled '+' and '-'.

At the bottom right hand portion of the front panel is a spring-loaded cover behind which are tertiary controls for selecting the clock reset, mode of play, PCM monitoring switches and input mode which selects inputs from tuner, line, simulcast or audio as well as the SP or LP modes. The audio monitor switches also provide for PCM monitoring of a tape which has been recorded with bilingual sound for FM simulcasts or monitoring an audio dubbed tape (either full PCM or standard track playback).

Adjacent to these controls is a switch for audio dubbing which, if pressed during playback pause mode, enables you to record music or commentary on the PCM track of a pre-recorded video tape. Immediately to the right is a recording level control which automatically sets the recording level if the two slide controls remain at the extreme left hand position and provides full attenuator controls. At the extreme right hand end of the flip-down panel are two 3.5 mm diameter tip and sleeve sockets which cater for inputs from external low impedance microphones.

On top of the recorder is a small plastic cover behind which are a series of video controls. The first of these is a small screwdriver slot, which allows you to stabilise still pictures. The second is the AFT switch, which is normally set to ON and facilitates automatic fine tuning to lock-in and maintain a sharp picture. The third is a SEARCH ON/OFF button which has to be activated to preset each of the numbered tuner channels. The fourth is a clear button which allows you to erase the preset station information. The fifth is an auto-stereo ON/OFF switch which is normally set to ON; during stereo broadcasts the reception is automatically set to stereo. The sixth is a sharpness control to adjust the clarity of picture, while the seventh is a pair of tuning buttons. Once pressed, these automatically search up or down in frequency for the next TV station carrier frequency.

The rear, sides and underneath of the

cover and chassis are slotted to allow adequate ventilation for the copious quantity of circuitry within. The rear panel contains a pair of video 75 ohm sockets for aerial input and output, but unlike other VCRs does not provide BNC sockets for connection to a video monitor. Instead it contains a 21-pin Euroconnector which greatly simplifies this task. Four RCA coaxial sockets are provided for left/right channel inputs and outputs, and two small switches provide for test signal generation as well as for local or DX video reception.

The remote control is slim, neat and effective. It provides direct channel changes for up to 30 preset TV channels as well as control of the primary deck functions, record functions, still picture, STEP and x2. It operates well at distances of up to 10 metres and over angles of  $\pm 30^{\circ}$ .

Although the description of these features may seem superfluous when our interest is in the audio capabilities of the recorder, they nonetheless provide you with useful information on the total capabilities of this feature-packed recorder. More significantly, prior to using the unit for audio recording, you have to be fully aware of the controls and their multi-functional uses.

The handbook for the VCR contains 34 pages of relatively complex and detailed instructions, but the service manual (which Sony fortunately provided) proved to be a veritable textbook with 274 pages of circuit diagrams and disassembly instructions. With a piece of equipment as complex as this, the servicing instructions obviously have to be very comprehensive.

#### **Objective testing**

The objective testing of the digital audio section of the unit proved to be quite straightforward. When recording a continuous sweep of 0 VU in the SP mode, which the handbook advises is the maximum recording level, the pre-emphasis circuit results in an observable non-linearity over the frequency range 5 kHz to 15 kHz.

When the sweep is recorded at -6 dB this characteristic disappears and you are left with a signal which is particularly smooth and better than  $\pm 2 \text{ dB}$  from 20 Hz to 20 kHz. This characteristic remains unchanged all the way down to -80 dB where noise affects the measurements. The low frequency record-to-replay characteristics of the recorder are particularly interesting as the recorder does not display any trace of the non-linearity of a conventional magnetic tape recorder and the low frequency response is remarkably smooth. At 10 Hz the frequency response is 10 dB down and at 5 Hz the response is 20 dB down.

The LP mode frequency response does not change from that measured in the SP mode and is still 20 Hz to 15 kHz  $\pm 2$  dB with a linearity which is still almost ruler flat.

I carefully checked the linearity between 0 dB and -90 dB which proved to be better than I have measured on typical CD players, particularly over the range -60 to -90 dB. This good result correlated reasonably well with the measured distortion figures of less than 0.5% all the way through to approximately -60 dB but which rise rapidly thereafter. At the lowest levels the distortion products are still well below the noise and generally inconsequential.

The measured signal-to-noise ratio of the unit relative to 0 dB is 78 dB unweighted and -88.5 dB(A) [Sony, it should be noted, quotes a figure of -88 dB(A)]. This dynamic range effectively cuts out the requirement to adjust volume controls for more than 70% of all typical recording situations.


The measurement of the wow and flutter proved to be a very difficult task and all that we could confirm in the end was that they are both most certainly less than 0.005% rms quoted in the specification sheet.


The cross-talk between Channel A and Channel B is -111 dB at 1 kHz, -58.4 dBat 10 kHz and -86.9 dB at 100 Hz, which is excellent. The erasure ratio at 1 kHz is -117 dB which is also excellent.


I carried out one supplementary test to measure the replay linearity using a 1 kHz signal recorded at -60 dB. This was intended to determine whether the unit exhibits any measurable drop-out or other nasty drift characteristics. Far from it; if one ignores the small and inconsequential level of superimposed noise, it is clear that the output is rock-steady and substantially better than that provided by any conventional magnetic tape recorder.

Taken overall, the objective test results proved to be outstanding and fully in keeping with what I would expect from a PCM digital recorder.

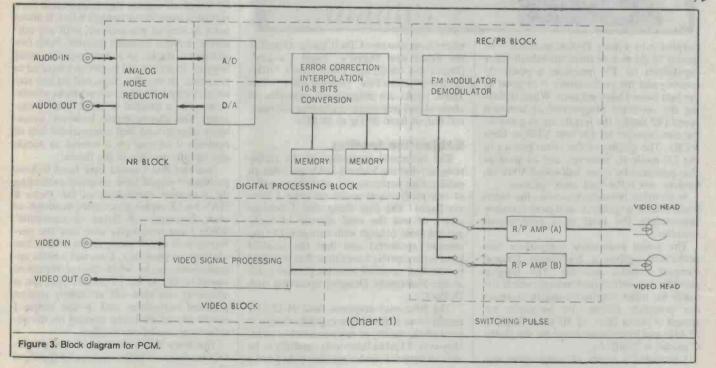Because the Video 8 DAV recorder had to be evaluated at home I decided to check its video performance before starting the audio performance evaluation. I directly



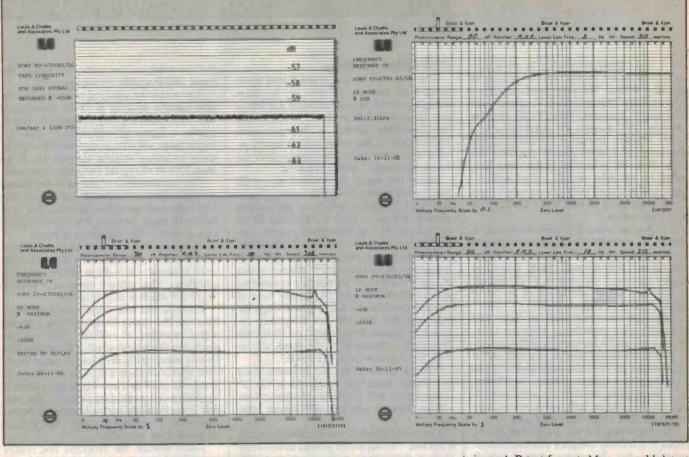

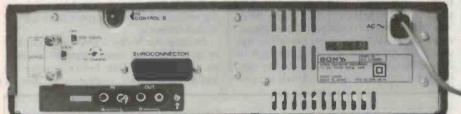

coupled it to a Sony Profeel monitor. The quality of the picture using the inbuilt tuner capabilities for TV reception is positively exciting and the performance is as good as the best tuner I have yet seen. When replaying the recorded programme at standard speed (SP mode) the results are as good as, but not superior to, the best VHS or Beta VCRs. The quality of the video picture in the LP mode is, however, not as good as that provided by other half-speed VHS recorders, nor is the 'still mode' picture.

In all other respects, however, the video performance is 'grade A' and most certainly approaching the level of a professional recorder.

The audio evaluation comparison was performed against a Nakamichi Dragon compact cassette recorder. The Dragon provides a quality of performance which virtually no other compact cassette recorder can presently eclipse. Its frequency response is better than  $\pm 2$  dB from 10 Hz to 23 kHz and its dynamic range (in the Dolby C mode) is 78 dB(A).

I recorded a series of programme seg-

26 - ETI March 1986

ments from two new CDs (Charles Dutoit in the Franz von Suppé's "Light Cavalry" (Decca 414 408-2) and Elton John's "Nikita" from "Ice on Fire" (Rocket 826 213-2)). These tracks are magnificent examples of classical and pop music containing full spectral output from 20 Hz to 19 kHz.

#### **Subjective testing**

The subjective evaluation of the replay revealed that the Video 8 DAV provides an exhilarating performance, almost the equal of any professional audio recorder I have yet heard. The first thing that I became aware of was the *total absence* of background noise (except with ears glued to the monitor speakers) and that the residual level is perceptibly lower than that provided by the best compact cassette players (such as the Nakamichi Dragon) operating with Dolby C.

The frequency response limit of 15 kHz results in an almost imperceptible change in the audible quality of some musical content. However, I had to listen very carefully to be able to detect it, and even then it had to be in an A-B test format. My son could detect the difference more readily than I could (ah — such is youth).

The point that most impressed me was that I could record a straight two-hour track of superlative music on a P5-60 cassette without having to turn the tape over. With a P5-90 (which was not supplied) I could have recorded three hours straight which is about twice as long as you achieve, with any reliability, using a compact cassette. With five additional tracks to record on, the mind boggles. In theory, if I had been prepared to re-record all my disc, tape and record material, I could readily convert stacks of software on to a handful of small Video 8 cassettes. This change would, however, necessitate copious and well documented lists of contents if anyone ever wanted to access any specific number in the future.

One test that I would have liked to have performed would have involved evaluating the long-term capabilities of the Video 8 DAV on LP replay mode after hundreds or even thousands of hours of operation. While I am reasonably sure that the performance in the SP mode would remain free of drop-out problems, I am still a trifle apprehensive as to what the performance would be like in the LP mode. That test is obviously one that will ultimately require practical evaluation, and in due course I would appreciate being advised on the results from one of our readers.

The Sony Video 8 DAV is a truly fabulous machine. It offers a range of technical

## **SIGHT & SOUND REVIEW**

capabilities which almost border on the sublime. Had the designers chosen a higher sampling frequency, every small amateur and professional studio would have rushed out to buy one (or more). As it happens, the more limited frequency response does not really justify any technical condemnation because virtually all of the material likely to be recorded in real situations contains so little by way of practical information above 15 kHz. In the end, I suspect more people are likely to buy the EV-S700ES for its digital audio than those who buy it for its far from basic VCR capabilities.

## MEASURED PERFORMANCE OF SONY EV-S700ES VIDEO 8 DIGITAL AUDIO VIDEO CASSETTE RECORDER Serial No. FTZ 24/585 SE/K

Measured Frequency Response (independent of level except in the range 0 VU to -6 VU where pre-emphasis affects the frequency response) LP and SP mode - 20 Hz to 15 kHz +2 dB.

#### LINEARITY (SP mode)

INPUT LEVEL dB	OUTPUT LEVEL o
	States and States in the
0.0	0.0
-1.0	-1.0
-2.0	-2.0
-3.0	-3.0
-6.0	-6.0
-10.0	-10.0
-20.0	-20.1
-30.0	-30.1
-40.0	-40.1
-50.0	-49.7
-60.0	-59.5
-70.0	-69.4
-80.0	-79.1
-90.0	-88.8

#### DISTORTION @ I kHz (SP mode)

Input Level	2nd	3rd	4th	5th	%
0.0	-58.3	-71.8		-	0.12
-3.0	-		-69.0	_	0.035
-6.0	-65.8		-66.3	-67.2	0.083
-10.0	-57.1	-62.9	-	-	0.16
-20.0	-53.6	-65.3	2.1		0.22
-30.0)					
-40.0)	Disto	ortion compo	ments helow	noise thre	shold
-50.0)			Seren Seren	noise une	.5110101
-60.0	-	- 1	-44.9	1.1	0.57
-70.0	_	-	-35.1	-	1.76
-80.0		11-11-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-	-23.5	1	6.7
-90.0	and the second	_	-14.7		18.4
the state of the s					
SIGNAL TO NOISE I	RATIO re	OdB @ IkH	z: 79.0 d	B (Lin)	88.5 dB(A)
ERASURE RATIO					
(for 1 kHz signal reco	orded at 0	VU)	-117 d	В	
and the second second					
CROSSTALK					
Channel A into Chan	inel B	@ 100 Hz	-86.9	dB	
	(	a l kHz	-111 d	В	
	(	ð 10 kHz	-58.4 (	dB	

**ETI READER SERVICE 127** 



## 65XXX — 68000 SAVE \$\$\$\$

6500 SERIES	DISPLAY
R6502P 8.50	CONTROLLERS
R6502AP 9.28	10937P-50 11.02
R6503AP 7 24	10951P-50 11.02
R6504AP	10938P 9.44
R6505AP 7.24	10939P 9.44
R6507AP 7.24	10941P 9.44
R6511Q 21.26	10941P 9.44
R6511AQ 23.28	10942P
	10943P 9.44
R6520P 5.19	16 BIT 68000
R6520AP 5.98	SERIES I.C.'s
R6522P 6.77	R68000C10 69.24
R6522AP 7.55	R68000Q10 33.04
R6532P 9.44	R68465P 16.52
R6532AP 10.39	R68C552P 27.07
R6541Q 19.17	R68561P 58.22 R68802P 61.37
R6541AQ 21.09	R68802P 61.37
R6545-1P 9.13	MEMORY I.C.'s
R6545-1AP 10.70	2114 1.35
R6545AP 12.27	4116 2.65
R6549P 60.58 R6551P 9.91	4164 1.35
R6551P 9.91	41256 6.67
R6551AP 10.70	6116 7.18
	6264 20.26
CHOC DEVICES	2716 4.81
CMOS DEVICES	2732 POA
R65CO2P1 10.39	2764 3.18
R65CO2P2 11.80	27128 5.75
R65C102P1 10.39	CRYSTALS
R65C102P2 11.80	32.768KHZ-CMOS
R65C21P1 5.82	Calendar 1.96
R65C21P2 6.77	1.8432MHz 3.08
R65C22P1 7.71	2.000MHz 3.08
R65C24P1 6.61	2.4576MHz 1.96
R65C24P2 7.71	3.6864MHz 1.96
R65C51P1 12.27 R65C51P2 13.53	4.000MHz 1.96
	4.9152MHz 2.80
R65C52P1 22.03	8.0000MHz 1.96
R65C52P2 24.86	12.000MHz 1.96
	Quip Socket
HIGH LEVEL	for 865110
HIGH LEVEL	for R6511Q, R680000 R65512
LANGUAGE	R68000Q, R65F12,
LANGUAGE CIRCUITS	R68000Q, R65F12, Modem I.C 3.12
LANGUAGE CIRCUITS R65F11P 32.42	R68000Q, R65F12, Modem I.C 3.12 PROTOTYPING
LANGUAGE CIRCUITS R65F11P	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33 R65F12AQ 46.58	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33 R65F12Q 46.58 R65FR1P 97.25	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65R12P 97.25	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65R712P 97.25	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25	R680000, R65F12,           Modem I.C.         3.12           PROTOTYPING           CIRCUITS —           Emulators for Mask           Programmable I.C.'s           R6500/1EAB3         69.24           R65/11EAB         69.24           R65/41EAB         69.24
LANGUAGE CIRCUITS R65F11P 32.42 R65F12A 42.33 R65F12A 46.58 R65FR1P 97.25 R65FR2P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212M	R68000Q, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FK2P 10.70 MODE R1212M R1212M	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F120 42.33 R65F120 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212M R1212DS R2424M	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12Q 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FK2P 10.70 MODE R1212M R1212M	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F120 42.33 R65F120 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR4P 10.70 MODE R1212M R1212DS R1212DS R2424M R2424DS	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F120 42.33 R65F120 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212M R1212DS R2424M	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR4P 10.70 MODE R1212M R1212DS R1212DS R2424M R2424DS Please includ	R680000, R65F12,           Modem I.C.         3.12           PROTOTYPING           CIRCUITS —           Emulators for Mask           Programmable I.C.'s           R6500/1EAB3         69.24           R65/11EB2         62.94           R65/11EAB         69.24           R65/200         267.51           S90.22         361.93           de         \$6.50         for
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR4P 10.70 MODE R1212M R1212DS R1212DS R2424M R2424DS Please includ	R680000, R65F12, Modem I.C
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR4P 10.70 MODE R1212M R1212DS R1212DS R2424M R2424DS	R680000, R65F12,           Modem I.C.         3.12           PROTOTYPING           CIRCUITS —           Emulators for Mask           Programmable I.C.'s           R6500/1EAB3         69.24           R65/11EB2         62.94           R65/11EAB         69.24           R65/200         267.51           S90.22         361.93           de         \$6.50         for
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R65001EAB3 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR4P 10.70 MODE R1212M R1212DS R1212DS R2424M R2424DS	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R65001EAB3 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R65001EAB3 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R1212DS R2424DS Please incluc packaging All prices incl	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 69.24 R65/11EA3 69.24 R65/11EA3 69.24 R65/11EA3 69.24 R65/11EA5 69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R1212DS R2424DS Please incluc packaging All prices incl	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 69.24 R65/11EA3 69.24 R65/11EA3 69.24 R65/11EA3 69.24 R65/11EA5 69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR3P 97.25	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB369.24 R65/11EB262.94 R65/11EAB69.24 R65/11EAB69.24 R65/11EAB69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax to alteration
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R1212DS R2424DS Please incluc packaging All prices incl	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB369.24 R65/11EB262.94 R65/11EAB69.24 R65/11EAB69.24 R65/11EAB69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax to alteration
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212DS R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212DS R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212DS R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12A0 46.58 R65F12A0 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R2424DS Please incluce packaging All prices incl Prices subject without ne	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 69.24 R65/11EA3 69.24 R65/11EA
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12A0 46.58 R65F12A0 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R2424DS Please incluce packaging All prices incl Prices subject without ne	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 69.24 R65/11EA3 69.24 R65/11EA
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 42.33 R65F12AQ 46.58 R65FR1P 97.25 R65FR2P 97.25 R65FR2P 97.25 R65FR2P 10.70 MODE R1212DS R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 69.24 R65/11EA3 69.24 R65/11EA
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR2P 10.70 MODU R12120M R12120M R12120S R2424M R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EB2 62.94 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax to alteration otification
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no CONTRO 73 Eric Street, 0	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 62.94 R65/11EA3 69.24 R65/11EA3 .
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AQ 46.58 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR1P 97.25 R65FR2P 10.70 MODU R12120M R12120M R12120S R2424M R2424DS Please includ packaging All prices incl Prices subject without no	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EA2 62.94 R65/11EA3 69.24 R65/11EA3 .
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R2424DS Please includ packaging All prices incl Prices subject without no CONTRO 73 Eric Street, 0	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 R65/11EAB 69.24 EMS 358.05 267.51 590.22 361.93 de \$6.50 for and freight Ude sales tax to alteration otification FOULD Goodna Q 4300 Goodna Q 4300
LANGUAGE CIRCUITS R65F11P 32.42 R65F11AP 35.72 R65F12AO 46.58 R65F12AO 46.58 R65FR1P 97.25 R65FR3P 97.25 R65FR3P 97.25 R65FR3P 10.70 MODE R1212M R1212DS R1212DS R2424DS Please incluce packaging All prices incl Prices subject without new CONTRO 73 Eric Street, C P.O. Box 6502,	R680000, R65F12, Modem I.C. 3.12 PROTOTYPING CIRCUITS — Emulators for Mask Programmable I.C.'s R6500/1EAB3 69.24 R65/11EAB69.24 R65/11EAB69.24 R65/11EAB69.24 R65/11EAB69.24 Emulators for Mask S90.22 361.93 de \$6.50 for and freight Ude sales tax to alteration Diffication COUD Goodna Q 4300 Goodna Q 4300 Goodna Q 4300 Coodna Q 430

## Check our test equipment range! Suitable for schools, OEM's, manufacturers, etc.

## HUNG CHANG (RITRON) 20 MHz **DUAL TRACE OSCILLOSCOPE**

•Wide bandwidth and high sensitivity Internal graticule rectangular bright CRT Built in component tester Front panel trace rotater •TV video sync filter •Z axis (Intensity modulation) •High sensitivity X-Y mode Very low power consumption Regulated power supply circuit

COMPONENT TESTER is the special circuit with which a single component or components in circuit can be easily tested. The display shows faults of components, size of a component value, and characteristics of components. This feature Is ideal to troubleshoot solid state circuits and components with no circuit power. Testing signal (AC Max 2 mA) is supplied from the COMPONENT TEST IN terminal and the result of the test is fed back to the scope through the same test lead wire at the same time.

#### CRT

CRT: 6" (150mm) Flat-laced high brightness CRT with Internal Graticule, Effective display area: 8 x 10 div (1 div = 10 mm) Acceleration potential; 2KV

#### VERTICAL

Operating Modes: CH-A, CH-B, DUAL, ADD (CH-B can be inverted.) Dual modes: Alter: 0.2ufs - 0.5ms/div. Chop: tms - 0.5s/div. CHOP frequency 200KHz approximately. Deflection factor: 5mV/div 20V/div -/ - 3%, 12 ranges in 1-2-5 step with fine

control. Bandwidth: DC; DC - 20MHz (-3dB), AC; 10Hz - 20MHz - 3dB), Rije Time; Less than 17ns, Overshoot; Less than 3%, Input Impedance; 1M ohm +/-5%, 20pF +/-3pF Maximum Input Voltage; 500Vp-p or 300V (DC + AC Peek) Channel Isolation; Belier than 60 dB at 1KHz.

HORIZONTAL Sweep Modes: NORMAL, and AUTO Time Base: 0.2uls - 0.5s/div +/-3%, 20 ranges in 1-2-5 step with line control. Sweep Magnifier: 5 times (5X MAG). Linearity: 3%.

TRIGGERING Senaltivity: INTERNAL: 1 div or better for 20Hz - 20MHz (Triggerable to more than 300Hz): EXTERNAL: 1Vp-p or better for DC - 20MHz (Triggerable to more then 20 MHz)

than 30MHz) EXTERNAL: 1Vp-p or befter for DC - 20MHz (Triggerable to more than 30MHz) Sources (INT, CH-A, CH-B, LINE and EXT Sources (INT, CH-A, CH-B, LINE and EXT Stope: Positive and Negative, continuosity vanable with level control PULL AU D) for free-run. Coupling: AC, HF-REJ and TV, TV SYNC Venical and Horizontal Sync Sources (INT, CH-RE) and TV, TV SYNC Venical and Horizontal Sync Sources (INT, CH-RE) and TV, TV SYNC Venical and Horizontal Sync Switched automatically by SWEEP TIME (INT) Video waveform to be switched automatically by SWEEP TIME (INT) Video Waveform (INT) TV-V (5stidit to 0, Insidiv TV-H 50ute/div to 0 2ufsidiv,

X-Y OPERATIONS X-Y Operations: CH-A: Y axis CH-B: X axis Highest Sensitivity: 5mV/div. COMPONENT TESTER

Component Tester: Max AC 9V a when the terminal is shorted, (Inter the terminal with no load. Max current 2mA

## OTHER SPECIFICATIONS

CHIEFIC SECURICATIONS Intensity Modulation: TL LEVEL (3V-p); Postive ......brighter. BANDWIDTH; DC - 1MHz MAXIMUM INPUT VOLTAGE: 50V (DC + AC Peak) Calibration Voltage: 0.5Vp.p.+/-5%, 1KHz +/-5% Square wave. Trace Rotation:Electrically adjustable on the front panel. Power Requirements: AC; 100, 120, 220, 240V 20W Weight: Tig approximately Size: 162(H) x 294(W) x 352(D)mm

Cat. Q12105

Cat. Q11040

#### ..... only \$695 (tax exempt only \$595)

Bulk orders, schools, please phone (03) 543 2166 for special low pricing.



## 605 3<sup>1</sup>/2 DIGIT MULTIMETER

(New replacement for YF1100) \$79.95 Cat. Q11035 .....

C API	tage	605	705A		
Range	Resolution	Acc	CUTBE J	Input impodence	Overland Protection
200mV	100#V				
28	1m¥	050-1			1.000
201	10m¥	0311-1	A20.7		1000V DC geen AC
200v	100m7			on all ranges	on all ranges
1000v	14	0.8% - 1	0811-1		
C Vol	tøge	805	7054		
Range	Resolution	Accuracy		Input Impodence	Overteed Protection
200mV	100,00				7507 Ims on 44
23	Imt		14.0	108HI on all	ranges except
20v	10mv	10.00	14.0	ranges Cabecitance	200mV AC -anges
2004	100mV			100007	15 seconds max
7904	Lv	25-4	21- 0		above 2500 ms AC
oc cu	etent	605	705A		71 . C . 84
Range	Resolution	Acci	elac.y	Burden Vorlage	Overtees Protection
200 p A	100mA	NC.			
2mā	3 jar A			-	7054 0 24 fuse up
20m-A	10.0 A	1111	1==1	034 mas	to 2504
200mA	100 mA				605 2A fuse up
2000m.d	ima	156-1	HC.	- 1-0	10A range not fused
10.6	10m.6	15-1	14-1	0.7¥ más	

## 705A 31/2 DIGIT **MULTI/CAPACITANCE** METER

\$119

**5A SPECIFICATIONS** AC Current NC LpA 605 24 tuse up 10 25CV range not 100-07 14-2-14-2 290V DC rms 164 3.54 LOV 0.254 00% -0.014 -108.0 24. - 5

Renge	Resolution	Accuracy		Test Signal	Nex Yest	
210	1pf			400m5 rms		
20m	10pf			-		
200rd	100pf	HC	394 - 6	512 44	34 DC peek AC on all ranges	
2000+1	Inf -		1.1	40m¥ 1ms	an an ranges	
20#1	10+0					

## ANALOG WORKHORSE KT370

Includes two free

probes!

2 months

warranty

ST CONTOATIONS	
Ranges:	
DC Voltage: C - 0.1, 0.5, 2.5, 10, 50, 250, 1000V (20k ohm/V)	1
AC Voltage: 0- 10, 50, 250, 500V, 1000V (8k ohm/V)	1
DC Current: 0- 0.05, (50uA), 2.5, 25, 250mA	
Posisianos 0 2K 20K 214 0014 chm	
Resistance: 0-2K, 20K, 2M, 20M ohm	
Load Current: 0- 150uA, 15mA, 150mA	
Load Voltage: 0- 3V	
Volume Level: - 10 -+ 22dB -+ 62dB	
DC Current Amplification Factor (hFE) 0- 1000	
ACCURACY	
DC Voltage & Current: Within +/-3% f.s.	
AC Voltage: Within +/-4% f.s.	
Resistance: Within +/-3% of arc.	
Battery: 1.5V (um-3) 2pcs. 9V (006p) 1pc.	
Fuse: 0.5A, 50 x 20mm	
Diode: 4148 x 2	
C.C. ,04uff x 50V	
Size & Weight: 147 x 99x 57mm & 400g approx.	
"The same type as I have carried in my toolbox since I started I	in
electronics 15 years ago."	
- Rod Irvin	
Cat, Q11030 \$27.9	15

FEATURES: • Fuse and diode protection

• hFE measurements 0 - 1000 (by x 10 range) Mirror scale for more accurate reading

#### SPECIFICATIONS

# NEW! NEW! NEW! NEW! an entire page full of NEW products! from Rod Irving Electronics!



#### CODE KEY PAD

- Telephone type digital keypad. our digit, changeable code over 5000 possible combinations ower consumption: 5mA standby
- Power consumption: 5mA standby 50mA alarm. Two sector LED and 1 arm LED. Wrong number lockout 12V DC operation. Relay output. Panic button.

- Panic button.
   Normally open tamper switch
   Dimensions: 145 x 100 x 37mm
   ACP3 compatible.



#### BURGULAR ALARM CONTROL PANEL

CONTROL PANEL A complete sit sector alarm control panel suitable for both commercial and residential use. Has all the features of larger units in a compact tamper proof metal cabinet. Inbuilt 240V - 50Hz power supply. • Armed and Disarmed with digital keypad. • Six independent supervised zone inputs.

- Will accept N/O or N/C sensors. Each is supervised with end of line

- Each is supervised with end of line resistor
   LED Indicator for each sector plus LED indicators for zone violation.
   May be either delayed or instant
   Separate zones may be disabled for service etc.
   Two 24 hour zones One is N/D for panc or fire alarm, the other is N/C for motion detector or siren box.
   Both are supervised with end of line resistors.
- Built-in Anti tamper switches
   N/C tamper switch on front and
- Audible alarm status indicator.
   Internal buzzer sounds for exit/
- Built-in siten driver output circuit,
   External horns have wire cut

- External horns have write cut protection
   Relay outputs.
   Timing relay dry contact output (SPDT).
   Timing relay 12V DC output.
   SoomA
   Regulated 12V DC output
   (and maximum) for passive or active detectors. Short circuit protection
- Backup battery circuit. Automatically charges backup
- Automatically charges backup battery.
   Built in test switch enables the sensors etc., to be tested without causing the strens to go off
   Phase II continual protection except for 24 hour zone.
   LCD indication of mains failure.
   LCD indication of anians failure.
   National or 270 x 80mm.
   National or 200 x 80mm.

\$269 Cal. S13013



**FELECOMMUNICATIONS** AUSTRALIAN TO U.S. ADAPTOR CABLE Australian socket to U.S plug
 Length 5 metres. \$7.95 Cal. ¥16017



## SPEAKER SYSTEM Designed specifically for compact disc. Excellent bass response to

Designed specifically for compact disc. Excellent bass response to fully utilize the output capabilities of a compact disc. 16° ingh, woodgrain finish cabinet with brown cloth grille. SPECIFICATONS: Speckers: Woolers of 1/2° carbon tiber emflored polypropylenc cone 10oz magnet. Tweeter 1° soft dome 6oz damped with ferro fluid. Power Input: 40 waits rms 85dB wim Impedance: 8 dnms Stat: 250 x 400 x 240mm Stat: 250 x 400 x 240mm Carbon Cone States States States 250 x 400 x 240mm Carbon Cone States States 250 x 400 x 240mm Carbon Cone States States 250 x 400 x 240mm Carbon Cone States States 250 x 400 x 240mm Carbon Cone States States States 250 x 400 x 240mm Carbon Cone States States 250 x 400 x 240mm Carbon Cone States States States 250 x 400 x 240mm Carbon Cone States States States 250 x 400 x 240mm Carbon Cone States States States 250 x 400 x 240mm Carbon Cone States States States States States 250 x 400 x 240mm Carbon Cone States St



## 2 WAY MINI BOOKSHELF SYSTEM

BOOKSHELF SYSTEM Designed specifically for compact dystem offex and basile and on performance for its size (9.5"). Woodgran canner allows it to stort with any audio or wideo system. SPECIFICATIONS: Speckers: Wooler 4" carbon fore-reinforced polyropythen cone 10oz magnet. Tweeter 1" soft soms com agnet, damped with there fluid. Power input: 30 watts rms 82dB with Impedance: 8 ohms Frequency response: 80-20.00Hz Jale: 150 z 420 x 160mm (AVALABLE MAL ONDER ONLY) Cat. C1070 \$179

\$179 Cat. C10760



## ARLEC "DISCO LITE" CONTROLLER

ave your parties a professional ouch with the arlec "Disco Lite" imply plug your light(s) into the Disco Lite" and you've instant party

If et 3 DIFFERENT MODES! Music Mode: Place the "Disco Lite" in range of the speakers and it flashes the lights to the beat of the

music! Strobe Mode: Simply adjust to desired speed! Great for mime or theatre! The christmas season or

advertising! Dim Mode: Allows you to dim the lights to create moods, effects etc.

\$49.50 Cat M22003



TELECOMMUNICATIONS AUSTRALIAN STYLE ADAPTOR CABLE Australian socket to plug/socket
 Length 10 metres Cat ¥16015 \$15.95



## WIRELESS INTERCOM

This quality 2 way handset type FM wrieless intercom, automatically calls the other phone the moment the handset is picked up. Simply plugs hind any 240V wall outlet and can be wall or bench mounted. Features LED indicators for itransmit and receive, and PLL. circuitry to 65 126km<sup>2</sup>. ensure reli 95,125kHz \$130 Cat #11506



OMNI-DIRECTIONAL WIRELESS MICROPHONE Tuneable: 92 - 104MHz Freq. Response: 50 - 15kHz Range: Over 300 feet in open field. Modulation: FM Power Source; 9V Battery Type: Electret Concenser. Dimenations: 185 x 27 x 38mm Weight: 160 grams

A10450 \$19.95



## CRYSTAL LOCKED WIRELESS MICROPHONE AND RECIEVER

MICROPHONE SPECIFICATIONS: Transmitting Frequency; 37, 1MHz Transmitting System; crystal oscillation Microphone: Electret condenser Power Supply: 9V battery Range: 300 feet in open field Dimensions: 165 x 27 x 38mm Weight: 160 grams

Weight: 160 grams RECIEVER SPECIFICATIONS: Recleving Freq; 37.1MHz Output Level; 30mV (maximum) Recleving System: Super heterodyne crystal oscillation. Power Suppity: 9V Battery or 9V DC power adgiter. Volume control Tuning LED Tuning LED imensions: 115 x 32 x 44mm (eight: 220 grams

\$89

Cat A10452



#### ECONOMY 4 CHANNEL MICROPHONE MIXER

- Its size and simplicity makes this mixer very portable and easy to
- SPECIFICATIONS:
- . 600 obm 4 low impedance 600 ohm microphone inputs,
  Individual gain control for each microphone

- Individual gan control for each microphone, microphone, experience control 
   Master volume control 
   Power on LED.
   Inputs/Outputs 6 3mm mono 
   Side of States, only, 
   Inputs/Outputs 6 3mm mono 
   Side of States, only, 
   Input impedance 6 560 ahm.
   Signahroise ratio 55d8.
   Frequency response 20Mx to 
   20M/Mx plus or minus 2d8.
   Weight 320 grams.
   Dimension 148 x 46 x 86mm.
   Torque variable range 1-22d8 
   Input sensitivity 1mV.
   Output imped Som (3 angut 5 mV).
   Tirtup. 2015.
   Signahroise Som (3 angut 5 mV).
   Tirtup.
   Signahroise Som (3 angut 5 mV).
   Tirtup. 2015.
   Signahroise Som (3 angut 5 mV).
   Tirtup.
   Signahroise Som (3 angut 5 mV).
   Tirtup.
   Signahroise Som (3 angut 5 mV).
   Tirtup.
   Signahroise Som (3 angut 5 mV).
   Signahroise Som (3

- Cat A12001 \$39.50



#### **3HR VIDEO TAPES** from only \$6.95! Rod Irving Electronics has made a sensational scoop purchase of quality Kyoto video tapes at unheard of prices! 25+ \$6.95 \$8.95 \$7.95

**INLINE SWITCHING BOX** 

\$32.95

\$59 95

19.51

\$295

\$25.95

\$24.95

25 pin "D" plug to 25 pi societ (RS232)
DIP switches allow easi switching of internal wiri Cat. P00000

COMPUTER LEAD

Length 2 metres.

LL.

IBM' COMPATIBLE

XT compatible mother boards 8 slots, room for 256K RAM

ARLEC ELECTRONIC

ARLEC ELECTRONIC DOOR CHIME 9 Quick easy Installation. 9 Variable tone control 9 "Ding. Dong" chime sound: 9 metre connecting wire and fraing screws 9 Runs approximately 12 months on one battery. 9 Uses 9 volt transistor battery (Not supplied) 2 yaar guarantee.

MOTHER BOARD

Cal. X18020

Cat. A11950

WIPER DELAY

Cat A15070

CONTROLLER AND LIGHT ON REMINDER • Tnggers If lights are left on and ignition is turned off. • Has both an audible and visible

Alas donnem.
 Allows windscreen wipers to be delayed for up to 20 seconds.
 Underdash or on dash mounting
 Designed for 12 voit negative earth electrical systems.
 Complete with mounting hardware \$24.9

Cat P19031

• 25 pin "D" plug to 25 pin "D" plug (R5232) DIP switches in each plug allow many combinations of internal wing, making this a truly universal lead.
 • Mylar shiekting against RF interdemone.

RS232 DATA SWITCH WITH TESTER

• 25 pin RS232 "D" connectors 2 in

25 pin R523 °D" connectors 2 in, 1 out or 1 in, 2 out.
1 ideal for 2 computers to one peripherals
No power required.
Six dual coloured LED indicators showing certain flow status.
T.D. Transmit Data R.D. Recieve Data R.J. Recieve Data R.T.S. Request To Send C.T.S. Clear To Send D.T.R. Data Terminal Ready D.T.R. Data Terminal Ready
Housed in heavy duly metal cabinet.

Houseann nach cabinet.
 Size' 200(W)x68(H)x150(D)mm
 S149

CENTRONICS DATA

PC BOARD HOLDER

ROD IRVING ELECTRONICS

425 High Street, NORTHCOTE, 3070 VICTORIA, AUSTRALIA Phone (03) 489 8866 18 A "Becket St. MELBOURNE, 3000 VICTORIA, AUSTRALIA Ph. (03) 663 8151

Mall Order and correspondance P.O. Box 620, CLAYTON 3168 TELEX: AA 151938

MAIL ORDER HOTLINE (03) 543 7877 (2 lines)

\$50,595,995,995,57,50 \$700,190 \$77,50 \$700,1499 \$700,149

Card

Errors and Omissions Excepted

\$2.00 \$3.00 \$4.00 \$5.00 \$7.50 \$10.00 \$12.50

VISA

POSTAGE RATES \$1-\$9.99 \$10-\$24.99 \$25-\$49.99 \$50-\$99 99

Ù

Better than an extra pair o A must for all PCB work.

Cat T12442

Cat. X19115

SWITCH WITH TESTER

•36 pin gold plated female Centronics connectors. • All other specs as for RS232 Data Switch with Tester.

\$169

\$7.95



CHANNEL 28 TO CHANNEL 0 CONVERTER If your TV doesn't have UHF, don't despart With one of these high quality, specially made converters you can have Channel 28 UHF converted to Channel 0 VHF. Cat. L15052 \$129



## DIGITAL SPEEDO/ DIGITAL TACHO/ SPEED ALERT

- Digital readout (LED) for both tacho and speedo.
   Alarm with sound at variable preset speed.
   Audible beeper and visual
- Indicator. In built light indicator for night illumination.
- In burningen answer Burnination 2. volt negative earth electrical systems Speedo: 0. 1991kph Tachometer 0. 9900kph Speed aleri: 40. 120kph Complete with mounting hardware. Cat. A15064 \$69.50

## -------

CASIO FX702P BASIC PROGRAMMABLE POCKET COMPUTER

# Maximum steps: 1680 (26 memories) Maximum memory: 226 (80 steps) Alphabetical keyboard 19 digit display Comprehensive manual Detail recorrammune book

- Comprehensive management Detail programming book Dimensions: 166 x 82 x 18mm
- rotective pouch \$139

COMPUTEH •One Key Functions. • Owerty Keyboard. • 11 digit display • Dimensions 163 x 82 x 15mm • Protective pouch • Options. Character pinnler. Cassette interface, RAM card. \$159

CASIO FX720F PORTABLE PERSONAL COMPUTER

## SOUND REVIEW

# WHARFEDALE WOOS THE MARKET – with the model 708 loudspeaker

Wharfedale has adopted a fairly untypical British strategy to woo buyers of its quality speakers. It has attacked the problem of speaker cabinet cost and come up with a new material (among other changes) which it claims is significantly cheaper.



## Louis Challis

WHARFEDALE HAS BUILT up an enviable reputation for the design and construction of quality loudspeakers over the last 50 years, during which time it developed some of the finest speakers available in the United Kingdom. Its products have been marketed in many countries, and Australia used to constitute one of its more important markets.

Over the last few years Wharfedale speakers have not been marketed in Australia with quite the same enthusiasm as they were, a fact that should not necessarily be attributed to the local marketing people. The basic problem appears to be that Wharfedale, like all the other English and European manufacturers, has faced significant problems with rising costs, lower productivity and much more aggressive competition in all of its market places.

However, in response to these pressures, Wharfedale has come out with a new product line described in its glossy brochures as "the best thing since sliced bread".

## **Claims and designs**

One very significant problem which most speakers have is that the speaker cabinets are expensive to manufacture and their percentage of the cost is disproportionately high in cheaper speakers. Where the drivers are expensive you can readily justify an expensive cabinet, and consequently an expensive price tag. When the manufacturer is really trying to lower his costs, the speaker drivers are the first components to be pared down, but the cabinet soon follows.


As a consequence, the more innovative of the continental and Japanese manufacturers have resorted to special plastic or diecast mouldings which can result in dramatic reductions in manufacturing costs.

While many other manufacturers now claim to have overcome these problems, in practical terms, very few actually have. Most of Wharfedale's UK competition has devoted considerable time and most of its ingenuity to reducing the cost of drivers and
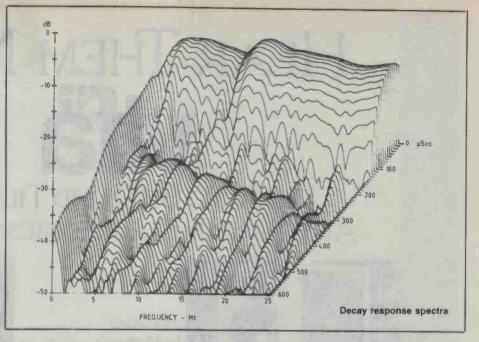
#### WHARFEDALE MODEL 708 LOUDSPEAKERS

Dimensions:

Manufacturer: RRP: 490 mm (high) x 250 mm (wide) x 225 mm (deep) Wharfedale Ltd, Leeds \$1500 (stands \$145 extra)



not nearly as much time on the cabinet design, which generally tends to be a critical element requiring much more effort in achieving a palatable solution.

Wharfedale, however, has not only reduced the cost of its drivers through the use of advanced diecasting techniques and the use of fancy ferrite magnet assemblies, but has developed an unusual technique to reduce the costs of its cabinets. This has been achieved through the use of a 'sandwich' construction in which two layers of melamine (laminex type material) are bonded to a polystyrene core which becomes 'the meat in that sandwich'. Wharfedale claims that this composite material is not only cheaper to manufacture and easier to machine, it is quicker in its assembly which thereby enables Wharfedale to market these speakers at half the price of its nearest competitor.

Such claims are most certainly 'eve-catching' but have to stand up to close scrutiny when the actual selling price is added to the equation. Amongst the attributes claimed for this composite sandwich material are that it is "lighter and more rigid than some of the most esoteric proprietary materials" available. Wharfedale also claims that it has used 'real' veneers and that the speaker has many other unusual attributes. It further claims that the new aluminium dome tweeter provides low distortion levels "with high sensitivity and relatively low cost" and that the "200 mm diameter mineral filled homopolymer polypropelene coned woof-er" is hand assembled in a "Build Ring" with "computer-assisted quality control"

Now, it is quite obvious that both the tweeter and woofer are unusual because of their bayonet mountings which have been carefully designed to match the complex cut-outs in the sandwich cabinet. This has been carefully planned so as to optimise the characteristics of the polystyrene which has a natural tendency to expand and thereby to achieve a tight fit in the cabinet.

With advertising like the above, one would reasonably expect a space-age design

with objective and subjective characteristics which put the system head and shoulders above all its competition. It has been my experience after more than 20 years of speaker testing and evaluation that cabinet stiffness when assessed in isolation is not the critical parameter which determines the quality of a loudspeaker's sound, but rather the combination of panel stiffness, effective damping and associated control of cabinet resonance. While Wharfedale's advertising agency would like us to belive that all you need is stiffness, stiffness without very high damping normally leads to a situation where you have one or more dominant resonant condition (or even multiple resonant conditions) and without mass normally leads to very low transmission loss characteristics.

My experimental work with testing polystyrene sandwich panels for their transmission loss has invariably shown that this material exhibits poor low frequency damping characteristics and nasty panel resonances at one or more points in the audible frequency range. Unless the speaker enclosure incorporates supplementary damping struts or added mass damping materials, the end result is normally poor and not necessarily what the designer intended. In the worst possible situation, a cabinet constructed with polystyrene sandwich structure can materially alter the overall speaker performance as a result of its re-radiation of multiple resonant frequency components that are both measurable and, more particularly, readily audible.

The 708 speaker does have other attributes including a printed circuit cross-over board, reasonable quality 4 mm binding posts and 52 strand copper wire for the internal connections. It also features a removable black mesh cloth speaker grille for which the adhesive velcro hook clips are provided on a separate piece of paper for the owner to apply him or herself (to save money). It is also available with optional speaker stands which appear to be heavier and more solid than the speakers themselves and sell for \$145.

#### **Objective testing**


The objective testing of this speaker soon revealed that in an anechoic test environment the frequency response is reasonably flat from 120 Hz through to 5 kHz at 1 m from the tweeter. The measured on-axis high frequency response is, however, relatively peaky, particularly in the 10 kHz region, and displays a general droop beyond 13 kHz. The bottom end frequency response is not particularly exciting and is about all that could be expected from a simple sealed enclosure with a 200 mm diameter low frequency driver installed in such a 27.5 litre cabinet.

When measured at 2 m on the tweeter axis, the response tends to be slightly more peaky than it was at 1 m, while the off-axis response is somewhat better. The underlying cause of this improvement is not easy to track down, particularly as the frequency response curves, which were performed on the first set of speakers we evaluated, do not correlate with the polar response curves which were measured on a second set.

The step in the frequency response between 40 Hz and 120 Hz would be materially improved in a residential situation by mounting the speakers on their supplementary stands. This improvement which results from floor reflections is one characteristic which is not readily assessed in our anechoic room but will be perceived by the user after careful placement of the speakers with respect to the rear and side walls.

The measured near-field frequency response at 5 cm from the woofer and tweeter confirmed that the tweeter response is reasonably good up to 16 kHz but is starting to droop fairly fast at higher frequencies. The phase response exhibits unusual characteristics in the 0 to 3 kHz region and these unu-
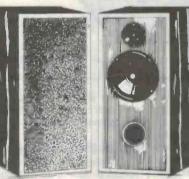
# HEAR THEM NOW! HEAR THEM NOW! HEAR THEM NOW! HEAR THEM NOW!



AEM-6102 \$680.00 pair

These two hot selling high performance kit speakers are now being demonstrated at the locations mentioned beneath. Hear for yourself how these speakers outperform well known fully imported speakers costing 2-3 times more. **How is it possible to get so much** 

## value for money?

Because these kit speakers don't suffer from the usual 25% import duty, no 30-35% freight cost into Australia, no costly freight expenses within Australia, no 30% sales tax on these cost factors and no profit margin added to all these links, which fully imported speakers suffer from.

## Isn't it difficult to build them?

Scan Audio, who is behind VIFA in Australia, has organized Australia-built x-overs, and professionally manufactured flat-pack cabinets to perform with David Tilbrook's specification. All you need is a simple toolbox, wood glue, soldering iron and some hours of your spare time—and you are the owner of a pair of Digital Monitors worth \$1500 or \$2500 respectively.

## What is the total price including cabinets?

Right, here are the prices all included: AEM-6102 2-way 8" PC-woofer **\$680.00 pair** AEM-6103 3-way 10" PC-woofer **\$1050.00 pair** 



## Who has the speakers on display?

The following hi-fi and electronic stores:

- VIC: Radioparts, 1097 Dandenong Rd, East Malvern Radioparts, 562 Spencer St., West Melbourne Footscray Audio, 142 Hopkins St., Footscray
- NSW: Hempel Sound, 455 Penshurst St., Roseville East Jaycar, 117 York St., Sydney Jaycar, 121 Forest Rd., Hurstville Hi-Fi House, Cnr. Crown/Corrimal St., Wollongong
- ACT: Duratone Hi-Fi, 3 Botany St., Phillip
- SA: Eagle Electronics, 55 Unley Rd., Unley International Sound, 11 Carrington St., Adelaide Miltronix, 125 Payneham Rd., St. Peters
- WA: Alberts Hi-Fi, 642 Albany Hwy, Victoria Park Alberts Hi-Fi, 396 Murray St., Perth
- QLD: Hando's Hi-Fi, 70 High St., Toowong Qld. Stereo/Visual Supply, Taigum Shp. Centre, Shop 28, Taigum
- TAS: Will's & Co., The Quadrant, Launceston Quantum Electronics, 194 Liverpool St., Hobart

**Scan**, Pike Lind **Scan**, Pike Lind **Solution For more information about speaker kits and reprints of the** 2 above mentioned speaker projects, please contact Sole Australian Distributor:

SCAN AUDIO PTY. LTD. 52 Crown St., Richmond 3122. Ph. (03) 429 2199.

32 - ETI March 1986

ETI READER SERVICE 116



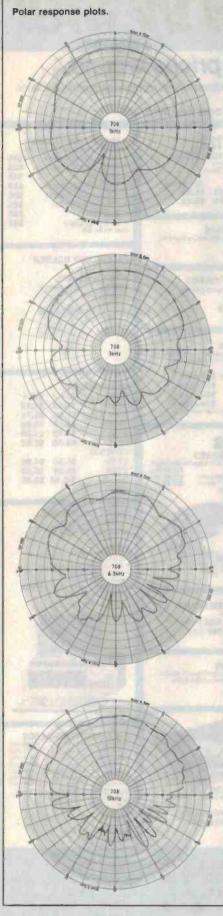
## That's right, we guarantee the lowest prices around.


Tell us the advertiser and price of any software or hardware item on this page currently advertised in any popular computer publication and we'll beat that price by \$10

This offer does not apply to items under \$100 or where the price is not lower than DataParts





34 - ETI March 1986

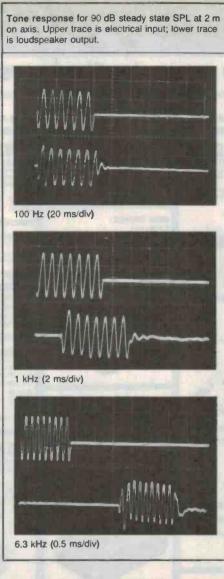

sual reversals are associated with the direct acoustical interaction between the drivers and the energy radiated by the cabinet. The tweeter, however, exhibits a particularly smooth phase response all the way up to 20 kHz. This tended to confirm that the polystyrene sandwich cabinet is stiff enough for high frequencies but not nearly good enough for the low frequency end of the spectrum.

The impedance characteristics of the speaker indicate that the energy transfer will not be as good as might be expected, primarily as a result of the rising impedance characteristics between 30 Hz and 90 Hz and between 500 Hz and 3 kHz, where the impedance rises to values as high as 25 ohms. In the 5 kHz to 20 kHz region, the impedance drops below 8 ohms to an acceptable low of 6 ohms.

The tone burst testing exhibits transient responses for both the mid-frequencies and high frequencies where the degree of tilt concerned me somewhat. This type of characteristic is normally associated with an audible component which my (and hopefully your) ears can usually detect. This shows up in the decay response spectra and this proved to be the case.


When subjected to the decay response spectra evaluation in our anechoic room, the Wharfedale 708 speaker exhibited some obvious and rather unusual resonance characteristics. These are readily observable at frequencies corresponding to ap-proximately 2 kHz, 3.5 kHz and 10 kHz. The lowest of these frequencies is a dominant resonance associated with the driver and cabinet and observable in the measured frequency response curves recorded at both 1 m and 2 m on axis. The 3.5 kHz resonant frequency characteristic is also readily observable on- and off-axis at 2 m while the 10 kHz resonant frequency is obviously the dominant resonant frequency of the tweeter diaphragm.

After the initial decay of the primary driver resonances, a large number of second order resonances are re-radiated by the speaker cabinet and these are not particularly well damped as the decay response spectra reveal. The broadband characteristics of these second order resonances are far

particular characteristic also normally



## SOUND REVIEW

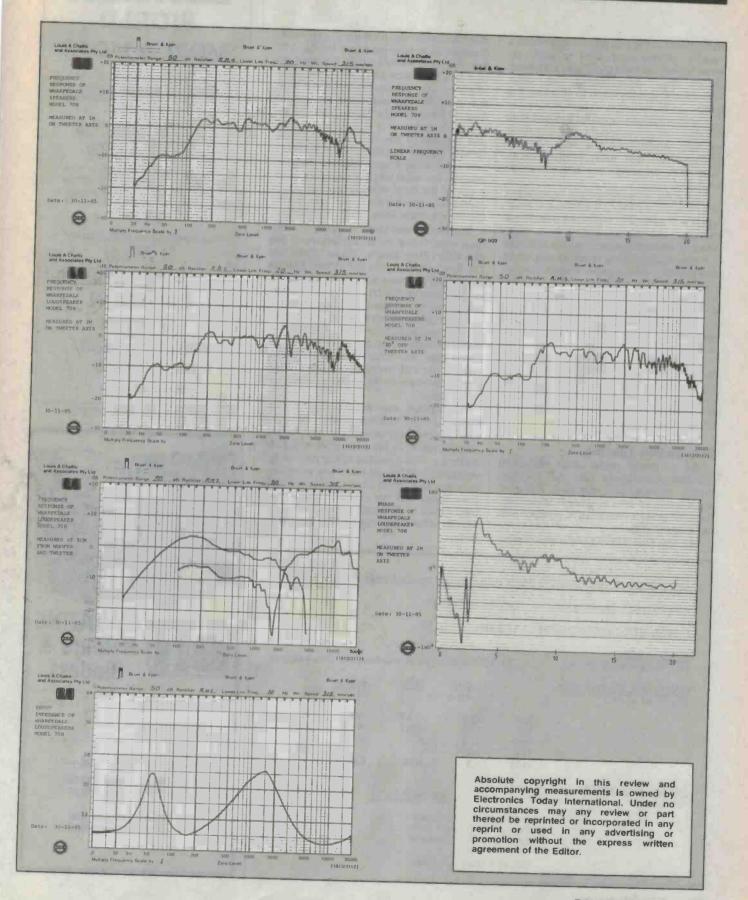

## SOUND REVIEW

more marked than one would expect from a 'quality speaker' and most certainly far more prominent than those that I have observed from measurements on other Wharfedale speakers during the last five years.

The overall impression that I gained from the decay response spectra was that these speakers would exhibit a very coloured response and that many musical instruments and, probably, speech would sound unnatural.

The polar response of the Wharfedale 708 speakers at 1 kHz is 3 dB down at  $\pm 40^{\circ}$ , which is considerably less than I would have expected; at 3 kHz it is 3 dB down at  $\pm 60^{\circ}$ , which is somewhat better. At 6.3 kHz, the response exhibited an unusual degree of non-linearity with a petal shaped primary response on-axis; a softening of the tweeter coil became evident in the response of the first set of speakers. At 10 kHz, the polar response was far more uniform and rather surprisingly extended to approximately  $\pm 50^{\circ}$ .

Taken overall, the objective performance characteristics of the Wharfedale 708 speakers was not as impressive as one might expect from the manufacturer's claims and not in keeping with a speaker system intended to sell at around \$1500 per pair.

## **Subjective testing**

The subjective performance evaluation revealed immediately that the low frequency response was very poor and even when mounted on the speaker stands still failed to provide an effective acoustic output below 100 Hz.

The first selection of programme content

that I evaluated was a special live recording demonstration tape produced by the ABC from the Bob Hudson Show. I played this tape on a Nakamichi Dragon cassette player which provides a frequency response which is remarkably flat and better than ±2 dB from 20 Hz to 20 kHz. The quality and timbre of the voices was decidedly unnatural and highlighted the lack of spectral uniformity of the speakers. This particular voice test, using known speakers and with material recorded under studio conditions, is one of the most critical tests that can be applied to a speaker for it evaluates the frequency spectrum from 150 Hz to 6 kHz.

The second and third programme selections were based on an evaluation of two new CDs (Elton John's "Nikita" from "Ice On Fire" (Rocket 826 213-2) and Charles Dutoit in Franz von Suppé's "Light Cavalry" (Decca 414 408-2)). The audible colouration was pronounced and many sections of the straight orchestral music sounded flat and not particularly exciting. I found that some sections of the music, including violins, cellos, and even the harp, sounded realistic but with every piece I listened to I was more aware of the speakers than I was of the music.

In England, the Wharfedale 708s are marketed as technologically advanced speakers which are intended to out-perform other speakers in the same price range. In Australia, with a mooted selling price of approximately \$1500 per pair, they do not appear to out-perform other speakers in their price range and the relation of the Australian price to the English price leads me to wonder what's happened to the Australian dollar.

	100 Hz 1 kHz 6.3 kH	. 22	8 ohms 1.5 ohms 2 ohms		
INPUT IMPEDANCE ONE TEST:			100Hz/7kHz	<u>4:1</u>	
	2nd 3rd 4th 5th THD	33.3 28.7 51.1 60.9 4.3	-49.8 -59.9 - 0.34	-45.0 -49.2 -62.4 - 0.66	dB dB dB dB %
HARMONIC DISTORTION: (for 96 dB at 1m)		100Hz 90dB @	lm Im	6.3kHz 96 dB @	
SENSITIVITY: (for 96 dB average at 1m)	11.	.5 V r.m.s.	= 16.5 Watts	(nominal In	to 8 Ol
CROSSOVER FREQUENCIES:	2.2	kHz			
FREQUENCY RESPONSE:	90	Hz to 20 k	Hz		
MEASURED PERFORMANCE	OF: WH	IARFEDAL	.E 708 LOUL	JSPEAKERS	

WORLD **MORE & MORE** People are discovering us each week. Both the home enthusiast through to the small manufacturer. COMPONENTS • TOOLS • KITS In any quantity, buy one, or one thousand, we're happy to oblige SCHOOLS • CLUBS FTC. Inquire about our bulk discount deals Save yourselt a trip to the city - come to **30 LACEY STREET** CROYDON OR PHONE (03) 723 3860/ 723 3094 Mail orders welcome. ETI READER SERVICE 106

Ian J. Truscott's

ELECTRONIC



## at the leading edge

## NEW 3.5" WINCHESTERS QUOTED AT 40G SHOCK RESISTANCE

MMI specialize in the manufacture of Hi-G resistant hard disk drives for portables and relocatable units used in shared mass storage situations. MMI's range covers 10, 20, 30 and 40MByte drives. Their small size allows them to be built inside equipment leaving the front panel uncluttered or available for the installation of floppy or cartridge tape drives. Incidentally, Western Digital Corporation have chosen the MMI product for their new FileCard product which plugs directly into the IBM-XT slot.

## WHEN YOUR OUTA SPACE, INNER-SPACE FROM PRIAM

Priam's Inner Space series offers high performance high capacity drives for the IBM-AT, XT and PC. The drives, which come complete with cables, software and mounting slides for slipping into the slots in the AT, are user installable and are available in formatted capacities of 42.7 and 59.8MByte.

## NEW SOFTWARE ALLOWS PCs TO ACCESS X.25 NETWORKS

Western Digital and TITN, Inc. have developed FLEX.25, a software package to link IBM PCs and compatibles using the X.25 network protocol. FLEX.25, together with the WD4025 controller board, manages the complete communication functions of a packet data network at the PC level. The network software has already been certified for direct connection to major U.S. and European networks.

#### TEXT-TO-SPEECH CHIPSET

General Instrument's CTS can synthesize an unlimited vocabulary from a string of ASCII characters representing ordinary English spellings. Comprising a CTS256A-AL2 microcomputer controlling a SP0256-AL2 allophone chip the combination examines incoming ASCII text, a code to speech algorithm scans it, examines left and right contexts and consults a rules table for translation into the appropriate allophone addresses. Exception rules are embedded within a total set of approximately 400 rules

\*IBM PC, XT, and AT are registered trade marks of International Business Machines



daneva australia pty Itd 66 Bay Rd Sandringham Vic 3191 P O Box 114. Sandringham Vic 3191 Telephone 598-5622 Telex AA34439 Suite 28 47 Falcon Street Crows Nest, NSW 2065 Telebhone 957-2464 Telex AA20801

Adetalde: DC Electronics (08) 223-6946 Brisbane: Baltec 1071 369-5900

DANOOS

## Intel's 386 family

The highest-performance general-purpose commercial microprocessor ever developed has been introduced by Intel Corp. The 80386 32-bit microprocessor along with a line of complimentary board and software products is expected to significantly expand the fledgling market for 32-bit microprocessorbased computers.

The 80386 chip is fully compatible with all software generated for Intel's iAPX 86 family, which includes the 8086, 8088, 80186, 80188 and 80286 processors.

The 80386 leads existing 32-bit microprocessors in a number of important areas. It operates at a sustained speed of 3 million to 4 million instructions per second (MIPS), which is substantially higher than the nearest competitor The 80386 contains on-chip support for the greatest 'virtual' memory addressability, more man 04 trillion bytes of information. As well, the chip provides a 'multiple-execution' environment that allows it to simultaneously run programs written for different operating systems, such as Unix and MS-DOS operating systems.

The 386 family of single-board

computers (SBCs) takes advantage of the enormous base of existing hardware through the new iSBC 386/20 80386-based singleboard computer. This is possible because the iSBC 386/20 board is based on Intel's Multibus I system bus architecture, which has been adopted as standard (IEEE 796) by the Institute of Electrical and Electronics Engineers. The iSBC 386/20 is therefore fully compatible with the largest hardware base available to any 32-bit microprocessor.

Included in the 386 family are the iSBC 386/20 Multibus I board, the iSBC 386/100 Multibus II board, 386 operating systems and 386 development software. Together with the new microprocessor, these products provide for a range of new applications: multiuser microcomputers that pack all the performance of today's minicomputers; advanced robots; machine vision and voice recognition systems; advanced PBXs (private branch exhanges); and sophisticated workstations that bring complementary disciplines together, such as engineering design automation and office automation, or manufacturing information systems and factory control.

The 80386 is designed using Intel's CHMOS-III (complementary high-performance metal-oxide semiconductor) 1.5micron process, which combines high performance with low power consumption and small transistor size. CHMOS allows the 80386 to reach the highest integration ever achieved on a commercial logic chip (more than 275,000 transistors) and clock speeds of 12 MHz and 16 MHz.

The 80386 features on-chip self-testing, debugging and memory management (which allows fast multitasking and multiple execution environments), as well as software protection, a requirement for reliable multitasking and high-security systems. The microprocessor supports both segmentation and paging memory-management techniques.

The 80386 can also take advantage of co-processors developed for use with Intel's 8086 and 80286 microprocessors. The 80287 numerics co-processor, for example, accelerates a range of mathematical functions in applictions such as industrial control, engineering processing and financial processing. Other available co-processors include the 82258 input/output co-processor, which off-loads input and output tasks that can slow the central processor, and the 82586 and 82588 local area network coprocessors, which provide for an easy implementation of comcommunications netputer works.

For further information contact Intel Aust, Level 6, 200 Pacific Hwy, Crows Nest, NSW 2065. (02)957-2744.

## Surface mounting aluminium electrolytics

Philips has announced the world's first solid aluminium electrolytic capacitors for surface mounting, the 126 series.


The caps are said to be suitable for all current soldering methods. They offer electrical and mechanical robustness, and long lifetimes because they avoid failure mechanisms such as drying-out or shorting. Other features are a high allowable reverse current of up to 80%, and no requirement for charge/discharge limiting resistors.

The 126 capacitors are SMD versions of the established 122 series; all electrical parameters are identical. Five case sizes are available with widths and heights of  $4 \times 2.5$ ,  $5 \times 3$ ,  $5 \times 4$ ,  $7.5 \times 4$  and  $7.5 \times 5$  mm; the length is 6.5 mm in each instance. This

length allows the capacitors to be used on existing pcbs designed for 5 mm leaded components in mixed print formats, thereby facilitating the transition from conventional mounting methods to SMD.

Specs are: a temperature range without derating of -55 to 125°C; possible temperature range with derating of -55 to 175°C. Under endurance test conditions, lifetimes at 85°C and 125°C are 5000 and 2000 hours respectively. Resistance to soldering heat is specified as 10 seconds at 260°C, however, the construction of the capacitors could allow for longer specified times in the future. Complete immersion in solder is permitted.

Nominal capacitance ranges

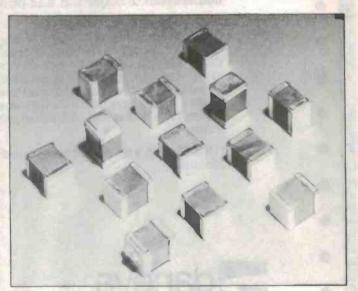

from 0.1 to 68  $\mu$ F, tolerance on nominal capacitance is  $\pm 20\%$ but  $\pm 10\%$  is available on special request. Rated voltage range is 6.3 to 40 V. For further information contact Philips Electronic Components & Materials, 11 Waltham St, Artarmon, NSW 2064. (02)439-3322.

38 - ETI March 1986

#### BRIEFS

#### Lab standard condenser mic

In response to growing demands for a high stability, laboratory standard half-inch microphone, Brüel & Kjaer has introduced the Type 4180. It has a frequency response which is flat  $(\pm 1, 5 \text{ dB})$  up to 20 kHz and it can be used for measurements up to 40 kHz. The Type 4180 will find applications in coupler measurements and in pressure and free-field reciprocity calibrations. For more information contact B&K at 33 Majors Bay Rd, Concord, NSW 2137. (02)736-1755.

#### **Dynamic memory**

Texas Instruments has begun volume production of its 256K x 1 dynamic random access memory. It's available in two versions, the TMS4256 page-mode device, and the TMS4257 nibble mode device, offering designers flexibility in system design. The 256K DRAM is directly upward compatible with TI's 64K DRAM, allowing an immediate quadrupling of system memory capacity without redesign or additional hardware. More information is available from TI at 6-10 Talavera Rd, North Ryde, NSW 2113. (02)887-1122.

#### **NEC fibres**

NEC Australia Pty Ltd has signed a distribution agreement with Data Cable establishing it as the Australian distributor for NEC's complete range of fibre optic components, semiconductor optical devices and gas lasers. For more information contact Data Cable, 538 Mountain Hwy, Bayswater, Vic 3153. (03)729-0044.

#### **FSK modem**

The EF7910 is a single-chip asynchronous frequency shift keying voiceband modem. It is pin selectable for baud rates of 300, 600 or 1200 bps and is compatible with the applicable Bell and CCITT recommended standards for 103/115 108, 202, V.21 and V.23 type modems. Five mode control lines select a desired modem configuration. They are available from Promark Electronics, PO Box 381, Crows Nest, NSW 2065.

#### TI ROM

The new TMS2364 64K ROM from Texas Instruments offers a fast 150 ns maximum access time along with the 28-pin industry standard package and is designed to complement TI's other 64K ROM, the TMS4764 24-pin package. This new ROM is designed as an alternative to EPROMs in high-volume applications such as automotive, and industrial controls, printers, personal computers and telecommunications equipment. It is designed to provide fast turnaround typically within an eight week lead time.

For further information contact Texas Instruments, 6-10 Talavera Rd, North Ryde, NSW 2065. (02)887-1122.

## **CMOS static RAM module**

National Semiconductor has introduced a 16K x 8-bit CMOS static RAM module, the MA2017L, featuring a replaceable lithium battery as its power supply backup.

The module is a 63.5 x 40.6 x 8.89 mm dual-in-package and includes the address decoder and the voltage comparator circuitry. It can decode up to 128K x 8-bits. Multiple MA2017L modules may be stacked in piggyback fashion, carrying the bus upward or, it can be soldered to a printed circuit board, like conventional DIPs.

For more information contact National Semiconductor, 21/3 High St, Bayswater, Vic 3153. (03)729-6333.



#### New dc servo motor controller

The Motorola MC33030 is a new monolithic dc servo motor controller-driver that contains all the active functions necessary for a complete closed loop system. It is ideally suited for bidirectional drive of fractional horsepower motors in applications where precise position sensing is required.

The MC33030 contains an error amplifier and window detector, both of which feature a wide input common-mode voltage range and a self-centring reference; drive and brake logic with direction memory, as well as an independently programmable over-current detector, over-current and over voltage shut-down delay. Motorola can be contacted on (02)438-1955.

#### **Microswitches**

A reliable low-profile microswitch for pcb mounting, available in single- and double-pole versions, has been released in Australia. The LPSP single-pole and LPDP double-pole switches are under 8 mm high and measure 19 x 7 mm and 19 x 14 mm, respectively. Both are capable of switching voltages up to 250 Vac or dc, and life is in excess of  $10^7$  cycles. For more information contact Email Ltd Relays Division, 15 Hume St, Huntingdale, Vic 3166.

#### **Depletion transistor**

Siemens has developed a new small-signal transistor for threshold voltages of negative value. The n-channel SIPMOS BSS 129 transistor, in a TO-92 plastic package, has a typical threshold voltage of 1 V. A maximum drain-source switch-on resistance of 20 ohms results from an 0 V gate source voltage and a drain current of 14 mA. For more information contact Siemens, 544 Church St, Richmond, Vic 3121. (03)429-7111.

#### IR LED/phototransistor pair

The OP293/OP298 is a gallium-aluminium-arsenide infrared LED, spectrally matched to the OP593/598 GaAlAs phototransistor. The OP293 diode has a broad emission angle, while the OP298 diode has a narrow angle. Used in a touch screen application, the CRT is framed with a row of LEDs along its left edge and a corresponding row of phototransistors along its right edge. The horizontal light beam emitted from any LED is sensed by the corresponding phototransistor and by no other. Similarly there is a row of LEDs along the bottom edge. The unit-to-unit spacing in any row is around 0.25 to 0.5 inch.

For further information, please contact Total Electronics, 9 Harker St, Burwood, Vic 3125. (03)288-4044.

## **NEW COMPONENTS**

## AMD introduces fuse-programmable controller


The first fuse-programmable controller chip, which allows designers to distribute intelligent control throughout a computer system, has been released by Advanced Micro Devices.

The Am29PL141, a 20 MHz, single-chip component, implements complex state machines and controllers. By distributing intelligent control throughout the system, it permits designers to off-load tasks from the central controller. The Am29PL141 consists of a sequencer, a 64word x 32-bit PROM, and a 32bit output register.

The Am29PL141 off-loads the central controller by allowing distribution of fuse-programmable controllers throughout the system. These serve as the control for self-contained functional units such as register file, ALU I/O, interrupt, diagnostic, and bus control. It contains AMD's Serial Shadow Register on-chip diagnostics that use serial-scan techniques to pinpoint system malfunctions at the board or component level.

The 28-pin, two-watt device functionally replaces 8.5 packages that have a total of 180 pins and use 6.5 watts.

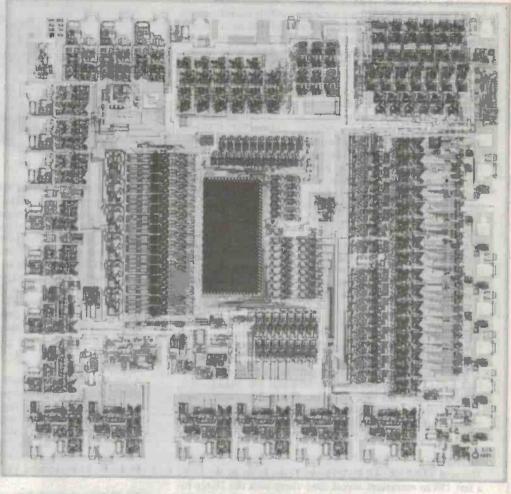Programming support for the Am29PL141 is via the Data I/O System 29 or Valley Data Series 160. To support software, AMD has developed an assembler, and is developing a software



simulator, which will be in the public domain.

For more information contact R&D Electronics, 4 Florence St,

Burwood, Vic, 3125. (03)288-8911.

## **New CMOS logic family**

A new family of advanced CMOS logic circuits that exceeds the performance of standard and advanced low-power Schottky as well as existing HCMOS devices has been introduced by Fairchild Camera and Instrument Corporation.

Called FACT (Fairchild Advanced CMOS Technology), the devices draw three orders of magnitude less power than equivalent Schottky TTL devices, according to Ray Becker, strategic marketing manager for Fairchild's Digital Products Division.

40 - ETI March 1986

Power consumption is as low as 0.1 milliwatt per gate at 1 MHz clock frequency, with propagation delays of just five ns. Devices will include more than 80 of the widely used industry-standard 54 and 74 series logic circuits.

The 74AC-Series devices are capable of driving 50 ohm and the 54 AC Series 75 ohm transmission lines. This makes the family ideally suited to busdriven systems, according to Becker, and is a first for CMOS logic circuits.

'Switching speed of the

FACT line is almost twice that achieved by the CMOS processes of other manufacturers, Becker said. "High speed is largely due to the fine geometry of the Fairchild process that produces gate lengths of 1.25 micrometres. The metallisation process reduces die size and interconnection capacitances which minimises waveform distortion and crosstalk, and improves reliability."

Devices immediately available in sample quantities include 54AC/74AC74 D-type positive edge-triggered flipflops, 54AC/ 74AC240 and 54ACT/ 74ACT244 octal buffers/line drivers with 3-state outputs, and 54AC/74AC373 octal transparent latches with 3-state outputs. These devices can be ordered in dual-in-line packages (DIL), small outline integrated circuit packages (SOIC), flatpack, leadless chip carrier (LCC) and plastic chip carrier (PCC) packages.

For more information contact Fairchild Aust, 366 Whitehorse Rd, Nunawading, Vic 3131. (03)877-5444.

consult of the district of the

1980	ECTRO ERIN	G
The brand-new 100 page 1986 Jaycar Ca		R od with thousands
Now by simply sending a large S * * SPECIAL EXCLU You can save \$10 on a 12 months subset the form below and receive not only the 12 months POSTAGE INCLUDED for subscription to NOTE This is an exclusive Jaycar/EII offer and is NOT CO	AE or posting the con SIVE OFFER!! Cription to Electronic Jaycar Catalogue for only \$20! This is the ETI available.*	In secure your copy upon below. <b>X</b> ★ <b>CS Today!</b> Fill out <b>FREE</b> but <b>ETI</b> for the cheapest current
YES:       Please rush me a copy of the 1986 Jaycar Engineering Catalogue.         Name:	subscription for 12	rn to left. r order for \$20 sa/American Express

## **NEW EQUIPMENT**

## Instrumenting the PC

With growing clouds obscuring the outlook for the personal computer market, there is at least one corner of it that seems to be continuing its rapid growth.

According to a new market research report from International Resource Development (IRD), the market for analogue input subsystems which convert a personal computer into a personal instrument is continuing to grow fast. The key to the rapid growth of this market has been the development of software packages which offer integration of set-up, data acquisition and analysis and display.

Typically such systems record data from scientific experiments, industrial research and design, and medical analysis. They can be used to analyse results, often in loop fashion so as to modify experimentation, adjusting controls when necessary.

The size of the personal instrument market, about \$U\$700 million this year, is likely to reach the \$U\$1 billion level in 1986 and to double to \$U\$2 billion by 1990. On average, according to the IRD report, about half of this shipment value is accounted for by the computers; the remainder is made up of instruments, interfaces and software.

Within the last few years the techniques of integrated circuit fabrication have been applied to the creation of micromechanical devices such as single chip pressure sensors and wafer scale gas chromatography channels. The ability to cut features as small as one micron wide, together with physical and electrical the properties of crystalline silicon and other materials, make it possible to reduce a wide variety of sensing devices to individual chips, and to integrate analogue and digital control and interface circuitry on chip. Precursors of the fully integrated single chip sensor will be hybrid devices in which micromechanical and integrated circuit chips will be packaged together in a single DIP, as



The HP PC Instrument System linked to the HP-150 computer.

hybrid analogue/digital electronic circuits are already.

The next step will be the building of integrated devices incorporating several sensors and all of the necessary circuitry on a chip together with devices such as lasers for providing the experimental stimulus. According to the IRD study the possible applications of integrated instrumentation technology have yet, in many cases, to be invented.

The general purpose instrument bus (GPIB) espoused by Hewlett-Packard and others, is the interface of choice for combining off-the-shelf instruments with a variety of computers. The IRD researchers expect that the increasing variety of low-cost, high-powered instruments, together with use of single-chip GPIB controllers, will increase the dominance of GPIB. There are, says the IRD report, some 2000 instruments now available on the market with GPIB interfaces.

More than one hundred companies are active as suppliers of computers, instruments, interfaces or software. To the surprise of no one, IBM is named as the principal supplier of computers used in personal instrument systems. Through its IBM Instruments subsidiary, IBM is also expected to be increasingly aggressive in the development of instruments, interfaces and software.

However, IBM has a long way to go before there is a real challenge to Hewlett-Packard's across-the-board leadership in the instrumentation end. It's not necessary for the smaller suppliers to get caught in the crossfire between HP and IBM. This market is particularly well-supplied with specialty niche opportunities for small companies.

## **RCL** meter

Philips has recently released a fully automatic, high accuracy RCL meter to take the pain out of capacitor and inductor measurements. The PM 6303 boasts a microprocessor controlled test sequence which is able to determine the dominant element (capacitance, resistance or inductance) in an unknown component and display its value and equivalent circuit on an LCD display screen.

Traditional measurement techniques generally make use of some kind of manually adjusted null-meter technique using bridge type circuitry. The main drawback of such an instrument is that accurate results can require some fiddly and time-consuming adjustments to the meter controls. The PM 6303 exploits the power of the

42 - ETI March 1986

micro to implement a comprehensive voltage/current measurement technique which allows the user to get a readout with an accuracy of 0.25% in 0.5 seconds, it is claimed.

The micro also controls the on-screen graphics which display an equivalent circuit of the component under test (CUT). An 'RCL Auto' range is provided which allows the user to insert a completely unknown component and the meter will determine its dominant characteristic and measure it. The meter will also determine whether a reactive component should be modelled with a series or parallel resistance and display the equivalent circuit on the screen. For more information contact

your local Philips dealer.



#### BRIEFS

#### Microwave training system

Terco's System TR 2300, developed in conjunction with the University of Technology in Sweden, offers a wide range of training applications. It can perform experiments like steady wave amplitude ratio measurements, steady wave in a waveguide with and without central conductor, antenna measurement in which the antenna is used as a matching device between a line and open space and doppler experiments using a directional coupler and doppler radar. For more information contact Electrical Equipment Ltd, Unit C, 8 Lyon Park Rd, North Ryde, NSW 2113.

#### Security dialler

Dick Smith Electronics has introduced a security system which automatically dials a central security office 'Voice Call' when activated. Authorities at Voice Call may call the police, your security service or yourself at work. The system can also be linked to your pocket pager and a series of beeps or tones will alert you instantly. The fee for this type of monitoring is from \$4 per week; the cost of the dialler is \$249.

#### **Off-line switchers**

The 50F Series of 50 W triple and quad output off-line switchers is now available. Each model in this series features a 32 ms hold-up time at nominal line and full load, allowing a greater amount of the critical time needed to save data and

## IEEE-488 bus analyser/monitor

National Instruments has released the GPIB-410, an IEEE-488 bus analyser. This new product consists of an interface card and software that converts an IBM-PC or compatible into an IEEE-488 bus analyser.

The product is designed for GPIB (also known as HP-IB and IEEE-488), troubleshooting and analysis applications, such as designing and debugging a network of test and measurement equipment controlled by a general-purpose computer. Using the GPIB-410, the operator can capture large blocks of data in the analyser memory as the network exchanges signals and Intermittent problems, data. such as a GPIB bus hangup can be analysed by scrolling through the captured data, which is a complete record of the events that led to the hangup.

The analyser can also be used in low-level operations to manipulate and monitor individual bus signals, or in high-level operations where it can run without operator intervention as it captures and stores data for later analysis. Product hardware consists of a single full-size circuit board, the standard IEEE-488 bus connector, and a BNC connector that handles trigger inputs and outputs.

The GPIB-410 software offers a range of functions or modes, including emulation. The PC monitor emulates a control panel that indicates GPIB line states. The emulated control panel is complete with simulated switches that can be toggled by keyboard entries. Users can assert signal lines and alter data lines by keyboard entries. Data is represented in both ASCII and hexadecimal forms.

The software also provides a pattern-generating mode called 'Auto-Talker', which allows the user to interactively place data and control-line patterns on the GPIB in various sequences that simulate actual operating conditions. The patterns can be stored in a file, and then loaded from the file into the GPIB at full bus speed.

For further information contact Elmeasco, PO Box 30, Concord, NSW 2137. (02)736-2888. ride through momentary power 'outages'. For further information, contact The George Brown Electronics Group, 174 Parramatta Rd, Camperdown, NSW 2050. (02) 519-5855.

#### 400 W dual output

The JPS-3 dual output lab power supply offers up to 200 W simultaneously from 0 V to 40 V, from each of its two outputs. Thus it can be operated as single power supply, delivering up to 400 W continuously, fully adjustable from 0 V to 80 V. It works at any ambient temperature in its operating range for limited periods or at slightly reduced ambient temperatures. Design of the JPS-3 is for up to 500 W to be delivered with the same overall performance characteristics. For more information contact Jacobs Radio, 4 Clare St, Bayswater, Vic 3153.

#### Catalogue

Tech Rentals has just released its rental catalogue. The catalogue is the largest yet and contains an improved range of test, measurement and computer equipment. It also includes, for the first time, a sale listing of ex-rental equipment. Tech-Rentals Pty Ltd is at 12 Maroondah Hwy, Ringwood, Vic 3134. (03)879-2266.

#### **Two Tektronix CROs**

Two portable digital storage oscilloscopes have been released by Tektronix. The 2230 offers 100 MHz equivalent time storage bandwidth; the 2220 offers a 60 MHz storage bandwidth. Both double as dual channel analogue oscilloscopes. They use a 20 m sample/s, 8-bit, two-step parallel digitiser. The sampler runs at 10 MHz on even the slowest sweep speeds.

## Video generator

The first in a new family of component analogue video products is being launched by Tektronix.

The TSG-300 Component Television Generator will provide direct digital test signal generation in a wide range of formats. Proposed applications range from research and development to routine maintenance of more component-based ENG equipment.

Signals include colour bars, linearity, pulse and bar, and

multiburst, as well as new component test signals.

The generator accommodates a number of component formats, including RGB, YUV (EBU or Betacam), YIQ (M Format) and Y, CTDM. It uses 10-bit digital signal generation at 13.5 MHz and can be used in either 525/60 or 625/50 systems.

For further information contact Tektronix, 80 Waterloo Rd, North Ryde, NSW 2113. (02)888-7066.

## Fibre optic power meter

Data Cable has introduced a new low-cost, hand-held fibre optic power meter manufactured by Fotec. It's called the M200 and is designed for testing computer and process control data communications links.

Using a silicon photodetector for greater sensitivity with typical 820 nM LED sources, the M200 offers both dB and watts ranges. It uses an autoranging preamplifier which provides a readout in watts and there is a dB converter that offers very good accuracy. The dynamic range of the instrument covers +3 to -60 dBm and 2 mW to 10 nW. Readings are displayed on a large 18 mm liquid crystal display with annunciators showing the range selected. To simplify operation further, only one control is provided — a switch for power and dB or watts selection.

The M200 is designed for troubleshooting computer datalinks, since its dB ranges make cable loss measurements easy and the watts ranges allow simple monitoring of source and received power.

For more information contact Data Cable, 538 Mountain Hwy, Bayswater, Vic 3153. (03)729-0044.

## NEW EQUIPMENT

## Mice 32 in-circuit emulator

Microtek has announced the release of the newest Mice generation. The Mice-32 is designed as a complete development station, with a powerful new incircuit emulator and all the software tools required for fully integrated system development.

The Mice-32 incorporates advanced hardware and software technology that permits an ordinary IBM PC/XT/AT or compatible system to be used for program development/debug, emulation/tracing, symbolic debug, logic state analysis and software performance analysis.

The menu mode features userfriendly softkey operation, with commands arranged in a tree structure. Other features are online editing with command parameters retained from previous specification; symbolic debug utilities; logic state analysis which displays signal waveform (up to 16 channels) for any of 104 trace points, including up to eight hardware trace points; and software performance analysis for module entry, module duration and execution interval analysis.

The command mode input method is compatible with Mice-II, and provides the command base required for batch files, as well as log file utility for recording entire debug session, and online assembly and disassembly.

The Mice-32 boasts fast memory manipulation commands (for examine, fill, search, compare, move, checksum and test); fast file transfer utilities: disable/enable control signals for bus error, bus request, interrupt and cache; disassembly, symbolic debug, cycle-step and instruction-step assist hard-ware/software debug; register display/modification, including display of flag status; and dynamic bus sizing. All settings are software programmable (eg memory map, clock select, DSACK, etc).

The real time trace is supported whenever the processor is running.

The trace buffer is 2048 cycles deep and 104 cycles wide (32-bit address, 32-bit data, 8-bit status, 8-bit external trace points and 24-bit timer).

Execution time for each cycle can be displayed at a resolution of  $1 \mu s \sim 10 \text{ ms}$  (max effective duration depends on selection).

For further information contact Macro Dynamics, 80 Lewis Rd, Wantirna Sth, Vic, 3152. (03)220-7260.

## Low cost microprocessor development system

The HDS-300 is a low-cost microprocessor/microcontroller hardware development station providing real-time hardware/software emulation support for the MC68HC11 microcomputer and the MC6809 and M6801 microprocessor families.

The HDS-300 is a stand-alone development system that requires only the target object file from the host system. Almost any terminal with a standard RS232C port can be used with the HDS-300. Emulator modules are used to interface the HDS-300 to a variety of microprocessors.

The HDS-300 consists of a control station with a built-in 5¼" disk drive for program execution to the target processor, user target code, user macros, and terminal configuration data. It also features a real-time sig-

nal-tracing bus state monitor and a built-in assembler/disassembler for the target processor.

The HDS-300 allows software and hardware to be developed and tested at an early stage of the development process, permitting hardware configuration and software code changes to be made while still at the prototyping stage.

Original algorithms and I/O parameters can be tested before the final software code is written. After this stage is completed, a source program is prepared by using the host's editing facilities.

For development support on the MC68HC11, the MC68HC11 Cross C compiler provides high-level language for product development.

For further information contact Motorola, on (02)438-1955.

## CMOS single card computer

The JED-STD/800 CPU card is designed to provide system developers with a CPU card usable either as a single card computer or as the main computing element in a multi-card system made up of a number of STD bus cards in a rack.

This Australian designed and manufactured computer is intended for a range of applications: its low power consumption (approximately 0.5 watt from a 5 volt supply) makes it appropriate in field data logging applications, as well as in industrial, commercial and educational applications.


The card includes parallel and serial (RS232) I/O, eight analogue inputs (8 or 10 bits), a real time clock, EEPROM, RAM, PROM, two 16-bit counters and full STD bus interfacing.


For program development, simply connect a terminal (or the new JED video board) and type in a BASIC program. When it all works, the JED PROM programmer plugs into the top end of the board, the program transfers into PROM, and the PROM(s) plugs into the USER sockets. Machine code debugging is easy with the single step monitor command, and programs assembled on a CP/M system are passed across as hex files.

The card uses the National Semiconductor CMOS NSC800 CPU, running at a 4 MHz clock rate, along with a number of other CMOS LSI peripheral chips, memory devices and STD bus support.

This CMOS CPU emulates the Zilog Z80 CPU instruction set. Thus, all Z80 software, operating systems, compilers, etc work in exactly the same way, and instruction timing (for an equivalent internal clock frequency) is identical (except that a wait state is automatically inserted into input and output instructions).

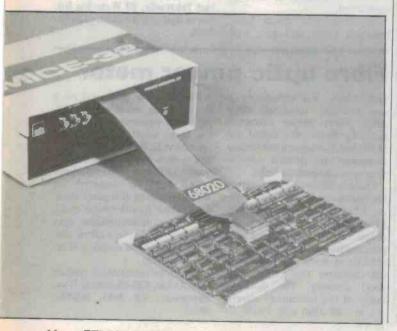For further information contact JED, 28 Anderson St, Boronia, Vic 3155. (03)762-3588.



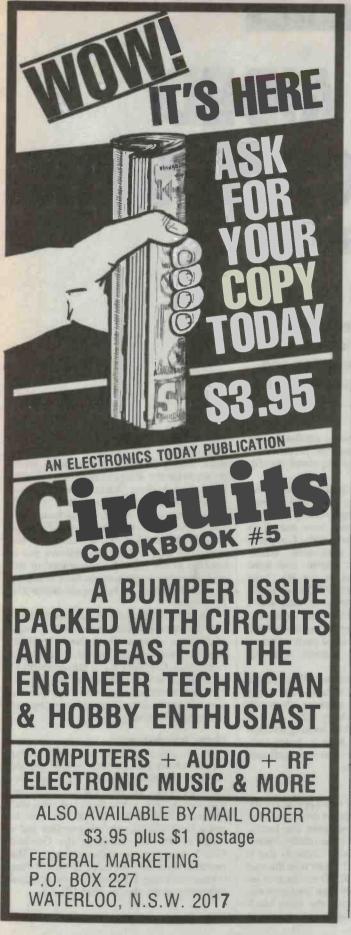

## MICROPHONE **OF THE MONTH**

... A CLOSE LOOK AT ONE OF OUR 100





**SM83** OMNI-CONDENSER



SM7 UNI-DYNAMIC 1

**SM82** LINE LEVEL CONDENSER



**SM91** HALF-CARDIOID CONDENSER

SM81 UNI-CONDENSER



SUPER-CARDIOID

## Studio cardioid dynamic

## 4 Mics in 1

Features two built-in frequencytailoring switches that provide a choice of four different response curves to match the response to the individual voice and situation. Can be wide range flat, or

with added presence, or roll off low end. Tight cardioid pattern cuts off-axis coloration.



## Sturdy, Silent

Integral foam windscreen covers a rugged steel cage that protects the cartridge. Patented air suspension shock mount for outstanding isolation from mechanical vibrations. Humbucking coil guards against electro magnetic interference. One of a kind. . . from Shure, of course.

For full details contact: Audio Engineers 342 Kent St, Sydney 2000 (02) 296731 Queensland (07) 44 8947 Western Aust. (09) 361 5954



### COMPUTING TODAY

## COMPUTER AIDED ELECTRONICS DESIGN Hewlett-Packard makes its bid

Using computers to help electronics designers design electronics is becoming an everyday event. Hewlett-Packard, a company with quite a bit of success in instrumentation and computers, thinks it can become the world's largest supplier of electronics computer aided design equipment.

IT IS NOT uncommon to hear of a piece of domestic or industrial electronics equipment that took 100,000 or even a million person-hours to develop. When you think of the design time involved in each IC and add some microcomputer software to the final product it's easy to see where the time goes.

This high design cost is the reason many electronic products enter the market at very high prices only to become considerably cheaper once the manufacturer has recovered the development cost. Ironically, it is the countries like Japan and the United States with the highest engineering and design costs that to date have been the most successful designers of electronic products.

But the fear in these countries is that one day these high design costs could bring an end to their success as electronics manufacturers. So it's not hard to see why computer aided electronics design products, intended to increase the productivity of electronics designers, have attracted so much research and development over the last few years.

#### **Hewlett-Packard**

The US electronics company, Hewlett-Packard, has established a Design Systems Group with several hardware and nearly a thousand software products for computer aided design. Recently HP opened a Design Systems Group support centre in Hong Kong to help it install computer aided design systems in Asia and Australia. HP will be able to rest on its laurels when it approaches electronics designers looking for CAD systems. It started its career as an electronics instrument maker 45 years ago with a 1% distortion audio oscillator. The company's reputation and the performance of its instruments have improved steadily ever since.

In the 70s HP surprised the electronics community with a range of general purpose mini computers. Although not as profitably, the company's computers now outsell its test and measuring instruments. Computer aided pc board test equipment, microprocessor development systems and some CAD systems followed in the 80s. Like many computer products HP knows it will have to sell its design hardware along with a bundle of mostly off-the-shelf software. Sometimes special design software will need to be written by HP, a third party software house or as a joint venture with the customer.

In Taiwan HP and Formosa Plastics have completed such a joint venture. The result is special board design software which will be sold around the world by HP.

Hewlett-Packard will be looking to companies in Australia to help it design software as a joint venture or to write software as a third party supplier.

#### **CAD** systems

It seems that in every new application the first generation of computer products is designed more to accommodate the limitations of computers than to be totally 'friendly' in the new application. Certainly this is true of electronics CAD. Even now the vast majority of electronics CAD products is intended for digital rather than analogue design tasks. This is because the more black and white world of digital design generation


### **David Kelly**

and verification better suits the way CAD systems work. For the same reasons there were, among the early CAD systems, many products for the design of integrated circuits even though there weren't many people working in this area. According to Dick Watts, who is in charge of marketing the CAD systems worldwide, the rapid growth in the CAD market in 1983 and 1984 has started to taper off. Watts believes this is because of the limited 'friendliness' of the early generation systems and their tendency to concentrate on esoteric applications like IC design.


As you would expect Watts says that HP now has these problems licked with a range of products aimed mainly at board level design in small to medium sized electronics companies. Certainly the company seems to have aimed at a very practical level of design, concentrating more on design generation and verification than on fancy routines like automatic routing.
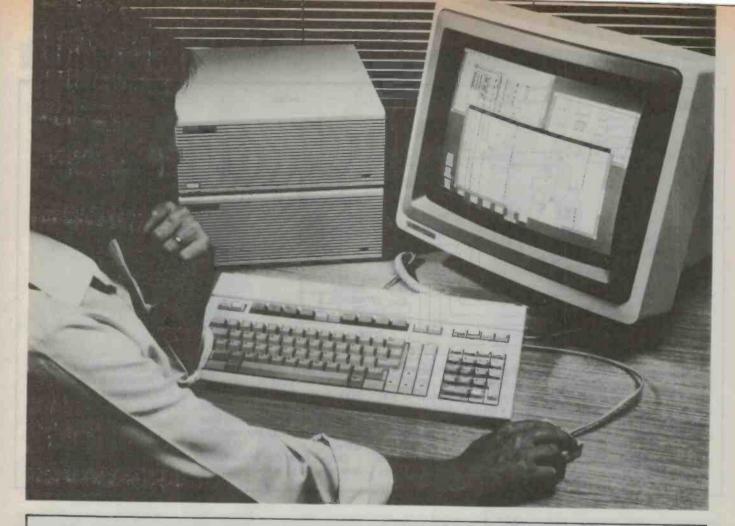
#### New hardware

At the opening of its new Hong Kong support centre Hewlett-Packard announced two CAD workstations, the HP Logic Design-station and the HP Personal Logic Design-station. The Logic Design-station uses workstations from the HP9000 300 series to run a Unix version operating system and a range of software including the GenRad Hilo-3 design verification packages. The personal version of the Logic Design-station is based on either HP's new Vectra personal computer or the similar IBM PC-AT.



## **LABORATORY POWER SUPPLIES**

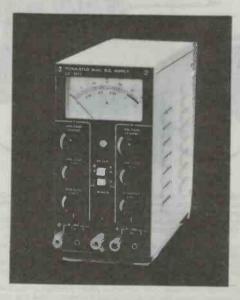

APLAB offer a complete range of regulated DC bench/ rack power supplies combining high precision and regulation capabilities with continuously adjustable outputs.

Designed with single, dual and multiple outputs, these power supplies can be used in either constant voltage or constant current mode of operation. Standard models include:

SINGLE OUTPUT OUTPUT: Output VOLTAGE: Current 0-30V 0-1A to 30A 0-70V 0-2A to 10A **DUAL OUTPUT** 0-30V 0-1A to 2A **MULTIPLE OUTPUT** 0-30V 0-2A to 5A



VIC.

SCIENTIFIC DEVICES AUSTRALIA PTY. LTD. 
 IIIIC DEVICES AUSTRALIA PTY, LID.

 2 JACKS RD., SOUTH OAKLEIGH, 3167

 PHONE: (03) 579 3622 TELEX: AA32742

 559A WILLOUGHBY RD., WILLOUGHBY 2068


 PHONE: (02) 95 2064 TELEX: AA22978

 31 HALSEY RD., ELIZABETH EAST. 5112

 PHONE: (08) 255 6575 TELEX: AA88125
 NSW:

**ETI READER SERVICE 120** 

### **IDEAS FOR EXPERIMENTERS**

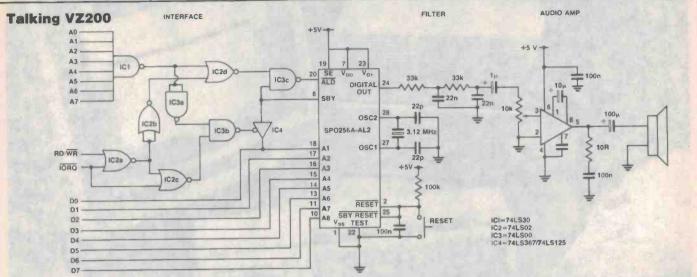

Matthew Bennets of Corowa NSW, sent us this circuit designed to allow speech processing from the VZ200 computer. You could adapt the idea to any computer where you can control seven address and seven data lines, plus two control lines.

Centrepiece of the circuit is

the Radio Shack SPO 256A AL2 monolithic speech processor. An application manual is supplied with the chip which will give full details of addressing the words available on the chip. Mr Bennets has provided interface circuitry such that an address of FFH is required on the port, with the R/W and IORQ both logic '0' in order to access it. SDY (active low) is only active when speech is being output from pin 24. To input data into the chip the ALD pin must be active.

Output from the chip is taken from pin 24 to a low pass filter

that removes the high frequency components from the output. It is then sent to an amplifier built around an op-amp.

## **'IDEA OF THE MONTH' CONTEST**

Scope Laboratories, which manufactures and distributes soldering irons and accessory tools, is sponsoring this contest with a prize given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column - one of the most consistently popular features in ETI Magazine. Each month we will be giving away a 60 W Portable Cordless Soldering Iron, a 240 Volt Charging Adaptor together with a Holder Bracket. The prize is worth approx. \$100.

Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, each person will be paid \$20 for an item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

#### COUPON

#### Cut and send to: Scope/ETI 'Idea of the Month' Contest, ETI Magazine, P.O. Box 227, Waterloo NSW 2017.

"I agree to the above terms and grant *Electronics Today International* all rights to publish my idea in ETI Magazine or other publications produced by it. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright." \* Breach of copyright is now a criminal offence.

Title of Idea	
Signature	Date
Name	
Address	
	Postcode



#### RULES

This contest is open to all persons normally resident in Australia, with the exception of members of the staff of Scope Laboratories. The Federal Publishing Company Pty Limited, ESN, The Litho Centre and or associated companies. Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked to and including the date of the last day of the month.

the month


The winning entry will be judged by the editor of ETI Magazine, whose decision will be final. No correspondence can be entered into regarding the decision. The winner will be advised by telegram the same day the result is declared. The name of

the winner, together with the winning idea, will be published in the next possible issue of ETI Magazine.

Contestants must enter their names and addresses where indicated on each entry form. Contestants must enter their names and addresses where indicated of each entry offic Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest, in other words, you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry. This contest is invalid in states where local laws prohibit entries. Entrants must sign the indicate on the queues that level have need the above rules and agree to ablied by their

declaration on the coupon that they have read the above rules and agree to abide by their conditions

### **IDEA OF THE MONTH**

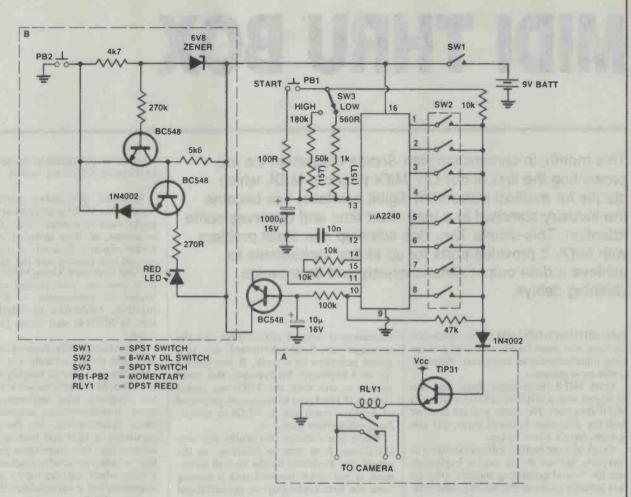

#### Lapsed timer

Lewis Dixon, Alstonville, NSW 2477

Some years ago Konica introduced the SF1, the first SLR camera with a built-in autowind. Now most manufacturers are producing auto-wind models in their SLR ranges.

These cameras lend themselves to be used for lapsed time photography, however, commercial lapsed timers are very expensive.

With this in mind a simple, relatively inexpensive lapsed timer was devised around a  $\mu$ A2240 programmable timer counter.

The external resistors and capacitor at pin 13 use 15 turn variable resistors for fine adjustment. Low gives 1 second at output 1. High gives 4 minutes. The binary output is wired to provide a wired-or function. The combined output will be low as long as any one of the outputs is low.

When switched to low, one can have exposures from 1 second to 4 minutes 15 seconds, at 1 second intervals; when set to high, 4 minutes to 17 hours in 4 minute intervals.

The  $\mu$ A2240 is used in its monostable application and is started by pressing the start button, SW2, switching on SW1 and immediately releasing SW2. This will allow the camera to fire once only and to start the IC counting (output low). At the end of the selected time the camera will fire again as the output goes high, putting a high on the reset pin 10 while the trigger pin 11 is momentarily held low by R9, C3 and Q3. The camera will therefore repeatedly fire at the fixed interval until switched off.

Section A is the camera firing mechanism for a Konica camera, the double reed switch being most convenient. Other cameras may require other types of relays depending on whether three or two leads are used. Power to fire the camera is supplied by the camera's own batteries, and only the connection of two, three or four leads is required to make an exposure.

Power for the circuit is from a 9 V 216 battery; section B is a simple battery tester. The cost is approximately \$30.

## **MIDI THRU BOX**

This month, in conjunction with *Sonics* magazine, we are presenting the first of our DIY MIDI projects. MIDI, which stands for musical instrument digital interface, has become the industry standard in a very short time and deserves some attention. This simple Thru Box tidies up one small problem with MIDI. It provides ports for up to four instruments to achieve a data output simultaneously and thus avoids chaining delays.

THE MIDI STANDARD allows synthesisers from one manufacturer to send and receive information from completely different synths or sequencers.

Most MIDI instruments these days are equipped with a MIDI-in, a MIDI-out and a MIDI-thru port. No doubt you are familiar with the difference between these, but just in case, here's a wee re-cap.

Think of your synth (or drum machine) in two parts, the 'controller' (eg the keyboard) and the 'sound generating module' (the bit that actually puts out the sound). MIDI information is control information; it's the messages sent from a keyboard, say, to a sound generator in a synth. If you press a 'D' on a keyboard, for example, this information is sent from the MIDI-out socket ('play a D') and goes to the sound-generator of another synth via its MIDI-in socket. Both synths then play a D.

When you connect two synths this way (MIDI-out from one to MIDI-in on the other), the keyboard on the second instrument is not active (control info is coming from the first keyboard), so no MIDI-out information is present at the second (slave) keyboard's MIDI-out socket. End of the line.

However, the clever people who developed the MIDI specification realised you might want to connect more than two instruments, so they included a MIDI-thru socket which is basically a replica of that control info coming into the MIDI-in from the first keyboard. Using MIDI-thru, therefore, you can pass control info down a 'chain' of instruments — MIDI-out to MIDI-in, MIDI-thru to MIDI-in, MIDIthru to MIDI-in and so on (see Figure 2 [top]).

Theoretically, this chaining can go on forever, but there's a catch. For various reasons, like the need to simplify the earthing situation, MIDI information is not transmitted *physically* from instrument to instrument. Instruments are coupled 'optically' using optocouplers, ie, the message is translated to light and back at each MIDI connection. This translation process takes time — not a noticeable amount of time for a setup which includes only a couple of instruments but it accumulates the more in-



### Simon Leadley & Michael Horn

struments you chain together. If you were to chain four or five keyboards one after the other (as in Figure 2 [top]), you might notice that the last one played a little after the first.

The MIDI Thru box will alleviate this problem by allowing you to connect your instruments in a 'star' configuration, rather than a chain (see Figure 2 [bottom]). In this case, the delay caused by the optocouplers is the same for all instruments connected to the MIDI-thru ports. It doesn't accumulate, and therefore shouldn't be noticeable.

#### The circuitry

The Thru Box is a very simple device, really only a buffer that takes one input and provides four identical outputs. The MIDI standard uses a current loop system for the


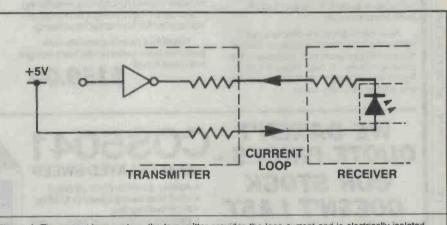


Figure 1. The current loop system; the transmitter provides the loop current and is electrically isolated to obviate loops that can cause earth hum.

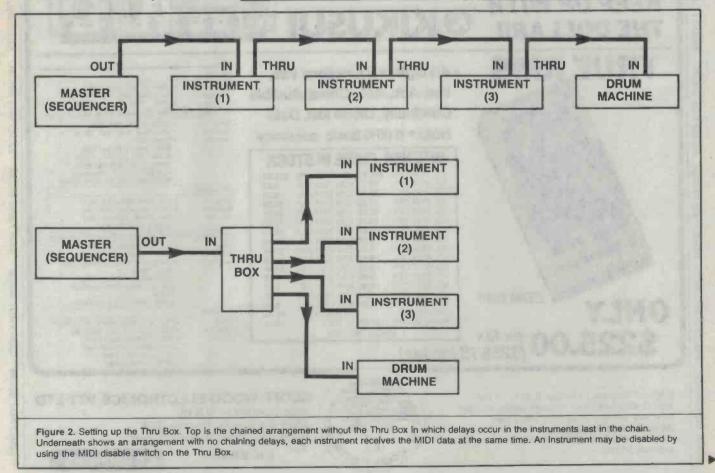

## WHEN GEOFF DOES A KIT HE DOES IT PROPERLY

FOR CHIPS

0001

WOOD FOR CHIPS

CHIPS

FOR

DOOM

WOOD FOR CHIPS

WOOD FUR CHIPS ...

:

... WOOD FOR CHIPS

WOOD FOR CHIPS ... WOOD FOR CHIPS ..

WOOD FOR CHIPS

Geoff's policy is to do a few kits and do them well. Rather than bundle up bits and pieces for everything under the sun, Geoff takes a lot of trouble to get all the RIGHT parts for just a few projects. As a result you can be assured that there are no dubious substitutions and that all parts are prime spec.

Also the projects are checked out before the kit is even considered. Both of this month's projects had mistakes in the original articles – in both cases the PCB layout was incorrect – and Geoff was the one who spotted the errors.

## AEM4600 DUAL SPEED MODEM

Geoff can't put this kit together fast enough. The queue started to form the moment the magazine came out.

Features both 300/300 baud full duplex and 1200/75 baud half duplex operation so it's ideal for Viatel. All functions are selected with quality C&K toggle switches with four LEDs to indicate correct functioning. Interfacing is standard RS232 using a minimum of signal lines for "universal" interfacing.

Geoff's kit comes complete with punched front panel (looks like a bought one!) and Is just \$159.00

## ETI 169 LOW DISTORTION OSCILLATOR

MOOD

FOR CHIPS ...

WOOD FOR CHIPS

WOOD FOR CHIPS ....

WOOD FOR CHIPS

WOOD FOR

CHIPS

WUUU FOR CHIPS

WOOD FOR CHIPS ....

WOOD FOR CHIPS

WOOD FOR

CHIPS

If you're checking out Hi Fi systems then an audio oscillator Is a must. The trouble is that the average el-cheapo probably has a higher level of distortion than a \$10 transistor radio. So with this kit there can be NO compromises. The distortion just has to be better than 0.001%. Covers the frequency range to 100kHz. Geoff has checked the whole thing through with lan Thomas (including pointing out the track error on the pcb).

Kit again includes a posh front panel and the top quality AB pot (available separately at \$9.00).



specialising in electronic components for the professional and hobbyist.


**ETI READER SERVICE 121** 


data transfer so that it is relatively immune to noise that could otherwise find its way on to the data lines, but MIDI Spec 1.0 limits the length of the connecting leads to 15 metres.

The incoming data is converted to a standard TTL level by the 6N138 optocoupler. This is buffered by the 7404 TTL hex inverter and converted to a current drive, presented at each MIDI-out socket. Four outputs are provided but this number may be increased simply by adding more of the inverter sections and connecting their inputs to the optocoupler output.

One inverter and an LED are used to provide the unit with a visual indication of incoming MIDI data.

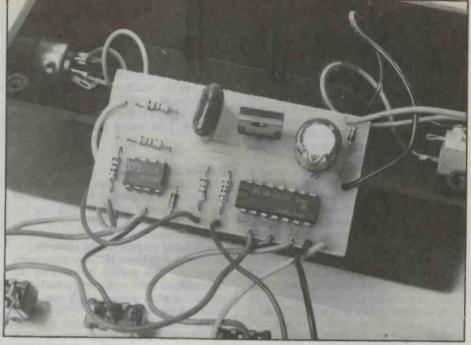The power supply is fed from a 9 V plugpack, filtered and regulated to give a 5 V supply. An LED is placed at the output of the regulator to give indication that power is being applied to the unit.



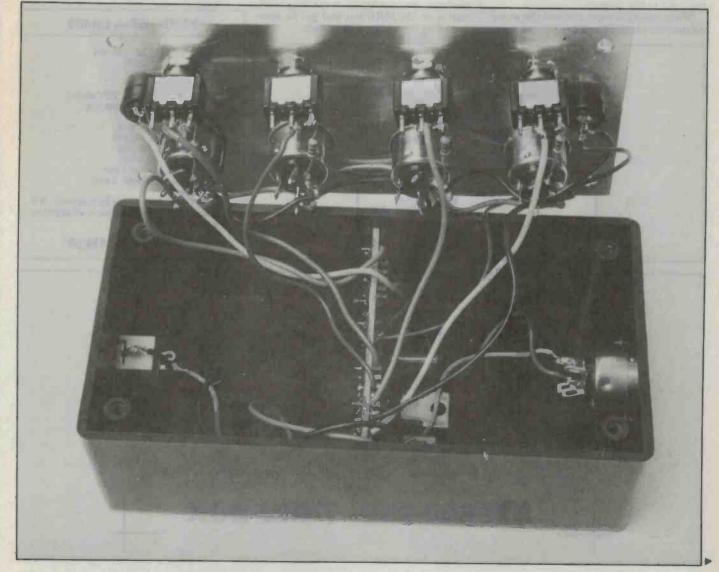

#### Construction

All the components are contained on a small pc board. Begin by placing all the resistors and capacitors on the board taking care to orient the electrolytic capacitor correctly. Next, mount all the integrated circuits, again checking the orientation against the component overlay.

When you are sure that they are all in the right place start wielding the soldering iron. Since all the resistors are the same value there should be no problems here. Wire up the LEDs with flying leads. The long lead on the LED denotes the anode so be careful that you have them the right way around when wiring them up.

All that is needed now is to connect the power input and the MIDI sockets to the board. It is essential that you wire them exactly as shown or the unit will fail to function. The pin numbers of the DIN plugs are usually found on the plugs themselves. If not refer to the diagram.

When you have triple checked the wiring connect the plugpack and confirm operation

of the power LED, then connect a MIDI keyboard to the MIDI-in jack on the Thru Box from the MIDI-out. Playing notes on the keyboard should cause the MIDI-in LED to light; if it doesn't power down and check all your wiring particularly to the LEDs.

#### **Optional extras**

If you wish to have more outputs, all you need to do is get another board and build the hex inverting section leaving out the power supply and the MIDI-in indicator and then connect up as shown.

Switchable outputs can be connected to the unit to disable the MIDI to a particular instrument. This practice of switching the data lines can cause problems particularly if you switch while playing which may cause notes to hang on because no MIDI note off info is received after the switch is turned off. Similarly some sequencers or drum machines are constantly outputting information on the MIDI bus and can be upset by having the connection broken.

#### HOW IT WORKS - ETI-1609


MIDI Information is applied to the input socket. A current loop is formed by the diode in the optocoupler sitting in parallel with the input pins. Diode, D1, guards against reverse polarity.

Output from the optocoupler is taken by an inverter at the beginning of the output chain. Since the 74LS04 is a TTL device up to eight inverters can be driven by the one output while still remaining within TTL rules. Provision has been made for four outputs on this board, although more could be added very simply in parallel.


The output current loop is provided via the 220 ohm resistor to pin 4 of the four output sockets, thence through the device hanging off the output and finally back in pin 5 of the Thru Box outputs. The state of the output buffers dictates whether current will flow.

To provide an indication of whether the MIDI input is being exercised, one of the inverters on IC1 is used to drive LED2. This will light whenever pin 12 of IC1 goes high. LED1 is taken from the output of the 7805 so it provides a power on indicator. D2 functions to protect the regulator IC3 against incorrect polarity on the connection, which needs to be a 9 Vdc.

PARTS LIST - ETI-609

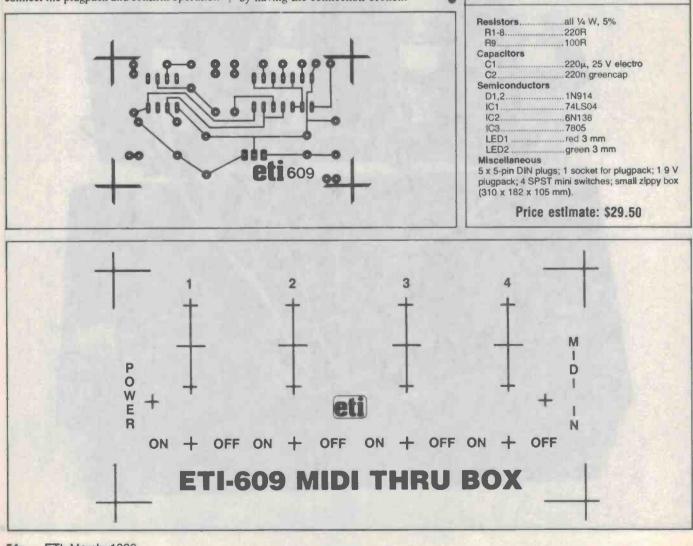

54 - ETI March 1986

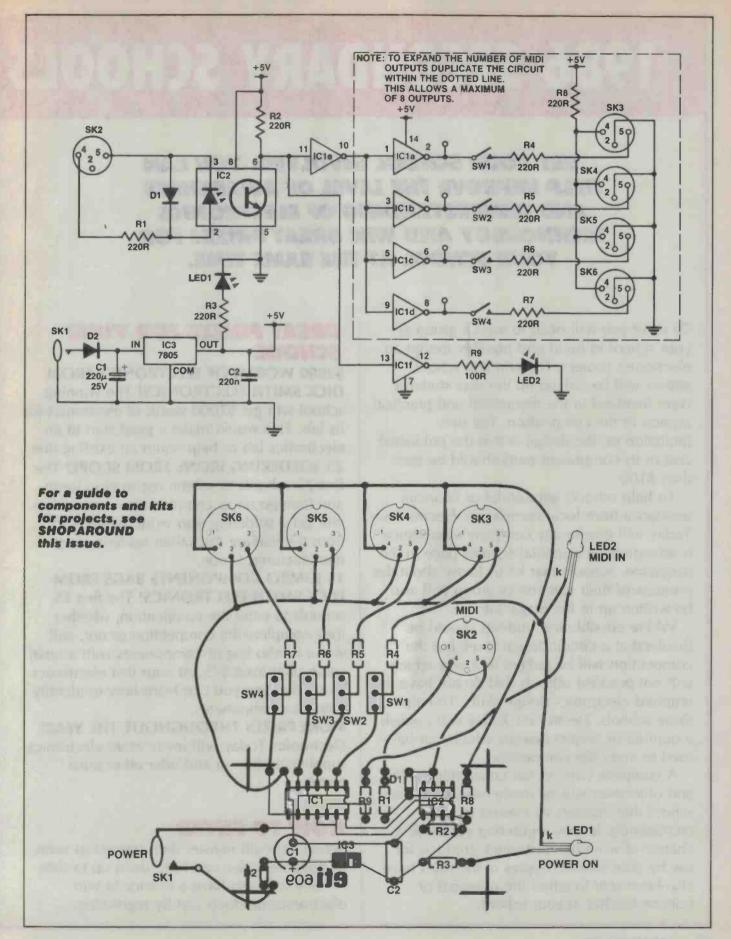

## **1986 SECONDARY SCHOOLS**

GET YOUR SCHOOL INVOLVED. YOU CAN HELP IMPROVE THE LEVEL OF AWARENESS AND UNDERSTANDING OF ELECTRONICS TECHNOLOGY AND WIN GREAT PRIZES FOR YOUR SCHOOL AT THE SAME TIME.

To enter you will need to form a group at your school to build and possibly design an electronics project. The winning school entries will be judged on the way students were involved in the theoretical and practical aspects of the competition. The only limitation on the design is that the published cost of its component parts should be less than \$100.

To help schools get tutorial or financial assistance from local companies, Electronics Today will ensure any company's assistance is advertised in a special schools page in the magazine. Schools that let us know about the progress of their electronics group will also be written up in the magazine.

Where possible the students should be involved at a circuit design level, but the competition will be judged in a way which will not penalise schools that do not have the required electronics design skills. To help these schools, Electronics Today will publish a number of project designs which can be used to enter the competition.

A complete copy of the competition rules and objectives will be made available to any school that registers its interest in the competition. Just by registering you have a chance of winning electronics products for use by your school. Copies of the rules have also been sent to either the principal or science teacher at your school.

## GREAT PRIZES FOR YOUR SCHOOL

\$2000 WORTH OF ELECTRONICS FROM DICK SMITH ELECTRONICS! The winning school will get \$2000 worth of electronics for its lab. This would make a great start to an electronics lab or help equip an existing one. 25 SOLDERING IRONS FROM SCOPE! The first 25 schools to submit registration forms and then go on to complete the competition will get a soldering iron worth nearly \$30 from the leading Australian soldering tools manufacturer, Scope.

**15 JUMBO COMPONENTS BAGS FROM DICK SMITH ELECTRONICS!** The first 15 schools to enter the competition, whether they complete the competition or not, will win a jumbo bag of components with a retail value of at least \$75. At your first electronics group meeting you can learn how to identify common components.

MORE PRIZES THROUGHOUT THE YEAR! Electronics Today will invite other electronics suppliers to join in and offer other great prizes.

## **HOW TO ENTER**

Schools should register their interest as soon as possible so we can keep them up to date — they will also have a chance to win electronics products just by registering.

## **ELECTRONICS COMPETITION**

sponsored by Electronics Today Dick Smith Electronics Scope



Registering brings no obligation on the school, but it allows us to supply free support material and to keep you up to date.

Entrants are required to submit a written report and hardware by August, 1986. Full details are available when you register. There will be one national winner and a finalist from each State or Territory. The judging panel will include members of the Australian Science Teachers Association, other science teachers, representatives of Electronics Today and Dick Smith Electronics. Electronics Today will have the responsibility of ensuring the fairness of the competition. REGISTRATION FORM COMPLETE AND SEND TO "SECONDARY SCHOOLS COMPETITION", ELECTRONICS TODAY INTERNATIONAL, PO BOX 227, WATERLOO, NSW 2017. SCHOOL ADDRESS GROUP LEADER'S NAME SCIENCE TEACHER'S NAME DOES YOUR SCHOOL ALREADY HAVE AN ELECTRONICS GROUP OR COURSE?

## SIMPLE FORTH CONTROLLER BOARD

This 65F12 system is designed as a minimum controller board. It can be used as a target for the Forth computer described in May 1985 or can be programmed directly using the extended 6502 instruction set.


### **David Jenkinson**

REGULAR READERS OF ETI will remember the ETI-694 Forth computer published in May 1985, and the ETI-696 extension card and disk drive from December 1985. The latest of our Forth projects is a controller board. In fact this is probably the key project of the entire series, because it utilises Forth in the optimum way, in controlling equipment in the external world.

As before, the resident micro is the 65F12, which consists of a 6502 with some user RAM and Forth in ROM. The board also contains up to 8K of RAM and ROM, a watchdog timer, RS232 serial link and provision for battery back-up.

To reduce cost, an initial design constraint was to keep this a minimal system, but at the same time allow for additional system expansion boards. A look at the parts list will show that only seven ICs have been used, allowing a board size of only 140 mm by 86 mm. Connectors J2 and J5 have all the necessary signals for additional boards. Functions such as analogue I/O, and bank-switched memory can be added later.

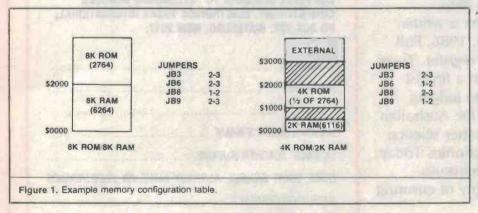This article will not contain a complete description of Forth, or indeed, even of the Energy Control system. If you want to get to know Forth we suggest you consult *Start*-




ing Forth by Leo Brodie (\$25), or Forth Programming by Leo Scanlan (\$24.25). Both are available through ETI book sales. (See the advertisement pages 98, 99.) For a better understanding of how these Forth boards work in practice, you should consult the relevant articles in ETI, and obtain a copy of the RSC Forth user's manual available from Energy Control. Incidentally, the Queensland Institute of Technology teaches Forth quite extensively.
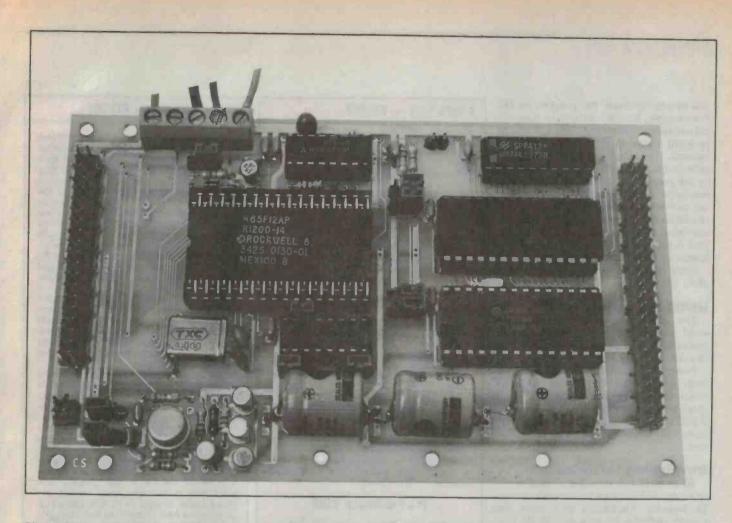
#### Construction

The double sided pc board from Energy Control is silk screened to proper professional quality. However, it is still a good idea to check it thoroughly before you begin construction. When you are happy with it, proceed to load the board in the usual way. Place the resistors, IC sockets, and pin headers in their correct positions and solder home. Notice that the 65F12 comes in a 64pin package, with its pins in a staggered configuration, so a conventional socket won't work. Also note, one of the pin headers needs surgery, to break it into a 40-pin section and 4-pin section, (JB3).

Next, insert the capacitors. Notice that one of these is tantalum, so its polarity is important. On most brands a small '+' sign is visible just above the appropriate leg. The other polarised component is the diode.



The project won't work if you get it wrong! Next, install the transistors, and slip the chips into their sockets. Be careful, once again, to get polarity correct. Also notice that the processor is an NMOS device, so take special care of it. Don't remove it from the foil until absolutely necessary. In fact, it's good practice not to even touch these devices until you need them.

At this stage, go over your work carefully, making sure that your soldering is up to scratch and all components are where they should be. A bit of time spent at this stage will save a mountain of tears and frustration later.

When you're happy with this, install the batteries, then the jumpers as required and hook it up. Now you should be ready to test it.

#### **Testing the board**

A convenient way of checking the board is to configure the jumpers for 8K memory chips (see Figure 1) using the Rockwell 65FR1P development ROM in the IC6 socket. If a terminal is connected to the serial port, the system will look like an RSC-Forth development system. See under the heading 'Using the serial port' for the correct protocols.

If the watchdog timer is connected the system will display RSC-Forth as normal,

but after a five second delay the message will reappear. This occurs because at power-on, the non-maskable interrupt vector (NMI) is set to point to the system reset routine. (So when an NMI occurs the system resets.)

If you do not have a development ROM things become a bit tedious. There is a micro-monitor in the 65F12 chip which can be accessed by typing CNTL R (\$12) from the terminal. A > prompt indicates the micro-monitor is operational. Details of how to use this monitor can be obtained from the RSC-Forth user's manual available from Energy Control.

#### **Memory configuration**

One limitation of the RSC-Forth development board is that Forth code cannot be generated to reside in the upper 8K of external memory. If you wish to use the full 8K ROM space, 6502 machine code will have to be used.

The normal configuration to run Forth target-code is 4K RAM and 4K ROM. Not all applications require RAM. In these cases just the 4K ROM need be inserted. 4K may not sound like much but let me assure you, 4K of headerless Forth is a *lot* of code. The 65F12 kernel already contains the Forth primitives so all your code must provide is a series of jumps to existing Forth words. Several possible memory configurations are shown in Figure 1.

If the processor is running at 2 MHz (4 meg crystal), the multiplexed data and address bus structure requires fast memory devices. It is essential that you use ROMs with an access time of at most 250 ns. If the process is run at 1 MHz (2 meg crystal), slower memory may be used. It may be difficult to obtain 2K or 4K chips with 250 ns access time. 250 ns 8K EPROMs (2764) are readily available. If 8K chips are used in the 4K configuration, it is the top 4K of the ROM that will be addressed.

#### **Battery backup**

The board has provision for backup of the RAM in IC7 and the 192 bytes of internal RAM in the 65F12. Jumpers, JB5 and JB1, may be used to select either +5 volts or Vbatt. If the battery backup circuitry is not installed, leave the jumpers in the +5 volt position. JB4 on the ROM socket was included for possible future expansion and should be left in the +5 volt position.

#### Using the watchdog timer

The concept of a watchdog may be unfamiliar to many readers. However, it is a technique frequently used by industry. If a processor is running continuously there is some probability that noise on the system

will eventually cause the program to fail. For example, if a JMP instruction is executing and noise corrupts the jump address, the program may leap off to some undefined location. The watchdog is a retriggerable monostable that must be reset periodically by the program. If control is lost for some reason the watchdog will time-out and initiate an NMI sequence. This can be used to re-initialise the program. On this system the watchdog is triggered by pulsing bit 1 of port A on the 65F12. The following Forthassembler word should do the trick.

CODE DOG PA 1 RMB, PA 1 SMB, NEXT JMP, END-CODE

#### Using the serial port

The serial port uses three-wire RS232 serial communication with default parameters of 2400 baud, seven data-bits, two stopbits and no parity.

Jumpers are provided to allow operation from either +12 V/-12 V or +5 V/0 Vlevels. It is recommended that +12/-12 be used, as the output will then be within true **RS232** standards. Some devices will operate from +5/0 V levels but there are no guarantees.

#### **Developing software**

When starting from either a warm or cold reset, the 65F12 examines memory at every 1K boundary for \$A55A bit pattern. This pattern indicates an auto-start ROM is installed. The following two bytes must point to the parameter field of the Forth word to be executed on reset.

PARTS LIST -	- ETI-697	
Resistors	ali 1/4 W, 5%	
R1	47k	
R2,4,10	100k	
R3	10k	
R5,6		
R7		
R8,9		
R11		
R12		
Capacitors	100 nF greencap	
	10 µF tantalum	
~2		
C4		
C5,6	15 pF	
C7-14	100 nF ceramic	
Semiconductors		
D1	IN914	
Q1,5	BC108,BC548	
Q2-4	BC179	
IC1		
IC2	74LS123	
1C3	65F12AQ 2 MHz part*	
IC4		
IC5		
	2764, 2732, 2716 (250NS)	
IC7		
Miscellaneous XTAL1	4 1411-	
	4 minz 2-pin jumper	
	2-pin jumper	
	socket". 3 x 1.2 V nicad	
batteries; 2 x 50-pin header.		
Durronios, E X CO P		

#### Price estimate: \$105


\*Available from Energy Control, 73 Eric St, Goodna, Old 4300. (07)288-2455. See special offer page 64.


#### HOW IT WORKS - ETI-697


The 65F12 uses several of its ports (PC and PD) to address external devices. An external 16K of address space is available, with data and the eight least-significant address bits being multiplexed. IC5 is an 8-bit latch that demuitiplexes A0-A8 under control of the EMS signal (IC3 pin 32). IC4 provides decoding for the ROM (IC6), RAM (IC7), and an external device select signal EXT IC2a provides a reset signal to the processor while IC2b provides the watchdog function. The time-out period for the watchdog is determined by R4 and C3. The actual time is not critical and with the values given should be approximately five seconds.

RS232 RXD is inverted by Q1 to provide a TTL compatible signal. D1 clamps the negative excursions of the input signal. RS232 TXD is provided by IC1, which is a comparator. The switching threshold is determined by R8 and R9. R7 is necessary as the output stage is open-collector.


The battery-backup circultry is based on the simplified circuit shown in Figure 3. The disadvantage of this circuit is the 7 volt drop across each diode. This is of some significance when only 3.6 volts are available from the nicads. To overcome this problem transistors were used. Q5 turns on Q4, when the 5 volt supply is present, and the nicads charge through R12. When supply is disconnected Vbatt is supplied from the nicads through Q2 and Q3. A Darlington-pair was used here to minimise base current and hence power dissipation in R11. R6 is provided on the RAM socket to pull up CS during battery backup. If this is not provided the RAM will not operate in power down mode, and current will be excessive.

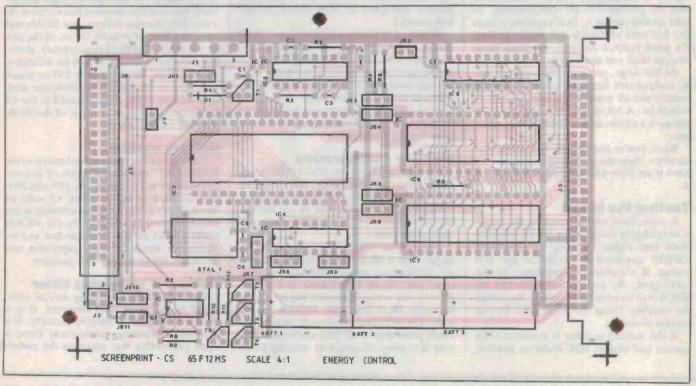

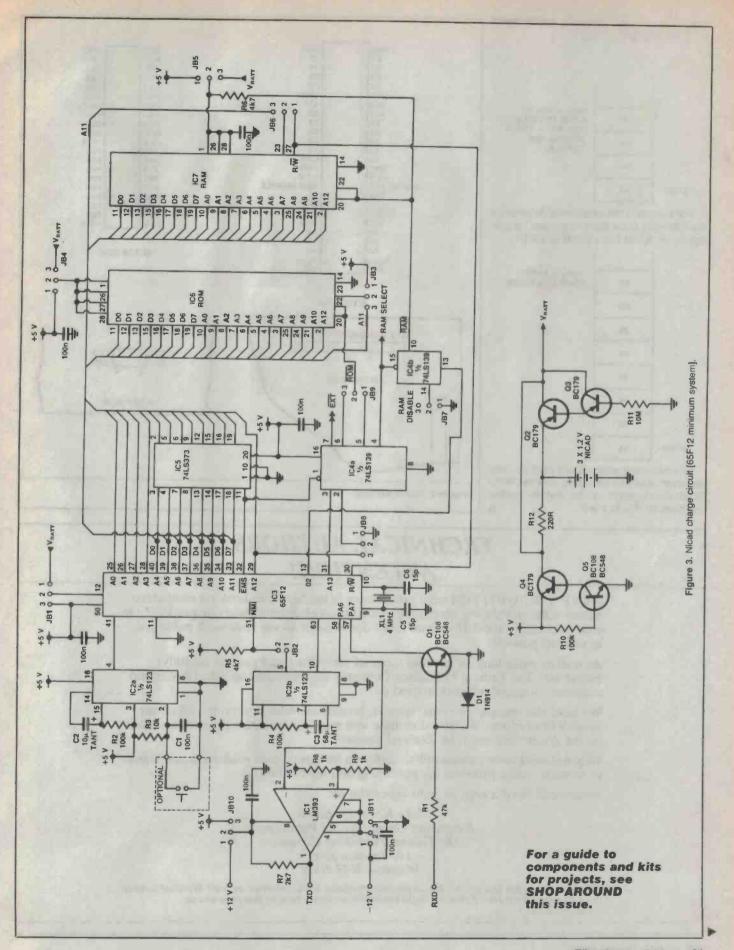


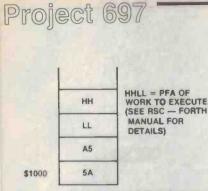

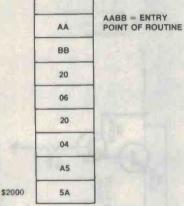For execution of a machine code program the following bytes must be present (assuming an 8K ROM from \$2000 to \$3FFF).



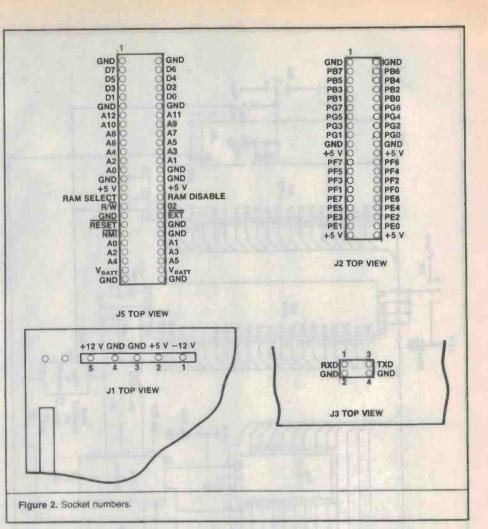In a following article I will look at some software examples and show how the RSC-Forth development system may be used to program ROMs in Forth.



#### **TECHNICAL AUTHORS ATTENTION!** HAVE YOU WRITTEN what you believe is the best ever book on computers or any other developing electronic field? Or on electronic theory or practice? Or consumer electronics? If so, you're no doubt eager to see your work published as soon as possible. As well as publishing an exciting range of electronics and general monthly magazines. The Federal Publishing Company also produces technical books and consumer oriented, electronic specials. We have the resources to edit, typeset, layout, assemble and print - all at our Sydney head office. We also distribute and market internationally with emphasis on the Australian and New Zealand markets. Why not send your manuscript to us for an obligation-free evaluation and allow us to make you a proposal for publishing and distribution? Interested? Send a copy of your typescript to: Jake Kennedy, Editor **Electronics Group Special Publications** The Federal Publishing Company, 140 Joynton Ave, Waterloo 2017 NSW (No manuscript, but just an idea for an electronics-related book, reference or text? We want to hear from you, too! Ring Jake Kennedy on (02) 663-9999 to discuss turning that idea into an accomplishment.)

## Excellence in design deserves excellence in packaging



When you're developing electronic systems you need packaging that is functional and flexible. Packaging that will aesthetically complement your design effort. Associated Controls range of Elmaset products offer you just that.

For small, self contained products you can't go past our extensive range of attractive free standing cases. Whether you require a single, one-off case or production quantities your exact needs can be met in standard or customised multi-colour configurations.

Where systems demand multiple plug-in PC boards our 2000 Series provides the widest number of configurations available. Subracks can be open or enclosed, and your choice of size and set up is practically endless. Whether you need EUROCARD standard connectability or prefer some other special arrangement you will find a 2000 system to fit your needs. Multiple subrack systems are catered for by our 19 inch rack cabinets. These are beautifully styled to present your equipment in a decor enhancing, professional manner. Many options are available including solid or transparent doors or fixed panels. All the options you would expect of a professional system are there. Your products and designs represent considerable effort on your part. Now you can present them in packaging that complements that effort. With Elmaset you get all the flexibility and adaptability that you will ever need.

Call us today for the full range of catalogues and put excellence in your packaging and equipment presentation.



In Sydney Call: Dorothy or Shirley on (02) 709 5700 In Melbourne: Jenifer or Sandra on (03) 561 2966



UHF/VHF/FM ANTENNA Covers all Australian requencies. Suitable for use in houses, caravans, boats etc. 9 1 x 75 ohm niput. 9 Can 2 x 5 ohm output. 9 Can 2 x 6 dB. 9 Maximum output 2 x 9648... SPLITTER. Cat. L15041 \$39.95



UHE/VHE MAST HEAD SPECIFICATIONS.

 
 SPECIFICATIONS.

 Galta: 40 - 150MHz 30dB

 (rejection 7.5dB al 94MHz)

 170 - 230MHz 40dB

 470 - 900MHz 15dB

 Max Outpoit: 100dB uF V

 Noise Figure: VHF 6.5dB UHF 7dB

 Input impedance: VHF (75300 ohm)

 UHF (75300 ohm)

 Output impedance: 70 ohm

 Power Supply: 12V DC 100mA
 \$89.95 Cat. L15046



IHE/VHE CONVERTER SPECIFICATIONS: Input (Channel 36): 75 ohm x 1. Output (Channel 1,3,4): 75 ohm x 1 Gain: 12dB. Gain: 12dB. Power Supply: AC adapter 240V AC, 50Hz/12V DC, 100mA, DC Plug. \$89.95 Cat. L15051

TV INTERFERENCE EII TER

uts CB/Ham signals interfe



OUTDOOR ANTENNA DIPLEXER \$14.95 Cat. L11044



## UHF TO VHF TUNEABLE DOWN CONVERTER

Suts all TV's and allows VHF sets to watch and listen to SBS Channel 28 Has built in amplifier to ensure no signal loss. Tuneable UHF band 4/5 to VHF channel 1.

- channel 1. Power supply 12V DC 100mA (included). Allows TV without UHF to recieve pn-air UHF signal or use VCR. Video Game, Computer, etc.
- \$99 Cat L15021



10dB IN-LINE AMPLIFIER Reduces loss from splitters and long cable runs. Suitable for use with antennas, coaxial feed lines and antennas, wc adaptor included. Cabler No. Antennas, coaxial feeo Inno. VCR's, A/C adaptor included. SPECIFICATIONS: Frequency Ranga: 5-900MHz Galin: 1008 Power Regulirements: 12V A/C Adaptor (included) Input Impedance: 75 ohm Output Impedance: 75 ohm Output Impedance: 75 ohm



**METEX 3530** MULTIMETER

METEX 3530 MULTIMETER The instrument is a compact. raged, battery operated, hand held 3/25 db AC voltage, DC and AC Compactinger, Transistor HFE and Continuity Test. The Dual-slope A-D Converter uses C-MOS lecthology for auto-zeroing, polarity selection and over-range indication. Full evision and over-range indication. Pastrument for use in the field. laboratory, workshop, hobby and home applications. Features. P Lab-Dution ON/OFF power switch 9 Jush-Dution CN/OFF power switch 15 KV/3 KV 9 Capacitance measurements to 1pF 9 Jush-Dution Switch Jush-Dution CN/OFF power switch 9 Jush-Dution Switch Jus

Capacitance measurements to 1pF
 Diode testing with 1 mA fixed

Copportance...
 Constraints...
 Constrai

NEW D PORT DIRECTIM

MIDRANGE HORNS MIDHANGE MOHNS Use these quality, all metal, Piezo tweeters for great top end sound in your band speakers, disco sound system, etc. Rated at 30 watts RMS, in a system they will handle over 100 watts RMS.

100 watts RMS Two sizes to choose from: Size: 4" x 10 <sup>1</sup>/2" Impedance: 8 ohms Rating: 30 watts RMS Response: 1.5kHz - 14 kHz Dimensions: 102 x 267 x 177mm Cat C92082 \$49.95

Size: 3" x 7" Impedance: 8 ohms Rating: 30 watts RMS Response: 2kHz - 15 kHz Dimensions: 76 x 177 x 145i Cat. C92084 \$29.95 Dealers, OEM's, etc., phone

(03) 543 166 for wholesale prices



#### VOLTAGE REGULATORS

Drai i Girai i G		
Description	1-9	10+
M309KC	\$1.80	\$1.60
805KC	\$1.80	\$1.60
812KC	\$1.80	\$1.60
8H05KC 5V 5A	\$7.80	\$6.95
8H12KC 12V 5A	\$7.80	\$6.95



UNIVERSAL BATTERY CHARGER AND TESTER money on expensive bat his universal battery char Save money considerately charger. Features include meter tester, and provisions for D. C. AA, AAA, N, button and cell batteries, 9V and 6V (square types). Comes complete with detailed instructions

Cat. M23533 \$27.95



Cat.No. Description Price \$1.95 \$13021 1 pol 2-12 pos. \$1.95 \$13022 2 pol 2-6 pos \$1.95 \$13033 4 pol 2-3 pos. \$1.95 \$13035 3 pol 2-4 pos



NEW TTL MONITORS Fantastic resolution! Enjoy a crisp, sharp image with these new Airton TL monitors! IBM' compatible, green display, swivel and tilt base. \$265 Cat. X14510

IC STORAGE CAS Electro static charge proof plastin IC case with conductive sponge. Dimensions: 75 x 130 x 19mm. \$7.95 Cat H10095


THE OWNER WATER SUPERB KAITEC

180 C.P.S. PRINTER Epson FX80 compatible, standard 80 column dot matrix, Near Letter Quilaity mode, and 3K buffer! Only \$499 Cat. C20020


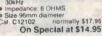
#### SUPER HORN TWEETER

- Requires no crossover and handles up to 100W! Sensitivity: 100dB/0.5m Frequency Response: 3kHz-30kHz
- 30kHz





#### SUPER HORN

- White dispersion tweeter, handles up to 100W.
   Sensitivity. 105dB/0.5m
   Frequency Response: 3kHz-30kHz
   Impedance: 8 OHMS
   Const disp form
- Cat C12103 normally \$17.95 On Special at \$14.95

#### 11 COMPUTER LEADS

We have a wide range of compute leads available, all at low prices?

- Apple II, Ile, II+, with parallel
- Interface card Dual 10 pin (20 contacts) connector to Centronics 36 pin plug Length 2.4 metres Cat. P19025 \$29.95
- IBM IBM • IBM PC, XT, and look alikes with 25 pin "D" plug on computer end to Centronics 36 pin plug on printer end. • Length 2 1 metres Cat. P19029 \$44,95
- \$44.95 TANDY

TANDY • For models IU12/16/168/2000, with dual 17 pin female on computer end to Centronics 36 pin plug on printer end (Equivalent to 26-1323) «Length 2.4 metres Cat. P19027 \$34.95

- For models UNV4/4P, with 34 pin edge connector on computer end to Centronics 36 pin plug on the printer end. (Equivalent to 26-1401) length 2.4 metres Cat. P19028 \$34.95

 Length 2.4 m Cat P19028 \$34.95



#### APPLE' COMPATIBLE SLIMLINE DISK DRIVE Japanese Chinon mechanism. compatible with 2E and 2 plus Cat. X19901 Normally \$225 NOW \$195 (\*Apple is a registered to



#### PUSH BUTTON DIALLERS

DIALLERS Tired of oid fashion dialling and re-dialling engaged numbers? These convenient push button dialiers include last number redial (up to 16 digits) and instructions fr an age of parameter easy changeover \$19.95 Cat. A12030



R COMPUTER PAPER ality paper at a low price! 2,500 eets of 11 x 9<sup>1</sup>/2", 60 gsm bond Cat C21001 \$44.95



HORN SIREN 12V DC, 8W Cat. C12012 1.9 \$14.95 \$13.95



RITRON KEYLESS

CAR ALARM AH ALAHM e lifts shipment sold out mediately to the trade. They didn't ach our cwn retail stores! Activated and disarmed by ignition key, so you never loget to tum it on. Multi-function, built in siren or external siren, car signal hom output.

- .
- output. Easy to install, no door switch required Automatic reset after 60 seconds .
- (avoids noise pollution) Special sensor protects Stereo .

• 12V DC Cat. \$15054 Normally \$39.95 NOW \$29.95



Tremendous Value! Dimensions 480(W) x 134(H) x 250(D)mm. Cat. H10415 Normally \$44.95 SPECIAL PRICE \$39.95



JIFFY BOXES Plastic boxes with aluminium top and available in four sizes. Very popular for projects and very ecconomical!

 
 acconomical
 \$ 3.25

 H10101 150x90x50mm
 \$ 3.25

 H10102 195x113x60mm
 \$ 4.50

 H10103 130x68x41mm
 \$ 2.75

 H10105 83x54x28mm
 \$ 1.95
 H10110 120x65x38mm \$ 2.95 H10112 120x65x38mm \$ 2.95 (Metal top)



ARLEC F.M. AUTOMATIC

INTERCOM Perfect for home, office, shop, farm factory, front door security, granny flat, etc.

Benericki or indrae, onted, snop, rafm, factory, front door security, granny flat, etc.
FAR UR-RS:
FM circulity for crisp clear sound of the security of an and talk.
Pully automatic, selects "transmit" and "receive" functions automatically without manual submatically without manual submatically without manual sensitivity.
Call signal.
Power or/off indicator i amp lights when you speak.
Transmiting indicator lamp lights when you speak.
Transmit lock swirch - suitable for control swirch.
Tensmit lock swirch - suitable for control swirch.
Besk or wall mounting.
12 monts guarantee.

MAGNETIC BULK

RAINBOW CABLE

Cat.No. W12714

W12716 W12720

W12726 W12734 W12740

\$79.50

\$99.00

\$59.95

\$34.95

IDC:

Description 28AWG 16W 28AWG 16W 28AWG 20W 28AWG 20W 28AWG 26W 28AWG 26W 28AWG 34W 28AWG 40W

CENTINE THE JOYSTICK JOYSTICK Features 2x150K pots, long shaft 40mm with 25mm control ball. **CENTRE RETURN** 

\$9.95 \$8.95

pots Cat. X15637 1-9

HOOK UP WIRE

\$5.95

\$12.00

\$14.00

\$20.00

W11260 14/ 20 BED

W11261 14/ 20 BLACK W11265 14/ 20 BLUE

W11270 24/.20 RED W11272 24/ 20 BLACK

W11280 32/.2 BROWN

HOUR UP WINE GaL No. Description W1125113/12 TLD BROWN W1125213/12 TLD BROWN W1125213/12 TLD BROWN W1125413/12 TLD PRELOW W1125413/12 TLD VRLOW W1125413/12 TLD VRLOW W1125713/12 TLD VRLOW PRICES PER 100 METRE ROLL 1-9. 10-

W11268 14/ 20 WHITE PRICES PER 100 METRE ROLL

W11274 244.20 GREEN PRICES PER 100 METRE ROLL 1-9 10

PRICES PER 100 METRE ROLL

\$5.00

\$10.00

\$12.00

\$18.00

\$1.80 \$1.80 \$2.20 \$3.60 \$3.60

ERASER The best and by far the quickest way to erase tapes, cassettes and computer disks! Reduces noise levels below recorders own erase head level, On/Off switch located in handle 240V AC operation Cat C14950 \$29,50

ERASER

Cat.

\$99

#### 51/4" FLOPPY DISK SPECIALS! XIDEX 1-9 10+ S/S D/D \$31.00 \$29.00 Cal C12401

D/S D/D \$38.95 \$36.50 Cat C12410 VERBATIM DATALIFE S/S D/D \$27.95 \$26.95 Cat. C12501 D/S D/D \$39.95 \$37.95 Cat. C12504 Cat. C12904 VERBATIM VALULIFE S/S D/D \$24.95 \$22.95 Cat. C12421 D/S D/D \$31.95 \$29.95 Cat. C12425



## IBM\* COMPATIBLES

from \$1,095!\* Incredible deals to built everyone Including our special package dealed deals 256K RAM,1 drive and printer port

For Apple
 Solutin function keys, BASIC and CPM command.
 Suser defined keys
 Built-in shift lock
 Made by ALPS, life time,
 10 million operations
 Dimension: L340XW130XH42mm
 Commension: L340XW130XH42mm



Cat. K12010

Cat. K12012

CORDLESS

RECHARGEABLE

SOLDERING IRON

Instruction manual
 12 months warranty

T12480

3

computers

Cat. C14200

1

APPLE JOYSTICKS

Ideal for games or word proc Fits most 6502 "compatible"

Built in solder point illumination Easy replacement of solder tip Protective stand which also functions as charging unit Sponge paid attach to stand Plug pack power adaptor Includes Nicad battery



INDIVIDUAL COMPONENTS TO MAKE UP A SUPERB HIFI SYSTEM! By directly importing and a more technically

## WHILE OUR CURRENCY IS **DEVALUING PRICES WILL** RISE, SO BE QUICK!

and tested

POWEER AMPLIFIER. WHY YOU SHOULD BUY A "ROD IRVING ELECTRONICS" SERIES 5000 POWER AMPLIFIER... 9 Series 5000 POWER AMPLIFIER... 9 Superimismum case as per the original article. 9 All components are top quality. 9 Over 1000 of these kirs now sold. 9 Super Finish front panel supplied at no extra cost. 9 Hease note that the "Superb Quality" Heatsink for the Power Amplifier was designed and developed by POD IRVING ELECTRONICS and is being supplied to other kit suppliers.

suppliers. SPECIFICATIONS: 150 W RMS into 4 ohms POWERA MPUIFIER: 100W RMS into 8 ohms (+ -55V Supply) FREQUENCY RESPONSE: 8Hz to 20Hz +0= 0.4 dB 2.8Hz to 55KHz. +0-3 dB. NOTE: These floures are determined solely by passive filters. INPUT SENSITIVITY: 1 V RMS for 100W ouput HUM: 100 db below full output (filt), with 118 d

(see above). INTERMODULATION DISTORTION: 0.003% at 100W, (50Hz and 7KHz

mixed 4:1). STABILITY: Unconditional

Cat. K44771 Will be \$359, limited stock available at \$339 Assembled and tested \$549 packing and post \$10

## dit s

PREAMPLIFIER THE ADVANTAGES OF BUYING A "ROD BAVING ELECTRONICS" SERIES 5000 PREAMPLIFIER KIT ARE... 9 1% Metal Film Resistors are supplied (a bit extra in case of mistakes). 9 English "Lorlin" switches are supplied (no substitutes here.) 9 Specially imported black anodised aluminium knobs. Available Assembled and Tested. (We believe that dollar for dollar there is not a commercial unit available that sounds as good!)

dollar there is not a commercial unit available that solution is a solution of the solution of

Will be \$319, Ilmited stock available at \$299 Assembled and tested \$599 packing and postage \$10

## and the product of the second second **THIRD OCTAVE**

**GRAPHIC EQUALIZER** SPECIFICATIONS:

SPECIFICATIONS: BANDS: 28 Bands from 31.5Hz to 16KHz. NOISE: 0.008mV, silders at 0, gain at 0(=103dB0). 20KHz BANDWIDTH DISTORTION: 0.007% at 300mV signal, silders at 0, gain at 0, maximum .01%, silders at minimum. FREQUENCY RESPONSE: 12Hz=105KHz, +0,=1dB, at

BOOST AND CUT: 14dB

Cat. K44590 1 unit: will be \$219, Ilmited stock availble at \$199 2 units: will be \$429, timited stock available at \$194. packing and postage \$10

## **SERIES 4000**

SPEAKERS 8 Speakers On 8 Speakers with Crossovers \$349 Speaker Boxes (assembled with gnll and speaker cutout) \$349 Crossover Kits \$249 Complete kit of parts (speakers, crossovers, screws, innerband boxes ;

.\$899 Assembled, tested and ready to

\$995 hook up to your system ......

Errors and Ommissions Excepted



#### GENERAL PURPOSE

PREAMPLIFIER A general purpose stereo preamplifier using a single LM382 IC which can be tailored for use with magnetic pickups, tape recorders or microphones by changing a lew components. (ETI445) (ETI July 76) \$9.95 Cal. K44490



#### **GENERAL PURPOSE**

AMPLIFIER CLASS B One of the handlest 'tools' for overonics experiments for the genuine purpose audio ang. This module will work from a wide range of supply voltages, has good sensitivity, is robust and reliable -easy to build tool (ETI 453) (ETI April '80) Cal. Cal. K44530 \$14.95

### 150W MOSFET POWER

AMPLIFIER Here's a high power, general purpose 150W Mostel Power Amp Module's Suitable for guitar and PA. applications and employing rugged reliable Mostels in the output stage. (ETI 499) (ETI March '82) Cat. K44990 (Heatsink not included) plus transformer \$97.50 \$49.50



### EA AM STEREO

AM stereo is now broadcast in Australia on an experimental basis This add-on decoder works with the Motorola C-QUAM system. (EA QCI 84) 84MS10 Cal. K84100 \$26,95



EFFECTS UNIT An "effects unit" that can create phasing, flanging, echo, reverb and vibrato effects (EA June: 83) 83GA6 Cat K83060 \$89.00

4 INPUT PREAMP Easy construction and versatile operation, this preamp is for coupling with the 300W "Brute" Power Amp. (E11457) (ET11407) S54.95

#### **BALANCED INPUT**

BALANCED INFOT PREAMP This project can be used as a balanced mic amp, with low impendance input, a low or high impendance input, a low or high impendance input differential amplifier or a balanced input (ETI-461) (ETI Dec 82). Cat. K44610 \$19.95

### PLAYMASTER 300 WATT

AMPLIFIER This module will deliver up to 200 watts into an 8 ohm load and up to 300 watts into a 4 ohm load. 300 wats into a 4 ohm load. Comprehensive protection is included and a printer circuit board brings it all together in a rugged easy-to-build module. It can be built in either fully-complementary versions, so output transistor shortages should be no problem at all (30PAG) (EA July 80) can venome Cat. K80060 \$97.95

SERIES 4000 STEREO PREAMP This high performance project is designed to complement ETT's 60 wet low distortion amplifier module and forms part of a complete stereo system, the "Series 4000" project. (ET1471) (Top Projects Vol. 6) Contract Vol. 6) \$59.95 at. K44710



# The amazing kit for the Microbes the amazing kit for the Microbes ta smazing kit for the Microbes ta must for all Microbes ownerst Most expansion units up to this time offered at best only one or other features; and this made timpossible to run, for example, complex sound effects migged with speech. The Enhancer I will do all this and much more as well. It's guite amazing how much has been shoe-homed into this compact unit. The Enhancer I s' many powerful teatures incude. • Two ATARICOMMODORE/ COLECOESE ARS type poystick insti-

- Two TRS COLOUR COMPUTER
- Two TRS COLOUR COMPUTER type (systek inputs)
   Allows the connection of Touch Pads, Paddies, Proportional Joysticks, Trakballs, Mice, temporature senors, lights level senors, transducers, act, etclf
   A 4 voice musicsound effects synthesizer.
   A real time clock.
   Unimitted vocabulary speech synthesizer (option).
   Parallel printer interface (option).
   Parallel printer interface (option).

.

- Installer partier miterace (copion)
   A buith-nipseaker with volume control.
   Listings of all necessary routines for use.
   An impressive demonstration program package.
   Compatible to all Microbess
   Digital recording and playback of speech and sound.
   An 8 channel analog to digital converter with variable voltage or variable resistance type analog imputs and laso user selectable resolution from 1 to 9 bits.
   A digital los nalog converter with seliciable resolution from 1-8 bits.
   A digital put lines.
   A digital out lines.

- A doprastport channel.
   A voice input channel.
   A do prie sportmenter socket with all 8 analog Inputs, 5 digital imputs, 4 digital ouputs, 3 58 MHz buffered clock, sound output (so that you can play the sound effects through your HI FI), 3 high resolution voltage comparators. DAC output etc.
   The amazing Microbee Enhancer is available exclusively from Rod Irving Electronics.

\$149

#### 1. 74 07

NOTORCYCLE INTERCOR

## MOTORCYLCE

INTERCOM OVER 300 SOLDI Motorcycling is fun, but the conversation between nder and passenger is usually ustor and you can converse with your passenger at any time while you are on the move. There are no "push-to-talk" buttons, adjustable volume and it's easy to build! it's easy to build? (EA Feb. 84) 84MC2 Cat. KB4020 \$45.00



#### RAILMASTER PULSE POWER TRAIN

CONTROLLER Here's an up-to-the-minute train controller offering all the most desirable features including mertia, all overload protection, walk-around throttle and excellent low-speed running characters. Probably the best controller available, regardless of the cost regardless of the cost! (EA Sept 84) 84TC9 Cat, K84091 \$79.50



#### ELECTRONIC

MOUSETRAP This clever electronic mousetrap disposes of mice instantly and mercfully, without fail, and resets iself automatically. They fill never away with the chease again! (ETI Aug BA) ETI 1524 Cal. K55240 \$34.5 \$34.95



SLIDE CROSS-FADER Mart to put on really professional side show? This side cross-later can provide smooth dissolves from one projector to another, initiate side changing automatically from an in-built variable timer, and synchronise side changes to pre-recorded commentary or music on a lape recorder. All this at a dost far less than comparable commercial unts (LA Nov 31) etsS11 Cet KB110

MICROBEE SERIAL -TO-

MICROBEE SERIAL-TO-PARALLEL INTERFACE Most microcomputers wort or port, through which serial communications (finout/output) is conducted II is a convention that, for listing on a printer, the BASIC LLIST or LPRINT command assumes a printer is connected to the RE322 port. Problem is, serial interface printers are more expensive than parallel 'Centronics interface printers are more expensive than parallel 'Centronics interface printers. Save morey by building this mierface. (ETI Jan 'B4) ETI 675 S59,50

\$59.50

\$19.95

\$59 50

\$19.95

Cat. K46750

ID of

1. 5. 14

RADIOTELETYPE CONVERTER FOR THE

CONVERTER FOR THE MICROBE Have your computer print the stass reves from the international shortwave news service, just hook up this project between your short wave receivers audio output and the MicroBee parallel port. As imple bit of software does the decoding. Can be hooked up to other computers too. (ETT Apr. 83)

FAIR DINKUM RS232

FAIR DINK UM RIS232 FOR MICROBEE The Microbee, among other home computers, has a 'sour of RS232 port in that it doesn't implement negative going portion of its ouput signal (TxD). Most perpherals with an RS232 input can cope with that but inevitably, there are those that can't, This project fixes that (ETI 676, ETI FEB 84)

CYLON VOICE Have your voice transformed into that of the sinister sounding Cylon Great fun and scary! (EA Jan 81)

ROD IRVING ELECTRONICS 425 High Street. NORTHCOTE, 3070 VICTORIA, AUSTRALIA Phone (03) 489 8866

Phone (03) 439 8866 48 A'Beckett St, MELBOURNE, 3000 VICTORIA, AUSTRALIA Ph. (03) 663 6151 Mail Order and correspondance: P.O. Box 620, CLAYTON 3168 TELEX: AA 151938

MAIL ORDER HOTLINE (03) 543 7877 (2 lines) POSTAGE RATES

 POSTAGE RATES

 \$1:35:39:90
 \$2:00

 \$25:34:49:0
 \$1:00

 \$25:34:39:0
 \$1:00

 \$50:59:99:9
 \$5:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-149:9
 \$10:00

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 \$200-10:00
 \$12:50

 <t

Errors and Omissions Excepted

VISA

Cat K47330

Cat K46760

Cal. K80012



## HEADPHONE AMPLIFIER PRACTICE WITHOUT ANNOYING THE FAMILY!

THE FAMILY! If you play any type of electronic instrument. It is headphone amplifier will surely interest you. It will fer you practice for house without upsetting the household or you can use it to monitor your own instrument an the midst of a rowdy jam session. (EA Feb. 84) 83MA11 Cat. K84111 \$29.95



#### WAUDIO AMPLIFIER A low-cost general-purpose, 1 w

Increasing your comput level, etc. (EA Nov 184) Cal. K84111 \$9.95



#### COMPUTER DRIVEN RADIO-TELETYPE

Cat. K47550

RADIO-TELETYPE TRANSCEIVER Here's what you ve been asking for, a full trasmit-receive system for computer driven radio teletype station. The software provides all the latest "whatz-bangs" like split-screen operation, automatically repeating test message, printer output and more. The hardware uses tried and proven techniques While designed to team with the popular Microbec, tips are available on interfacing the unit to other computers (ETI Nov. 64) ETI 755) Cal. M47550 \$139



\$139

#### PREAMP FOR PAGING AMP A versatile preamp with separate bass, treble and volume. (ETI 1421) Cat K54210 \$24.95

**15V DUAL POWER** 

VIDEO ENHANCER

VIDEO ENHANCER 100's SOLD Like tone controls in a hi-fi ampliti touch up the signal with this Vide Enhancer. (EA Oct '83) 83VE10

-


POWER

Cat. K83100

SUPPLY This simple project is suitable for most projects requiring a dual voltage (ETI 581, June 76) Cet. K45810 \$19.50


ENDLARCE


\$39.50

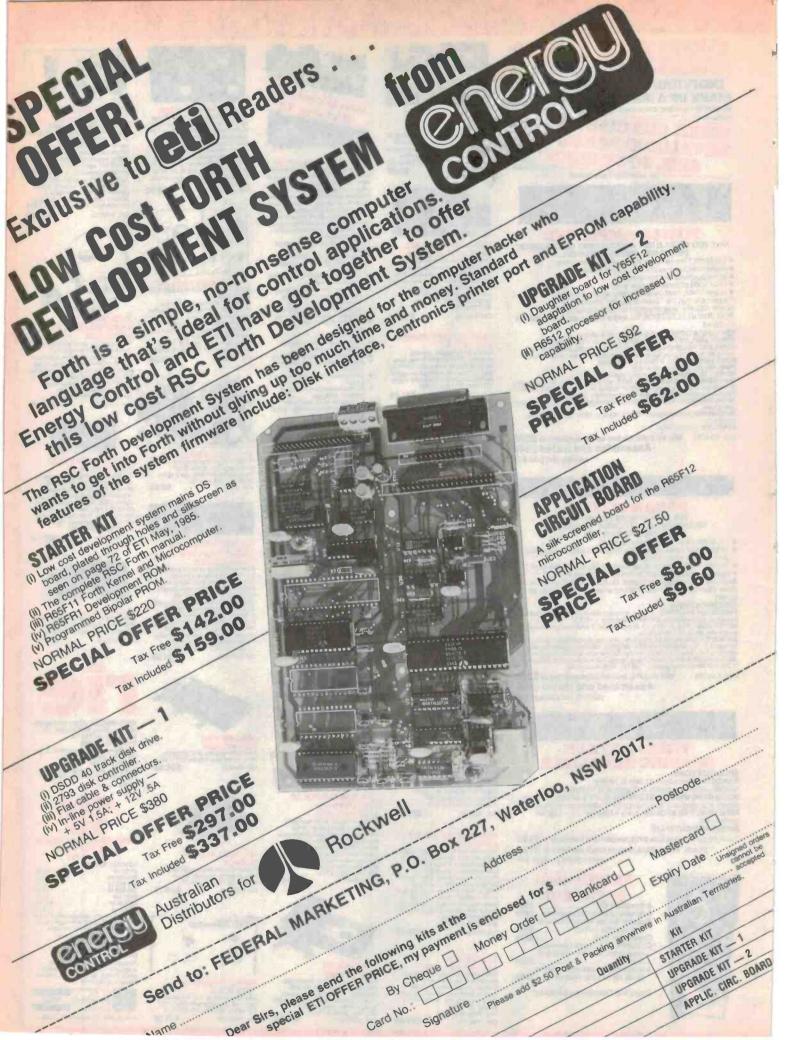
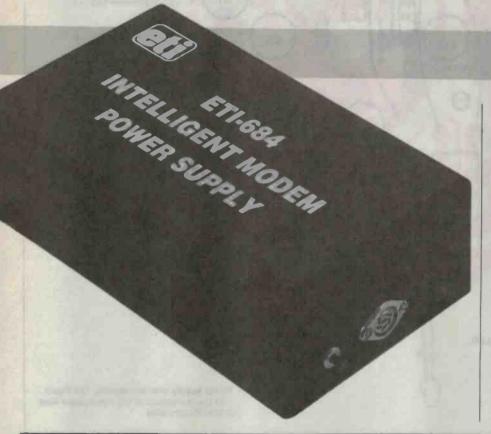
## **INTELLIGENT MODEM**

This is the first of our series of articles on the ETI-684 1200/75 modem to detail the construction of the project. We have chosen to concentrate on the power supply this month, and will publish the rest of the circuit plus the software next month.



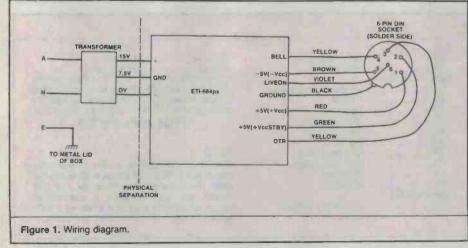

## S.K. Hui Part 3


BECAUSE THE MODEM has auto answer and auto dial facilities it is designed to be left unattended for long periods without soaking up too much power. The result is that it needs a power supply with sufficient intelligence to realise when it's required and when not. Other considerations have influenced the design as well, notably that modems must meet stringent specifications from Telecom if they are to be approved. Fundamentally, these insist that it should be physically impossible for mains power to interfere with the Telecom lines. Another extremely important consideration is price, or lack of.

We believe we have met all these criteria with this power supply. For a start, it is extremely safe. The transformer is physically shielded from the rest of the power supply board, and the entire thing is encased in a box, separate from the main modem board. Output from the box to the board is strictly at TTL levels: +5, -5 and standby +5 volts are the only outputs.

Apart from the logic circuits the design is simplicity itself, and should represent no great challenge to even the most impecunious of you. It consists of a transformer, regulator and some smoothing caps all laid out in the usual fashion. To provide the special control needed, there are three ICs and a relay, which connect the power to the modem when required.
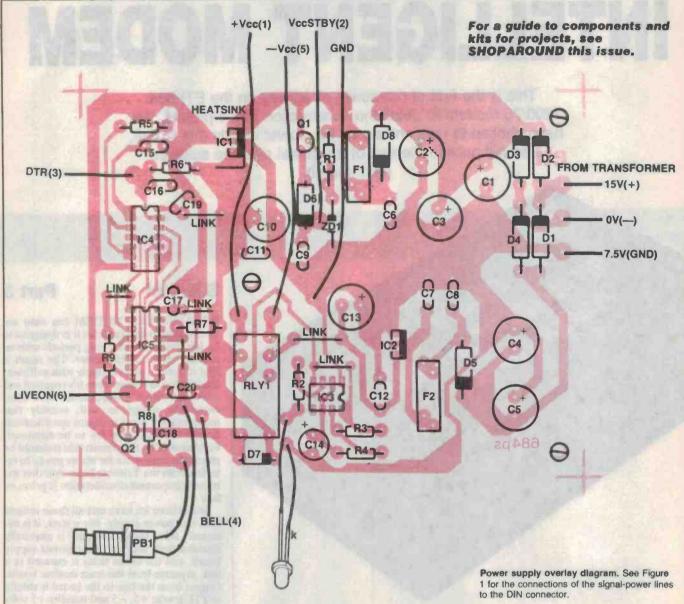
#### Logic

The power supply wakes up in the standby mode. A red LED flashes, and +5 volts is provided on the STBY line. This drives a few volatile memory circuits in the main board. Otherwise the supply is completely shut down, and the power supply leads are completely open circuited by a relay.



#### PARTS LIST - ETI-684 Power Supply


Resistors .all 1/4 W, 5% R1. 349 R2. 180R R3. 10k R4. 100k R5 47k R6.7 8k2 R8 4k7 R9. 2k7 Capacitors C1,2,3,4,5. 1000µ electro, 25 V or higher C6,7,8,9,11, 12,20 ... C10,13. 68n greencap 470µ electro C14. 10µ electro

#### C15,17,19..... 15n greencap C16,18. 100p ceramic Semiconductors D1-7 1N4007 or equivalent D8. 1N5004 ZD1 BZX85 6V2 IC1 7805 regulator IC2 7905 regulator IC3 555 timer 4093 quad NAND 4027 dual flipflop BC337 npn IC4 IC5. Q1 Q2 BC549 npn Miscellaneous PB1 ..... momentary switch (optional)

#### 
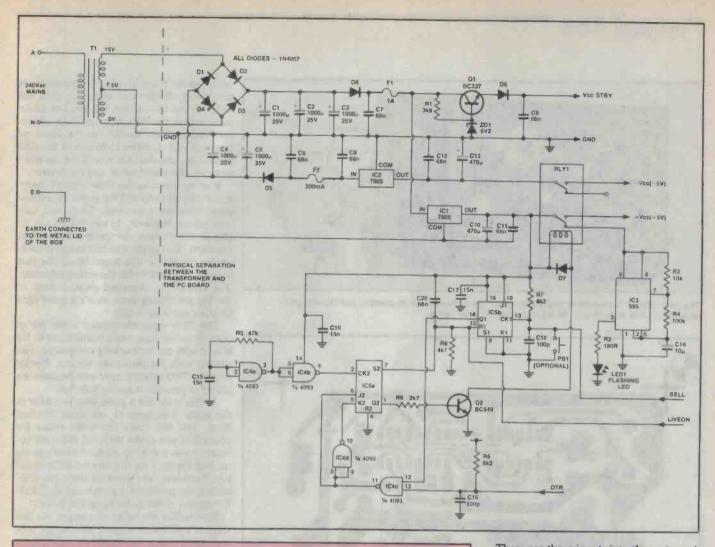
#### NOTE

There are a few popular makes of computer that do not have a DTR signal available to the user. These include the Microbee. For that reason we have supplied a pushbutton switch, which has the same effect as a DTR signal. To wake up the modem, just press.



#### HOW IT WORKS - ETI-684

Power is applied via the transformer, T1, and rectified by the diodes, D1 to D4. Smoothing and further rectification is supplied by C1 to C8 and the two diodes, D5 and D8. The dc ievel here will be about  $\pm$ 7.5 Vdc, which is applied to the regulators and transformed into 5 Vdc positive and negative. This is then connected to the modem board via the relay, RLY1.

The rest of the circuit is taken up with controlling the operation of the relay. The relay is driven by Q2, which is protected against back emf by D7. IC5a controls the operation of the transistor, IC5a is a JK master-slave flipflop, clocked by an oscillator made up of two NAND gates IC4a and IC4b. Output is determined by the condition of its two inputs, J and K, plus the set and reset pins.

Operation is as follows: as long as R2 is low, which it always is, Q2 will go high whenever S2 is taken high. S2 is tied to ground via R8, but may be pulled up by the LIVEON input. This is the override which allows the modem to control its own power supply.

Otherwise the state of Q2 will be controlled by the operation of J2 and K2. Because these two are connected so that K2 is always the inverse of J2, whenever the J2 input is high, Q2 will be high, and when It's low, Q2 will be iow. This input is derived

-

from IC4c, functioning as a NAND gate. Thus, we require that either or both its inputs be low to trigger the flipflop. One side of the gate is connected to Q1 of IC5b, which is in standby mode, with its Q1 high. However, the other side of the NAND input, pin 13, is held high by R6, except when a negative going signal from the DTR input pulls it down. Thus, the relay will trigger when DTR goes low, and reset when it is released, (unless it is held up by the LIVEON signal).

The other way of triggering flipflop IC5a Is by making the  $\overline{O1}$  of IC5b low. This will happen whenever a positive going signal is applied to the clock input, which occurs in the presence of the first pulse of the Bell tone, or on the release of the pushbutton switch. Notice that IC5b will hold itself up irrespective of future trigger pulses on the clock. The only way it can be reset is by activating its reset line, which is connected to the LIVEON input.

Both DTR and BELL are held at their correct levels by networks consisting of 8.2k resistors and 100 pF capacitors. The LIVEON input is tied to ground via R8.


The LED is pulsed by a 555 set up in traditional fashion with a network composed of R3, R4 and C14, which sets up its oscillation frequency. R2 functions as a current limiter on the LED.

There are three inputs into the system. A DTR line (data terminal ready), indicates to the power supply that the terminal operator wishes to make an outward call. When this goes active (is pulled low), the power supply provides full power to the modem. In actual fact the DTR signal is derived from an RS232 receiver chip on the modem board, powered by the STBY line. Alternatively, an inward call may be detected by the presence of Bell current. This signal is provided by another chip on the modem board that is kept active by the STBY line. Ring tone is optically coupled to the BELL line, and conditioned to TTL levels.


The third input is the LIVEON signal. This is a software controlled signal derived from the micro on the modem. Its primary function is to hold the power supply active even when the original DTR signal has disappeared. It also resets the power supply after an incoming call is detected by the BELL input.
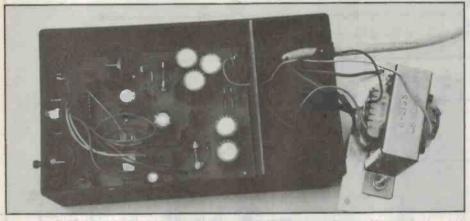
#### Construction

Construction should present few problems. As usual, check the pc board for blemishes, broken or bridged tracks, and so on before starting work. If mounting holes are not predrilled, it's a good idea to do it



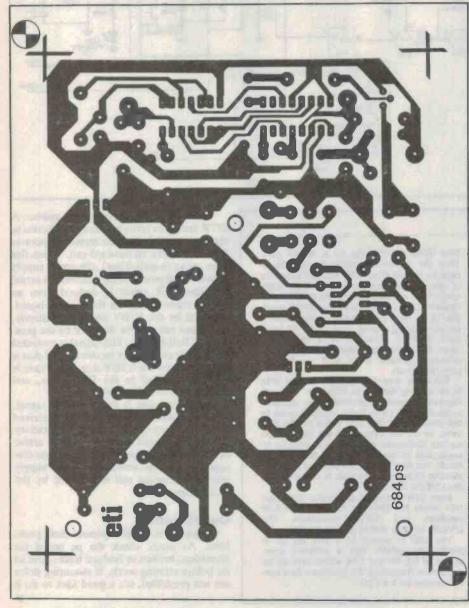The hole size on the isolating (separating) plate has to be as small as possible, just big enough to allow three wires to go through from transformer to the pc board.



now, before there are any components on the board. While you are at it, drill out holes in the side of the box for the LED, cable access, the DIN plug and the pushbutton switch. You should have a blank pc board as well. Cut this to fit one of the slots in the box, and drill a hole in it for the leads between the transformer and the board.

Start by inserting the most robust components: the six links and the resistors. Follow these with the greencaps. There are only two values involved, 15 nF and 68 nF, so you shouldn't have any trouble distinguishing them. You might also like to insert sockets for the ICs at this stage. Insert the fuse holders, then start with the semiconductors. The diodes are clustered around some of the big smoothing caps, so it's a good idea to leave these until last.

The 7805 regulator carries a fair bit of current, so we have put a heatsink on it. Be liberal with the heatsinking compound, and careful with the insulating washer. Notice that the 7905 doesn't have one because we found in practice it barely gets hot.

At this stage it's a good idea to solder in the leads. You need 11, all about 150 mm long. You will make life a lot easier for yourself if you make these all different colours so you can keep track of what's going on. See Figure 1 for the way we did it in the lab. Terminate the wires on the 6-pin DIN socket, the pushbutton switch and the LED. Be careful of the polarity on the latter.

Now solder the relay into place. At this stage it's probably a good idea to go over your work with a fine toothed comb. Check for solder bridges, dry joints, and above all, the wrong polarity in any components. It's also a good idea to make sure that all the components are where they should be.


The assembled board is now ready to be inserted into the box. Push the power leads through the hole in the back of the pc board, then solder them on to the board and the transformer. Push the mains cable through the hole in the box and solder it on to the relevant lugs. Be very careful wiring up the transformer. When you've done this, bolt the transformer down on the metal lid on the box. Remember to secure the mains earth lead between the box and the transformer.

Finally, insert the LED, pushbutton switch and DIN plug into their holes in the side of the box, push the divider plate into the slot and the board down on to its mounting posts. Then screw down the lid and stick the Scotchcal label on the top of the box.

To allow good ventilation for the heatsink, small holes may be drilled on the walls of the box.
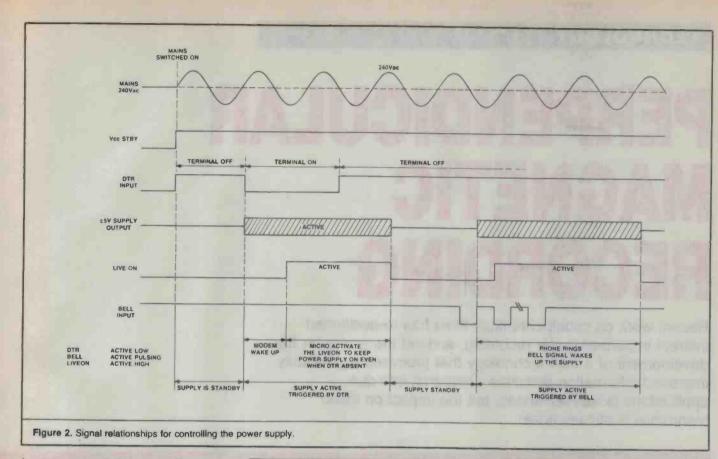
#### Testing

To test the unit, especially if you haven't got hold of the modem itself, the best solution is to wire up a DIN plug so that you




have access to all the control lines outside the box. Turn on and observe the LED flashing. If it doesn't, tap the LIVEON lead against the STBY. If this doesn't work at once then you have a problem. Switch off and start checking.

Assuming the LED is flashing you have a pretty good indication that the power supply has achieved standby mode. To confirm. probe pin 2 of the DIN socket. You should find 5 volts, and nothing anywhere else. Press the button. This should result in the relay clicking audibly. If you now probe pin 1 you should find +5 volts, and pin 5 should show -5 volts, in addition to the 5 volts on pin 2. Return to standby mode by tapping LIVEON against STBY, then the ground which is connected to the shield. Tap the BELL lead against either STBY or GND and the same thing should happen. Once again you will need to reset by using the STBY lead.

Short the DTR terminal, pin 3, to ground. The relay should click and the LED go out. Once again check for supply on the Vcc leads. As soon as you remove the short, the modem should return to standby.

Finally, confirm that LIVEON is working. When this is tied high the relay should be triggered, irrespective of the state of BELL or DTR. Check that nothing happens if these are shorted to either STBY or GND. When you release LIVEON the power supply should return to standby mode.

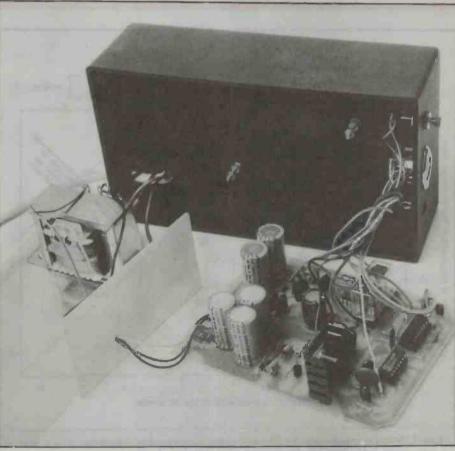If all this works as it should, you have a fully working power supply. Now you just have to wait for the next issue.




Super safe power supply with an isolating plate dividing the box into two separate compartments: one for housing the transformer and the other for the pcb. Note that the 240 Vac cable enters the box at one end while the dc voltage outputs leave the box at the other via a DIN connector.

### TECHNOLOGY
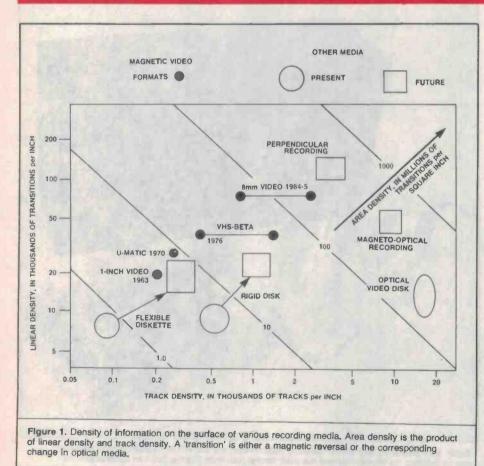
## PERPENDICULAR MAGNETIC RECORDING

Recent work on cobalt-chromium films has re-awakened interest in perpendicular recording, and set the scene for the development of a new technology that promises significantly improved information densities. Research into disk applications is well advanced, but the impact on video recordings is still uncertain.




PERPENDICULAR MAGNETIC recording is a relatively new technological procedure. As the name suggests, the direction of magnetization is predominately perpendicular to the plane of the tape or disk, and this innovation promises information densities significantly higher than those now used. New recording media and heads are being developed, and already impressive results can be demonstrated. However, just as in conventional magnetic recording, the head design and the proximity of the head to the recording surface remain factors of critical importance to high-density information storage.

The goal of any research and development in magnetic recording is, of course, to increase the information density stored on the surface of tapes and disks. An increased density can then be used by the video system designer to achieve various objectives including higher image resolution, a more compact physical format or the implementation of digital technology.

Information density in magnetic recording is related to the number of magnetic flux reversals, or transitions, per unit area of the tape or disk and also to the detected signalto-noise ratio. We are concerned here only with the enhanced transition density and signal strength; minimizing noise is an additional matter which involves control of magnetic domain size and surface irregularities.

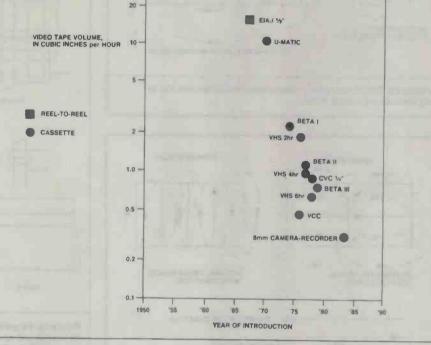With conventional magnetic recording technology, magnetization directions lie predominately in the plane of the medium.



100

50

OUAD 2

TYPE BAC 1"

## M. P. Sharrock and D. P. Stubbs


whether tape or disk. Dramatic improvement in information density has come about largely through improved head design and the use of media with higher coercivities and smoother surfaces. Since the coercivity of a magnetic material is the field needed to reverse the direction of its magnetization, it is closely related to the stability of a highdensity recording pattern. Surface smoothness determines how closely the recording or playback head can approach the magnetic surface. The 30 year achievement of increasing surface information density in various recording systems and volume storage density in video media is illustrated in Figures 1 and 2.


#### **Advantages**


An area of potential improvement in magnetic recording media is the magnetization intensity of materials. Most of the presently used media are of particulate construction, that is, they employ small discrete magnetic particles dispersed in a tough, flexible binder. The presence of the organic binder dilutes the magnetization of the recording material, reducing the available signal strength. Advanced media, now being developed, use continuous thin films of magnetic metal alloys to achieve higher magnetization intensity and also exceptionally smooth surfaces.


Hand-in-hand with the increased attention to continuous films has come a strong interest in perpendicular recording (also

Figure 2. Volume storage density of video media, expressed in terms of tape volume per hour of playback plotted against year of introduction.

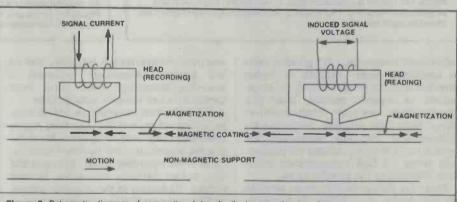

 

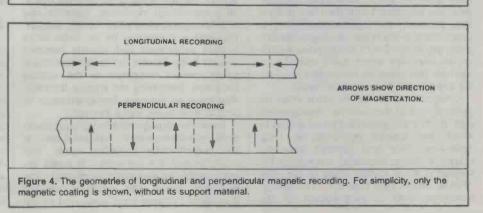

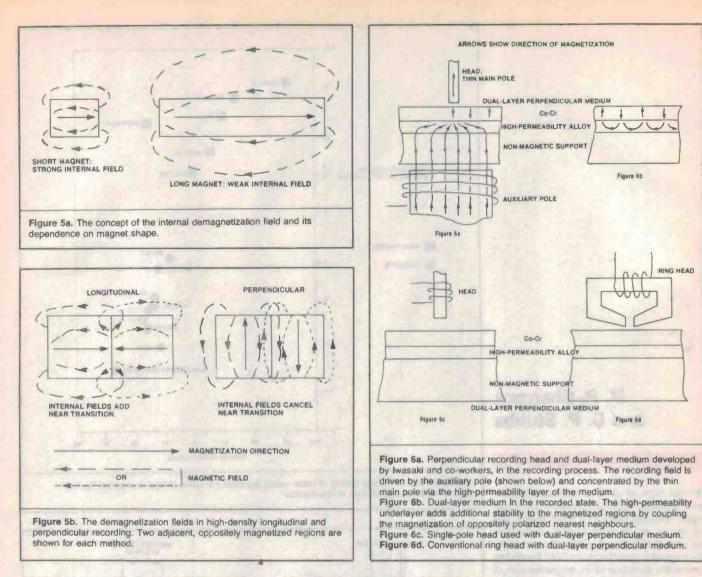

called vertical recording) as a possible route to acceptable signal strength at higher densities than can be achieved by the longitudinal, or in-plane, method. Some thin metallic films, especially cobalt-chromium alloys, have ideal magnetic properties for perpendicular recording; moreover, the vertical mode is highly suitable for productively using the high magnetization intensities afforded by the metallic films.

There are significant differences between the two modes of recording. In longitudinally recorded media small magnetized regions are positioned with their like poles in close proximity and repelling each other; in perpendicular recording, the magnetized regions are arrayed with unlike poles together, an intuitively more stable situation and one that provides motivation for moving towards the perpendicular mode.

Comparison can also be made from the point of view of the so-called 'demagnetization' field, a self-generated internal field by which every magnet opposes its own magnetization. This field depends upon the magnet's shape, becoming stronger if the magnet is made shorter along its direction of polarization. (See Figure 5.) The demagnetization field is proportional to the material's magnetization intensity, and so will become increasingly important if recording technology moves away from particulates and towards metallic films.

In longitudinal recording, the self-demagnetization effect in each magnetized region is not only compounded by the fields of the nearest neighbours, but becomes more intense as the recording density increases and the regions between transitions become shorter. Reduction of the magnetic coating or film thickness decreases demagnetization effects, but also tends to weaken the signal. In perpendicular recording, however, the self-demagnetization effect in one magnetized region is opposed by the fields of its nearest neighbours and actually becomes weaker if the distance between transitions is made smaller compared to the coating thickness. Increasing the coating thickness thus tends to decrease demagnetization as well as to enhance signal strength.

Since the demagnetization phenomenon weakens with increased transition density in the perpendicular recording mode, one might expect that conversely it could become highly unfavourable at relatively low densities, where the distance between transitions becomes large compared to the magnetic film thickness. This is true, but only at positions far from the transitions. The transitions themselves remain sharp and distinct and thus useful in systems of interest for video recording, where the information is contained in the timing or frequency of transitions. Thus a large, useful bandwidth is available. If using a direct analogue format to record a low-frequency signal such as the audio track that accompanies video, a pulse-width modulation scheme can be used, which is comparable to ac-bias in conventional recording.

#### **Developments**

Perpendicular recording was first proposed and discussed decades ago but the recent intense development began with the work of Iwasaki and co-workers on cobaltchromium films. This group also pioneered the use of a high permeability metal film beneath the Co-Cr layer; the composite structure provides magnetic flux linkage, which reduces demagnetization and enhances the effectiveness of the special head used. Numerous other laboratories have since become active in developing Co-Cr media, both with and without the underlayer, and a variety of head designs have been used.

Figure 6 shows the double-sided head and the dual-layer medium developed by Iwasaki and co-workers (Figures 6a and 6b), and a simpler perpendicular head (Figure 6c), less efficient than the Iwasaki configuration, but which requires access from only one side of the tape or disk. A conventional ring head (Figure 6d) can also be used with a perpendicular medium. This combination has been found effective in both theoretical modelling and experiment, and has been incorporated into a practical flexible-disk system.

Although the ring head is a very sensitive device for reading signals, questions have been raised concerning its effectiveness in recording truly perpendicular magnetiza-tion patterns. The use of two separate heads, a single perpendicular pole for recording and a ring head for reading, has been found advantageous. This combines the perpendicular recording abilities of the single pole with the reading sensitivity of the ring, and the arrangement gives a high output amplitude requiring access from only one side of the recording medium.

If one head is to be used for both recording and reading, then the ring head has a number of advantages. It apparently offers adequate recording performance, and when made with a very small gap has good reading sensitivity up to very high densities. The technology of ring head design and manufacture is well established.

Current materials research for perpendic-

magnetization.

ular recording involves the use of continuous thin films other than Co-Cr as well as barium ferrite particles. The latter are dispersed in a binder and coated on a flexible backing as in conventional videotapes. They thus may have some economic advantages over continuous metal films, which are made by plating, sputtering, or vapour deposition. Efforts are also being made to produce recording tapes that have needleshaped magnetic particles similar to those used in conventional audio and video tapes. oriented perpendicular to the surface.

#### **Current directions**


Proponents of perpendicular recording on Co-Cr claim that it not only has a relative freedom from demagnetization effects, but also a magnetic microstructure that lends itself to sharp, well-defined magnetic transi-Some longitudinally magnetized tions. metal films, in contrast, have been observed to form jagged, 'saw-tooth' transitions between regions of opposite magnetizations (see Figure 7); this characteristic, if applicable to longitudinal media generally would tend to limit transition sharpness and thus the achievable recording density.

Despite the importance of demagnetization phenomena and magnetic microstructure, a major limitation on magnetic recording density is the inherent resolution with which the head can record or read. This resolution necessarily deteriorates with increased spacing between the head and the

medium, but it is also affected by the head design. Head-to-medium spacing, which depends upon the smoothness of the recording surface, is a consideration that is common to perpendicular and longitudinal recording and may well prove to be the ultimate limiting factor in both.

But while all methods of magnetic recording operate under limitations imposed by head-to-surface spacing, they need not be equally sensitive to this aspect. There is some evidence that the use of a ring head with a perpendicular medium is subject to a stronger dependence upon spacing than that encountered with other head-medium combinations. The extra sensitivity to spacing appears to be involved in the recording, as opposed to reading, process. These findings do not imply that the ring head is undesirable for perpendicular recording, but they do emphasize the importance of the spacing phenomena and the need for further research in head design.

Research and development work on Co-Cr films, as well as other advanced recording materials, was begun at 3M some years ago. Figure 8a shows a plot of output amplitude v transition density for a Co-Cr coated flexible disk. It was recorded and read with a conventional ferrite ring head of the type used in VHS video cassette recorder. Performance is clearly superior to that of a disk coated with typical particulate material designed for VHS cassette tape, with respect to both the maximum output and the rate at

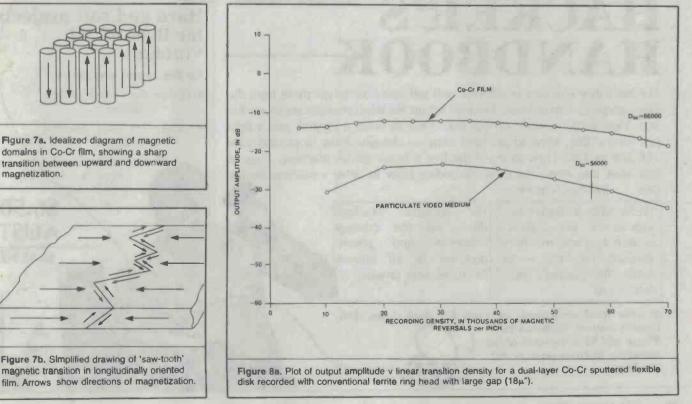

## TECHNOLOGY

which the output falls off with increasing density. Figure 8b shows results for the same media with an advanced video head of very small gap but still of conventional ring construction.

So what of the future?

The competition between the various modes of recording is to some extent a competition between the practical characteristics of the materials that make them possible. These characteristics include wear properties, chemical stability, and the economics of manufacturing. Also important are freedom from information 'drop-outs', due to defects, and noise properties, which depend upon surface smoothness and magnetization structure. Almost certainly, no one material will be found best for all applications.

The advanced materials designed for perpendicular magnetization have achieved impressive recording densities in the laboratory and are now moving into practical applications. The first will apparently be in the area of disks for digital data. However, only further development and extensive testing in the field will be able to determine the ultimate impact of materials such as Co-Cr upon video recording.


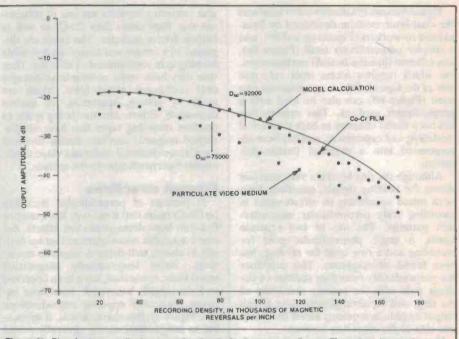


Figure 8b. Plot of output amplitude v recording density for the same medium as Figure 8a, with an advanced video head with a small gap (10.5u").

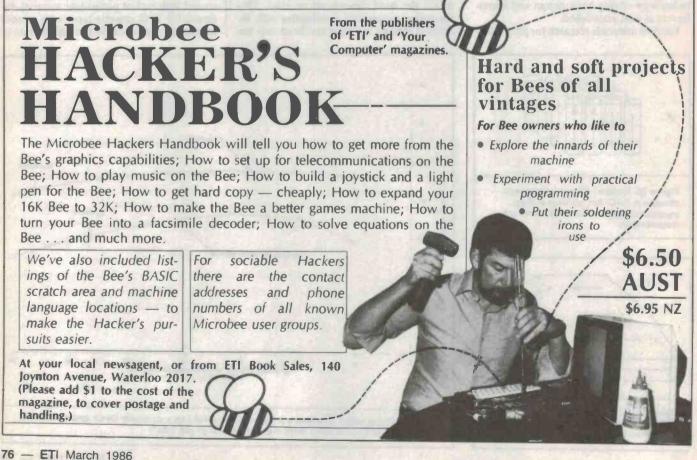

## **STARTING ELECTRONICS 12**


# FINDING THOSE FAULTS

Building a project is often the easiest part; getting it going is where the fun really begins. Fault finding is like trying to solve a murder mystery, clues abound, but the 'red herrings' confuse the issue. However, with a little perseverance and 'knowhow' many faults can be traced without needing expensive equipment and a high technical knowledge. Too good to be true? Read on, and find out the things the text books don't tell you!
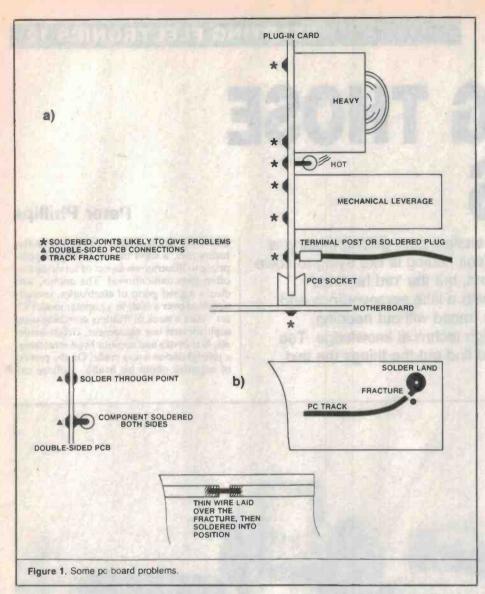
## **Peter Phillips**

BEFORE DESCRIBING FAULT finding techniques, a short but true story is appropriate to illustrate an aspect of servicing that often goes unmentioned. The author, who claims a good grasp of electronics, recently agonised over a fault in a popular model TV set. After a week of fruitless searching using sophisticated test equipment, circuit manuals, text books and copious head scratching, a painful decision was made. On the pretext of inquiring about his health, a phone call





was finally made to a friend whose livelihood is TV servicing.

Following his advice and a spot of soldering around a terminal post totally remote to the area where the fault *should have been*, the set was soon working perfectly. Embarrassed and humbled, the next question was how the fault had been found in the first place. "By carefully going around the set with the back end of a screwdriver, tapping here and there." He then continued to rub it in by suggesting that technical knowledge was often a hindrance, and that many faults could be found using the 'non textbook' approach.

Before the more technically minded readers wince in horror, it is not intended to promote the 'hit it with a hammer' technique, but rather to impart some of the more commonly used ploys in tracing the problem.

#### **Fault categories**

A fault in a piece of equipment can be classified in three ways. The first is the problem occurring in a unit that, prior to the fault, worked normally. Classified as a breakdown, this type of fault is the most typical, and is generally the result of a component failure. Another fault category is a construction error in a circuit, likely to be encountered by hobbyists, both experienced or otherwise. The final type, the design error, is the nastiest and is often assumed by frustrated project builders. It should however be considered only when all else fails.

Another fault variety, not so much a category as it can fit into those already described, is the intermittent fault. Intermittents are very difficult faults to find; Murphy's law will ensure that the problem occurs only when your back is turned. Even so, the beginner can often solve these faults, given the right approach. Yet another variation on the theme is the possibility of two or more independent faults occurring simultaneously.

If a project fails to work after its construction, try to determine which of the three categories the fault fits. If this is done prior to fault finding, a lot of time wasting can be avoided. For example, rule out design error by asking around to see if anyone else has experienced problems. Where a category cannot be determined, assume the error is a constructional one, as it is unlikely the components are faulty if they were purchased new.

#### The breakdown

A fault in previously proven equipment will be in a component, a faulty connection, a printed circuit board or will be the result of an accident — such as a watering when the pot plant was attended to. The servicing approach should commence by examining the events surrounding the fault. If the appliance belongs to someone else, don't always take their story as gospel. Few people are truly objective in describing a fault, particularly if they are embarrassed about the circumstances. Dropping the thing down two flights of stairs is often described as "a minor bump". Details to establish include any previous history of the fault, other related problems, even weather conditions at the time. Like solving a crime, any information that can give a lead should be sought.

Before removing covers, identify for yourself what symptoms the device is exhibiting. Identify unusual sounds, smells, visuals, vibrations, or odd behaviour of any sort. Try all controls, identify exactly what is working and what is not, and become very familiar with the specific problems. Once clear on the symptoms, remove the necessary covers and repeat the exercise, this time looking all around the circuitry. A bit of gentle probing may bring to light possible problems. Ensure all plug-in cards are correctly positioned, and wobble any plug and socket combinations. Also apply pressure to any components (ICs etc) that are socketted, generally satisfying yourself that the problem is not the 'poor connection' variety. Naturally, do all of this with great care, turning off the power if any doubt exists as to safety for yourself or the equipment.

If the device is more than a few years old, it often pays to spray contact cleaner on all switches, plugs and sockets. Do this with the power off and methodically separate all connectors, applying the spray (the non-oily sort) to both unions. Removing ICs from their sockets (use an IC extractor), and spraying the sockets is a part of this exercise which even if unsuccessful in establishing the fault, constitutes maintenance of a useful type. Observe the orientation, and don't mix the ICs around.

#### The printed circuit board

Having ensured that the problem is more than a bad connection in a terminal or plug and socket combination, try the 'tap' test. Tapping lightly with the plastic end of a small screwdriver can often bring to light a poorly soldered joint. As solder has little mechanical strength, likely problem areas are those where some physical strain is involved. Soldering in areas with heavy components, or where subject to heating, with pc mounted plugs or sockets should be examined carefully. Gently wobbling large components or terminal posts and observing the soldered joint can often identify a dry or broken connection. Badly soldered joints may not manifest themselves for a number of years, and are the cause of many problems. Figure 1(a) shows some of the 'classic' instances where soldered joints are likely to fail.

Flexing the board (gently) can identify possible problems with pc tracks or connection points. If the fault is apparently corrected by distorting the pcb, localise the area as much as possible, then go to work with a soldering iron and a magnifying glass. Double sided pcbs are more prone to soldering failures where no physical strain on the connection is involved compared to single sided boards. Careful resoldering of all connections in the suspect area often does wonders.

Breaks in pc tracks are not uncommon, particularly at the point where the track joins the solder land. Some servicemen, after having tried everything else, run solder over every pc track in the hope of fixing invisible fractures. Repairing a track fracture should be done by cleaning the track where soldering is to occur then overlaying a piece of wire across the break and soldering it into position. Figure 1(b) illustrates these points.

#### Locating faulty components

If the appliance has not responded to the 'prod and probe' test, then a component is probably the problem source. The simplest way to find out which one, is to replace each component, one by one, until the fault is encountered. This basic method is known as component 'jockeying', and is often the quickest way where the component count is small. Start with the plug-in components, usually the ICs, replacing one at a time those ICs you have replacements for. Sometimes two similar ICs on the board can be swapped, and the effect noted. Always observe the behaviour of the unit after each component change, and be continually on the lookout for clues.

As a basic rule, try all the active components first. If a replacement is not available, test each component as best as possible using the methods described further on in this article. Where there is a large number of components, an attempt should be made to identify the *area* containing the fault. Touching each component to determine its operating temperature can often identify either a faulty component or the problem area. A cold component, or one that is too hot may be the clue. Cold components usually indicate a lack of power to the section, overheating can suggest many things., Sometimes the faulty section can be isolated using basic tests. If the equipment contains an audio amplifier, applying a signal to the volume control will help identify if the amplifier section is operating. This is done by touching the centre terminal of the volume control with the blade of a screwdriver held in contact with the fingers. Listen for hum or noise that only occurs when the signal is applied. If an output results, the problem is before the volume control. No output suggests a fault in the power supply, the amplifier or the speaker circuitry. Power supplies can be tested using a voltmeter, or even a test lamp. If heat is being generated within the power supply circuit it is probably working, but further tests should be conducted to confirm that all sections of the circuit are producing the required voltages.

#### Faults in active components

Active components generally break down more often than passive ones. As ICs are often in sockets, searching for a faulty chip is usually the best place to start. The quickest way to establish if an IC is faulty is to replace it, but it should be remembered that there might be more than one fault. So leave the new IC in the circuit even if the problem is not found, and go on to the next.

However, some faults, particularly those in the power supply, may have caused the demise of every on-board IC, and as fast as you replace them, the fault destroys them. To avoid burning out your entire stock of components try to test each IC as it is removed. This is often difficult, but is preferable to losing all your ICs. Trying each chip in another known piece of equipment can help find the faulty one, or at least prove that all the ICs are working.

Transistor replacement should follow the integrated circuit check, unless all the ICs happen to be soldered in. The idea is to test the easiest things first, and transistors are more easily replaced than ICs if sockets have not been used. Often a replacement transistor is unavailable, thus requiring the testing of each of the transistors. Generally transistors should be removed from the circuit for testing, as parallel components can give rise to incorrect readings. Figure 2 illustrates how to test a transistor using a multimeter. When using an analogue meter, set it to its low ohms range, and remember that the polarity of the leads is reversed for ohms measurement, that is, the black lead becomes the positive potential. A digital multimeter should be on the diode check setting, and its lead polarity not reversed.

If all the ICs and transistors appear to be working, and checks have shown no bad connections, pc track break or power supply problem, then the remaining components should be examined. Be wary of accidentally introducing more faults during component replacing, taking care not to bridge pcb tracks, or to put a component in the wrong way. Only deal with one device at a time to prevent mixing them around, and always test the unit after each component replacement.

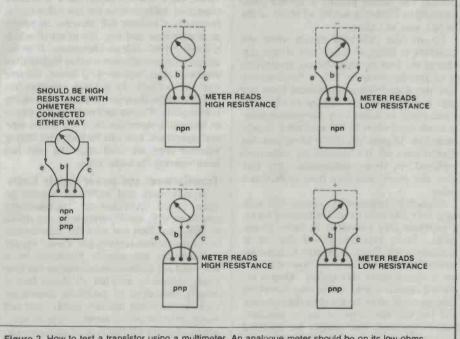


Figure 2. How to test a transistor using a multimeter. An analogue meter should be on its low ohms range. Note that the polarity of the meter will reverse; the black lead (---) becomes the positive potential. Digital meters should be on 'diode' test without reversed lead polarity.

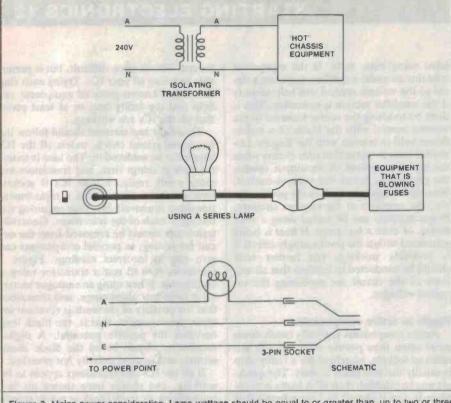


Figure 3. Mains power consideration. Lamp wattage should be equal to or greater than, up to two or three times, that of the equipment being serviced.

#### **Faults in capacitors**

A valuable hint on servicing equipment exhibiting peculiar faults is to test the capacitors associated with the power supply. If hum is present in a loudspeaker, a likely cause is a filter capacitor. Many a peculiar fault has been found by merely going around the circuit placing a known good electrolytic capacitor across all those in the circuit, one at a time.

Ensure the polarities match when the subsitute is being attached and always discharge the test capacitor before reapplying it to another section. This is necessary in case the stored voltages obtained from one part of the circuit do damage to the next. Electrolytic capacitors are the passive components most likely to fail with time. Equipment over 10 years old that is being restored should have all the electrolytic capacitors replaced, as these components 'dry out' over the years, and lose their capacitance value.

Capacitors required to operate with voltages over 100 volts or so can become leaky, a problem very prevalent in valve equipment. Again replacement of the lot is recommended. Some capacitors become intermittently open circuit; the Styroseal variety is notorious in this regard. Always replace a capacitor with one having a working voltage equal to or better than the original, and use the same type as far as possible. Paper capacitors can usually be replaced with polyestor types, but this is about the only exception.

#### **Faults in resistors**

Resistors, diodes, transformers, wiring and so on can all become faulty. But the possibility of this is less than for those components already discussed, meaning these items are best checked last. Resistors, particularly old style types can change their value; high value resistors have a greater chance of doing so than the low value types. Normally a resistor will increase its resistance with time and use, the effect of which is easily tested with an ohmmeter. If an incircuit resistor indicates a value higher than marked value, replace it, if lower, lift one end and recheck. In general, resistors are reliable unless their power dissipation rating is exceeded. Wire wound resistors are prone to becoming open circuit, even under normal operation, and can be found by testing whether they are cold after the unit has been running for some time.

#### Transformers and power supply faults

Transformers and inductors usually go open circuit. Alternatively, transformers can 'burn out', made obvious by the smell. In this case, find out why the transformer burnt out before replacing it. Power supply transformers are usually protected by a fuse, and any inclination to increase the fuse rating should be avoided. A blown fuse is usually indicative of problems associated with circuitry that handles power, and not necessarily the power supply. A good servicing technique for this type of problem is to apply mains power to the unit being repaired through a 240 volt lamp in series with the power point and the device. Choose a wattage up to twice that required by the unit under test, and don't re-apply the mains directly until the fault is fixed. Figure 3 shows an arrangement that can be easily constructed for this.

Many domestic appliances are 'hot chassis'. This means that regardless of the way the active and neutral wires are connected, the metal chassis, or 'ground' of the device, is above the earth potential. Connecting an earth wire from a piece of test equipment can result in damage to the device being repaired, blown mains fuses, or similar disasters. Likewise, the serviceman runs a great chance of receiving a lethal electric shock. The use of an isolating transformer, a 240 volt to 240 volt transformer is essential. The power rating of the isolating transformer should equal or exceed that of the equipment. Note particularly that a 'Variac', or variable transformer is not suitable for this task

Diodes can become open or short circuit. Power diodes in a bridge circuit usually go faulty in pairs, but it is good practice to replace the lot anyway. Be careful to use diodes that match the original, particularly as regards their PIV. As already mentioned, power supply capacitors often become faulty, particularly the main filter capacitors. This is best confirmed by placing a similar value capacitor across the existing component. Be wary of the spark during charging, and discharge the test capacitor after its removal. This is necessary to prevent the possibility of it being picked up, (perhaps by the family dog), with the recipient being the discharge path for the often high potentials that can be stored for hours.

#### The intermittent fault

Intermittent faults are the bane of the serviceman. Difficult to find, you can never be sure if you have really fixed the fault. Bad soldered joints are typical intermittent faults, and are best found by the 'prod and probe' method. It often pays to simply spend time carefully resoldering every connection, taking care to note that each connection is in fact a good one. The possibility of merely dressing up a dry joint or a faulty connection is high, and the use of a magnifying glass is recommended.

An intermittent fault in a component can often be found using a can of freeze spray. If the general area of the fault can't be identified, spray methodically over the whole board. If the component is temperature sensitive, this technique will often find the problem. Often the fault will only appear after a certain operating temperature has been reached, in which case normal operation will follow when the faulty component is cooled down by the spray. By using a nozzle on the spray can, its effect can be localised, helping considerably in establishing the fault in a crowded layout. Heating a suspected component with a soldering iron, then cooling it with the spray is another effective method of seeking out these types of problems.

In some cases, particularly in complex equipment, it is impractical to use the methods described above. When the intermittent fault is not temperature sensitive and all soldered joints have been tested, it becomes essential to narrow the problem down by identifying the area causing the problems. Various methods are used, including transferring plug-in cards from another unit of the same type, or attaching analysing equipment. The main requirement for this type of fault finding is patience. If parts are available, components from a whole section can be replaced, repeating the process until the fault is found.

#### Fault finding flow chart

Figure 4 shows a flow chart that summarises the fault finding technique described so far. No flow chart can cover all situations, but the suggested 'plan of attack' is a good way to start. Critics may suggest the chart is too simple or that the order is wrong. Experience will soon show you how to adapt the chart to particular situations, and its presentation is included merely as a pictorial means of helping the budding serviceman.

With the chart are four basic rules. The rules are not in any specific order, but the intended message is to be scientific about the task. Luck has always played a part in servicing, but you can never rely on it. Remember that if the device used to work, given enough time and effort it will again.

#### **Typical construction errors**

It is oft quoted that 'he who never made a mistake never made anything'. The construction error is not necessarily the province of the amateur, although experience generally helps in minimising these types of problems. Typical errors in circuit building are faulty soldering or pc track bridging, incorrect component orientation, incorrect components, mixed up wiring in external hardware, and so on. The likelihood of poor soldering decreases with experience, and for this and other obvious reasons, complex projects should only be undertaken after success with simpler exercises.


An incorrect component, or incorrect device orientation sound obvious enough problems but some bizarre possibilities are worth mentioning. Figure 5 shows some of the possibilities that constructors should be aware of. If a kit has been purchased it is possible that some components, particularly transistors, may have been substituted for that specified with the alternative having a different lead configuration from the original. Don't assume that the replacement device will always match the pcb layout provided for it. Similarly, components from several manufacturers may make up the kit,

with different standards being employed to identify the polarisation. Typical of this is the way manufacturers show the polarity of an electrolytic capacitor. Some employ an arrow to point to the negative lead, others use the arrow to identify the positive lead.

Zener diodes can often be mistaken for conventional diodes, just as FETs, thyristors and other active devices may look the same. More insidious is the possibility of confusing the colour code of a resistor. A 12 ohm resistor, coloured brown, red, black can be easily mistaken for a 1k ohm resistor the code of which is brown, black, red. Low value resistors using silver or gold as part of the code for the value can be confused with others using these colours for the tolerance band. Another problem concerns capacitor value markings. It is very easy to mix up the decades, for example, a 0.01  $\mu$ F capacitor with a 0.001  $\mu$ F capacitor. Integrated circuit polarising is usually identified with a recess on one end, or maybe with a dot next to pin 1. Some manufacturers mould two recesses in the case, one at either end, with one deeper than the other. The likelihood of inserting it the wrong way round is obvious. Switch connections are often confusing, and it usually pays to test which terminal is which with an ohmmeter.

#### Soldering errors

To help minimise soldering errors, particularly in missing a connection altogether, cut the component leads *after* they have been soldered. Generally a project kit will include instructions on the best way to go about building the circuit, with a preferred order of component installation. Ordinarily, wire links are first, followed by passive components, and active devices are in-

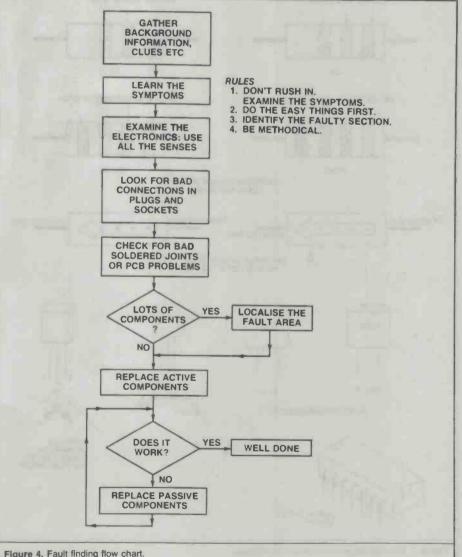

re 4. Fault finding now chart.

## **STARTING ELECTRONICS 12**


stalled last. To expedite construction, the builder will often insert a number of components, then proceed to solder them in. By trimming the soldering leads after soldering, missed joints can be found as construction proceeds. By methodically doing a section at a time, a constant check can be maintained on the soldering processing, with simultaneous checks being made for solder bridges.

The rule is, check as you go, and recheck again and again. A magnifying glass is an excellent way of examining the board. Provide good lighting, and always fix an error as soon as you find it. Look also for strands of wire from multi-stranded cables that may be shorting across to another area. Wire of this type should be tinned before connecting it to the pcb, in order to solder the individual strands together.
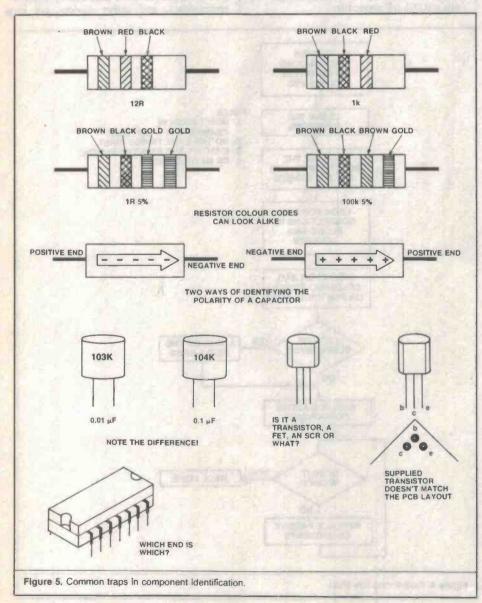
#### Finding construction errors

As in all fault finding situations, an organised approach is essential. Being very open-minded about the fault is essential. All too often an issue is clouded with preconceptions about the nature of the fault. For example, a component that is too hot on the left side of the board may well mean that the fault is on the opposite side. How often have servicemen stared at a dead board only to find later that the power point wasn't turned on? Worse still is the possibility of replacing a good component with a faulty one, thus introducing another fault, having found the even fault or unknowingly.

Locating a construction error is similar to finding any fault, except many more possibilities are likely. Being aware of these possibilities is a good start, and the reader



82 - ETI March 1986

should note carefully the information already presented. Where possible, each section of a board should be proven as construction proceeds, particularly in complex circuits. For example, the power supply can often be constructed first and checked before anything else is built. Fault finding by confirming a section at a time, either during construction or servicing, is often the best means of narrowing down the area containing the problem.

Many constructors, when confronted with a problem in a newly built project proceed to strip it down and rebuild it. This is not a good idea, as apart from the work involved, the chances of reintroducing the fault are high. The probability of more faults occurring is also enhanced, as by now each component has undergone a lot of stress, just as the pcb will have received a caning. Unless the original job is of a very poor standard, persevere with the first attempt.

#### **Design errors**

As much as project designers try their best to prevent mistakes in the final presentation, errors do occur. These can be either printing errors, or a straight out problem in the design. With some designs values of components are critical and because of possible variation between individual items, duplicating the device may be a matter of chance. Others may under-rate component specifications, causing a premature demise of the unit. Designs with these faults are unusual, and represent a poorly researched product.

In general, if a project has been around for a while, printing errors will have been discovered and listed in an errata section in the relevant magazine. The smart constructor always waits until the next issue before building the project! The assumption that a design error is present is often made prematurely; it is always easy to blame someone else when the thing doesn't work. It is worthwhile remembering that an electronics magazine relies on the quality of its construction projects, as a reputation is at stake.

#### Summary

This article has purposely stayed away from describing any technical fault finding methods. A knowledge of Ohm's law and its implications is very useful, and in many cases is indispensible. Given this background and a multimeter, servicing becomes easier, as faults can often be found very quickly. By noting the hints presented here, those starting out in electronics can give it a try.

Although they may not care to admit it, many servicemen repair equipment that they know nothing about by using the methods that have been outlined.

## **COMPUTING NEWS**

## **The DSE Multitech PC**

DSE and Multitech, one of the largest PC manufacturers outside the US, have released an IBM-compatible computer, the **DSE** Multitech.

It incorporates such features as RS-232C serial port, real time clock/calendar with battery backup, sound circuitry, parallel printer port and an IBM-compatible expansion slot (on Systems One and Two only).

Other features include an 8088 16-bit internal processor running at 4.77 MHz; 256 expanded ASCII character set; an IBMcompatible colour graphics interface with 640 x 200, 320 x 400 graphics resolutions and 16colour text mode; a video interface with special flicker free circuitry to reduce eve strain; RGB and composite video monitor outputs; joystick/game adapter port; and an inbuilt speaker.

The PC is compatible with the MS-DOS operating system, so there is a large software base from which to draw, including the Flight Simulator, Jet, Sidekick, Lotus 1-2-3, Open Access, Aura or Enable. Most of the popular software is ready to run.

The computer is available in

three pre-configured versions:

The System One (Cat X-8000) for \$1345 is the low cost entry level version. It comes complete with 360K floppy disk drive, 128K of RAM, MS-DOS version 2.11 and three months warranty.

The System Two (Cat X-8001) for \$1995 comes with two 360K floppy disk drives, 256K of RAM, MS-DOS 2.11, the Easy wordprocessing package from MicroPro, complete with spelling checker and six months onsite service in major capital centres.


The System Three (Cat X-8002) for \$3995 is the DSE Multitech business system with 512K of RAM, one 360K floppy disk drive, one 10 MB hard disk drive, and the Aura package which will perform all normal business operations such as wordprocessing, spreadsheet, database and information management. It also comes with six months on-site service agreement (major capital centres



Using the DSE Multitech.

only). System Three can be in- See our review on page 89. stalled free in your home or business (again, major capital centres only).
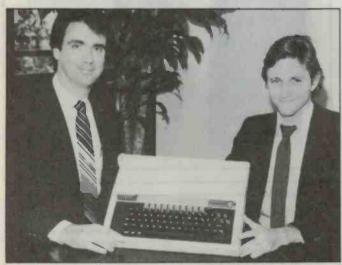
## **Modem development** by Barson in Australia



Bruce Reid of Netcom and Barson Research's Steve Lucket with the internal modern card mounted on the lid of the BBC microcomputer.

Barson Computers Australasia is receiving both Australian orders and international inquiries. for an innovative modem product the company has developed for the BBC microcomputer.

The auto-dial modem, developed in NSW by Barson Research and DataNetComm Australia, is being manufactured by Netcom in Sydney, and built into the BBC systems at Barson's manufacturing plant in North Rvde.

Netcom has already begun delivery of the first 500 units of the product, sold to fill an order from Thorn-EMI.

According to Julian Barson. Barson's Managing Director, "The unit uses new chip technology, which has enabled us to design a unit compact enough to fit inside the slim BBC computer cabinet. We were fortunate that Netcom had both the technology and the equipment to manufacture the unit for us."

The new modem also includes on-board software that can turn the BBC computer into a videotex terminal. Other features allow the user to dial up other systems automatically, to store the text they receive, and a printer driver enabling information to be sent to a printer.

The software also enables the user to select either 300/300 or 1200/75 baud communication speeds.

Mr Barson said development of the product began in June this year. "Since then we have received a number of serious inquiries from places such as Hong Kong and the USA. Product shipped to these countries will all be manufactured in NSW."

For further information contact Barson Computers, 335 Johnston Street, Abbotsford, Vic 3067. (03)419-3033.

#### X.25 gateway for BBC networks

BBC/Acorn has released the Econet-X.25 gateway to allow those with Econet terminals access to host computers connected to X.25 networks such as Austpac. Econet-X.25 supports up to seven window sizes and data packet sizes up to 128 bytes. The system hardware is based on a BBC 6502 microcomputer and two separate Z80 processors running at 6 MHz, 96K of RAM and a 32K EPROM. For more information contact Barson Computers, 335 Johnston St, Abbotsford, Vic 3067. (03)419-3033.

#### Graphics emulation software for IBM-PC

Grafpoint Corp has released the TGRAF-07 software package for the IBM-PC, XT and AT. The package emulates such functions as zoom and pan, which can be assigned to each of the 64 windows that are possible on the screen. The package, with appropriate hardware, promises to be cheaper than the Tektronix (R) terminal. It is available from Dimension Graphics, 265 Miller St, Nth Sydney, NSW 2060. (02)929-5855.

#### **Microsoft COBOL tools**

Microsoft has introduced a set of utilities — or COBOL tools — for programmers developing, debugging, maintaining and enhancing on MS-DOS operating systems. The tools include a symbolic debugger, a cross-reference utility, a menu handler and a mouse input module.

#### \$4m worth from IBM Aust

Idaps Australia has recently installed \$4m worth of hardware and software from IBM Aust in its Melbourne data centre. The equipment includes a 3083EX mainframe with 16 Mbytes of main memory and 16 channels, seven 2.5 Mbyte 3380 disk drives, three 3880 disk controllers, a 3725 communications controller as well as workstations and workstation controllers.

#### Intel source code editor for PC-DOS

Intel has introduced an editor for creating and editing source and object code as well as text. It's called Aedit-DOS, designed specifically for engineering software needs. It runs on computers using the PC-DOS 3.0 operating system, Intel's Intellec Series III and IV development systems and on Intel's iRMX operating system. For more information contact Intel Aust, Level 6, 200 Pacific Hwy, Crows Nest, NSW 2065. (02)957-2744.

#### Tasman word processor

The Tasword 6128 word processor for the Amstrad CPC-6128, published by Tasman Software of the UK is being distributed in Australia by Dolphin Computers. Dolphin is also distributing a spelling check program called Tas-spell for the Amstrad CPC-664 and 6128 computers, and the Sureshot Supreme joystick. Dolphin computers is at 2/7 Waltham St, Artarmon, NSW 2064. (02)438-4933.

#### Forth for IBM-PC and Apple lle

Forth language programs and data are now available from Waveonic Associates. A full screen editor and assembler are provided in relocatable, binary overlays. A CForth compiler is also available to speed up critical applications. This series of Forth implementations is also available for 8080, Z80, 8086/88

#### CLUB CALL

Those interested in the LE'VZ200/300 User Group can contact John D'Alton, 39 Agnes St, Toowong, Qid 4066. (07)371-3707.

The electronics and computer club of the Randwick-Botany Police Citizens Youth Club meets at 6 pm on Thursdays at Bunnerong Rd, Daceyville, NSW. Membership is free.

### BRIEFS

and 68000 based processors. For more information contact Waveonic at 199 Watts Rd, Wilson, WA 6107. (09)451-2946.

#### Aust developed LAN product

The first LAN component developed by Digital Equipment's Artarmon design and manufacturing centre is a statistical multiplexer server. Called the MUXserver 100, it connects remote, non-intelligent terminals to hosts in the Ethernet local area network. It's available for \$10,000 or so. Digital Equipment is at the Northern Tower, Chatswood Plaza, Railway St, Chatswood, NSW 2067.

#### File saving system

Datacraft Office Systems has available the Irwin Backup Tape subsystem which creates duplicate file copies on hard disk, with assured compatibility between tape drives. The subsystem plugs into an existing floppy connector on the back of a PC and is said to store 10 million bytes on a single cartridge, in about 16 minutes which includes the verification process. For more information contact Datacraft at 1st Floor, 30 Atchison St, St Leonards, NSW 2065. (02)438-3688.

#### **Diskette copying**

Nashua is distributing three devices to facilitate disk copying processes. The Nashua Automatic Diskette Copier formats a blank diskette for the computer concerned, copies information on it from an original and checks it. The more complex Series One Duplicator can be configured in various formats and reportedly copies one double sided diskette in up to 60 seconds. The Formaster Sprint, another copying device, consists of a board/software arrangement which uses an IBM-XT as host to produce Apple, Commodore or IBM formatted disks. For further information contact Nashua, 34 Chandos St, St Leonards, NSW 2065. (02)925-3111.



#### The main event - PC86

The sixth Australian Computer Show (PC86) is to be held this month, from 12 to 16 March at Centrepoint in Sydney. Companies exhibiting include IBM, Apple, Commodore, Tandy, Hewlett-Packard, Sperry, Barson, Teleco, Epson, Microsoft and Ericsson.

## MICROBEE COLUMN

## **Halley's Comet** Noel Bailey, Maryland, NSW 2287

This program calculates the declination and right ascension for Halley's Comet. All one need enter is the date. The algorithm has been taken from the 2nd edition of Practical astronomy with your calculator by P. Durfett-Smith, published by Cambridge University Press. The author states that the precision of the algorithm will be limited due to the influences of the planets, however the comet should still be within one degree of the calculated position.

The accuracy of the program has been checked against published values for 1985 and this program is within one degree. For 1986 I have no published values, however, the calculated values do appear very close to a track drawn on a published star chart right up to 1 June, 1986.



```
00100 REM "HALLEY" PROGRAM TO FIND THE DECLINATION AND RIGHT
00110 REM ASCENSION OF HALLEY'S COMET - FROM "PRACTICAL
00120 REM ASTRONOMY WITH YOUR CALCULATOR" - P DUFFETT-SMITH
00130 REM PUBLISHED BY CAMBRIDGE UNIVERSITY PRESS, 2ND ED 1981.
 00140 REM WRITTEN IN BASIC BY NOEL BAILEY 27 OCTOBER 1985
 00150 PRINT*HALLEY'S COMET PROGRAM. GIVE ME THE DAY, MONTH*
00160 PRINT*AND YEAR AND I WILL CALCULATE THE RIGHT ASCENSION*
00170 PRINT*AND DECLINATION FOR THE COMET.*
 00180 INPUT DAY, MONTH, YEAR", D7, M7, Y6
00190 Y=INT(Y6): Y7=Y6
 00200 IF M7 > 2 THEN 260
00210 M7 = M7-1
 00220 IF Y-Y/4#4=0 THEN LET M7=M7#62ELSE LET M7=M7#63
00230 M7=M7/2
 00240 M7=FLT(INT(M7))
 00250 0010 300
 00260 M7=M7+1
 00270 M7=M7+30.6
 00280 M7=FLT(INT(M7))
00290 IF Y-Y/4#4=0 THEN LET M7=M7-62 ELSE LET M7=M7-63
00300 M7 = M7+D7
00310 D6=0
 00320 IF Y6 = 1980 THEN 360
00330 FOR Y=1980 TO INT (YA)-1
 00340 IF Y-Y/4#4=0 THEN LET D6=D6+366 ELSE LET D6=D6+365
00350 NEXT Y
00360 D6 = D6+M7: REM TOTAL DAYS SINCE THE EPOCH 1980
 00370 D1=D6
00370 D1=D6
00380 Y1=D6/365.2422+1980
00390 Y2 = Y1-1986.112
00400 T1 = 76.0081: M1 = 360*Y2/T1
00410 IF ABS(M1)>360 THEN LET M1 = M1 - FLT(INT(M1/360)*360)
00430 P1 = 355/113
00440 M1 = M1*P1/180
00450 REM NEWTON'S METHOD OF SOLVING FOR E
00460 T1 = 1
00470 D0 = T1/1E5
00480 T0 = T1
00490 GOSUB 590
00500 F1 = F0
00510 T0 = T1 + D0
 00520 GOSUB 590
00530 G1 = (F0 - F1)/D0
00540 T2 = T1 - F1/G1
00550 IF ABS(T1-T2) ( IE-5 THEN 570
00560 T1 = T2: GOTO 470
00570 REM
00580 GOTO 610
00590 F0 = (T0-0.9673#SIN(T0))-M1
00600 RETURN
00610 E0 = T1
00620 V0 = 2*ATAN(7.7564215*SIN(E0/2)/COS(E0/2))
00630 V0=V0*180/P1
00640 L0 = V00170.0110
00650 R0 = 1.1543197/(1+0.9673*COS(V0*P1/180))
00660 P0 = 0.3050573*SIN((L0-58.1540)*P1/180)
00670 P0 = ATAN(P0/SQR(1-P0*P0))*180/P1
00680 Y0 = SIN((L0-58.1540)*P1/180)*COS(162.2384*P1/180)
00490 X0 = COS((L0-58.1540)*P1/180)
00700 L1 = ATAN(Y0/X0)*180/P1
03710 IF Y0>0 AND X0 <0 THEN LET L1 = L1+180
00720 IF Y0<0 AND X0 <0 THEN LET L1 = L1+180
```

```
00730 IF YOKO AND X0 >0 THEN LET L1 = L1+360
 00740 L1 = L1+58.1540
00750 IF L1 > 360 THEN LET L1 = L1-360
00730 IF LI > 360 THEN LET LI = LI-360
00760 RI=R0¢COS(PORFI/180)
00770 REM NOW THE CALCS FOR THE EARTH
00780 NI = 360/365.2422*DI/1.00004
00790 NI = NI-FEL(INT(NI/360)*360)
00800 M0 = NI*98.83354-102.59640
 00810 Z0 =360/P1#0.016718
00820 Z1 = SIN(M0*P1/180)
00830 L2 = N1+Z0*Z1+98.83354
00840 IF L2 > 360 THEN LET L2 = L2-360
00850 IF L2 < 0 THEN LET L2 = L2+360
00860 VI = L2-102.59640
00870 R2 = (1-.016718*,016718)/(1*.016718*COS(VI*P1/190))
00890 IF R1 > R2 THEN 930
00890 Z0 = R1*SIN((L2-L1)*P1/180)
00900 Z1 = R2-R1*COS((L2-L1)*P1/180)
 00910 D2 = 180+L2+ATAN(20/21)+180/P1
00910 D2 = 100+L2+ATAN(20/Z1)+100/P1

00920 C0TO 940

00930 Z0 = R2*SIN((L1-L2)*P1/180)

00940 Z1 = R1-R2*COS((L1-L2)*P1/180)

00940 Z1 = R1-R2*COS((L1-L2)*P1/180)

00950 D2 = ATAN(20/Z1)*100/P1+L1

00960 IF D2 < 0 THEN LET D2 = D2+360

00970 Z0 = R1*SIN(P0*P1/180)/COS(P0*P1/180)*SIN((D2-L1)*P1/180)

00970 Z0 = R1*SIN(P0*P1/180)/COS(P0*P1/180)*SIN((D2-L1)*P1/180)

00990 B0 = ATAN(20/Z1)*180/P1

01000 Z0 = SIN(D2*P1/180)*COS(23.44185*P1/180)

01010 Z1 = SIN(D2*P1/180)/COS(80*P1/190)*SIN(23.44185*P1/180)
 01010 Z1 = SIN(B0*P1/180)/COS(B0*P1/180)*SIN(23.44188*P1/180)
01020 20 = 20-21
01020 20 = 20-21
01030 21 = COS(D2*P1/180/P1
01040 A1 = ATAN(20/21)*180/P1
01050 IF 20/0 AND 21(0 THEN LET A1 = 180*A1
01050 IF 20(0 AND 21(0 THEN LET A1 = 180*A1
01070 IF 20(0 AND 21)0 THEN LET A1 = 360+A1
01080 A1=A1/15
 01090 Z0=SIN(B0+P1/180)+COS(23.44188+P1/180)
01100 Z1=COS(80*P1/180)*SIN(23,44198*P1/180)*SIN(D2*P1/180)
01110 Z2= Z0+Z1
01120 51 = ATAN(22/SQR(1-52#52))#180/P1
01120 H = INT(A1);H = INT(A1-FLT(H))#60)
01140 PRINT*RIGHT ASCENSION = ";H;" MOURS ";H;" MINUTES"
01150 D = INT(S1):M = INT((S1-FLT(D))+60)
 01160 PRINT DECLINATION
                                                           = ";D; DEGREES ";M; MINUTES"
```

#### >D RUN

HALLEY'S COMET PROGRAM. GIVE ME THE DAY, MONTH AND YEAR AND I WILL CALCULATE THE RIGHT ASCENSION AND DECLINATION FOR THE COMET. DAY, MONTH, YEAR 17, 5, 1985 RIGHT ASCENSION = 5 HOURS 5 MINUTES DECLINATION = 16 DEGREES 6 MINUTES

#### >RUN

HALLEY'S COMET PROGRAM. GIVE ME THE DAY, MONTH AND YEAR AND I WILL CALCULATE THE RIGHT ASCENSION AND DECLINATION FOR THE COMET. DAY, MONTH, YEAR 1,12,1985 RIGHT ASCENSION = 1 HOURS 3 MINUJES DECLINATION = 13 DEGREES 3 MINUTES

#### RUN

HALLEY'S COMET PROGRAM. GIVE ME THE DAY, MONTH AND YEAR AND I WILL CALCULATE THE RIGHT ASCENSION AND DECLINATION FOR THE COMET. DAY, MONTH, YEAR 20,3,1986 RIGHT ASCENSION = 19 MOURS 42 MINUTES DECLINATION = -23 DEGREES -40 MINUTES

#### RUN

HALLEY'S COMET PROGRAM. GIVE ME THE DAY. MONTH AND YEAR AND I WILL CALCULATE THE RIGHT ASCENSION AND DECLINATION FOR THE COMET. DAY, MONTH, YEAR 10, 4, 1986 RIGHT ASCENSION = 15 HOURS 15 MINUTES DECLINATION = -36 DEGREES -23 MINUTES

#### RUN

HALLEY'S COMET PROGRAM. GIVE ME THE DAY, MONTH AAD YEAR AND I WILL CALCULATE THE RIGHT ASCENSION AND DECLINATION FOR THE COMET. DAY, MONTH, YEAR 1,5,1986 RIGHT ASCENSION = 10 HOURS 23 MINUTES DECLINATION = ~6 DEGREES ~27 MINUTES


#### DUTH: DEE

## MICROBEE COLUMN

#### Three dimensional **PI** chart
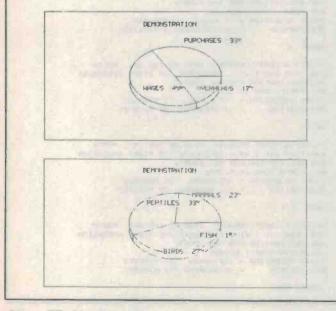
#### **Richard Bushell.** Baulkham Hills, NSW 2153

This program will plot a 3D PI chart to The printer port can be changed by your specification in hi-res graphics. editing line 530. The screen can be dumped to an XX-For best results, the number of 80 type printer. The printer is set up segments should be restricted to a to run on the serial port at 300 baud. maximum of five. 00100 DN ERNOR 0010 670 00110 DIM A1(20), X(20), Y(20), S1(20), S2(20), P1(20) 00120 CL5 00130 PRINT TAB(22) "PI CHART" \TAB(19) "R. BUSHELL 1985" \ 00130 PRINT TABE221-PI CHART'\TABE149'R, BUSHELL 1985'\ 00140 REM Gesss INPUT DATA 00150 INPUT 'NEADING 7 'INIG 00160 INPUT 'NO. OF SECTIONS 7 'IS 00170 FOR 0-1 TO S: CLS 1 PRINT 'Section No. '0" name \*1:INPUT SIG(0) 00180 PRINT 'Data (or segment '0' '1:INPUT S2(0) 00180 TI-TI-S2(0) I NEXT 0 00200 FOR 0=1 TO S 00210 PI(0)=PI(0-1)\*52(0)/TIS100 00270 AI(0)=PI(0)=1344/50 00210 P1(0)=P1(0-1)+92(0)/T19100 00220 A1(0)=P1(0)=3.1416/50 00230 X10)=INT(255-COS(A1(0))+90) 00240 Y10)=INT(125-SIN(A1(0))+80) 00250 P1(0-1)=52(0-1)/T19100 00260 NEXT G 00270 P1(5)=52(0)/T19100 00280 CLS: MIRES 00500 IF A26(>Y\* AND A26(>Y\* TMEM END 00510 CUPS 10,15: PRINT (A35 32); 00520 PEM 408984 START PRINTER DUMP 00530 OUTLM4: RESTORE 630 00540 FOR X=336 TO 371 : READ Y 1 POKE X,Y 1 MEXT X 00500 FOR Y=0 TO 15 00500 FOR V=0 TO 6 STEP 8 : LPRINT CHR(27)\*K\*CHR(0)CHR(2); 00500 FOR V=0 TO 6 STEP 8 : LPRINT CHR(27)\*K\*CHR(0)CHR(2); 00500 FORV=0 TO 6 A-USR(336,61440+U\*168PEEK(61440+Y864+X); ; MEXT X 00500 LPRINT CHR(10); 00500 FORV=1 U : MEXT Y 00600 NEXT U : NEXT Y 00610 LPRINT CHR (27) \* 2\*CHR (7) 1 00610 LPRINT CHR (27):2\*CHR (7): C0202 END C03030 DATA 62,01,211,11,96,105,14,128,229,6,8,203,34,126,161 00640 DATA 60,23,203,194,35,16,245,122,205,69,128,225,203,57 00650 DATA 68,233,610,211,11,201 70660 TEN PREWER PCO OVERFLOW C0307 CLS : PPINT \*CATASTROPHIC SYSTEM ERROR - PROGRAM WILL RE-RUN \*:PLAY 1,215, 219,1 : RUN



## Reactance R. Wilkinson, Nelson Bay, NSW 2315 BBD18 CLS D022 PRINT 'NAME 'REACT'ance..... 10/0/04...R.WILKINSON." P0330 PRINT 'NAME 'REACT'ance..... 10/0/04...R.WILKINSON." P0300 PRINT 'A capacitor to a certain frequency." 00070 PRINT - a capacitor to a certain frequency." 00070 PRINT - based on frequency and 100 Pf Capacitor' 00070 PRINT - based on frequency and 100 Pf Capacitor' 00070 PRINT - based on frequency and 100 Pf Capacitor' 00070 PRINT - based on frequency is 00 Pf Capacitor' 00070 PRINT - based on frequency (10 Pf Capacitor' 000120 FOR Del TO Subo: NEXT 7 00120 FOR Del TO Subo: NEXT 7 00120 FOR Del TO Subo: NEXT 8 00120 FOR DEL TERSON 8 00120 FOR T 00230 U00+KEY01 IF U00+\*\*\* THEN GOT0230 ELSE IF U00+\*1\* THEN GOT0240 ELSE IF U00+ \*\* THEN GOT0130 ELSE IF U00+\*\*\* THEN GOT0 420 00240 INPUT \*(INDUCT) FREQUENCY IN MHZ. \*IFI 00250 FI=10F11 FRINT MI 'P INDUCTANCE IN MICROHENRIES\*:PRINT 00250 FPIHT DO YOU WANT TO GO BACK Y/N \* 00260 FPIHT R0:500 PRINT 00:300 FRINT 00:300 IF V00-'Y'OR V00-'Y' THEN 220 ELSE IF V00-'N' OR V00-'N'THEN 420 00:30 URES 00:315 CURS 30:3: PRINT WAIT' 00:320 PLOT 65:0 TO 300;0 00:300 CURS 24:12:PRINT' 00:300 CURS 15:13:13FRINT' 20: 4 C' 00:300 CURS 15:13:13FRINT' 00:300 CURS 15:13:13FRINT' 00:300 CURS 15:13:13FRINT' 00:300 CURS 15:13:13FRINT' 00:300 CURS 15:13FRINT' 00:300 CURS 15:15FRINT' 00:300 CURS 15:15FR 00410 0010 120 00420 CURS 45, 16: PRINT "THATS THE END"

#### CONTRIBUTORS PLEASE NOTE

All contributions to this column should be accompanied by a listing of the program from a printer. Hand written or typed listings are not acceptable.

There are two reasons for this. The first is that a listing from your computer gives us some guarantee that you have the listing correct

Secondly, if you present us with a neat final copy of your program we can use photographic techniques to reproduce it in the magazine, without risk of errors.

Contributors will be paid \$20 for each item published in this column. Submissions must be original programs which have not been previously published. You may send as many programs as you wish with the accompanying declaration.

"I agree to the above terms and grant Electronics Today International all rights to publish my program in ETI Magazine or other publications produced by it. I declare that it has not been previously published and that its publication does not violate any other copyright." \*Breach of copyright is now a criminal offence.

Name	
Signature	Date
Address	
	Postcode

### **COMMODORE COLUMN**

STREM INITIALIZE P

#### Hard Lo-res Sean Machin, Lismore, NSW 2480

This program allows you to draw lo-res plctures on the screen and then dump them to your printer. It consists of two parts, a simple lo-res drawing routine (lines 130 to 290) and the printer routine (310-350). In the drawing section there are three modes of operation: 'set' where the plxel moves according to your key instructions, 'reset', where it moves destructively and 'move', where it is non-destructive. The relevant keys are Q for up, A for down, [ for left and ] for right.

Tab activates the print routine. Different effects can be obtained by changing the vertical line spacing (CHR(27);"3";CHR(n)) and by changing the print character in line 330.

OUTIO REM BY SEAN MACHIN
00120 CLS: OUTL#1: LPRINT CHR (27)   "@"; CHR (27)   "3"; CHR (20) ; CHR (15
RINTER
00130 LORES: X=63: Y=24: R=3: GOTO 260: REM START IN MOVE MODE
OOI40 KIS=KEY
00150 IF K14="8":Y=Y+1:REM UP
00160 IF KIS="A":Y=Y-1:REM DOWN
00170 IF K18+*1*:X=X+1:REM RIGHT
00180 IF K15="(":X=X-1:REM LEFT
00190 IF K1S=CHR(9): PLAY 22,4:00TO 300: REM DUMP SCREEN
00200 IF K18="C":R=R+1:IF R>3:R=1:REM CHANGE MODE
00210 IF KIS="" AND R()1: INVERT X, Y: INVERT X, Y: GOTO 140
00220 IF x(0:x=0
00230 IF X>127:X=127
00240 IF Y(0:Y=0
00250 IF Y>47:Y=47
00260 IF R=1:SET X, Y:CURSO:PRINT'SET';SPC(2)
00270 IF R=2: INVERT X, Y: INVERT X, Y:RESET X, Y:CURSO: PRINT RESET
00280 IF R=3: INVERT X, Y: INVERT X, Y: CURSO: PRINT MOVE ; SPC(1)
00290 GOTO 140
00300 CURSO: PRINT SPC (5) : REM ERASE PRINTED MODE
00310 FORY=47 TO 0 STEP-1
00320 W05="":FORX=0 TO 127
00330 IF POINT(X,Y):WOS=WOS+CHR(17) ELSE LET WOS=WOS+* *
00340 NEXTX: IF WOR()" THEN LPRINT WOR ELSE LPRINT
00350 NEYTY

00100 REM LORES TO PRINTER DUMP

00360 GOTO 120 Sample:

#### **Balloon Dodge**

G. Gajic, Kensington, Vic 3031

You must dodge arrows being shot up at you from the ground. Your position is represented by a balloon. If the arrows hit you then the balloon bursts.

# 

10 REM OBSTICAL COURSE FOR COMMODORE 64 20 REM (C) COPYRIGHT BY GARY GAJIC 30 POKE53280,0:POKE53281,0 40 PRINT " DODDON"; : PRINTTAB (11) " DBSTICAL COURSE " 50 PRINTTAB(13) "MORPLEASE WAIT": FORTT=1T01000:NEXT: PRINTTAB(13) "MACHIT ANY KEY" 60 PRINTTAB(9)" TO Z - LEFT C - RIGHT": PRINTTAB(10)" TOTAL(C) BY GARY GAJIC" 70 GETR\$: IFR\$= " THEN70 80 DIMA\$(9):FORT=1T09:READA\$(T):NEXT 100 GETA\$: IFA\$= " "ANDPEEK (56320) = 127THEN130 110 JFA\$="Z"ORPEEK (56320)=123ANDA>1040THENA=A-1 120 IFA\$= "C"ORPEEK (56320)=119ANDA(1047THENA=A+1 130 POKEA,81:SC=SC+1: IFPEEK (A+40)=102THEN300 140 PRINTTAB(15)A\$(INT(RND(1)+8)+1) 150 POKEA,81 160 FORT=1T030:NEXT 170 GOTO 100 200 DATA" 叢 220 DATA"# -230 DATA" 100 240 DATA" 250 OATA" 260 DATA" 270 OATA\* 280 DATA \* 101 300 PRINT JE YOU ECRASHED INTO AN OBSLTICAL !!!" 310 PRINT" YOU SCORED'SC 340 IFDS="Y"THENRUN 350 IFD\$="N"THENPRINT \*\* \*\* POKE53280,254 \* POKE53281,246 \* END 360 GOTO 330

### **COMMODORE COLUMN**

#### FUR ELISE

10 REM++(C) 1984 BYI #+
20 REMACHRIS GROENHOUT
30 PRINTCHR#(B)+CHR#(14)
40 PRINT " JODDOND   AGATELLE IN . \INDR "IPRINT " JODDA '-UR "LISE'
SO PRINT B BY: L.X.IEETHOVEN"
60 PRINT ######## 1770-1827)"
70 PRINT #05213V5"
80 PRINT DEWDEWDEO2803DC
90 PRINT #510145202401E402CEA"
100 PRINT" #5101ES2028D1E#G02E#GB"
110 PRINT"#6101AS203C01EA02E03E#D"
120 PRINT" DEMOEO28030C"
130 PRINT " 15101AS202A01EA02CEA"
140 PRINT # 101ES2028D1E#G02D033C028*
150 PRINT # 101A5202A01EA03T2RT3END*
160 PRINT DEMOEO2BO3DC PPRINT ""
170 PRINT # 101AS202AD1EAD2CEA
IGO FRINT "SIDIES202801ENGD2ENGB"
130 PR INT * #6101AS203C01EA02E03E#D*
200 PRINT" #ENDED28030C"
210 FRINT SIDIAS202A01EA02CEA
220 PR11IT # 101ES202B01E#G02003C02B*
238 PE INT " E 101AS202A01EA02B03C0 "
240 PRINT #V7S102CS203E01G02CG03FE
250 FRINT # 101652030016802F03ED
260 PR 114T #5 101AS203C01EA02E030C " : PR INT #*
270 PR 1NT * #V35 101ES202B01E02EE03E02E03ES303RES2RT2RT3#0E *
280 PRINT : MOENDENDENDENDE028030C -
230 PRINT #5101AS202A01EA02CEA*
300 PRINT " S101ES202B01E#G02E#GB"
310 PRINT*#6101A5203C01EA02E03EWD*
320 PRINT #EW0E028030C *
330 PRINT BIOIASEDEADIEADECEA
348 PR INT #5101ES2028D1E#602003C028*
356 FRINT* \$101AS2D2A01EA02803CD*
360 FRINT #/75102CS203E01G02CG03FE . PRINT
370 PRINT * 15101652030016802F03ED *
380 FRINT # 101AS203CD1EA02E03DC*
390 PRINT WSSIDIES202801E02EE03ES303RES2RT2RT3#0E#0E*
400 PRINT #V4NDENDENDENDE028030C
410 PRINT SIDIAS202A01EA02CEA
420 FRINT #SIDIES202BDIENGD2ENGB*
430 PRINT
440 PRINT" ENDED2B03DC "
450 PRINT
460 FRINT #5101ES202801E#602003C028" IPRINT #
470 PRINT #7510165202601EA
400 PRINT . EAO2CEAO3CEAS3RT8AS2A .
490 PRINT # 1951014*
500 FORA-1T01500 INEXT
S10 PRINT MANAGAMANAN
520 END

#### **CONTRIBUTORS PLEASE NOTE**

All contributions to this column should be accompanied by a listing of the program from a printer. Hand written or typed listings are not acceptable.

There are two reasons for this. The first Is that a listing from your computer gives us some guarantee that you have the listing correct.

Secondly, if you present us with a neat final copy of your program we can use photographic techniques to reproduce it in the magazine, without risk of errors.

Contributors will be paid \$20 for each item published in this column. Submissions must be original programs which have not been previously published. You may send as many programs as you wish with the accompanying declaration.

"I agree to the above terms and grant *Electronics Today International* all rights to publish my program in ETI Magazine or other publications produced by it. I declare that it has not been previously published and that its publication does not violate any other copyright." "Breach of copyright is now a criminal offence.

Name		
Signature	Date	
Address		
	Postcode	

#### 88 - ETI March 1986

#### Play Maestro C. Groenhout,

## Watson, ACT 2602

FRELUDE

"Prelude" is a direct transposition of J.S. Bach's "Prelude" #1 in C major for the VIC-20 + Super Expander. The program uses the Super Expander's powerful musical generating capabiities starting each musical line with CTRL-back arrow. This produces a reverse capital F. Every ten lines or so, a home is printed so as not to scroil the screen with excessive PRINT statements and lose the credits. "Fur Elise", by Ludwig Van Beethoven, is here as a greatly shortened and simplified version for Super Expander users. Being only 52 lines long, the program plays this piece with its controversial name changing sound levels when necessary in accordance with the music.

.51

10 /	
	REM++(C) 1984 BY:++
20 1	REMICHRIS GROENHOUT
30 1	PPINTCHR8(8)+CHR8(14)
40 1	PRINT "LINUKAR DOBRITL"LATT IN -"IPRINT ROOMARIYE " IACH"
50 1	PRINT
	PRINT " TZSZOZV4CEGO3CEOZGO3CE "
	PRINT D2CEG03CE02G03CE
	PRINT " INCOAD3DFD2A03DF "
	PRINT DECOROSOFDEROSOF
	PP INT * #0 180206030F 026030F *
	PP INT * 10 180206030F026030F *
	PP IIIT "D2CEG03CE02G03CE "
130	PR IIIT "D2CEG03CE02G03CE "
140	PFINT #V602CEAD3CA02A03CA
	PRINT "DECEAO3CADEAO3CA" IPRINT "#"
	PRINT #D2CONFA03D02#FA03D"
	PRINT "D2CDWFA03002WFA030"
	PF 1: IT " 10 18020003000200300 "
	FR INT " 10 18020603060260306 *
200	PF INT "DIBO2CEG03C02EG03C"
510	FR 1HT * DIBOZCEGO3CD2EGO3C*
	FRINT" DIAO2CEGO3CO2EGO3C"
	FRINT "DIAD2CEG03C02EG03C"
240	PRINT "DIDAO2D#F03CD2D#F03C"
250	PRINT #DIDA02D#F03C02D#F03C*:PRINT #*
	FRINT # 4016802068068 *
270	FP1HT #01GB020GB0GB
	PRINT #DIGHAOZEGO3HCOZEGO3HC*
	FRINT* DIGNAO2EGO3NC02EGO3NC*
2500	FRINT #01FA020A030020A030
	PRINT " 10 IFA02040300204030 "
	PRINT DIFNGO2DFBOFB
	PF 1117 * #D 1F #5020FB0F8 *
240	FR1HT * D1EG02CG03C02CG03C*
3.50	FRINT DIEGO2CG03C02CG03C" IPRINT a
360	PRINT "DIEFAO2CF01A02CF"
	FA INT " DIEFAORCFDIAORCF"
	PRINT PIDEAO2CFDIAO2CF*
	FRINT "DIDFAORCFOIAORCF"
	PR 1147 # 60151G52RD6802F016802F*
410	PRINT DISIGS2RDGB02F016B02F
1.0.	PRINT "DICEGO2CEDIGO2CE"
430	
5.2.3	
	PRINT MDICGHAO2CEOIWAO2CE*
450	PRINT "DICGWAO2CEOIWAO2CE" PRINT DICGWAO2CEOIWAO2CE" PRINT DICGWAO2CEOIWAO2CE"
450 460	FRINT * 2010 GRADECED INADECE * PRINT * 2010 GRADECED INADECE * PRINT * 2010 GRADECED INADECE * PRINT * 2010 SIFSERFADECED INADECE *
450 460 470	PRINT*201CG#A02CE01WA02CE* PRINT*201CG#A02CE01WA02CE*1PRINT*20* FRINT*20301S1FS2RFA02CE01A02CE* PRINT*201S1FS2RFA02CE01A02CE*
450 460 470 460	PR IIIT "#DICG#A02CE0IWA02CE" PR IIIT #DICG#A02CE0IWA02CE" IPR INT ## PK INT #W30ISIFS2RFA02CE0IA02CE" PR INT #DISIFS2RFA02CE0IA02CE" FR INT #DISIFS2RFA02CE0IA02CE"
450 460 470 480 490	FRINT*#DICG#A02CE0I#A02CE* PRINT*#DICG#A02CE0I#A02CE*PRINT*#* FRINT*#DISIFS2RFA02CE0IA02CE* PRINT*#DISIFS2RFA02CE0IA02CE* FRINT*#DISIFS2RFA02CE00IA02C#0* FRINT*#DISI#FS2RFA02C#00IA02C#0*
450 460 470 480 490 500	FR III * #DICG#A02CE01#A02CE* PR III * #DICG#A02CE01#A02CE* IPR III * #* FR III * #00151F52RFA02CE01A02CE* PR III * #DIS1F52RFA02CE01A02CE0* FR III * #DIS1#F52RCA02CH001A02CH0* FR III * #DIS1#F52RCA02CH001A02CH0* FR III * #DIS1#F52RCA02CH001A02CH0*
450 460 470 480 490 500 510	FR IIIT * #DICG#A02CE01WA02CE *         PR (INT * #DICG#A02CE01WA02CE * IPR INT * #*         FK INT * #DISIFS2RFA02CE01A02CE *         PR INT * #DISIFS2RFA02CE01A02CE *         FR INT * #DISIFS2RCA02CH001A02CH0 *         FR INT * #DISI#FS2RCA02CH001A02CH0 *         FR INT * #DISI#FS2RCA02CH001B02CD *
450 460 470 460 480 500 510 520	FR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE         FK INT*#DIS1F52RFA02CE01A02CE*         PR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01A02C#0*         FR INT*#DIS1F52RFA02CE01B02C0*         PR INT*#DIS1F652RFE02CE01B02C0*         PR INT*#DIS1F5602D01B02C0*
460 460 470 460 490 500 510 520 520	FR INT "DICG#A02CE01WA02CE" PR INT "DICG#A02CE01WA02CE" PR INT "W" FK INT "W015IFS2RFA02CE01A02CE" PR INT "DISIF52RFA02CE01A02CE" FR INT "DISIF52RFA02CE01A02CE0" FR INT "DISIF52RFA02CE01A02CE0" FR INT "DISIF52RFA02CE01A02CE0" PR INT "DISIG52RF602C001B02C0" PR INT "DISIG52RF602C001B02C0" PR INT "DISIG52RF602D01G8020"
450 460 470 480 500 510 520 520 520 520	FR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE*         PR INT*#DIS1FS2RFA02CE01A02CE*         PR INT*#DIS1FS2RFA02CE01A02CE*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1#FS2RFA02CE001A02C#0*         FR INT*#DIS1#FS2RFA02CE001A02C0*         FR INT*#DIS1#FS2RF602C001B02C0*         PR INT*#DIS1#FS2RF602C001B02C0*         PR INT*#DIS1632RF602C001B02C0*         PR INT*#DIS1632RF602C001B02C0*         PR INT*#DIS1632RF602C001G02C0*         PR INT*#DIS151652RF602C001G02C0*         PR INT*#DIS151652RF602C001G02C0*
450 460 470 480 500 510 520 520 520 520 520	FR INT*@D1CG#A02CE01#A02CE*         PR INT*@D1CG#A02CE01#A02CE*         PR INT*@D1CG#A02CE01#A02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01B02C0*         PR INT*@D1S1F52RF6022001B02C0*         PR INT*@D1S1652RF660200168020*         PR INT*@D1S1652RF660200168020*         PR INT*@D1S1652RF6602C0168020*         PR INT*@D1S1652RF6602C0168020*         PR INT*@D1S1652RF602CE01602CE*         PR INT*@D1S15652RF602CE01602CE*
450 460 470 460 490 500 510 520 520 520 520 520 540 550 560	FR [IIT * 10] (G#A02CE01#A02CE*         PR [IIT * 10] (G#A02CE01#A02CE*         PR [IIT * 10] (G#A02CE01#A02CE*         PR [IIT * 10] (S] [S2RFA02CE01A02CE*         PR [IIT * 10] (S] [S2RFF02CD01A02CE*         PR [IIT * 10] (S] [S2RFF02CD01B02C0*         PR [IIT * 10] (S] [S2RFF02CD01B02C0*         PR [IIT * 10] (S] [S2RFF02CD01B02C0*         PR [IIT * 10] (S] [S2RF602CD01B02C0*
450 460 470 460 500 500 510 520 520 520 520 520 520 520 520 520	FR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE*         PR INT*#DICG#A02CE01#A02CE*         PR INT*#DIS1FS2RFA02CE01A02CE*         PR INT*#DIS1FS2RFA02CE01A02CE*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1FS2RFA02CE001A02C#0*         FR INT*#DIS1FS2RF602C001B02C0*         PR INT*#DIS1652RF602C00168020*
450 460 470 480 500 510 520 520 520 520 520 520 520 520 520 52	FR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01A02CE0*         FR INT*@D1S1F52RFA02CE01A02CE0*         FR INT*@D1S1F52RFA02CE01B02C0*         PR INT*@D1S1F52RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001B02C0*         PR INT*@D1S1652RF6022001G02CE*         PR INT*@D1S1652RF6022001B02CF*
450 460 470 480 500 510 520 520 520 520 520 520 520 520 520 52	FR INT *#01CG#A02CE01#A02CE*         PR INT *#01CG#A02CE01#A02CE*         PR INT *#01S1FS2RFA02CE01A02CE*         PR INT *#01S1FS2RFA02CE001A02CE0*         PR INT *#01S1FS2RFA02CE001A02CE0*         PR INT *#01S1FS2RF602CD01B02C0*         PR INT *#01S1652RF602CD01B02C0*         PR INT *#01S1652RF602CF01B02CF*         PR INT *#101652R0602CF01B02CF*         PR INT *#101652R0602CF01G02CF*
450 460 470 480 500 510 520 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CE01#A02CE*         PR INT * DICG#A02CE01#A02CE*         PR INT * DICG#A02CE01#A02CE*         PR INT * DISIFS2RFA02CE01A02CE*         PR INT * DISIFS2RFA02CE01A02CE*         FR INT * DISIFS2RFA02CE01A02CE*         FR INT * DISIFS2RFA02CE01A02CE*         FR INT * DISIFS2RFA02CE01A02CE*         FR INT * DISIFS2RFA02CE01002C0*         FR INT * DISIFS2RFA02CE01002C0*         PR INT * DISIFS2RF602C001002C0*         PR INT * DISIFS2RF602C001002CF*         PR INT * DIOI052PD0602F010802F*         PR INT * DIOI052PD0602F016802F*         PR INT * DIOI052PPD0602F016802F*         PR INT * DIOI052PPD0602F016802F*
450 460 470 460 500 500 510 520 520 520 520 520 520 520 520 520 52	FR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1CG#A02CE01MA02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01A02CE0*         PR INT*@D1S1F52RFA02CE01B02C0*         PR INT*@D1S1652RF602001B02C0*         PR INT*@D1S1652RF602001B02CF*         PK INT*@D1S1652RF002CF01602CF*         PK INT*@L01652RF00402CF016802F*         PK INT*@L01652RF00402CFF01A02CFF         PK INT*@L01652RF00402CFF01A02CFF*         PK INT*@L01652RF00402CFF01A02CFF*         PK INT*@L01652RF00402CFF01A02CFF*         PK INT*@L01652RF00402CFF01A02CFF*
450 460 470 480 500 500 500 520 520 520 520 520 520 52	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02C#O         FR INT * DISIFS2RFA02CEOIB02CO*         FR INT * DISIFS2RF602COIB02CO*         PR INT * DISIFS2RF602COIG02CE*         PR INT * DISIGS2RF602CEOIG02CE*         PR INT * DISIGS2RF602CE0IG02CE*
450 460 470 480 500 540 520 540 520 540 550 540 550 540 550 540 540 540 54	FR INT*#D1CG#A02CE01#A02CE*         PR INT*#D1CG#A02CE01#A02CE*         PR INT*#D1CG#A02CE01#A02CE*         PR INT*#D1S1FS2RFA02CE01A02CE*         PR INT*#D1S1FS2RFA02CE01A02CE*         FR INT*#D1S1FS2RFA02CE01A02CE*         FR INT*#D1S1FS2RFA02CE001A02C#0*         FR INT*#D1S1FS2RFA02CE001A02C#0*         FR INT*#D1S1FS2RFA02CE01A02C#0*         FR INT*#D1S1FS2RFA02CE01B02C0*         PR INT*#D1S1FS2RF602CD016802D*         PR INT*#D1S1652RF6602C016802D*         PR INT*#D1S1652RF6602C016802D*         PR INT*#D1S1652RF6602C016802C*         PR INT*#D101652RF6002C*
450 460 470 460 500 540 540 540 550 540 550 540 550 540 54	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RF602COIB02C0*         PR INT * DISISES2RF602COIG02CE*         PR INT * DISIGS2REG02CEOIG02CE*         PR INT * DISIGS2REG02CE*
450 463 470 463 500 520 520 520 520 520 520 520 520 520	FR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RFA02C*         FR INT * DIA02C*         PR INT * DIA052RF002C*         PR INT * DIA052RF
+500 460 470 460 500 500 500 500 500 500 500 500 500 5	FR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02C#0*         FR INT * DISIFS2RFA02CEOIA02C0*         PR INT * DISIFS2RF602COI602C0*         PR INT * DISI6S2RF602COI602C0*         PR INT * DISI6S2RF602C01602C0*         PK INT * DISI6S2RF602C01602C0*         PK INT * DISI6S2RF602C01602C0*         PK INT * DISI6S2RF602C01602C0*         PK INT * DIOI6S2RF002C0*         PK INT * DIOI6S2RF602C01602C0*         PK INT * DIOI6S2RF602C01602C0*         PK INT * DIOI6S2RF602C01602C0*         PK INT * DIOI6S2RF602C01602C0*         PK I
450 460 470 490 500 510 520 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOI0A02C#0*         PR INT * DISIFS2RFA02CEOI002C0*         PR INT * DISIFS2RFA02CEOI002CE*         PR INT * DISIFS2RFA02CEF0102CE*         PR INT * DIOI052PR0A02C#F01A02C#F         PR INT * 3I01052PR0A02C#F01A02C#F         PR INT * 3I01052PR0A02C#F0
+500 460 470 490 500 500 500 500 500 500 500 500 500 600 6	FR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CO*         FR INT * DISIFS2RF602COOIB02CO*         PR INT * DISIFS2RF602COOIB02CO*         PR INT * DISIFS2RF602COOIB02CO*         PR INT * DISIFS2RF602COOIB02CO*         PR INT * DISIFS2RF602COOIB02CF*         FR INT * DISIFS2RF602CEOIB02CF*         PR INT * DISIFS2RF602CEOIB02CF*         FR INT * DISIFS2RF002CF01602CF*         PR INT * DIOIS2RD602CF01602CF*         PR INT * DIOIS2RF002CF01602CF*
+150 4-63 4-75 5-80 5-80 5-80 5-80 5-80 5-80 5-80 5-8	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RF602COIB02C0*         PR INT * DISISES2RF602COIG02CE*         PR INT * DISIGS2RF602COIG02CE*         PR INT * DISIGS2RF002CEOIG02CE*         PR INT * DISIGS2RF002CEOIG02CE*         PR INT * DISIGS2RF002CEF0IG02CF*         PK INT * DISIGS2RC000000000000000000000000000000000000
450 440 470 500 510 510 520 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RFA02CEOIA02CO*         PR INT * DISIFS2RF602COIB02CO*         PR INT * DISIFS2RF602COIG02CE*         PR INT * DISIFS2RF602COIG02CF*         PK INT * DIGS2RF602CF0IG02CF*         PK INT * SIOIGS2RF602CF0IG02CF*
450 440 470 500 510 510 520 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RF602COIB02C0*         PR INT * DISISES2RF602COIG02CE*         PR INT * DISIGS2RF602COIG02CE*         PR INT * DISIGS2RF002CEOIG02CE*         PR INT * DISIGS2RF002CEOIG02CE*         PR INT * DISIGS2RF002CEF0IG02CF*         PK INT * DISIGS2RC000000000000000000000000000000000000
450 463 470 500 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOIMA02CE*         PR INT * DICG#A02CEOIMA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         FR INT * DISIFS2RFA02CEOIA02CO*         FR INT * DISIFS2RFA02CEOIA02CO*         FR INT * DISIFS2RFA02CEOIA02CO*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEFOIA02CE*         PR INT * DISIFS2RFA02CEFOIA02CE*         PR INT * DIA022RF002CFOIA02CF*         PK INT * DIA052RF002CFOIA02CF*         PK INT * SIDIFS2RF002CFOIA02CF*         PK INT * DIA052RF002CFOIA02CF*
450 463 470 490 500 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DICG#A02CEOI#A02CE*         PR INT * DISIFS2RFA02CEOIA02CE*         PR INT * DISIFS2RFA02CEOIA02C*         PR INT * DISIFS2RFA02CEOIA02CO*         PR INT * DISIFS2RF602COIB02CO*         PR INT * DISIFS2RF602COIG02CE*         PR INT * DISIFS2RF602COIG02CF*         PK INT * DIGS2RF602CF0IG02CF*         PK INT * SIOIGS2RF602CF0IG02CF*
450 463 470 450 500 510 520 520 520 520 520 520 520 520 520 52	FR INT * DICG#A02CEOIMA02CE * PR INT * #* PR INT * DICG#A02CEOIMA02CE * PR INT * #* FK INT * JOISIFS2RFA02CEOIA02CE * PR INT * JOISIFS2RFA02CEOIA02CE * FR INT * JOISIFS2RFA02CEOIA02CE * FR INT * JOISIFS2RFA02CEOIA02CE * FR INT * JOISIFS2RFA02CEOIA02CO * PR INT * JOISIFS2RF602COIB02CO * PR INT * JOISIFS2RF602COIB02CO * PR INT * JOISI6S2RF602COIB02CO * PR INT * JOISI6S2RF602CEOIG02CE * PR INT * JOISI6S2RF602CEOIG02CE * PR INT * JOISIS2RF602CEOIG02CE * PR INT * JOISIS2RF602CEOIG02CE * PR INT * JOIGS2RD602CF0IG02CF * FK INT * JOIGS2RC602C60IG02C6 * FK INT * JOIGS2RC602C60IG02C6 * FK INT * JOIGS2RC602C60IG02C6 * FK INT * JOIGS2RC602CF0IG02CF * FK INT * JOISS2RC602CF0IG02CF * FK INT * JOISS2RC602CF0IG02
4503 4633 4700 4500 5000 5180 5200 5200 5200 5200 5200 5200 5200 52	<pre>FR INT * D1CG#A02CE01#A02CE * PR INT * #* PR INT * D1CG#A02CE01#A02CE * PR INT * #* PR INT * D1S1FS2RFA02CE01A02CE * PR INT * D1S1FS2RFA02CE01B02C0 * PR INT * D1S1FS2RF602CD01B02C0 * PR INT * D1S1FS2RF602CD01B02C0 * PR INT * D1S1FS2RF602CD01B02C0 * PR INT * D1S1FS2RF602CD01G02CE * PR INT * D1S1FS2RF602CD01G02CE * PR INT * D1S1FS2RF602CD01G02CE * PR INT * D1S1FS2RF602CD01G02CF * PR INT * D151FS2RF602CD01G02CF * PR INT * D151FS2RF602CD01G02CF * PR INT * D10FS2RF0602CF01G02CF * PR INT * D10FS2RF0602CF01F02CF * PR INT * D10FS2RF0F02CF01F02CF * PR INT * D10FS2RF0F02F01F02F * PR INT * D10FS2RF0F02F01F02F * PR INT * D10FS2RF0F02F01F02F * PR INT * D1FS1F0FV*15T</pre>
4503 4633 4700 4500 5000 5180 5200 5200 5200 5200 5200 5200 5200 52	FR INT "DICGMADZCEDIMADZCE" PR INT "DICGMADZCEDIMADZCE" PR INT "DISIFS2RFADZCEDIADZCE" PR INT "DISIFS2RFADZCEDIADZCE" PR INT "DISIFS2RFADZCEDIADZCE" FR INT "DISIFS2RFADZCEDIADZCE" FR INT "DISIFS2RFADZCEDIADZCO" FR INT "DISIFS2RFADZCEDIBDZCO" PR INT "DISIFS2RF6DZCDIBDZCO" PR INT "DISIFS2RF6DZCDIBDZCO" PR INT "DISIFS2RFGDZCEDIGDZCE" PR INT "DISIFS2RFGDZCEDIGDZCE" PR INT "DISIFS2RFGDZCEDIGDZCE" PR INT "DISIFS2RFGDZCEDIGDZCE" PR INT "DISIFS2RFGDZCEDIGDZCE" PR INT "DISIFS2RFGDZCEDIGDZCE" FR INT "DISIFS2RFGDZCEDIGDZCE" FR INT "DISIFS2RFGDZCEDIGDZCE" FR INT "DISIFS2RFGDZCEDIGDZCE" FK INT "DISIFS2RFGDZCEDIGDZCF" FK INT "DIGS2RFGDZCEDIGDZCF" FK INT "DIGS2RFGDZZEDIGMDZE" FK INT "DIGS2RFGCDZEDIGMDZE" FK INT "DIGS2RFGCDZEGDIGMDZE" FK INT "DIGS2RFGCDZEGDZFCIADZEDIFAPOFD" FK INT "DIGS2RFGCDZEGDZFCIADZEDIFAPOFD" FK INT "DIGS2FFGCJZEGDZFGDZEDIGMDZE" FK INT "DIGS2FFGCJZEGDZFGDZEGDZEDIGMDZE" FK INT "DIGZZFCFMADZECIADZEDIFAPOFD" FK INT "DIGZZFCFMADZECIADZEDIFAPOFD" FK IN

## **COMPUTER REVIEW**

## LOW COST IBM COMPATIBILITY — The DSE Multitech Popular 500



Dick Smith Electronics' venture into business computers has been so successful it even surprised the people at DSE. Now the company has released three computers that run IBM software and bridge the ground between its business and hobbyist users.

## **David Kelly**

SOME YEARS AGO when IBM announced that it would make a personal computer and give it an operating system incompatible with the rest of the industry I thought it was crazy. Changing the attitudes of an entire industry was, I thought, a bit like getting all Australians to drive on the right hand side of the road.

While IBM has not by any means got the market to itself, even the most ardent Apple user would have to agree that IBM has gained an unprecedented level of support from software houses and the makers of complementary or even competing hardware. The only disappointing thing for me and a lot of other hobbyists is that all this activity has gone on at a prohibitive cost.

My interest in computers was sparked in the early seventies when I learned to talk Fortran and other languages on largish IBM and DEC machines. Since that time there have been many microprocessors released that have instruction sets at least equivalent to the machines I learnt on. Few of these have turned up in small computers and the cost of memory, mundane thing that it is,

ETI March 1986 - 89

### COMPUTER REVIEW

has made the capabilities of many of these machines totally uninspiring.

Of course IBM compatibility is not the most important criterion for buying a computer; in almost all cases software is! This is as true for the software you write yourself as it is for the off-the-shelf stuff. If the software you really need only resides on a dinosauric computer then that's the one you should buy.

Fortunately for IBM, the cost of memory fell at the right time to make the capabilities of its computers affordable.

What makes this market situation interesting is that a few companies have quite low-cost machines that have varying levels of compatibility with IBM personal computers. Among them are three machines from DSE, the most expensive a 10 megabyte hard disk computer for less than \$4000.

#### **DSE's Multitechs**

The three personal computers in the DSE Multitech range have prices from \$1345 to \$3995. The smallest has one floppy drive and 128K bytes of RAM, the next has two drives and 256K of RAM and the biggest has a 10M byte Winchester Drive, a floppy and 512K of RAM. Wordprocessing software comes with the dual floppy drive machine, and an extensive wordprocessing, spreadsheet and graphics package called Aura comes with the top model.

When DSE asked us if we would like to review one of the machines we asked for the top model because we had some pc board CAD software we wanted to try out. With a hard disk drive it was delightfully fast in reading from disk, but in all other respects for most of the software I ran it behaved as either of the other machines would.

I found the hardware, namely the keyboard quite easy to use. I liked its size and the layout of its keys. It didn't have a caps lock light, which I would have liked and I found the keys a bit too light to touch. That might be because I'm used to a steam age manual typewriter, but it is certainly lighter than most keyboards I've used.

The RGB monitor at first sight doesn't look as smart as the rest of the hardware and I was deceived into thinking it would be of moderate quality. In fact it turns out to be a stable and sharp colour display.

I quite liked the look of the processor/ disk drive box. If anything it looks smarter

than the IBM. Unlike the IBM the processor, I/O, display and hard disk drive cards mount horizontally.


If you buy the hard disk system you will find that all of the motherboard slots are taken up. However the bus is available on an edge connector so if you can supply the power and you know what you're doing, expansion shouldn't be too much of a problem.

#### **Road test**

An exhaustive road test of most contemporary personal computers would take months or years. On the Multitech offered for review, I ran the Protel PCB Layout System, the Aura package, Color Wordstar, GW BASIC, Basica and the perennial Flight Simulator,

DSE as yet hasn't offered a BASIC written for the Multitech. I ran scores of the most common BASIC commands without trouble.

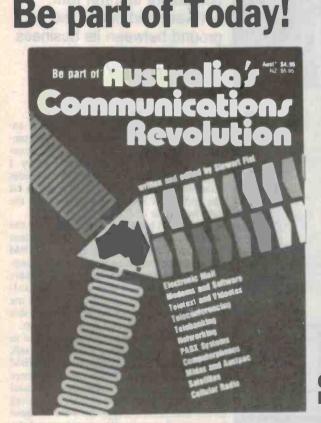Overall I was quite impressed with the Multitech, especially its value for money. It's one of those terrible products that have you going off to check the balance of you bank account.



When we analyse the recent past and project the immediate future, computers and communications technologies play a vital part, but we must avoid the tendency to look only to the hardware level. The fact that technologists have appropriated words like 'communications', 'information' and 'data' and given them electronic rather than social meanings, should not disguise the fact that in the final analysis, communications involves people and ideas, not electronic bit and bytes.

People and Ideas . . . that's the side of Australia's Communications Revolution we tell about in this informal look at today's world of computers and telecommunications.

#### At your Newsagent now!

Or simply send \$4.95 plus \$1.00 post and packing to — Federal Marketing Book Sales, P.O. Box 227, Waterloo 2017 NSW.

## **Digital radio trunk system**

## Telecom has completed the installation of the world's largest digital radio trunk system.

Stretching 5100 km from Perth to Brisbane, this new 'superhighway' will carry large volumes of traffic — voice, data, text, sound and television with high reliability.

Known as a 140 megabit per second system, it can accommodate up to six radio bearers each of which could carry the equivalent of almost 2000 simultaneous telephone conversations or a number of television relays.

The route follows the microwave radio system linking Perth, Adelaide, Melbourne, Sydney and Brisbane. New antennas and electronic equipment were installed at the capital city terminals and at the 120 repeater stations along the route.

Installation costs totalled \$73 million and include duplicated power systems, and remote supervision and control facilities. Each 'hop' has a protection radio bearer which is automatically switched into use should a fault develop on a main bearer.

Special high performance an-

tennas and radio circuitry were used to eliminate interference and overcome fading of the radio signals.

Telecom's General Manager, Network Engineering, Mr Bob McKinnon said that the installation of the system was a significant engineering achievement. "Australia is well up with other leading countries in this move towards modern digital systems.

"All the new electronic telephone exchanges we are installing are digital and we have a joint venture with a manufacturer to produce the world's first small digital rural telephone exchange. Our next step is to complement this system by linking the capitals and major centress such as Darwin with an optical fibre trunk system by 1990. This will give Australia a digital network of great route diversity and high reliability.

"Work has already started on the Sydney-Melbourne optical fibre link", Mr McKinnon said, "our aim is to have it in service on Australia Day 1988".

#### Electronic communications explained

The word "informatics" might sound a novel coining but it is established enough to be listed in the *Macquarie*: "a discipline of science which investigates the structures and properties of scientific information as opposed to the content". That rather abstract and elusive definition is given a much wider and more concrete interpretation in a new publication Be Part of Australia's Communications Revolution, which invites the public to study informatics by becoming aware of what's around in communications technology and what the social implications of this technology are.

The publication is a comprehensive and pragmatic treatment of recent developments in electronic communications. It covers the fairly familiar territory of modems, communications software, FAX, satellites, teletext and videotex, and networking, for example, with discussions of standards and the newer (at least to Australia) technologies such as electronic mail systems and cellular radio — all from the user's point of view.

It is the discussion of the application or usability of these facilities that really gives the book its edge, particularly in its concentration on business use. So the treatment covers the use of teleconferencing (including video conferencing and computer conferencing) and electronic mail systems as channels of communication within a single business centre or its branches, or between Interested individuals, perhaps in a seminar, etc.

Placing these communications techniques in the business context gives a picture complete with economics and psychological practicalities that the less imaginative among us can use as a solid departure point for assessing advantages and disadvantages, whether we agree with the author or not. The use of these communications techniques in industry is, of course, particularly important as developments usually ride on industry.

The book is probably most valuable for its systematic description (or cataloguing) of the sorts of technology and hardware available, what it does and how people use it to benefit, and for its resume of available data bases, videotex and teletext information, and charges. It provides some guiding questions to ask of the device or package you might be interested in and evaluates products and systems in the present Australian situation. Rather briefly, the book outlines a bit of the science involved in both the new technologies like cellular radio and the old standards (like BMAC), however, it never loses its practical thrust which makes it a handy reference for the interested user rather than the technologist.

Be Part of Australia's Communications Revolution is available from newsagencies for \$4.95 or from the Federal Publishing Co, 140 Joynton Ave, Waterloo, NSW 2017 for \$4.95 plus \$1 p&p.

## NT served by shortwave

In the past the isolated areas of the Northern Territory have received their radio entertainment from three small mediumwave stations at Alice Springs, Tennant Creek and Katherine and on shortwave from Radio Australia. All this has now changed with the installation of three 50,000 watt SW transmitters at these sites, to ensure excellent reception of the ABC programmes.

The idea was mooted some 20 years ago with the programmes being fed from Darwin, but in 1975 when Cyclone Tracey struck the Darwin area the project had to be cancelled, and those three transmitters on order for the new NT service were resited at Carnarvon and Shepparton.

The new plan includes a specialised type of aerial, a vertical incidence of a log periodic design, specifically constructed for this type of transmission, as the aim of the station is to lay down a strong signal in a restricted area.

The idea is to provide a signal from these transmitters which will be relatively clean in the service area, and will not suffer from distortion as can be the case in this type of transmission. The basic transmission pattern is that the lower frequencies will be used during the hours of darkness and the higher frequencies during daylight; at the present time only the 60 and 120 metre bands are being used. Due to the low sunspot activity, these frequencies are in operation but the transmitters can move up as high as the 19 metre band when transmission conditions improve.

The transmitters will be unattended, and will be linked to the Darwin transmitting site on Cox Peninsula, the site of Radio Australia's high powered transmitters. Facilities have been provided to take over any programme failure and the operation of the three transmitters is controlled by its own microprocessor system.

The Alice Springs station has the call sign VL8A and uses 2310 kHz 0700-2230 UTC and 4835 kHz 2230-0700 UTC. The station at Tennant Creek has the call sign VL8T and operates on 2325 kHz and 4910 kHz and from Katherine broadcasts will be on VL8K 2485 and 5025 kHz. In the case of the latter two stations, the tentative plan is for the lower frequency to be operating 0700-2230 UTC and the higher channel 2230-0700 UTC. — Arthur Cushen

## COMMUNICATIONS NEWS


## New tube for Marconi transmitter

The new YL1660 500 kW tube from Philips Elcoma has just gone into full production, following the successful completion of trials at the BBC's Rampisham transmitter station.

Philips, the BBC and Marconi Communication Systems of Chelmsford, UK, conducted joint trials during which the tube was fitted into the existing socket of Sender No 48 — a Marconi B6127 at Rampisham in the UK. The tube underwent the full range of transmitter functions, from start up to full operation and frequency changing, and successfully delivered its full rated output power. Unlike many comparable tubes, no black-heat switch-on procedure is required. This reduces costs as less power is needed.

Philips is the second manufacturer to have a tube accepted by Marconi for its 500 kW transmitter. This is the first time such a high-power transmitter has had two different sources for its output valve.

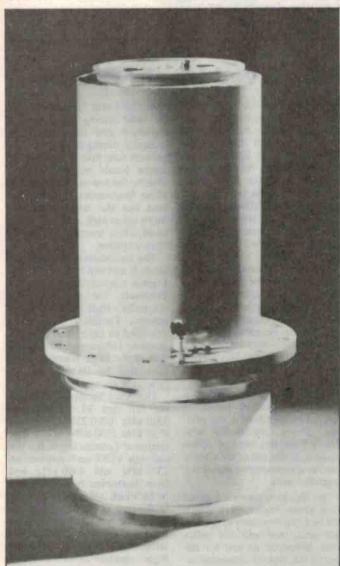For further information contact Philips Electronic Components and Materials (02)439-3322.



## **Telecom's ISDN plans** announced

Telecom is planning to introduce the first stage of its Integrated Service Digital Network (ISDN) over the next three years.

Mel Ward, Telecom's chief general manager described it as an exciting step forward in telecommunications. "Over the past decade we have been developing our digital switching and transmission capacity and we now have a digital network as modern as any in the world.

"The next step — ISDN — is to transform this network into one which will not only carry voice traffic, but all forms of data, text and image. This will mean that one single 'pipeline' into the network can accommodate a variety of terminal equipment and give a wide range of services.

"It represents the real convergence of computer and telecommunications technologies," Mr Ward said. "Initially it will carry traffic at speeds of up to 64 kilobits per second and enable information systems like Viatel to use high speed colour of photographic quality. It could pave the way for colour facsimile transmissions."

Mr Ward said that the first step would be to offer ISDN service in each mainland capital, giving access to business customers with modern PABXs.

#### **KILOHERTZ COMMENT**

AUSTRALIA: Radio Australia's "Talkback" programme which is now hosted by Brendon Telfer and contains informatlon for those interested in radio communications, has been retimed. Broadcasts are now Friday 1610 UTC, Saturday 0310, 0810 and 1240 UTC. The session contains a weekly report on propagation conditions and a look at future prospects on the higher frequencles.

CANADA: Radio Canada's "Shortwave Digest" is now heard at 0405 UTC on Monday on 9755 kHz. The session is conducted by Ian McFarland and includes a weekly round-up of news on station schedule changes and new frequencies observed in North America. A session more sulted for Australian reception is broadcast on Saturday 2130 UTC on 11945, 15325 and 17875 kHz.

ECUADOR: HCJB broadcasts "DX Party Line" three times each week, and compere John Beck is heard on Monday 0930, Wednesday 0700, and Saturday 0930 UTC. The transmissions to the South Pacific of this 30 minute feature are carried on 6130, 9745 and 11925 kHz. "DX Party Line" includes a report from the South Pacific on the third Monday of each month, while on the fourth Monday information on the South Pacific Association of Radio Clubs is featured.

GUAM: Station KTWR "DX Listeners Log" has been retimed to Saturday 0800-0815 UTC and is now on 15115 kHz. This programme also features a report from the South Pacific on the third Saturday, and an SPARC news release on the fourth Saturday of each month. NEDERLAND: Radio Nederland "Media Network" programme is now heard at the earlier time of 0450 UTC on Thursday on 9895 kHz. The broadcasts for the South Pacific are carried at 0750 UTC on 9630 and 9715 kHz and again at 1050 UTC on 9650 kHz. The session is compered by Jonathan Marks and includes a report from New Zealand on the first Thursday of each month.

SWEDEN: Radio Sweden has a transmission to Australia in English at 1100 UTC on 15115 kHz and the session on Tuesday includes "Sweden Calling DXers". A new transmission 0400-0430 UTC on 9665 and 9695 kHz, also has the DX programme during the Wednesday broadcast.

UNITED KINGDOM: The popular BBC session Waveguide has been retimed and is now broadcast to the Pacific on Sunday 0745 UTC with 7150, 9510 and 9640 kHz giving the best reception. The programme is repeated Tuesday 1115, Wednesday 0430, and Thursday 0130 UTC. The session is designed to help listeners hear the BBC World Service better, and also includes schedule changes with receiver reviews and tips on improving reception through the use of more efficient aenals.

This item was contributed by Arthur Cushen, 212 Earn St, Invercarglil, New Zealand, who would be pleased to supply additional information on medium and shortwave listening. All times quoted are UTC (GMT) which is 10 hours behind Australian Eastern Standard Time; areas observing Daylight Time should add a further hour to these schedules.

## Red Cross radio in world trouble spots

casts.

The Red Cross radio conducts regular tests on its frequency as a precautionary measure to ensure that in the event of any major disasters communication is available from Geneva to ICRC staff in outlying areas.

The Red Cross had its beginnings in Italy in 1859 during the war between Italy and Austria when a young Swiss, Henry Dunant, was moved to action by the ghastly plight of the wounded. Henry Dunant improvised relief for them with the assistance of the local population. Following this five men met in Geneva in 1863 and decided to create what is now the ICRC. In 1864 the first convention was adopted, a red cross on a white background.

During World War II the

**DOC** news

A report commissioned earlier this year by the Department of Communications has warned against selling off profitable aspects of the operations of Telecom and OTC. It also says Australia should reject any proposals from private international satellite companies for direct access to Australian users.

Australia should also look at ways in which its Aussat satellite system could provide coverage to the South-west Pacific and South-east Asian regions, the report says.

These and other recommendations are contained in a report entitled Transborder Data Flow and International Trade in Electronic Information Services: an Australian Perspective, by Dr John Langdale, a senior lecturer in geography at Macquarie University.

Mr Michael Duffy has announced that the Government has taken the first step towards achieving the equalisation and aggregation of regional commercial television by agreeing in principle to the upgrading of facilities at many of the Commonwealth's multi-purpose transmitting stations in regional areas of Australia — an essential step if its broadcasting objec-

manently for its radio broad-

the use of a frequency in time of

major crisis, and then began test

transmissions on the frequency

of 7210 kHz using the technical

facilities of the Swiss Post &

Telegraphs which also provide

its own studio in Geneva; broad-

casting facilities are provided

In 1948 the ICRC was granted

tives were to be met. The Minister said these objectives included the expansion of commercial television services in regional Australia through equalisation (three commercial services in regional areas), development of commercial FM radio and the provision of a second regional radio network for the ABC.

The Illawarra television operator, WIN-4, has been informed that it would be required to move to the UHF band within three years.

The Minister says it forms part of the Government's plan to bring more commercial television services to regional Australia.

In the specific case of WIN-4, the move to UHF had to be made because the station, by its presence on VHF channel 4, was blocking further development of FM radio services in the region.

Two new proposed local commercial services will transmit on the VHF band along with SBS and part of the ABC service. The ABC will move totally to UHF, making Wollongong a UHF-only city.

free of charge by the Swiss PTT

and Swiss Radio International.

The programmes (in English,

French, German, Spanish, Por-

tuguese and Arabic) give news

of Red Cross action around the

Over the past few months Red

Cross Radio has increased its bi-

monthly tests on 7210 kHz

which are mainly for Europe.

Broadcasts in English are on the

Geneva.

world

A Department of Communications spokesman has appealed to farmers across Australia to ensure all their two-way radio equipment is licensed so that any threat of interference to other services is averted.

The spokesman warned that under the *Radiocommunications Act 1983* penalties for unlicensed use of radio equipment include confiscation of equipment and a fine of up to \$2000, or imprisonment for a maximum of twelve months.

A prominent National Party spokesman has described claims that a coalition Government would sell Telecom as "alarmist and untrue". Mr Bruce Lloyd, spoke of Telecom as "the key safeguard for country people".

This puts Mr Lloyd squarely at odds with Opposition Leader John Howard, and the Opposition spokesman on Treasury matters, Mr Jim Carlton.

DOC Minister Duffy reaffirmed the figure of \$490 million as the estimated value of the cross-subsidisation from profit last Sunday of each month 1100-1130 UTC, and the following Monday 1700-1730 UTC.

Transmissions over Swiss Radio International to Australia are at 0740-0757 UTC on 9560, 15305, 15570 and 17830 kHz. These broadcasts are on the last Monday of each month, and the following Thursday.


- Arthur Cushen

making services to loss making services in Telecom in 1984-85, a matter vitally affecting country people.

Work on installing new earth stations in remote communities to tap into Aussat television transmissions is gathering momentum the DOC Minister has noted. Special decoders being used in the program are under manufacture in Toronto, Canada, and will be tested at the DOC's lab in Canberra before being despatched to the outback sites. In all, 61 new earth stations are to be installed.

The Government has decided to walve sales tax on earth stations for domestic use bought to receive satellite radio and television services from Aussat. The Minister has predicted the benefit to country people should be at least \$500.

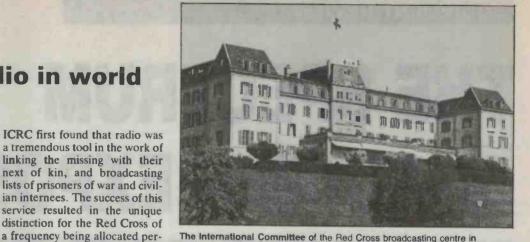The cost of each station, as already indicated by distributors, ranges from \$2250 (excluding sales tax) for a 1.5 metre diameter dish. Exact prices would be subject to usual market place negotiations between seller and buyer.



te what is now the ICRC. In the first convention was oted, a red cross on a white

## EQUIPMENT REVIEW

# THE SPECTRUM ANALYSER EXPOSED

IT WAS WITH some trepidation that I asked the editor "why not review a spectrum analyser?", a caution not out of place as spectrum analysers have been surrounded by some doubtful mystery in the technical world. They do not lie thick on the benches of labs or service departments. Even today, the price of models goes well into five figures, so it is not surprising that they are few and far between, with the result that design engineers are almost the only users.

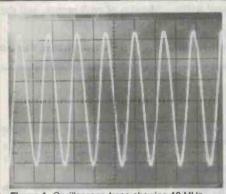


Figure 1. Oscilloscope trace showing 10 MHz signal. If you expect this to be a pure sine wave then see Figure 2.

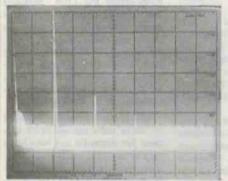


Figure 2. Same 10 MHz signal on the spectrum analyser shows that signal, thought to be a pure sine wave, has harmonics. Analyser dispersion is set at 5 MHz/div and shows first and second harmonics at 20 and 40 MHz. The fundamental (10 MHz) is set to top of screen and the relative amplitudes of the harmonics, referenced to the signal are seen to be 40 dB and 50 dB below the signal.

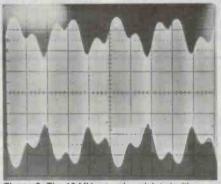


Figure 3. The 10 MHz signal modulated with audio tones of approximately 1.5 and 2.5 kHz. Frequency components are impossible to recognise, when viewed on an oscilloscope.

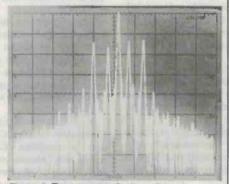


Figure 4. The same amplitude modulated signal on the analyser, set so that resolution shows 2 kHz per division. The two audio sidebands can be seen above and below the carrier frequency. Also notice additional lower level sidebands possibly caused by intermodulation or harmonics from the audio frequencies also modulating the 10 MHz signal. Obviously a spectrum analyser would be useful for further investigation if this was an unexpected development!

To allow lower orders of technical staff to use a spectrum analyser used to be standard heresy. The secrets of this 'black box' were literally kept under wraps by management nervous about unknowing hands wrecking the instrument.

Today the picture isn't so grim and spectrum analysers are finding a role alongside more commonly used instruments such as the CRO and signal generator.

#### **Hertz history**

First, a definition. A spectrum analyser is like an oscilloscope in that both present, via a CRT screen, a graphical representation of an electrical signal. The oscilloscope is used to look at signals in the time domain, which is a technical way of saying amplitude as a function of time.

The spectrum analyser allows you to look at signals in the frequency domain, which simply means that the amplitude is looked at as a function of frequency. Maybe a diagram or two will show you the difference. The familiar pure sine wave display on the screen of an oscilloscope is shown in Figure 1. The display shows the amplitude (measured in volts) as a function of the time base selected.


The same signal displayed on a spectrum analyser looks like that in Figure 2.

Instead of the base line representing time, the spectrum analyser base line is calibrated in terms of frequency. Thus, each vertical line may represent an interval of 2 MHz, which means in our example we are looking at a 10 MHz signal with a certain amplitude — not usually measured in volts but in power (dBm).

The capacity of the spectrum analyser to look at discrete frequencies is valuable when more complex signals are involved. Figure 3 shows a more complex signal displayed on the oscilloscope, which I will describe as multitone amplitude modulation of an rf carrier. The frequency components of the signal are summed together and are impossible to separate, as you can see.

The same signal displayed on a spectrum analyser would appear as in Figure 4. This shows the carrier as well as the two moduBringing the spectrum analyser out of the closet and on to the bench! If you work with rf, this attractive tool is now available at affordable prices.

Peter D. Williams

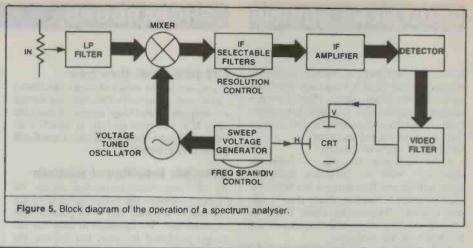

lating frequencies. The other important feature that can be seen from all this is the percentage level of modulation of each of the two tones. One might ask, why, when there are only two tones modulating, you can see the carrier in the centre and two frequencies each side. The answer is that AM or amplitude modulation gives a sum and difference product so the spectrum analyser looks at what is produced above and below the carrier frequency.

One of the major differences between the oscilloscope and a spectrum analyser is the frequency at which each can operate: an oscilloscope capable of operating above 400 MHz is an extremely rare device, whereas spectrum analysers are available to look at signals up to and beyond 40 gigahertz. But it is important to emphasise that spectrum analysers do not replace oscilloscopes; rather their advantage lies in gathering information in the frequency domain.

#### How does it work?

Very simply, a spectrum analyser is a narrow bandwidth, superheterodyne receiver which can be electronically tuned in frequency. The detector output is coupled to the vertical display of the CRT and the sweep generator providing the electronic tuning is coupled to the horizontal display. A simplified block diagram looks something like Figure 5.

The spectrum analyser has different controls from the CRO. FREQUENCY SPAN or FREQUENCY SPAN/DIVISION, together with FREQUENCY, are two functions to be found on the front panel. RESO-LUTION (or RESOLUTION BAND-WIDTH) may not be immediately obvious, as it is usually coupled or locked to other interrelated controls.

As a receiver, the spectrum analyser is subject to the same 'ills' that any receiver might have designed into it and precautions have to be taken to minimise images and intermodulation effects; you have to pay attention to good dynamic range, noise figures and sensitivity.

In operation, the signal requiring investi-

gation is passed to the mixer after being reduced to a suitable level. The bane of the spectrum-analyser-keeper is the ever present possibility of accidentally feeding a transmitter output into the front end. Repairing the damage is always expensive and the perpetrator often finds himself in the job market! The attenuator is designed to reduce signal level, but will not act as a fuse!

The lowpass filter minimises the analyser's IF image response and after mixing with the signal from the VCO (voltage controlled oscillator), the signal passes through the IF filter. This filter's bandwidth is adjustable and determines the resolution of the analyser.

'Resolution' simply means the ability of the analyser to separate signals for closer examination. Very high resolutions of 10 Hz or bandwidths of 300 kHz can be found in low frequency analysers operating up to 120 MHz. Very expensive analysers covering up to 20 GHz may have small bandwidths too. If a bandwidth of 10 Hz is selected, it should be possible to resolve and see displayed on the screen, signals that are 10 Hz apart — but not without difficulty and the ability to do this is a function of analyser design and operator technique.

The resolved signal then passes through the IF amplifier where it may have its amplitude controlled in exactly the same way as it would in a communications receiver. The detector then applies the signal to the vertical plates of the CRT — the stronger the input signal, the greater the vertical deflection.

The video filter serves the purpose of enhancing the display especially when signals are of low level and near the level of internally generated noise or 'grass'.

Since one may not want to sweep the full range of frequencies that the analyser is capable of receiving, some means is employed to control the sweep range or disper sion. This is the frequency control span mentioned earlier. Usually there are three modes employed. Full scan or full span are used where the complete spectrum is displayed, and in the case of the Anritsu we are reviewing (see page 101) this would show any signals in the complete range of 0 to 2 GHz. This position is used when trying to locate signals.

Alternatively, when the wanted signal has been located, the frequency per division mode (10 divisions on the Anritsu) is employed. This means that the span control can narrow the scan range over the screen so that the vertical lines on the graticule represent 10 MHz, 1 MHz, 10 kHz, or even 1 kHz for each division. Thus, it is possible to 'zero in' or focus on a particular signal.

For example you might want to see if there is any noise on the sidebands of an oscillator, or whether there are frequency modulation or other instabilities present. This technique is employed in analysis of defence radar signals; it is possible to analyse the pulses to estimate the type of equipment being used. Klystrons and other high power radar generators have 'finger prints' of their own.

The third mode that can be employed is zero-scan, when the analyser becomes a fixed tune receiver with the selectable bandwidths that I mentioned earlier — quite useful for real time analysis of a single signal.

Of course the selected signal can be tuned to the centre of the screen when the analyser is in any of the scan range positions and a tuning control shows the frequency that the centre of the screen represents. Some analysers have mechanical numeric indication; others have digital LED readouts or a slide rule with pointer indications.

These features are to be found on almost all spectrum analysers. Variations on the theme, especially with higher priced units, can give you digital display, storage, control and readout with the use of controllers and an instrumentation interface bus.

#### Using the analyser

The spectrum analyser does nothing more than its title suggests: it analyses signals. The most frequent use for the analyser is to determine *relative* amplitude and *relative* frequency.

The vertical divisions usually represent 10 dB steps, although 2 dB per division can be used. Linear steps are usually in volts.

### EQUIPMENT REVIEW

## SHOPAROUND

Most analysers have a built-in calibrator which provides both a frequency reference and a known power level. Having such a reference means that the absolute amplitude of signals under investigation can be assessed with limited accuracy. Some other applications are:

1. To check pure sine wave — harmonic distortion. With no harmonic distortion there will be one line only on the screen at the frequency of the sine wave. If an rf carrier contains frequencies other than the wanted one, the levels and frequencies will be shown on the analyser.

2. Amplitude modulation. Not only is the carrier displayed but also sidebands at a distance from the carrier equal to the modulation frequency. Additionally the power in the sidebands is dependent on the percentage of modulation so that if you have 100 per cent modulation, you will see that each sideband is 6 dB below the carrier, ie, 50% power in sidebands. This is quite a convenient way to check a modulation meter — at least at full scale.

3. Frequency modulation. Frequency modulation produces sidebands that are centred around the carrier as in AM except that more than one sideband is generated, and all are multiples of the modulating frequency.

4. Field strength. Of increasing concern today is the compatibility of electronic equipment. Electromagnetic interference has been the subject of recent seminars in Australia. Unwanted radiation from systems can be rapidly detected with the spectrum analyser and if engineering is done to effect improvements, any changes can be readily seen.

5. *Transmitter testing*. When testing sideband transmitters, intermodulation distortion levels can be readily seen. SSB transmitters and amplifiers must be linear and the appropriate two audio tones fed to the transmitter and viewed on the screen can indicate how linear or clean the signal will be. In evaluating signal generators two fea-

tures should be considered.

Dynamic Range. A practical definition limits the maximum and minimum levels to those that can be simultaneously observed on the screen. A 100 dB display range would be considered very good. Most are 80 dB but 'grass' reduces this. This limitation at the low end is the sensitivity of the analyser and at the top end one might call it the 'burn out' specification. Usually spectrum analysers can accept a +13 dBm power level without damage. However, it is not possible to display the complete range at the same setting.

Stability. A spectrum analyser is not usually as stable as a good signal generator. A drift of less than 50 kHz per 10 minutes is very good. If you are in the world of drum machines, synths and sequencers this low cost device will help you keep things in sync. It has only three ICs, the most esoteric of which is an HP 6N138 optocoupler available from Geoff Wood (02) 810-6845.

#### **ETI-684: Intelligent modem**

As with any micro-controlled design we cannot guarantee the full parts list until the last line of software has been proven with the hardware. We intended to have the full design published by now, but we are not willing to do so if there is a chance a part or the pc board may change. To get things started we have published the intelligent power supply for the intelligent modem. We won't actively chase kit suppliers until we can give them a full and reliable parts list.

## ETI-697: Simple Forth board controller

The relevant pc board and IC are available from Energy Control, see offer page 66.

#### ETI-171: Arbitrary waveform generator

The ability of this instrument to generate standard or arbitrary waveforms has until now only been found in instruments worth thousands of dollars. Last month's project 171 can be programmed with toggle switches, by entering waveform slopes or from the parallel bus of your computer. At the time of writing All Electronic Components in Melbourne (03) 662-3506 was getting a kit together. Rod Irving Electronics (03) 543-7877 has all the ICs and Jaycar is ordering in the ones it doesn't have in stock. Dick Smith has the National Semiconductor DAC800.

#### **ETI-1530: Vibration detector**

This project from last month is surprisingly simple and surprisingly useful, especially if you are bothered by rattles and other gremlins in things mechanical. It can be used on cars, electronic equipment, even plumbing. The key to the detector is the use of a multimeter probe to transmit vibrations. All Electronic Components will have a complete kit. The parts are very garden variety, though the pcb will have to be bought from RCS Radio in Sydney (02) 587-3491.

#### Artwork

For those willing and able to make their own pc boards and/or front panels, we can supply same size film transparencies of the artwork, positives or negatives as required. If this art is not reproduced in the magazine because of space we will supply a photocopy free if you send us a stamped envelope. From the list given below, select what you want and address your request/order to:

'ETI-xxx Artwork'

ETI Magazine PO Box 227

Waterloo NSW 2017

When ordering, make sure you specify positives or negatives, according to the process you use. Your cheque or money order should be made payable to ETI Artwork Sales. Prices for the artwork for these project are:

#### MINIMART

FOR SALE: CONIAN C-126 Four band radio, double cassette deck hi-fi ghettoblaster. In brand new condition, still under warranty, \$500 ono. Ph (02)605-8221, ask for Paul.

WANTED: TELEQUIPMENT OSCILLOSCOPE type S51 for spare parts. Ph after 7pm. (045)79-6176.

FOR SALE: REALISTIC MINI stereo amplifier. SA-150. Cat no 31-1955, unused \$80 ono. Ph Ted (02)331-2872, 12 Leichhardt St, Darlinghurst, NSW 2010.

FOR SALE: VIDEO HEADS for Toshiba V8600A or V8700A VCR, still In unopened package, \$40. Bruce Cooke, (02)645-4060.

FOR SALE: VIC-20 programme library. High quality games, utilities, educational and misc programmes available. Send SAE to Chris Groenhout, 25 Kerlerd St, Watson ACT 2602, for list. FOR SALE: TI 810 printer in excellent condition worth \$2000. Sell for \$750 for quick sale. Peter Kelly (02)450-2522.

FOR SALE: VZ200 SOFTWARE. 25 exciting games on one cassette for the incredible price of \$20 (inc p&p). Send cheque or money order to Lee Tait, PO Box 13, Auburn, SA, 5451 for prompt delivery.

 We'll publish up to 24 words free of charge for you. Copy must be with us by the first of the month preceding the month of issue. Please print or type advertisements clearly! Every effort will be made to publish all advertisements received; however, no responsibility for so doing is accepted or implied. We reserve the right to refuse advertisements considered unsuitable.

 Conditions: Your name and address plus phone number (if required) must be included with the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Advertisements must be private and relate to electronics, audio, communications, computing, etc — general advertisements cannot be accepted. Send your advertisement to: ETI Mint-Mart, P.O. Box 227. Waterioo NSW 2017.



## **ELECTRONICS** ENGINEE

An outstanding career opportunity is available for a dynamic Junior Engineer wishing to achieve their full potential. A Tertiary qualification is not essential for this position

You will be working with the latest state-of-the-art technology for a Public Electronics, Research and Development Company located in Perth. You must be able to use your initiative to think, act and develop ideas in a research and development team.

You will have a minimum of 12 months experience as an Electronics Technician or Engineer and have the ability to undertake all aspects of research projects from design specification through to development and testing. You will be working with many and varied products and must be able to demonstrate a working knowledge of analog and digital

electronics plus be a proficient programmer in micro computers, preferably with Z80 experience. A top salary is offered for the right person plus the opportunity to travel within Australia and overseas. Relocation expenses to Perth will be negotiated with the successful applicant.

For further details call Vicki Landre on (09)322 4911 or submit a written application quoting file no. 5120 to Price Waterhouse Urwick, P.O. Box 7188, Cloisters Square, Perth, W.A. 6000.

**Price Waterhouse Urwick** 


MANAGEMENT CONSULTANTS

**ELECTRON ALARM** 
 
#### HIGH SECURITY DIGITALY CODER KEY ACCESS SYSTEM Direct from manufacturers and importers

High security digital key (easily installed) No batteries The system comprises of keybit control user, reader and control box. Features include:

- Miniature electronic memory that uses the same language as the most sophisticated computers and works by means of a password.
- Equipped with waterproof and anti-tampering reader.
- Uses no batteries.



Easy installation:

If installed in a domestic alarm system, it can be placed near the doorbell, or on the door frame, or on the door itself. When installed in a car alarm system, it can be placed on one of the doors or on the mudguard. It has the great advantage of commanding a quick-alarm anti-theft device from outside (how much can be stolen from a car protected by a delayed anti-theft device!)



Models available: From \$156.00

**KEYBIT** 

KEYBIT 101 TYPE: Command system for car alarms. Engine remains off. Control box inhibited when car in motion. It puts the alarm on when it receives a false code. It is equipped with an on/off bleeper. 12V negative to earth. KEYBIT 102 TYPE: Command system for car door blocking. It can be used with any type of system. 12V negative to earth.

KEYBIT 103 TYPE: It includes in one system the performances of the 101 and 102 types.

KEYBIT 104 TYPE: Command system for domestic alarms. Command system for electric locks. It has an ON/OFF mono/bistable relay. It has a relay for separate alarm. 12V. This product is patented.

**INFRA-RED** PASSIVE DETECTOR

\$96 MADE IN ITALY

**Technical Features.** 

Twin elements sensor - Anti-tamper microswitch - Three vertical fixing positions -Stand-by possibility (automatic with AVS control units) - Built in alarm memory (automatic reset with AVS control units) - Internal links to choose LED function (alarm walk, test, memory) - Sensor screening against spikes and RF - Supply voltage 13.8 V ±20% - Current absorption: 20mA typical (both stand-by and normal operation) - Rel output (normally energized in quiet-condition) - Dimensions 105mm × 70mm × 50mm Weight: 140g - Range; 12 metres - Slot: 90° on horizontal plane (on 11 x 2 rays). 50mm

**GULLIVER MINIATURE REMOTE CONTROL** TRANSMITTER AND RECEIVER 305HHz Frequency 305HHz Working range 80-100m

60mm 35mm 12mm Height Width From \$112.00 Weight 21gm

Over 13,000 possible, code combinations. Will open and close auto and de-energise anti-theft systems plus lots more.

**ELECTRON ALARM SUPPLIES** 225 RAMSAY ROAD, HABERFIELD, 2045 PHONE: (02) 799 4745 MAIL ORDERS WELCOME PLEASE INCLUDE \$8.00 P&P BANKCARD BY PHONE

ETI READER SERVICE 128



## **BOOKS** OF SPECIAL INTEREST

#### electronics textbooks

#### **ELEMENTS OF ELECTRONICS- BOOK 1**

This five book series is an introduction to modern electronics. All of the necessary mathematics is introduced and explained as required. The emphasis is on understanding concepts rather than digressing over the whole field. The author anticipates difficulties the beginner may have and explains them as they occur. BOOK 1 covers all of the fundamental theory necessary to understand simple electronic circuits and components. 209pp. \$9.95 A0003B

#### **ELEMENTS OF ELECTRONICS- BOOK 2**

See Book 1: Covers alternating current theory. 216pp. \$9.95 40004R

#### **ELEMENTS OF ELECTRONICS- BOOK 3** See Book 1: Covers semiconductor technology and introduces transistors and ICs. 204pp. A0005B \$9.95

**COIL DESIGN AND CONSTRUCTION MANUAL** How to make RF, IF, audio and power colls, chokes and transformers. Covers Am and FM radio and TV. An essential addition to the library of anyone Interested in electronics. 106pp.

#### Now Reprinted! \$7.95

Postage and packing additional: Please refer to reply card for charges.

#### electronics for beginners

#### **BEGINNER'S GUIDE TO ELECTRONIC** PROJECTS

B0413B

This guide enables the complete beginner to tackle the practical side of electronics so that the projects featured regularly in popular magazines can be approached with confidence. The basics are covered in detail using practical examples in the form of simple projects. 107pp. C0030B \$6.95

#### RADIO CONTROL FOR BEGINNERS

Newcomers to the fascinating hobby of radio control will find this practical introduction invaluable. A number of constructional projects, many with complete board layouts, are included to help the beginner simply and successfully build up the circuits. 92pp. C0034B \$5.95

SOLID STATE SHORTWAVE RECEIVERS FOR BEGINNERS Details the design and construction of several solid state

shortwave receivers giving a high level of performance yet utilising few components. 93pp. C0044B \$5.95

### constructional projects

#### HOW TO MAKE WALKIE-TALKIES

This treatise on low power transmitter-receivers (walkletalkies) covers many aspects, from licensing requirements and bands, through practical circuitry and construction to the types of aerials that may be used, 104pp. D0056B \$6.95

#### **REMOTE CONTROL PROJECTS**

Primarily for the enthusiast who wishes to experiment with remote control. Full explanations of the how the circuits work are given and many of the designs can be adapted to circuits that have been published elsewhere. Covers remote control by ultra-sound and infra- red as well as radio control. 164pp. D0046B \$7 95

#### ELECTRONIC SECURITY DEVICES

Besides including both simple and sophisticated burglar alarm circuits using light, infra-red and ultra-sonics, this book also gives circuits for gas and smoke detectors, flood alarms, fire alarms, doorphones, etc. 102pp. D0059B \$6.95

#### PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE

For the practical person's workbench, Bridges the gap between practical theory and cut-and- dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias and higher maths are avoided where possible, 249pp. \$9.95 B0027B

INTERNATIONAL DIODE EQUIVALENTS GUIDE Includes zener diodes, LEDs, diacs, triacs, thyristors, OCIs; photo, display, and simple rectifier diodes. 130pp. B0339B \$6.95

#### ELECTRONIC MUSIC PROJECTS

Provides constructors with practical circuits for the less complex music equipment including fuzz box, waa-waa pedal, sustain unit, reverb and phaser, tremolo generator, and the like. Text covers guitar effects, general effects, sound generators, and accessories. 106pp. G0135B Now Reprinted! \$5.95



#### HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

Helps you to overcome the problem of a circuit that doesn't work after assembly by indicating how and where to start looking. Covers most of the common faults that occur when constructing an electronic project. 81pp F0114B

#### \$6.95

#### TROUBLESHOOTING WITH THE OSCILLO-SCOPE

nous hobbyist. It combines step by step procedures for using the 'scope with the specific nuts and bolts of television receiver troubleshooting. 92pp. F0121P \$17.95

#### USE OF THE DUAL-TRACE OSCILLOSCOPE

This programmed text breaks down the process of operating a 'scope into a series of logical steps. It starts with the deflection of the electron beam and continues through the proper use of the triggering controls to measure the phase difference between two waveforms E0259H \$43 50

### circuit techniques and design

#### HOW TO DESIGN ELECTRONIC PROJECTS

Tackles the problem of combining and integrating components into a complete working project with the minimum of trial and error and without advanced mathematics. Guides the reader through examples with circuit analysis, possible solutions and practical designs including component values. 101pp. E0082B \$6.55

#### BASIC ELECTRICITY/ELECTRONICS

Volume 2 gives a detailed coverage of AC and DC circuits including series and parallel circuits, electro-magnetism, resistance, capacitance and inductance with explanations of the associated calculations. 318pp. \$15.95 A0009H

## electronic music and audio/video

#### AUDIO AMPLIFIER CONSTRUCTION

Provides a wide range of preamplifier and power amplifier designs including a low noise microphone, tape head and guitar preamps, and various tone controls. Written for those with limited experience in construction, but certainly useful for the more advanced hobbyist. 99pp. G0132B \$6.55

#### ELECTRONIC SYNTHESISER PROJECTS

For the electronic music enthusiast. This invaluable reference is full of circuits and information on how to build analogue delay lines, sequencers, voltage control oscillators, envelope shapers, etc. The author takes a clear and logical approach to the subject that enables even the beginning enthusiast to understand and build up what appear to be quite complex Instruments. 81pp, G0133B \$5.95

#### SINGLE-CAMERA VIDEO PRODUCTION

Step by step diagrams and illustrations show you how to produce low-budget, high quality video programs using only one camera. There are chapters on audio, lighting, shooting, editing, graphics and set design. 241pp. \$33.50 G0379H

#### AUDIO

A theoretical study of sound waves and acoustical quantities which leads into a study of hearing and room acoustics. A discussion of microphones and loudspeakers is developed into sections on amplifiers and record-Ings, covers digital as well as magnetic and disc record-Ing. 308pp. G0332B

#### \$7.55



**ORDER TODAY** — Simply return the Freepost reply card!

## Excellent for the professional service technician or se-

## **TO OUR READERS...**

### computer hardware and techniques

#### AN INTRODUCTION TO MSX BASIC

K0047B

For those wanting to learn to program, Microsoft Ex-tended (MSX) Basic offers a powerful and flexible version of the most popular computing language. This comprehensive introduction starts with the basics and progresses by stages to the more advanced programming techniques and Includes coverage of advanced multicolour, sprite graphics, and the programmable sound generator. 88pp.

#### \$6.95 THE USER'S GUIDE TO COMMODORE 64 & **VIC 20**

The editors of Consumer Guide have compiled a thorough introduction to the Commodore 64 and Vic 20 computers, software and peripherals. With colour illustrations and a clearly written text, this reference will guide the newcomer through all phases of learning how to use the computer: From setting the system up, learning what each key does, expanding the system with peripherals, to buying new software. Specific exercises are included for each of the keys. Spiral bound, 80pp. H0065G \$8,50

#### EASY-TO-UNDERSTAND GUIDE TO HOME COMPUTERS

Confused by all those computer terms? This clearly written book from the editors of Consumer Guide tells exactly what computers are, how they work and why they are so amazingly useful, all in plain English. Here is all of the information needed to understand and use computers. and even to start programming. A special buying section compares the most popular home computers. This book is your ticket to the computer age! Spiral bound, 96pp. H0066G \$8.50

#### APPLE II ASSEMBLY LANGUAGE

Teaches assembly language programming at the beginning level: No prior knowledge of 6502 assembly language is needed. Includes hands-on excercises and experiments with both software and hardware. Provides Interfacing circults and programs that can be used on the Apple II without modification. 334pp. K0195P \$23.95

\$5 05

Stock of some titles may be limited.

#### COMPUTER TERMINOLOGY EXPLAINED

Concisely explains the most common terms encountered by the home computer enthusiast as well as many of those used with mini- and mainframe computers. Includes tables of ASCII codes and BASIC control codes. 81pp.

#### H0143B ALMOST EVERYBODY'S PERSONAL

COMPUTER BOOK Written for the computing beginner to break the enormous barrier of jargon and mystique that seems to surround computers. With a highly readable approach, the author introduces the basic concepts and developes them into a general discussion on personal computers including choosing and caring for a PC. Also offers an introduction to BASIC programming. 160pp. H0144Z \$8.95

#### SPOTLIGHT ON COMPUTER AWARENESS

An introduction to speaking confidently about how computers work, their applications, their history (from abacus to IBM) and employment prospects in computer related fields. Includes a comprehensive glossary. 84pp. H0145P \$6.95

#### AN INTRODUCTION TO Z80 MACHINE CODE

Starts with a general background to microprocessing and then details the full set of Z80/Z80A instructions. Also covers the use of address modes and gives machine specific listings and sample programs. 107pp. K0180B \$6.55

#### INTRODUCING THE APPLE IIC

This introduction to the remarkable features of the Apple Ilc is also an excellent resource manual: Each chapter starts with elementary explanations, moves on to more technical descriptions and ends with detailed references. The thorough text is supplemented by exhaustive appendices and a full glossary. 400pp. 10084P \$27 95

#### **Z80 MICROCOMPUTER DESIGN PROJECTS**

A complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip. J0156P \$20.75

#### THE BEST APPLE SOFTWARE

Trying to find the most suitable software for personal computers can be frustrating. The editors of Consumer Guide have compiled comprehensive reviews of Apple II, Il Plus and Ile programs based on ratings by user groups; further evaluation is given by the editors and Apple soft-ware expert Roe Adams. Each review describes the program's purpose and features, detailing both the good points and bad. Each program has been rated for ease of use, clarity of written and on-screen instructions, and overall performance. The program's price, publisher, format and hardware requirements are also included. The reviews are presented in sets by topic: Word Processing, Business, Home, Education, Networking, Strategy Games, Arcade Games and Programming Aids. Spiral bound, 160pp KOOGOG \$8.50

#### A PRACTICAL INTRODUCTION TO

#### MICROPROCESSORS

Takes the reader through the construction of a simple microprocessor and experimenting with it to gain an insight into the complexities of microprocessing. The book assumes a general knowledge of electronics J0158B \$5.95

#### MICROCOMPUTING DESIGN & TROUBLESHOOTING

Explains designing microcomputer systems and making them work without expensive commercial development systems or the need for costly test instrumentation. Includes a complete description of two microprocessorsthe 8085 and the 6502. 346pp. .10161P

#### STD BUS INTERFACING

Tells what the STD bus is, why it should be used and how to interface it with various peripherals. Explains addressing I/O devices, the use of different techniques to assign or decode addresses and the transfer of data and control signal timing. 286pp. J0164P

#### EASY ADD-ON PROJECTS FOR COMMODORE

The simple and Inexpensive projects include a pulse detector, model controller, light pen, lap sensor and more plus six projects that make up a weather station. 191pp. J0165B

FORTH PROGRAMMING

Describes both FORTH-79 and fig-FORTH and shows how to write software using these languages and how to add new operations (words) and manipulate the stack. Includes more than 50 useful programs. 246pp. K0298P



#### A Z80 WORKSHOP MANUAL

Intended for those who want to progress beyond programming in BASIC to topics such as machine code and assembly language programming or who need hardware details of the Z80-based computers. 184pp. J0283B \$8.95

#### SECRETS OF THE COMMODORE 64

A beginner's guide to the C64 with masses of useful information and programming tips as well as describing how to get the best from the powerful sound and graphics facilities. Includes two useful chapters on machine code. 109pp. J0297B \$5.95

#### MICRO INTERFACING CIRCUITS: BOOK 1

Guides those who are unaccustomed to microprocessor techniques but have some knowledge of electronics, through a practical approach to address decoding, parallel and serial interfacing, analogue to digital and digital to analogue converters, etc. 96pp. .10325B

\$6.55

#### **MICRO INTERFACING CIRCUITS: BOOK 2**

Developes the practical side of interfacing introduced in Book 1. Discusses sound and speech generators, temperature and optical sensors, motor controllers, etc. 87pp. J0326E

#### \$6.55

#### THE BEST VIC/COMMODORE SOFTWARE

Trying to find the most suitable software for personal computers can be frustrating. The editors of Consume Guide have compiled comprehensive reviews of VIC 20 and Commodore 64 programs based on ratings by user groups; further evaluation is given by the editors and Commodore software experts Jim and Ellen Strasma. Each review describes the program's purpose and features, detailing both the good points and bad. Each program has been rated for ease of use, clarity of written and on-screen instructions, and overall performance. The program's price, publisher, format and hardware require-ments are also Included. The reviews are presented in sets by topic: Word Processing, Business, Home, Education, Networking, Strategy Games, Arcade Games and Programming Aids. Spiral bound, 192pp. K0052G \$8.50

#### WILDCARDS: VOLUME THREE

This collection of programs, tips and techniques for all models of Applied Technology's Microbee personal computer takes a 'hands-on' approach. Small business applications are given, as well as utilities and graphics, and there is a machine language game tutorial included. 122pp

#### \$15.95

Prices subject to change without notice.

This clear and complete guide to FORTH, covers fundamental principles and then a full set of high-level commands. It concludes with advanced techniques and

\$37.95

AN INTRODUCTION TO 6502 MACHINE CODE Starts with a general background to microprocessing and then details all of the legal 6502 Instructions. Also covers the use of address modes and gives machine specific listings and sample programs. 107pp. K0178B \$6.55

FEDERAL MARKETING BOOK SALES

PO Box 227, Waterloo 2017, NSW

\$26.95

## 64, VIC-20, BBC MICRO & ACORN ELECTRON

\$21.95


#### style. 348pp. K0177H

STARTING FORTH

## K0054P

\$6.95

## \$26.75

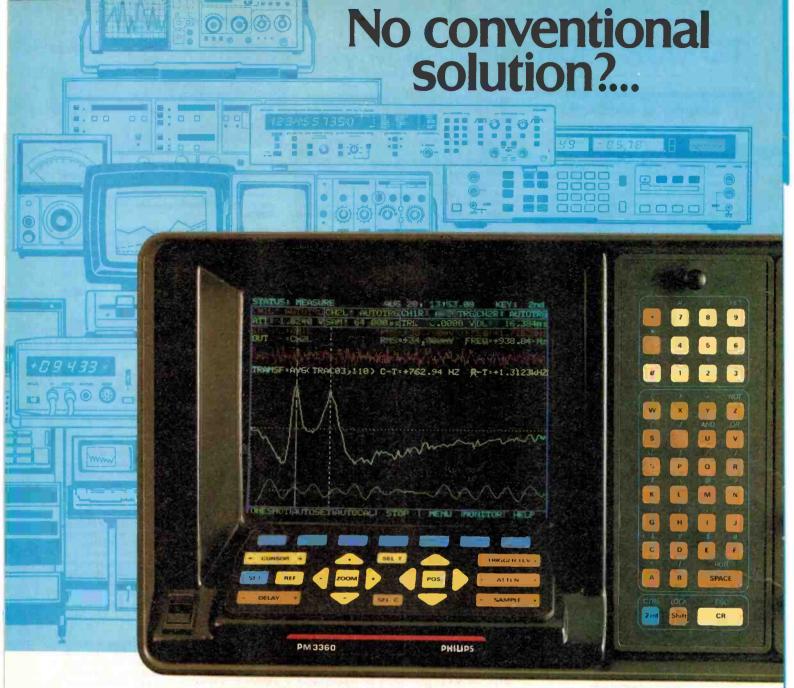

## ... Try the unique PM 3360 Waveform Analyzing System

If you have a specific measurement requirement that's hard to solve with conventional instruments, it's time you tried something really different ... the unique Philips PM 3360 Waveform Analyzing System. It's so versatile, you can use it as a digital storage oscilloscope, BASIC-programmable computer, audio and video signal analyzer, signal averager, distortion and vibration analyzer, counter/timer, digital multimeter, power monitor, FFT analyzer... and a lot more besides. Just look at these superb features: Its powerful Advanced Mathematical Software (AMS II) package includes averaging, differentiation and integra-



Test & Measurement tion, auto- and cross-correlation, cut-function and FFT analysis. • There's a 16-bit BASIC

You get a choice of plug-in input modules, each with its own independent ADC, memory, trigger, timebase and delay.

Data storage options include reference memory (128 to 320 Kbytes), non-volatile memory and built-in single- or dual-floppy disk drive.
Up to 7 different colors are available to facilitate interpretation of results.
You can display up to 10 separate traces, plus 2 color-related alphanumeric measurements for each trace, and name each one yourself.
And there's a wide choice of modular hardware and software to match requirements, e.g. external keyboard, color printer, choice of interface (RS232C, IEEE-488) and plotter packages, etc. Contact your nearest Philips office for further information:

Philips Scientific & Industrial SYDNEY: Box 119 North Ryde 2113 Tel (02) 888 8222 (Toll Free (008) 226 661) MELBOURNE: Locked bag No. 5 Oakleigh South 3167 Tel (03) 542 3600

PHILIPS

### EQUIPMENT REVIEW

## UNDER ANALYSIS —Anritsu MS610A spectrum analyser

A versatile, 8085 processor controlled tool, the Anritsu MS610A spectrum analyser looks like one of the best lab buys around. It's easy to operate with a fine range of frequencies for a reasonable price.


THE SPECTRUM ANALYSER must now be considered as an everyday test instrument, even in smaller service organisations, and a must in all production enterprises charged with radio frequency engineering and maintenance.

The background and capabilities of such an instrument have been covered elsewhere in this issue (see page 94) and when the opportunity came to test a Japanese version, we jumped to see how our northern technologists plan to attack the strongholds of HP and Tektronix. Priced at under \$10,000 (exchange rates notwithstanding) this instrument must be considered seriously.

The Anritsu analyser covers from 10 kHz to 2 GHz and comes from a well known and technically able Japanese company, as the lowest priced instrument in its range.
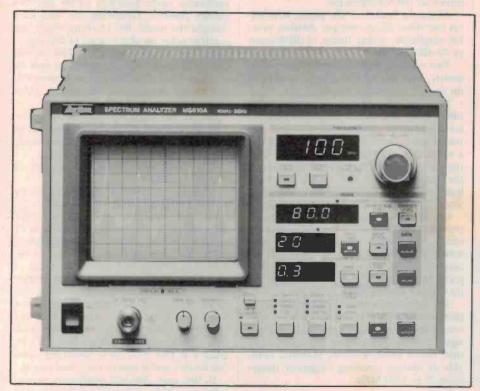
#### **Features**

The frequency coverage is ideal. With a response to 2 GHz, transmitter harmonics and spurious signals can be readily observed. Other 'spectrum monitors' in the market place, especially those in combina-



### Peter D. Williams

tion type instruments, seeming to check out at 1 GHz, make no allowance for checking cellular radio transmitters and some microwave systems. Such radio telephones will operate around 800 MHz and it is useful to be able to look at first harmonics. Other two-way services are moving higher in frequency too, and one suspects that an upper limit of 2 GHz may need to be increased in a year or so.

For those unfamiliar with hands on operation of spectrum analysers, it would be useful to review what to look for if ease of operation is to be a consideration. A large percentage of your time is going to be involved in searching for signals and assessing their relative amplitude.

The three simple procedures are as follows:

1. Tune to the signal to be measured.

2. Zoom in on the signal to be measured by decreasing the frequency span.

3. Operate the attenuator control (gain) to put the signal at the top of the screen and read its amplitude in dBm.

You will also have to ensure that as the bandwidth and frequency span is reduced, so is the sweep time. As bandwidths are reduced, the band pass filters must have time to respond or amplitude calibration will be lost.

Any respectable analyser has the ability to couple the frequency span, the resolution bandwidth and sweep time so that optimum values are selected and the Anritsu MS610A does this very well.

Looking at top right hand side of the MS610A, the frequency tuning knob is a concentric control with the outer knob for coarse tuning and the inner dial for fine tuning. The four-digit LED display shows the frequency with a 1 MHz resolution. Immediately below the display are two push-buttons which put the dialled signal display

ETI March 1986 - 101

#### TABLE 1. OPTIMUM SETTINGS

FREQUENCY SPAN	RESOLUTION BANDWIDTH (RBW)	SWEEP TIME VIDEO FILTER OFF	SWEEP TIME VIDEO FILTER 10 kHz
2 GHz	300 kHz	0.1 s	2.0 s
1 GHz	100 kHz	0.2 s	2.0 s
0.5 GHz	100 kHz	0.1 s	1.0 s
0.2 GHz	100 kHz	0.1 s	0.5 s
0.1 GHz	30 kHz	0.2 s	1.0 s
50 MHz	30 kHz	0.1 s	0.5 s
20 MHz	30 kHz	0.1 s	0.2 s
10 MHz	10 kHz	0.2 s	0.2 s
5 MHz	10 kHz	0.1 s	0.1 s
2 MHz	10 kHz	0.1 s	0.1 s
1 MHz	3 kHz	0.2 s	0.2 s
500 kHz	3 kHz	0.1 s	0.1 s
200 kHz	3 kHz	0.1 s	0.1 s
100 kHz	1 kHz	0.2 s	0.2 s
0	30 kHz	0.1 s	0.1 s

at the start or at the centre of the screen. Each key is illuminated, if its function is active, with a built-in LED. It is usual to put the frequency in the centre as frequency or modulation components may show up either side of the signal under investigation, such as with AM.

The pushbuttons are colour coded for easy identification — blue buttons for mode, green for a function controls, orange for the parameter and white for data.

Below the frequency group the mode group of controls with data keys does most of the business you want from an analyser.

The digital display in this panel shows the reference level which is the value of the level selected at the top of the screen, either as dBm or dB $\mu$ , or, if the LEVEL is depressed, a section at the top of a trace is brightened and the actual value of the trace peak amplitude is then shown on the display. This is a very useful parameter to have displayed as you can not only take a value reading from the screen, but get additional verification from the digital display.

Immediately below the REF and marker keys are the FREQUENCY SPAN and INPUT ATTENUATOR controls with their LED displays. Further down is a row covering the RBW (resolution bandwidth) and sweep time. Two data keys on the extreme right hand panel are used to increment or decrement any of the parameters of frequency span, reference level resolution bandwidth, input attenuator or sweep time.

The MS610A couples frequency span, bandwidth, and sweep time with the keys COUPLED TO REFERENCE and COU-PLED TO SPAN. Thus, when using the couple functions all you have to do is set the REFERENCE LEVEL and FREQ SPAN and all other measuring conditions are set at their optimum values. This includes the attenuator which ensures that the incoming signal has a level no greater than -30 dBm at the mixer for good intermodulation performance.

Table 1 shows the optimum settings for each of the parameters and also serves the added purpose of outlining the resolution bandwidths that can be selected, and the

102 - ETI March 1986

frequency span available on the analyser. It is also possible to put the analyser into the uncoupled condition by depressing the function setting keys. When this is done, the DISPLAY UNCALIBRATED light might illuminate (located right under the CRT graticule) if incorrect combinations of RBW and sweep are selected. It is then possible to operate the DATA keys to select bandwidths and frequency spans to suit particular requirements. Repressing both COUP-LED keys restores the analyser to the preordained condition.

When viewing the frequency span on the digital display, it should be kept in mind that the figures show the full width of the screen as being the frequency span. Other manufacturers show vertical graticules as so many MHz per division. For example, in Table 1, the 1 GHz frequency span could be shown as 100 MHz/division.

Along the bottom of the panel, keys select the video filters, the per division value for amplitude, either linear, 2 dB/division or 10 dB/division.

Two variable controls handle gain and intensity, with the type N rf input connector on the left hand front panel.

The six-inch display is a conventional tube, oddly with focus control and horizontal adjustments missing. We did find that under some conditions of display, there was a need for a slightly finer trace focus. Taking the covers off didn't reveal anything and the local distributor, STC couldn't shed any light on it. (No doubt the service manual when it appears, will explain everything.)

On the rear panel is a BNC socket providing 50 MHz at a level of -30 dBm which was within 0.1 dB of our power meter. A reference level switch is also accessible and can be switched so the front panel can show on the REF/MARKER display either dBm, dB $\mu$ /m (dB $\mu$  per metre).

The latter has interesting possibilities for field strength measurements. With a calibrated antenna, dB $\mu$  per metre of received signals can be displayed on the screen. Anritsu makes three different antennas available as options covering frequency ranges from 25 to 1700 MHz.

#### Options

Noise field strength measurements can also be done as the instrument has the option of being fitted with a QP (quasipeak) detector conforming to the appropriate international specifications. Quasipeak simply means that the detector has a circuit that holds the peak amplitude for a selectable amount of time. This is because noise signals are impulses in character which are difficult to see on the CRT.

Although not fitted to the test unit, the GPIB, IEEE-488 compatible bus can control all functions except power on-off, CRT intensity, frequency zero adjust, gain adjust and frequency setting. For automated test programs this facility is recommended.

Another option is the tracking generator, a swept signal source controlled by the spectrum analyser and enables responses of transmission lines, wideband amplifiers, filters and other networks to be optimised. Again, we did not have the opportunity to evaluate this option.

## Performance/technical design

Routine measurements of signals were easily done although the span readout, as mentioned earlier gives the total span of frequency on the screen and not the frequency per division which is usual.

We found the panel layout excellent and a lack of rotary mechanical switches contributed to ease of operation. The two major points of criticism were the analyser's unobvious mode selection LEDs and frequency readout. Operating the data keys changes the mode, but knowing which one is active relies on observation of the appropriate key being illuminated. This indication is not bright enough unless you look directly at the key, (others who were using the instrument adjusted to this after a short time).

As far as frequency readout was concerned, we found erroneous readings above 1000 MHz. An error of 30 MHz must surely be adjustment.

The frequency conversion circuit is shown herewith.

Frequency control of the first LO is by way of a YIG oscillator. YIG stands for yttrium iron garnet. A small sphere of this material, about 0.5 mm in diameter, can be made to oscillate and is tuned by magnetic fields. YIG oscillators are useful at microwave frequencies and those who sneer at such devices in favour of PLL and synthesised oscillators, should consider that synthesis can actually result in a degraded system unless great care is taken to engineer out phase noise and other spurious products. The inherent advantage of a YIG oscillator is that it is quite spectrally clean (relatively) and it makes for linear tuning.

In this case, the first oscillator operates between 2.5214 and 4.5214 GHz; the first

## EQUIPMENT REVIEW

IF of 2.5214 GHz contributes to very good image performance.

The second oscillator at 2.5 GHz downconverts to 21.4 MHz and a further conversion to 3.5 MHz where relative bandwidth filters, and video filter circuitry take care of the signal before it is applied to the vertical plates of the CRT.

We liked the comparative lack of controls on the front panel and the 8085 processor handles each section particularly well very friendly.

Internally, the layout and construction is of a high order. The manual, in the usual Japanese tradition, falls somewhat short in the technical department in so far as schematics are concerned. Operating information is, however satisfactory.

#### Conclusion

This Anritsu MS610A analyser may not have digital display, PLL or storage facilities yet manages to produce a performance equal to other instruments in its class and at less expense.

It has the advantage of simple, clean cut design and engineering without the problems of sophisticated circuitry that must be employed for PLL, storage, etc.

As far as we could determine, specifications were met or exceeded with the exception of frequency readout above 1 GHz, and I would refer you to the test figures/specifications.

On the negative side, battery operation is not possible although the instrument is billed as portable. We understand that battery operation is on the way. The YIG oscillator is subject to magnetic influences which can distort the trace. (Try a soldering iron along side it when switched on. The trace from a signal generator looked very sick until we realised the ac magnetic field was upsetting the YIG oscillator.)

With its options of tracking generator, emi and field strength measurement potential, the MS610A is good value. No instrument is perfect but good features and practicality make it worthy of consideration if you plan to update your workshop, test lab or production line.


Peter D. Williams is director of Associated Calibration Laboratories in Melbourne.

#### **TECHNICAL SPECIFICATIONS**

We evaluated the essential specifications which we believe are most meaningful in terms of adequate performance.

adequate performance	e.
Model Supplied Power Dimensions & Weight	ANRITSU MS 610A Serial No M77195 STC SI Georges Rd, Thombury, Vic. ac 240 V 48 to 63 Hz 85 VA 177 x 284 x 351 mm; 13.5 kg
Manufacturers Spe	ec:
Range	10 kHz to 2 GHz
Display/accuracy	4 digit LED 1 MHz resolution ±10 MHz
Span	zero, 0.1 MHz to 1 GHz in 1.2.5 sequence (see Table 1)
Resolution bandwidth	
Stability	better than 100 kHz/5 min after 1 hour
Residual FM	better than 5 kHz p-p at less than 0.1 s sweep
Frequency response	±1.5 dB, 100 kHz to 1.5 GHz +2 dB -3 dB, 1.5 GHz to 2 GHz
As tested in Labora	atory:
Resolution	bandwidth 30 kHz; at 3 dB down Intersection of two close in frequencies, the observed bandwidth p-p was 32.4 kHz; all other bandwidths within 5%
Residual FM	sweep time: 0.1 s measured result: 2 kHz p-p spec: 5 kHz p-p
Stability A	1 minute - 1 MHz drift from switch on
В	2 minute — 2.5 MHz drift from switch on 5 kHz/5 min 1 hour from switch on spec: 100 kHz/5 mm from switch on
Frequency response	±1 dB to 1 GHz spec: ±1.5 dB (100 kHz to 1.5 GHz)
Residual spurious	input attenuator: 0 dB
Response	as tested: -115 dBm noise level spec: -100 dBm or less
Noise sidebands	resolution bandwidth: 1 kHz video filter: 100 Hz measured 30 kHz from signal as tested: better than 80 dB spec: better than 70 dB
AMPLITUDE	
Log scale linearity	scale selected: 10 dB/div

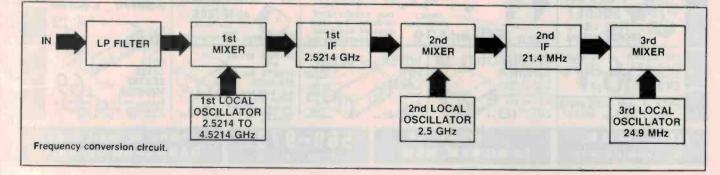as tested: ±0.5 dB spec: ±1.5 dB scale selected 2 dB/div as tested: ±0.3 dB spec: ±1 dB Input attenuator: 20 dB as tested: 1.05:1 spec: 1.5:1 or less intermodulation (2nd/3rd harmonic distortion) Input attenuator: 0 dB Input level: -30 dB as tested: less than 70 dB spec: 70 dB or less



Input VSWR

Dynamic range



## SIEMENS

## **RFI PROTECTION COMPONENTS** Five ranges of components to counter problems of electrical interference ... outside the lab.

Because there is no <u>one</u> solution to radio frequency interference (RFI), Siemens makes 5 main ranges of interference suppression components. From these, additional equipment can be customised to cope with your RFI problems.

As you know, outside interference often only raises its ugly head <u>outside</u> the lab. So consider this basic Siemens range that can counter most causes... and see an end to customer complaints, warranty costs, service expenses and legal battles.


1. Surge Voltage Protectors ... ideal for very large energy spikes such as are induced into wiring by nearby lightning strikes to the ground.


2. Varistors ... for lower energy spikes. Also useful as secondary back-up behind gas arrestors; and can be used directly across mains wiring to remove spikes riding on the 50 Hz waveform.

3. RFI Filters ... used on the mains outlet to keep out the most notorious interference; and also to prevent your equipment interfering with others.

4. Ceramic Capacitors . . . to be scattered over circuits and across all the input/outlet lines on data communication points.

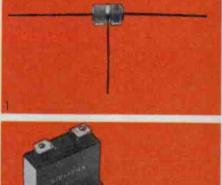5. Specialised Components . . . including X capacitors, Y capacitors, current compensated chokes and micro chokes.



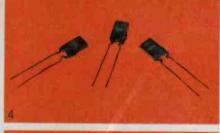





#### **Special Siemens advantages**

- Because Siemens parts are <u>already</u> used by major local manufacturers, substantial stocks are in ready supply.
- Siemens staff are skilled in all the available protection technologies; so can offer real help to designers who encounter tricky problems.

Call us now, for quick supply or helpful consultation.

Siemens Ltd. 544 Church St., Richmond, Vic. 3121. Sales Offices Melbourne: (03) 420 7318 Sydney: (02) 436 8730

Distributors:

Victoria: Promark Electronics (Vic.) (03) 878 1255 New South Wales: Nexus Electronics Pty. Ltd. (02) 439 5800 New South Wales: Promark Electronics Pty. Ltd. (02) 439 6477 Queensland: ECO Electronics (07) 376 5677 South Australia: R.G. Pank Pty. Ltd. (08) 51 2411 South Australia: Protronics Pty. Ltd. (08) 212 3111 Western Australia: Reserve Electronics (09) 328 9755

## **INGENIOUS ELECTRONIC ENGINEERING**

ETI READER SERVICE 105 766/2454 CSA

## WIN A SENSATIONAL 4 WHEEL DRIVE **DAIHATSU 'ROCKY'!**



## **EVERY NEW SUBSCRIBER WILL ALSO GET A** FANTASTIC 35mm CAMERA (Valued at \$25) absolutely FREE!!

magine ... you'll receive 12 feature-packed issues of Electronics Today, Australia's dynamic electronics magazine (delivered to your home FREE). Plus - you'll also get a FREE 35mm Camera (worth \$25)!!

### AND THAT'S NOT ALL . . .

YOU COULD ALSO WIN A DAIHATSU 'ROCKY' 4WD, LONG-WHEEL-BASE DIESEL WAGON.

ALL FOR JUST \$30! Now that's real WINNING VALUE!!

## YES! YOU COULD WIN 'ROCKY' (Worth over \$21,500)

With this powerful 4 Wheel Drive vehicle, you'll always be where the action is! Just look at the incredible FEATURES:

- Power Steering 3-Way Suspension AM/FM Stereo Radio/Cas. Tilt Steering 215 SR Wide Tyres & Wheels
   Carpeting Throughout Full Fabric Seats

PLUS ALL THESE SPECIAL EXTRAS:

Bull Bar 
 Tow Bar 
 Side Steps 
 Weather Shield 
 Exterior Striping 
 Sunroof 
 Headlamp Covers

PLUS A UNIQUE PAINT JOB - ONLY ONE OF ITS KIND!!!

(The vehicle is the same one shown on this page)



## NOW, ALL THAT ADDS UP TO AN OFFER YOU JUST CAN'T REFUSE!! BUT HURRY! This is a limited offer . . . YOU MUST ACT NOW!!! HOW TO WIN, AND CLAIM YOUR FREE GIFT:

Simply complete your special PRIVILEGE OFFER SUBSCIPTION CARD between pages 82 & 83, and

mail it

FREE POST (no postage stamp required) to us. We'll automatically send you your FREE camera with your first issue ... and your name will be entered into the draw to WIN the DAIHATSU 'ROCKY'.



AC T. PERMIT NO. TT85680 ISSUED UNDER LOTTERIES ORDINANCE 1964 VIC. RAFFLES AND BINGO PERMITS BOARD PERMIT NO. 851 237 ISSUED ON 16/12/85, N.S.W. PERMIT NO. TC85/2867 ISSUED UNDER THE LOTTERY AND ART UNION ACT. (Offer valid until 30 April, 1986, All Federal Publishing New Subscribers during Feb., March and April are eligible to win)

DON'T DELAY ... MAIL YOUR SUBSCRIPTION CARD TODAY TO RECEIVE YOUR FREE GIFTI If the Subscription Card has been removed, please write to: ELECTRONICS TODAY FREE POST No. 4 (No postage stamp is required) The Federal Publishing Co. Pty Ltd P.O. Box 227, Waterloo, NSW 2017

## **ADVERTISERS'** INDEX

Alfatron	14
Associated Controls	63
Audio Engineers	
Current Solutions	
Daneva Australia	
Data Parts	
Data Peopie	97
Disco World	4
ETI books	98,99
	97
Energy Control	27
Energy Control offer	66
Geoff Wood Electronics	
Hewlett-Packard	18
Jaycar	41
Macrodynamics	15
NZ Marketing	IFC
Parameters	9
Philips Electronic Components .	
Philips Test and Measurement .	
Prepak Electronics	
Rod Irving Electronics17,2	8,29,64,65
Rose Music	OBC
Scan Audio	32
Scientific Devices	47
Siemens Ltd	105
STC	100
Truscott Electronics	36
Subcriptions offer	106,107
Valrian	97

IT'S A TRUISM that microprocessors are changing the world around us, but somehow one expects electronic measurement to be spared the ravages of computerisation. After all, a CRO is a CRO and multimeter is a multimeter and they're all quite different from spectrum analysers and frequency counters. Right? Wrong. Philips has come up with an instrument that uses computerisation to integrate the functions of all these instruments plus power meters, Fourier analysers and

CH2L : ENAB

CHIL

ADAN SAN : 486.00. STRL 1 0.0000

ENAR

131.00m

+82.875m

rus

timers. The link, as one might expect, is a computer, and it results in a test instrument, the PM 3360, of quite awesome power. It's called a waveform analyser. At \$30,000 odd, it is not for the faint hearted, but it comes with a battery of features that are sure to create interest in labs and on assembly lines all over the country.

The quickest way to come to terms with the PM 3360 is to consider it as two distinct instruments. On the one hand a digital CRO, on the other a computer. The CRO has four possible inputs, and 10 possible traces, defined in seven different colours. The relationship between the channels and the traces is entirely up to the operator. It is possible, for instance, to assign all 10 traces to a single input, or two to each input, or whatever other combination you want.

The traces are important because all the measurements in the system are done on the traces, not the inputs. Thirty-one different measurements can be defined on any one trace, but it's only possible to make two measurements at any one time. If you want more information you have to assign more traces to the input.

This sounds complicated, and indeed, one could make the same measurements a lot quicker with a CRO. That's where the computer comes in. If you select the MONITOR option on the console you wind up with an ordinary computer screen in front of you, fully programmable in a standard, dull as ditchwater, BASIC. If the mood takes you, you can make it jump through all the same hoops your home micro does. However, there are a few addenda. These are the commands for controlling the CRO, and give the device unique power.

From the program it is possible to control all the parameters one can control from the front panel. For instance: TRL = 0 sets the default channel trigger level to 0 V. CPL\$=''AC'' sets it to ac coupled mode. You have complete control of the trace. COL\$ sets its colour, TRS\$ selects the trace for working on (default), and so on. One of the most important words is VAL, which asks for some measurement to be performed on the default trace. For instance PRINT VAL ''FREQ'' will return the frequency of the trace.

This type of programming has obvious

108 - ETI March 1986

# OS JOIN THE SURENT REVOLUTION

## — Philips PM 3360 waveform analyser

Increasing computer power is changing the nature of test and measuring instruments. The PM 3360 is just such a changed beast. Neither a CRO nor a spectrum analyser nor a frequency counter, it winds up being greater than the sum of its parts.

advantages in routine testing type applications or troubleshooting. It is possible, for instance, to make the computer display a message like ''PLACE PROBE ON POINT A'', wait for an input, measure it, then display further messages according to whether the measured inputs are within certain limits.

One thing that impressed me was the softkeys. The softkeys are a line of buttons across the top of the keyboard. Each has associated with it an area at the bottom of the display that can be labelled with the SKY\$ command. Thus SKY\$(1)=''ready'' puts the word READY into the label space, and the command KEY% is used to test whether the appropriate softkey has been pressed.

In many instances it might not be an advantage to do things in real time. The PM 3360 has the ability to store a waveform in memory for later retrieval and manipulation. You can also create new traces by performing mathematical calculations on existing ones. For instance, if you have set TRACE1 to measuring volts, and TRACE2 to measuring amps, you can see a power curve simply by defining a third trace to be TRACE1 x TRACE2.

Even more complex operations are possible because of the disk drives. These can be used to load and save specialised programs, or Philips' own AMS 11 (advanced mathematical processing) package. This gives access to things like real time spectrum analysis using a Fast Fourier Transform on the input signals, and auto correlation, a statistical function that allows one to extract the significant elements of a noisy signal.

This really only scratches the surface of the systems capabilities. The triggering capabilities alone would fill a thousand word article, and so would a description of the peripherals. It's possible to buy different input modules that go up to 50 MHz, all with two fully independent channels. It's fully programmable from either an external keyboard or IEEE-488 bus. Output peripherals include RGB monitors and colour printers.

The biggest problem with the PM 3360 is a psychological one. Like anyone with an electronics background, I expect CRO to look and act like a CRO and when it doesn't I get quite judgmental. According to Graham Blanchett, who leads Philips' marketing effort on the PM 3360, it's a common enough failing. "The biggest problem we have is convincing people that it's not a CRO and should not be judged as one. You might as well call it a signal analyser."

According to Philips, it's wrong to see it as a replacement for a digital CRO. It doesn't work at that level. Typical applications include vibration analysis, FET testing and so on. There must also be strong

## **Jon Fairall**

interest from people with any kind of reasonably low frequency testing requirements.

All in all, I was impressed with the PM 3360. Philips deserves to have a winner with this one. There are only two beefs worth mentioning. I would have liked to have seen Philips put a bit more time and energy into creating a good manual for this machine. Some parts of it are written with such a thick Dutch accent it's quite incomprehensible, and trial and error becomes indispensible. At \$30,000 we are entitled to better.

The other thing that made me wince was the slow response from the keyboard. Even with the terrible design Philips has come up with for the front panel I could beat the computer easily, leading to all kinds of errors and the constant necessity for retyping. I don't understand why this should be so; the thing has a 16-bit data bus, and five processors inside, so you'd think it would really motor along. Such is not the case.

However, these are idiosyncracies. I got used to them in the first half hour. What begins to impress then is the tremendous versatility and power of the instrument. The next generation should take ergonomics a little more seriously. Regular as clockwork, once every 76 years, a spectacular Comet hurtles into the solar system to sweep through the night skies of planet Earth. For a few tantalising weeks the Comet is plainly visible to the naked eye -

SPECIAL COMMEMORATIVE OFFER FROM

DISCOVERING

Exclusive

limited

period offer


A COMET Halley

trailing a fantastic tail hundreds of thousands of kilometres long. A Comet Called Halley tells where to look and how to photograph the Comet, what comets are and where they come from. Throughout history the Comet has terrified and fascinated people. Thanks to the work of Edmond Halley those fears were finally allaved, and our excitement now stems from the possibilities of learning more about comets from ground-based telescopes and
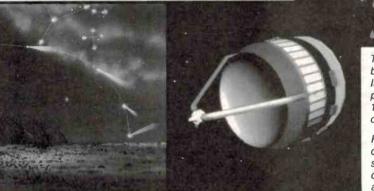
## It's in our skies once more... Now, everything that scientists know so far

the space probes flying to intercept Halley's Comet.

A commemorative Family Record of the 1986 visit of Halley's **Comet Free with each** Video purchased.



The Comet was seen by Edmond Halley at Islington in 1682. He predicted its return in 1759. It was sighted on December 15, 1758.

Far from the sun, a comet resembles a snowball of ice and dust a few kilometres across

The appearance of Halley's Comet relative to the horizon for 30°s.

Giotto is the European Space Agency's probe to Halley's Comet, named after the Italian artist who depicted the Comet in his painting of the "Adoration of the Magi".

Running time approx 30 minutes, Available VHS or Beta Format

Send your order complete with payment to:	NAME: Mr/Mrs/Ms	s			-
FOCAL VIOEO	ADDRESS:				
P.O. Box 227 WATERLOO 2017			POSTCODE		
Delivery within 14 days	TELEPHONE:				
Please send me your video "A					TOTAL
Please send me your video "A		ley" (Comp FORMAT VHS	No. REQUIRED	S carefully) UNIT PRICE \$39.95	TOTAL \$
Money Order or Cheque included a OR WE ACCEPT		FORMAT		UNIT PRICE	

(required if using credit card)


### STARTING DXING

LOCKING FOR CLEARER FREQUENCIES

There are many reasons for the mysterious appearance or disappearance of signals on various frequencies. In fact, integrating the whole caboodle of countries and schedules is a bit of a headache for a whole lot of people.

NEW LISTENERS OFTEN remark that stations change frequency without reason, often reappearing on another channel which gives better reception.

This move towards clearer signals via a new frequency does not just happen. Many hours of listening are involved in finding a clearer frequency so that the station can make the change assured of better reception. This writer has been monitoring for the BBC for 43 years and reports to London to indicate any interference. A monitor is requested to take a painstaking look at the occupancy of the band to find a clearer fre-

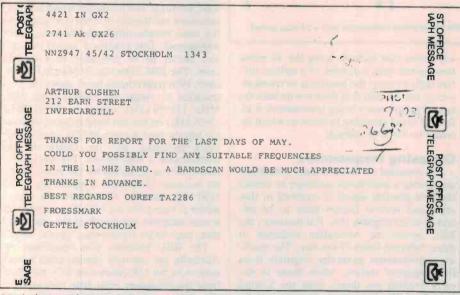

A typical request for a new frequency — in this case Radio Sweden asks for a check in the 11 MHz band and a survey of frequency occupancy.

## **Arthur Cushen**

quency region. This involves running receivers on the new frequency over a given period to ensure that no one else is using the channel before a decision is made to telex the BBC with the suggested channel.


The sharing of frequencies in an orderly manner is the prime intention of the International Frequency Board (in Geneva). International broadcasters submit their operating plans to the IFB several weeks in advance and it attempts to co-ordinate these requests. No country has a right to any frequency though traditionally countries try to stay on the same spot on the dial so that listeners have no problems locating their favourite station. For instance the BBC's oldest call sign GSA was assigned to 6050 kHz, GSB 9510 kHz and GSC 95-80 kHz and these frequencies are still looked on as being for BBC use, though they were assigned 50 years ago.

The seasonal changes which occur on the first Sunday in March, May, September and November result in some frequency and schedule readjustments as stations move from winter to summer and so try to serve their listening area on the best available frequency.

There are changes made at other times of the year. These days also, the change from standard to daylight time is often used as a period of adjustment. Changes occur for various reasons. Sunspots appear every 11

B	[:	3	C	7									Fro	m	291	h S	Sep	ten	nbe	r 1	98	5 T	0 2	911	Marcl	h 1986
M			?	7	50	)	6		2	27	75	7(1	25	2	(	2	0	25	7	0)	10	]]	3	N	GI	BS
Austr				_	eal									F												
etH z	00	01	02	03	04	05	06	07 0	00 (	59 10	11	GHT	13	14	15	16	17	18	19	20	21	22	23	24	HH2	Hotres
21.550	P							FEFFF	(* * * * *	b b	6666	a sele a			de .						*			-	21.550	13.92
15.310				1			b b	EEEE		FEFFE	FFFF	CEFE	FFFF	-	+							-	-		15.310	19.60
15.280									*	F P		*	*		-	84		-	-	-				p.	15.200	19.63
13.070			-	4			-	p.		666666	- F.		*	e-		8-			-				p.		15.070	19.91
11.955			-		8-		P	6666	66660	0 P		- 0-			1				P-		-	-		0-	11.955	25.09
11.775	-	de .	4	÷.	44	÷.		P.	P.	a a	NH NH			- 10	-	8-	-		- 20	-	der.	4-		- Pr	11.775	25.48
11.750		-	-		-	Dr.	P.	Þ	<b>a</b> .	FFFFFF	FFFF	- 14	- Pr	- Pr		81	*	P-	-	. Pr.	P-	- Pr.	0-	- Pr	11.750	25.53
9.915	der .	4.	400	40	der .	-	00	86		b b	P1	de .	ðr.	der .	de-	de.	8-	- 44		40	÷	-	- Pr	-	9.915	30.26
9.640	Br.	p.			-	0-	8-	6666	66666	36 ⊳	e-		P	Dr.	p.	-	-		8-	be.	94	8-	-	0-	9.640	31.12
9.370	-	a.	8×	a-		8-	- Pr	le .	te .	p. p.	8-		- B-	-	9-	÷-	8×	- P-	8×	FF	FFFF	FFFF	FFFF	- P	9.570	31.35
9.510	<b>8</b> ×	4			- P- 1	UNNU				4 H H	- D-	-	B-	(Prot		8-	- 84		0-	-	÷.	. Pr		*	9.510	31.55
9.410	a-		-	*	-00	6868	68688	668	P*	P P	br.	- 14	de.		- 84	- B+	9-	- 0×		0-		-	8-	-	9.410	31.00
7.150	8*	p.	-		-	1	*	0666	6666	36 ►	. Pr		8-	P-		P*	- 01	÷.	8-	30			P1	1	7.150	41.90
7.145	the state	de .	-		de .			p.	P-	P P	br.	<b>8</b> =	br .	der .	- P	de .	P		81	FF	FFFF	FFF	-	1.10	7.145	41.99
6.175	D-	0-	84		+ 1			NAA		P - F	P*		8-	8*	*	*	-		8×	8*	- P-	-	8*	-	6-175	48.58
3.975	de .	- 84	-	0-		Dr.	- P	0000	00000	4 DE	÷.	De .	÷.	÷.	P	p.			p.			*	P.	- Pr	5.975	50.23
	p							-		the second party of																

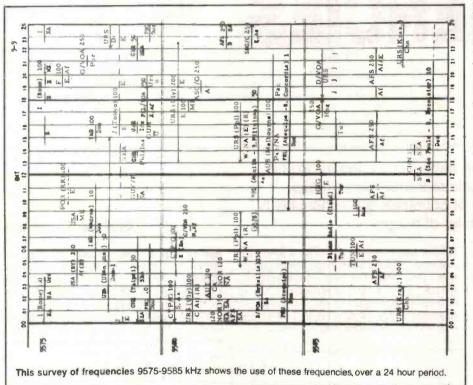This chart shows BBC transmissions to Australia which are in operation at the moment. Information covers the frequency in use, the length of transmission and the location of the transmitting station.



years. At the moment the sunspot count is only around six which means that we are at the low of the 11 year cycle. Congestion on the 49 metre band is typical during the low sunspot count as only the lower frequencies are available to SW stations. In a few months the spots will increase which will mean that the higher frequencies such as the 13 and 11 metre bands will again be open for transmissions.

Some comment on the 49 metre band shows how bands are divided up. On this band, between 5950 and 6200 kHz, 49 channels are available. By international agreement, stations should not be closer than 5 kHz apart; BBC engineers prefer 10 kHz separation because of interference on adjacent frequencies. This would leave only 25 channels available in this band, which is used by many stations in Europe to provide reception to the immediate vicinity. A sur-

112 - ETI March 1986

vey shows that stations using the 49 metre band spend over a quarter of a million dollars daily to keep the hundreds of transmitters on the air, and that does not include the cost of programmes being transmitted or efforts to avoid jamming by stations which attempt to block broadcasts.

#### **Choosing frequencies**

It is essential for international broadcasters serving a worldwide audience to ensure the best possible signal is received in that area, and several factors have to be observed to accomplish this. For instance, the BBC serves the Australian audience at three different times of the day. The morning transmissions generally originate from the Singapore station, while those in the early evening are direct from the United Kingdom. The Singapore signal travels directly to Australia, but from the UK there is a choice of a short path across Asia or the long path across the Pacific. The signals from the UK generally use the long path and lower frequencies until dark and after that transmissions are switched to the short path. At dusk there is a problem period of unsettled reception. Of course the frequencies should be those not used by any other broadcaster during the transmission period.

The complete scheduling of worldwide broadcasts is conducted by the International Telecommunication Union in Geneva. Switzerland where the mammoth jigsaw develops fitting stations' requests for frequencies into the channels available. Not uncommon, is to find two stations using the same frequency, but broadcasting in different directions, which while technically possible is not really practicable. There are many examples of this; I can recall Radio Canada 9630 kHz broadcasting to New Zealand and Radio Sweden broadcasting to the USSR, being allocated the same times for transmission; interference to both signals was severe as shortwave transmissions cannot be restricted to a certain area. Radio Sweden moved 5 kHz to the next clear channel which resulted in both signals being clearly received.

There are examples of very good cooperation between broadcasters and recently I suggested Radio Nederland use 9650 kHz for its transmission to Australia 1030-1125 UTC from Bonaire. This frequency is now used by Spain up to 0900 UTC, Germany 0930-1025 UTC, Holland 1030-1125 UTC and Canada from 1200 UTC.

#### **Understanding schedules**

Broadcasters continue to present their schedules in printed form indicating the time, language and frequency which is being broadcast but the use of a bar type graph by the main broadcasting organisations is also widespread. This enables a variety of subject matter to be presented in a simple form. The BBC schedule 29 March-27 October, 1986 (reproduced here) shows the frequencies in megahertz (MHz) from 21.5 MHz (21550 kHz) down to 5.975 MHz (5975 kHz) on the left hand column. Across the top the time is given in UTC, each hour being indicated, and the length of the transmission is then shown. The site of the transmitter is indicated by the letter used: for instance 21.55 MHz is operating 1030-1130 UTC and the 'G' indicates the transmitter is located in the UK. The number of letters indicates the length of the transmission; each letter represents a quarter hour.

The BBC indicates that broadcasts to Australia are not only carried from transmitters in the UK (shown as 'G'), but also from the Singapore relay base indicated as 'F', Antigua in the Caribbean, 'W', and from Masirah in the Persian Gulf shown as

## STARTING DXING

'E'. The BBC also indicates transmissions from the Atlantic relay on Ascension as 'A', Eastern Mediterranean relay, Cyprus as 'C', while 'K' indicates the relay from the Voice of America at Greenville and 'S' a relay from Radio Canada International at Sackville.

This style of frequency information is used by the Voice of America which indicates the site of the transmitter and the power into the area being served on its transmission line. Most other broadcasters present their information in a standard form which indicates information in order of time, followed by the language, frequency, target area and the bearing of the aerial system.

#### **Band survey**

There is a tremendous amount of information available from radio stations including schedules of programme information. In Geneva, the International Telecommunication Union produces a book showing the frequencies assigned to shortwave stations throughout the world. This information can only be taken as tentative, as often the frequencies offered by the ITU are not accepted by the broadcaster, while many stations in Eastern Europe do not adhere to frequency allocations, and are likely to be received on any frequency without prior notice, (thus causing considerable havoc to the orderly allocation of channels).

Most international broadcasters have agreed that there should be a limited number of frequencies used by one station in a shortwave band and, as well, that the total number of transmitters carrying the same programme should be restricted. Looking at the schedule of Radio Moscow World Service in English at 0700 UTC, it shows there are 41 frequencies in use to carry this single programme which means complete domination on most of the shortwave bands by this single programme. It is obvious that good frequency choice could reduce the number of transmitters to 10 and still provide an effective service.

Each month this writer has the task of identifying the source of transmissions and the length and time of broadcasts, and to rate their signal strengths. This work is aided by scheduling information from over 70 broadcasters, but practical listening is paramount as many stations are found not to be operating as they advise. This practical exercise, for instance from 0200-0430 UTC, enables identification of over 120 signals in the 25 metre band from 11700-11975 kHz. The information is plotted on a graph, and the country from which the broadcast originates is identified by a symbol. This symbol should not be confused with the call sign which is assigned to all countries for use by radio amateurs, (for instance Australia is identified as AUS.

£

whereas the amateur radio prefix is VK; New Zealand is identified as NZL although the amateur prefix is ZL). See the accompanying complete list of the abbreviations for the various countries.

When surveying a shortwave band, a log should be kept showing each frequency listened to and stations identified. New stations to a frequency are soon recognised: identification of languages is important and the sound of the various transmissions enables one to identify a signal even before the announcement is made. Even knowing that stations announce on the hour, it can take several days to fully identify the mystery signals one receives. The Moscow Home Service programmes, for example, are found on many unlisted frequencies. To overcome this problem one receiver can be left running on such a transmission so that when a similar programme is heard on another frequency, identification can be made.

The increasing number of Arabic speaking stations coming on to the shortwave bands also causes problems. The main broadcasts in the Russian language from stations in Western Europe between 0315-0345 UTC is the reason for increased jamming of channels during that time period. There are many frequencies which listeners will find are jammed continually. Generally the broadcasts of Radio Liberty or Radio Free Europe are completely buried by this deliberate interference.

After a survey is completed one can see at a glance those frequencies that are not being used. This is essential information for any shortwave broadcaster looking for new channels.

A list of abbreviations is used internationally to identify location of the various countries using the shortwave bands.

AFS GAB South Africa AGL Angola CHA AL.B Albania GIL Algeria Andorra ALC AND GRC ARG Argentina GRL ARS Saudi Arabia GTM ASC Ascension Islands GUR ATN Netherlands Antilles GUF Australia AUS AUT Austria GUT Brazil BBC British Broadcasting Corp. HND BDI Burundi HNG BEL Belgium HOL BEN Benin HTI Bangladesh BGD HVO BHR Bahrain HWA BHU Bhutan BLR Bylorussia IND BOL Bolivia INS BOT Botswana IOB RRN Burma IRN BFU Brunei IRQ BUL Bulgaria ISL CAF Central African Republic ISR CAN Canada Cambodia (Khmer Republic) CBG JOR CHL Chile KEN People's Republic of China Republic of China (Taiwan) CHN KON CHR KRE CKN Cook Islands KWT CLM Colombia LAO CLN Sri Lanka LBN CME Cameroon 1.8R Canary Islands CNR LBY Congo Comoro Islands COG LUX COM MAU CPV Cape Verde Islands MCO Ivory Coast CTI MDG CTR Costa Rica MEX Cuba CVA Vatican State MLD CYP Cyprus Federal Republic of Germany D MLT DAH Benin MNG German Democratic Republic DDP MOZ DNK Denmark MRC Dominican Republic DOM MRT DW Voice of Germany MIN Spain NWI EGY Egypt NCG EOA Ecuador NCL Equatorial Guinea EQG NGR Ethiopa ETH NHB France Fiji NIG FJI NOR Finland FNL NPL

Gabon Ghana Gilbert and Ellice Islands Gambia Greece Greenland Guatemala Guyana French Guiana Guam Guinea Belize Honduras Hungary Holland, Radio Netherlands Haiti Haiti Upper Volta Hawaii Italy India Indonesia British West Indies 1ran Iraq Iceland Israel Japan Jordan Kenya Korea (Republic of) Kores(People's Dem. Rep. of) Kuwait Laos Lebanon Liberia Libya Luxembourg Mauritius Monaco Malagasy Mexico Malaysia Maldive Islands Mali Malta Mongolia Mozanbique Morocco Martinique Mauritania Malawi Nicaragua New Caledonia Niger New Hebrides Nigeria Norway Nepal

OAS Org. of Am. States Tahiti OCE Oman PAK Pakistan Philippines PHL PNG Papus New Guines PNR Panama POL Poland POR Portugal PRG Paraguay Peru UAT Qatar REU Reunion RFE Radio Free Europe RHS Rhodesia RI. Radio Liberty ROU Romania RRW Ryanda RTU Ryukyu Islands Sveden SDN Sudan SEN Senegal SEY Seychelles SHN Saint Helens SLM Solomon Island SLY El Salvador Singapore Somalia Sierra Leone SOM SRL SUI Switzerland SUR Surinam SWZ Swaziland SYR Syria TCD Chad TCH Czechoslovakia TCK Tanzania Togo TGO THA Thailand Tunisia TUR Turkey Transworld Radio TWR United Arab Emirates UGA Uganda UKR Ukraine TIN United Nations Uruguay Union of Soviet Socialists Republics URG URS USA United States of America VEN Venezuela VOA Voice of America. Vietnam Yemen Southern Yemen YEM YMS YUG Yugoslavia ZAI Zaire Zanzibar Zambia ZAN ZMB

#### DREGS

#### DBASIC

#### by Paul Jones

Types of BASIC proliferate like rabbits. There is CBASIC, ZBASIC, MBASIC, Extended BASIC, Tiny BASIC etc. Well, here is Dregs BASIC (DBASIC), for the person tired of 'USER FRIENDLY'.

It was written by a depressed systems analyst who had just left his job after seeing another 'USER ERROR' notice on his VDU. It is designed to enable anyone, familiar with basic BASIC, to write error free programs.

Program structure in DBASIC does not exist, so you can build your program any way you like. DBASIC starts at a randomly selected line number and continues haphazardly through the uncompiled list of statements until it finds an OBJECT statement. This contains the REASON and RESULT data which is then examined by a Decentralised Processing Element, called COMMITTEE. If the REA-SON is reasonable and allocated resources are high enough then the RESULT data is printed on the screen.

A summary of commands:

+-\*/

These are used in character strings to represent a cross, a dash, a star and a slash.

**REM** Provided to take up memory space and make the programmer look like an idiot by writing stupid comments.

PAUSE

A long way of representing a ','. STOP

The only statement which can be relied upon to work most of the time.

#### BRIBE

Allocation of resources to COMMIT-TEE.

IF...THEN...SO WHAT

An extension of the classic IF...THEN, except that ALL results are ignored and the program continues on the next line anyway.

#### HO-HUM

Printed on screen during FOR...NEXT loops.

#### **ON ERROR, IGNORE**

Guarantees a result even if the result is wrong.

#### HOW ABOUT

Precedes complex functions to show that you are not really expecting a quick result.

#### HAVE A GO AT

Precedes complex functions to show that you think the function is beyond the abilities of the computer.

#### NO WAY

Computer reply to a HAVE A GO AT statement.

#### INTEREST LOST

Automatic power down and program halt.

#### INTEREST REGAINED

Automatic power on.

POKE

Writes important data into an unknown memory location.

#### DELAY

Used to ensure you can get overtime while waiting for the program to produce a result.

#### LIST

A list of people who could answer your problem without the need of a computer.

This DBASIC is supplied with a complete, two page leaflet, detailing where to send more money for more information. A listing is available, in Chinese, and the program is supplied on 32 old wax cylinders and is not compatible with current computers. Should become an industry standard by 1892.





Two of Anritsu's Best Ideas To Cut Testing Time

#### MS710A Spectrum Analyzer

For fewer errors, an internal tracking pre-selector keeps distortion down. And peak signal search and half-screen shift let you locate the desired signal spike sooner.

The MS710A covers the entire spectrum from 100kHz to 23GHz, so there's no need to overload your bench with instruments.

And it's ergonomically designed for no eyestrain and fewer headaches in operation. Pushbuttons handle signal averaging for noisy or low-amplitude signals. And digital storage keeps the display flicker free.

#### MS610A Spectrum Analyzer

The MS610A automatically sets all measurement conditions at optimum values — you just set frequency, reference level, and frequency span. And that saves you time *and* cuts errors in measurement. Two keys, COUPLED TO REF, and COUPLED TO SPAN, set all measurement parameters, so fewer dial operations are required.

And like the MS710A, it's smaller and more portable than ever. So you get full console performance in a personal, portable tester.

The test of the best is still the name Anritsu. Contact Anritsu today for more information.



STANDARD TELEPHONES AND CABLES PTY. LIMITED (Incorporated in N.S.W.) P.O. Box 42, THORNBURY, VICTORIA 3071 TELEPHONE: (03) 480-1255 TELEX: AA30878

# Get all of Yamaha's latest audio quipment foronly 33 cents.



Fill in this coupon and you'll get Yamaha's free catalogue featuring the latest and complete range of compact disc players, cassette decks, turntables, cartridges, integrated amps, separate amps, tuners, receivers, graphic equalizers, headphones and system components. With each component comes something you wouldn't expect.

Name.

Address.

Postcode.

Yamaha Consumer Electronics Division, 17-33 Market Street, South Melbourne, Victoria 3205.



**ETI READER SERVICE 103**